 


PRENTICE  
HALL

# Modern VLSI Design

## IP-BASED DESIGN

FOURTH EDITION



Wayne Wolf

Prentice Hall Modern Semiconductor Design Series

## Table of Contents

<b>Copyright.....</b>	<b>1</b>
<b>Prentice Hall Modern Semiconductor Design Series.....</b>	<b>4</b>
<b>Preface to the Fourth Edition.....</b>	<b>5</b>
<b>Preface to the Third Edition.....</b>	<b>7</b>
<b>Preface to the Second Edition.....</b>	<b>8</b>
<b>Preface.....</b>	<b>9</b>
<b>About the Author.....</b>	<b>12</b>
<b>Chapter 1. Digital Systems and VLSI.....</b>	<b>13</b>
Section 1.1. Why Design Integrated Circuits?.....	15
Section 1.2. Integrated Circuit Manufacturing.....	17
Section 1.3. CMOS Technology.....	30
Section 1.4. Integrated Circuit Design Techniques.....	33
Section 1.5. IP-Based Design.....	45
Section 1.6. A Look into the Future.....	52
Section 1.7. Summary.....	53
Section 1.8. References.....	54
Section 1.9. Problems.....	54
<b>Chapter 2. Fabrication and Devices.....</b>	<b>55</b>
Section 2.1. Introduction.....	57
Section 2.2. Fabrication Processes.....	57
Section 2.3. Transistors.....	64
Section 2.4. Wires and Vias.....	86
Section 2.5. Fabrication Theory and Practice.....	96
Section 2.6. Reliability.....	110
Section 2.7. Layout Design and Tools.....	115
Section 2.8. References.....	131
Section 2.9. Problems.....	132
<b>Chapter 3. Logic Gates.....</b>	<b>135</b>
Section 3.1. Introduction.....	137
Section 3.2. Combinational Logic Functions.....	137
Section 3.3. Static Complementary Gates.....	140
Section 3.4. Switch Logic.....	169
Section 3.5. Alternative Gate Circuits.....	171
Section 3.6. Low-Power Gates.....	181
Section 3.7. Delay through Resistive Interconnect.....	187
Section 3.8. Delay through Inductive Interconnect.....	199
Section 3.9. Design-for-Yield.....	205
Section 3.10. Gates as IP.....	207
Section 3.11. References.....	210
Section 3.12. Problems.....	211
<b>Chapter 4. Combinational Logic Networks.....</b>	<b>217</b>
Section 4.1. Introduction.....	219
Section 4.2. Standard Cell-Based Layout.....	219
Section 4.3. Combinational Network Delay.....	231
Section 4.4. Logic and Interconnect Design.....	247
Section 4.5. Power Optimization.....	258
Section 4.6. Switch Logic Networks.....	263
Section 4.7. Combinational Logic Testing.....	267
Section 4.8. References.....	274
Section 4.9. Problems.....	274
<b>Chapter 5. Sequential Machines.....</b>	<b>279</b>
Section 5.1. Introduction.....	281

---

Section 5.2. Latches and Flip-Flops.....	281
Section 5.3. Sequential Systems and Clocking Disciplines.....	293
Section 5.4. Performance Analysis.....	304
Section 5.5. Clock Generation.....	322
Section 5.6. Sequential System Design.....	324
Section 5.7. Power Optimization.....	341
Section 5.8. Design Validation.....	342
Section 5.9. Sequential Testing.....	344
Section 5.10. References.....	352
Section 5.11. Problems.....	352
<b>Chapter 6. Subsystem Design.....</b>	<b>357</b>
Section 6.1. Introduction.....	359
Section 6.2. Combinational Shifters.....	361
Section 6.3. Adders.....	364
Section 6.4. ALUs.....	372
Section 6.5. Multipliers.....	372
Section 6.6. High-Density Memory.....	381
Section 6.7. Image Sensors.....	394
Section 6.8. Field-Programmable Gate Arrays.....	397
Section 6.9. Programmable Logic Arrays.....	399
Section 6.10. Buses and Networks-on-Chips.....	403
Section 6.11. Data Paths.....	427
Section 6.12. Subsystems as IP.....	429
Section 6.13. References.....	434
Section 6.14. Problems.....	434
<b>Chapter 7. Floorplanning.....</b>	<b>437</b>
Section 7.1. Introduction.....	439
Section 7.2. Floorplanning Methods.....	439
Section 7.3. Global Interconnect.....	451
Section 7.4. Floorplan Design.....	462
Section 7.5. Off-Chip Connections.....	464
Section 7.6. References.....	473
Section 7.7. Problems.....	474
<b>Chapter 8. Architecture Design.....</b>	<b>483</b>
Section 8.1. Introduction.....	485
Section 8.2. Hardware Description Languages.....	485
Section 8.3. Register-Transfer Design.....	507
Section 8.4. Pipelining.....	521
Section 8.5. High-Level Synthesis.....	530
Section 8.6. Architectures for Low Power.....	551
Section 8.7. GALS Systems.....	556
Section 8.8. Architecture Testing.....	557
Section 8.9. IP Components.....	562
Section 8.10. Design Methodologies.....	563
Section 8.11. Multiprocessor System-on-Chip Design.....	571
Section 8.12. References.....	577
Section 8.13. Problems.....	577
<b>Appendices.....</b>	<b>581</b>
Appendix A. A Chip Designer's Lexicon.....	583
Appendix B. Hardware Description Languages.....	601
Section B.1. Introduction.....	601
Section B.2. Verilog.....	601
Section B.3. VHDL.....	606
<b>References.....</b>	<b>611</b>
<b>Inside Front Cover.....</b>	<b>625</b>
<b>Inside Back Cover.....</b>	<b>627</b>

---

---

# Modern VLSI Design

---

*IP-Based Design*  
*Fourth Edition*

**Wayne Wolf**



PRENTICE  
HALL

Upper Saddle River, NJ • Boston • Indianapolis • San Francisco  
New York • Toronto • Montreal • London • Munich • Paris • Madrid  
Capetown • Sydney • Tokyo • Singapore • Mexico City

---

---

Many of the designations used by manufacturers and sellers to distinguish their products are claimed as trademarks. Where those designations appear in this book, and the publisher was aware of a trademark claim, the designations have been printed with initial capital letters or in all capitals.

The author and publisher have taken care in the preparation of this book, but make no expressed or implied warranty of any kind and assume no responsibility for errors or omissions. No liability is assumed for incidental or consequential damages in connection with or arising out of the use of the information or programs contained herein.

The publisher offers excellent discounts on this book when ordered in quantity for bulk purchases or special sales, which may include electronic versions and/or custom covers and content particular to your business, training goals, marketing focus, and branding interests. For more information, please contact:

U.S. Corporate and Government Sales  
(800) 382-3419  
corpsales@pearsontechgroup.com

For sales outside the United States please contact:

International Sales  
international@pearson.com

Visit us on the Web: [informit.com/ph](http://informit.com/ph)

*Library of Congress Cataloging-in-Publication Data*

Wolf, Wayne Hendrix.

Modern VLSI design : IP-based design / Wayne Wolf.—4th ed.

p. cm.

Includes bibliographical references and index.

ISBN 0-13-714500-4 (hardback : alk. paper) 1. Digital integrated circuits—Computer-aided design. 2. Logic circuits—Computer-aided design. 3. Design protection. 4. Intellectual property. I. Title.

TK7874.65.W65 2008

621.39'5—dc22

2008040479

Copyright © 2009 Pearson Education, Inc.

All rights reserved. Printed in the United States of America. This publication is protected by copyright, and permission must be obtained from the publisher prior to any prohibited reproduction, storage in a retrieval system, or transmission in any form or by any means, electronic, mechanical, photocopying, recording, or likewise. For information regarding permissions, write to:

Pearson Education, Inc.  
Rights and Contracts Department  
501 Boylston Street, Suite 900  
Boston, MA 02116  
Fax (617) 671-3447

Illustrated and typeset by the author. This book was typeset using FrameMaker. Illustrations were drawn using Adobe Illustrator, with layout plots generated by cif2ps.

ISBN-13: 978-0-13-714500-3

ISBN-10: 0-13-714500-4


Text printed in the United States on recycled paper at Courier in Westford, Massachusetts.

First printing, December 2008

---

---

**for Nancy and Alec**

 

---

## ***Prentice Hall Modern Semiconductor Design Series***

---

- James R. Armstrong and F. Gail Gray  
*VHDL Design Representation and Synthesis*
- Mark Gordon Arnold  
*Verilog Digital Computer Design: Algorithms into Hardware*
- Jayaram Bhasker  
*A VHDL Primer, Third Edition*
- Mark D. Birnbaum  
*Essential Electronic Design Automation (EDA)*
- Eric Bogatin  
*Signal Integrity: Simplified*
- Douglas Brooks  
*Signal Integrity Issues and Printed Circuit Board Design*
- Ken Coffman  
*Real World FPGA Design with Verilog*
- Alfred Crouch  
*Design-for-Test for Digital IC's and Embedded Core Systems*
- Dennis Derickson and Marcus Müller (Editors)  
*Digital Communications Test and Measurement*
- Greg Edlund  
*Timing Analysis and Simulation for Signal Integrity Engineers*
- Daniel P. Foty  
*MOSFET Modeling with SPICE: Principles and Practice*
- Tom Granberg  
*Handbook of Digital Techniques for High-Speed Design*
- Nigel Horspool and Peter Gorman  
*The ASIC Handbook*
- Geoff Lawday, David Ireland, and Greg Edlund  
*A Signal Integrity Engineer's Companion*
- Mike Peng Li  
*Jitter, Noise, and Signal Integrity at High-Speed*
- Farzad Nekoogar and Faranak Nekoogar  
*From ASICs to SOCs: A Practical Approach*
- Farzad Nekoogar  
*Timing Verification of Application-Specific Integrated Circuits (ASICs)*
- Samir Palnitkar  
*Design Verification with e*
- David Pellerin and Scott Thibault  
*Practical FPGA Programming in C*
- Christopher T. Robertson  
*Printed Circuit Board Designer's Reference: Basics*
- Chris Rowen  
*Engineering the Complex SOC*
- Madhavan Swaminathan and A. Ege Engin  
*Power Integrity Modeling and Design for Semiconductors and Systems*
- Wayne Wolf  
*FPGA-Based System Design*
- Wayne Wolf  
*Modern VLSI Design, Fourth Edition: IP-Based Design*
- 
-

---

## Preface to the Fourth Edition

---

I set for myself two goals in producing this fourth edition of *Modern VLSI Design*. First, I wanted to update the book for more modern technologies and design methods. This includes obvious changes like smaller design rules. But it also includes emphasizing more system-level topics such as IP-based design. Second, I wanted to continue to improve the book's treatment of the fundamentals of logic design. VLSI is often treated as circuit design, meaning that traditional logic design topics like pipelining can easily become lost.

In between the third and fourth editions of this book, I respun the third edition as *FPGA-Based System Design*. That book added new FPGA-oriented material to material from *Modern VLSI Design*. In this edition, I've decided to borrow back some material from the FPGA book. The largest inclusion was the section on sequential system performance. I had never been happy with my treatment of that material. After 10 years of trying, I came up with a more acceptable description of clocking and timing in the FPGA book and I am now bringing it back to VLSI. I included material on busses, Rent's Rule, pipelining, and hardware description languages. I also borrowed some material on FPGAs themselves to flesh out that treatment from the third edition. An increasing number of designs include FPGA fabrics to add flexibility; FPGAs also make good design projects for VLSI classes. Material on IP-based design is presented at several levels of hierarchy: gates, subsystems, and architecture.

As part of this update, I eliminated the CAD chapter from this edition because I finally decided that such detailed treatment of many of the CAD tools is not strictly necessary. I also deleted the chapter on chip design.

Chip design has changed fundamentally in the past 20 years since I started to work on this book. Chip designers think less about rectangles and more about large blocks. To reflect this shift, I added a new chapter on system-on-chip design. Intellectual property is a fundamental fact of life in VLSI design—either you will design IP modules or you will use someone else's IP modules.

In addition to changing the chapters themselves, I also substantially revised the problems at the end of each chapter. These new problems better reflect the new material and they provide new challenges for students.



While I was at it, I also made some cosmetic changes to the book. I changed the typesetting to use the same format for left- and right-hand pages, an unfortunate necessity with today's tools. I also added margin headers—those phrases you see in the left-hand margin.

I have set up a new Web site for my books: look for “Wayne Wolf books” using your favorite search engine or use the URL <http://www.waynewolf.us>. This site includes overheads and errata for this book plus some useful links on VLSI design.

I'd like to thank Saibal Mukhopadhyay for his advice on low power, Jeremy Tolbert for his help with Spice, Massoud Pedram for his advice on thermal issues, Shekhar Borkhar for his advice on reliability, Deepu Talla and Cathy Wicks for the Da Vinci die photo, Axel Jantsch for his advice on networks-on-chips, Don Bouldin for his many helpful suggestions on IP-based design and other topics, Yuan Xie for his advice on both reliability and 3-D, Shekhar Borkar for his help on reliability, and my editor, Bernard Goodwin, for his everlasting patience. All errors in the book are, of course, mine.

Wayne Wolf  
Atlanta, Georgia

---

---

---

## Preface to the Third Edition

---

This third edition of *Modern VLSI Design* includes both incremental refinements and new topics. All these changes are designed to help keep up with the fast pace of advancements in VLSI technology and design.

The incremental refinements in the book include improvements in the discussion of low power design, the chip project, and the lexicon. Low power design was discussed in the second edition, but has become even more complex due to the higher leakages found at smaller transistor sizes. The PDP-8 used in previous editions has been replaced with a more modern data path design. Designing a complete computer is beyond the scope of most VLSI courses, but a data path makes a good class project. I have also tried to make the lexicon a more comprehensive guide to the terms in the book.

This edition shows more major improvements to the discussions of interconnect and hardware description languages. Interconnect has become increasingly important over the past few years, with interconnect delays often dominating total delay. I decided it was time to fully embrace the importance of interconnect, especially with the advent of copper interconnect. This third edition now talks more thoroughly about interconnect models, crosstalk, and interconnect-centric logic design.

The third edition also incorporates a much more thorough discussion of hardware description languages. Chapter 8, which describes architectural design, now introduces VHDL and Verilog as the major hardware description languages. Though these sections are not meant to be thorough manuals for these languages, they should provide enough information for the reader to understand the major concepts of the languages and to be able to read design examples in those languages.

As with the second edition, you can find additional helpful material on the World Wide Web at <http://www.ee.princeton.edu/~wolf/modern-vlsi>. This site includes overheads useful either for teaching or for self-paced learning. The site also includes supplementary materials, such as layouts and HDL descriptions. Instructors may request a book of answers to the problems in the book by calling Prentice Hall directly.

I'd like to thank Al Casavant and Ken Shepard for their advice on interconnect analysis and Joerg Henkel for his advice on design. I'd also like to thank Fred Rosenberger for his many helpful comments on the book. As always, any mistakes are mine.

Wayne Wolf  
Princeton, New Jersey

---

## Preface to the Second Edition

---

Every chapter in this second edition of *Modern VLSI Design* has been updated to reflect the challenges looming in VLSI system design. Today's VLSI design projects are, in many cases, mega-chips which not only contain tens (and soon hundreds) of millions of transistors, but must also run at very high frequencies. As a result, I have emphasized circuit design in a number of ways: the fabrication chapter spends much more time on transistor characteristics; the chapter on gate design covers a wider variety of gate designs; the combinational logic chapter enhances the description of interconnect delay and adds an important new section on crosstalk; the sequential logic chapter covers clock period determination more thoroughly; the subsystems chapter gives much more detailed descriptions of both multiplication and RAM design; the floorplanning chapter spends much more time on clock distribution.

Beyond being large and fast, modern VLSI systems must frequently be designed for low power consumption. Low-power design is of course critical for battery-operated devices, but the sheer size of these VLSI systems means that excessive power consumption can lead to heat problems. Like testing, low-power design cuts across all levels of abstraction, and you will find new sections on low power throughout the book.

The reader familiar with the first edition of this book will notice that the combinational logic material formerly covered in one chapter (Chapter 3) has been split into two chapters, one of logic gates and another on combinational networks. This split was the result of the great amount of material added on circuit design added to the early chapters of the book. Other, smaller rearrangements have also been made in the book, hopefully aiding clarity.

You can find additional helpful material on the World Wide Web at <http://www.ee.princeton.edu/~wolf/modern-vlsi>. This site includes overheads useful either for teaching or for self-paced learning. The site also includes supplementary materials, such as layouts and VHDL descriptions. Instructors may request a book of answers to the problems in the book by calling Prentice Hall directly.

I would especially like to thank Derek Beatty, Luc Claesen, John Darringer, Srinivas Devadas, Santanu Dutta, Michaela Guiney, Alex Ishii, Steve Lin, Rob Mathews, Cherrice Traver, and Steve Trimmerger for their comments and suggestions on this second edition.

Wayne Wolf  
Princeton, New Jersey

---

## Preface

---

This book was written in the belief that VLSI design is *system* design. Designing fast inverters is fun, but designing a high-performance, cost-effective integrated circuit demands knowledge of all aspects of digital design, from application algorithms to fabrication and packaging. Carver Mead and Lynn Conway dubbed this approach the tall-thin designer approach. Today's hot designer is a little fatter than his or her 1979 ancestor, since we now know a lot more about VLSI design than we did when Mead and Conway first spoke. But the same principle applies: you must be well-versed in both high-level and low-level design skills to make the most of your design opportunities.

Since VLSI has moved from an exotic, expensive curiosity to an everyday necessity, universities have refocused their VLSI design classes away from circuit design and toward advanced logic and system design. Studying VLSI design as a system design discipline requires such a class to consider a somewhat different set of areas than does the study of circuit design. Topics such as ALU and multiplexer design or advanced clocking strategies used to be discussed using TTL and board-level components, with only occasional nods toward VLSI implementations of very large components. However, the push toward higher levels of integration means that most advanced logic design projects will be designed for integrated circuit implementation.

I have tried to include in this book the range of topics required to grow and train today's tall, moderately-chubby IC designer. Traditional logic design topics, such as adders and state machines, are balanced on the one hand by discussions of circuits and layout techniques and on the other hand by the architectural choices implied by scheduling and allocation. Very large ICs are sufficiently complex that we can't tackle them using circuit design techniques alone; the top-notch designer must understand enough about architecture and logic design to know which parts of the circuit and layout require close attention. The integration of system-level design techniques, such as scheduling, with the more traditional logic design topics is essential for a full understanding of VLSI-size systems.

In an effort to systematically cover all the problems encountered while designing digital systems in VLSI, I have organized the material in this book relatively bottom-up, from fabrication to architecture. Though I am a strong fan of top-down design, the technological limitations which drive architecture are best learned starting with fabrication and layout. You can't expect to fully appreciate all the nuances of why a particular design step is formulated in a certain way until you have completed a chip design yourself, but referring to the steps as you proceed on your own chip design should help guide you. As a

result of the bottom-up organization, some topics may be broken up in unexpected ways. For example, placement and routing are not treated as a single subject, but separately at each level of abstraction: transistor, cell, and floor plan. In many instances I purposely tried to juxtapose topics in unexpected ways to encourage new ways of thinking about their interrelationships.

This book is designed to emphasize several topics that are essential to the practice of VLSI design as a system design discipline:

- **A systematic design methodology reaching from circuits to architecture.** Modern logic design includes more than the traditional topics of adder design and two-level minimization—register-transfer design, scheduling, and allocation are all essential tools for the design of complex digital systems. Circuit and layout design tell us which logic and architectural designs make the most sense for CMOS VLSI.
- **Emphasis on top-down design starting from high-level models.** While no high-performance chip can be designed completely top-down, it is excellent discipline to start from a complete (hopefully executable) description of what the chip is to do; a number of experts estimate that half the application-specific ICs designed execute their delivery tests but don't work in their target system because the designer didn't work from a complete specification.
- **Testing and design-for-testability.** Today's customers demand both high quality and short design turnaround. Every designer must understand how chips are tested and what makes them hard to test. Relatively small changes to the architecture can make a chip drastically easier to test, while a poorly designed architecture cannot be adequately tested by even the best testing engineer.
- **Design algorithms.** We must use analysis and synthesis tools to design almost any type of chip: large chips, to be able to complete them at all; relatively small ASICs, to meet performance and time-to-market goals. Making the best use of those tools requires understanding how the tools work and exactly what design problem they are intended to solve.

The design methodologies described in this book make heavy use of computer-aided design (CAD) tools of all varieties: synthesis and analysis; layout, circuit, logic, and architecture design. CAD is more than a collection of programs. CAD is a way of thinking, a way of life, like Zen. CAD's greatest contribution to design is breaking the process up into manageable steps. That is a conceptual advance you can apply with no computer in sight. A designer can—and should—formulate a narrow problem and apply well-understood methods to solve that problem. Whether the designer uses CAD tools or solves the problem by hand is much less important than the fact that the chip design isn't a jumble of vaguely competing concerns but a well-understood set of tasks.

I have explicitly avoided talking about the operation of particular CAD tools. Different people have different tools available to them and a textbook should not be a user's guide. More importantly, the details of how a particular program works are a diversion—what counts is the underlying problem formulations used to define the problem and the algorithms used to solve them. Many CAD algorithms

---

---

are relatively intuitive and I have tried to walk through examples to show how you can think like a CAD algorithm. Some of the less intuitive CAD algorithms have been relegated to a separate chapter; understanding these algorithms helps explain what the tool does, but isn't directly important to manual design.

Both the practicing professional and the advanced undergraduate or graduate student should benefit from this book. Students will probably undertake their most complex logic design project to date in a VLSI class. For a student, the most rewarding aspect of a VLSI design class is to put together previously-learned basics on circuit, logic, and architecture design to understand the tradeoffs between the different levels of abstraction. Professionals who either practice VLSI design or develop VLSI CAD tools can use this book to brush up on parts of the design process with which they have less-frequent involvement. Doing a truly good job of each step of design requires a solid understanding of the big picture.

A number of people have improved this book through their criticism. The students of COS/ELE 420 at Princeton University have been both patient and enthusiastic. Profs. C.-K. Cheng, Andrea La Paugh, Miriam Leaser, and John "Wild Man" Nestor all used drafts in their classes and gave me valuable feedback. Profs. Giovanni De Micheli, Steven Johnson, Sharad Malik, Robert Rutenbar, and James Sturm also gave me detailed and important advice after struggling through early drafts. Profs. Malik and Niraj Jha also patiently answered my questions about the literature. Any errors in this book are, of course, my own.

Thanks to Dr. Mark Pinto and David Boulin of AT&T for the transistor cross section photo and to Chong Hao and Dr. Michael Tong of AT&T for the ASIC photo. Dr. Robert Mathews, formerly of Stanford University and now of Performance Processors, indoctrinated me in pedagogical methods for VLSI design from an impressionable age. John Redford of DEC supplied many of the colorful terms in the lexicon.

Wayne Wolf  
Princeton, New Jersey

---

---

---

## About the Author

---

Wayne Wolf is Rhesa “Ray” S. Farmer Jr. Distinguished Chair in Embedded Computing Systems and Georgia Research Alliance Eminent Scholar at the Georgia Institute of Technology. Before joining Georgia Tech, he was with Princeton University from 1989 to 2007 and AT&T Bell Laboratories from 1984 to 1989. He received the B.S., M.S., and Ph.D. degrees in electrical engineering from Stanford University in 1980, 1981, and 1984, respectively. His research interests include VLSI systems, embedded computing, cyber-physical systems, and embedded computer vision. He has chaired several conferences, including CODES, EMSOFT, CASES, and ICCD. He was founding editor-in-chief of *ACM Transactions on Embedded Computing Systems* and founding co-editor-in-chief of *Design Automation for Embedded Systems*. He is a Fellow of the ACM and IEEE. He received the ASEE/CSE and HP Frederick E. Terman Award in 2003 and the IEEE Circuits and Systems Education Award in 2006.



**1**

# Digital Systems and VLSI

## **Highlights:**

VLSI and Moore's Law.

CMOS technology.

Hierarchical design.


The VLSI design process.

IP-based design.

---

---



 

Moore's Law (Figure 1-3).

---

## 1.1 Why Design Integrated Circuits?

---

This book describes design methods for integrated circuits. That may seem like a specialized topic. But, in fact, integrated circuit (IC) technology is the enabling technology for a whole host of innovative devices and systems that have changed the way we live. Jack Kilby and Robert Noyce received the 2000 Nobel Prize in Physics for their invention of the integrated circuit; without the integrated circuit, neither transistors nor computers would be as important as they are today. VLSI systems are much smaller and consume less power than the discrete components used to build electronic systems before the 1960s. Integration allows us to build systems with many more transistors, allowing much more computing power to be applied to solving a problem. Integrated circuits are also much easier to design and manufacture and are more reliable than discrete systems; that makes it possible to develop special-purpose systems that are more efficient than general-purpose computers for the task at hand.

### *applications of VLSI*

Electronic systems now perform a wide variety of tasks in daily life. Electronic systems in some cases have replaced mechanisms that operated mechanically, hydraulically, or by other means; electronics are usually smaller, more flexible, and easier to service. In other cases electronic systems have created totally new applications. Electronic systems perform a variety of tasks, some of them visible, some more hidden:

- Personal entertainment systems such as portable MP3 players and DVD players perform sophisticated algorithms with remarkably little energy.
  - Electronic systems in cars operate stereo systems and displays; they also control fuel injection systems, adjust suspensions to varying terrain, and perform the control functions required for anti-lock braking (ABS) systems.
  - Digital electronics compress and decompress video, even at high-definition data rates, on-the-fly in consumer electronics.
  - Low-cost terminals for Web browsing still require sophisticated electronics, despite their dedicated function.
  - Personal computers and workstations provide word-processing, financial analysis, and games. Computers include both central processing units (CPUs) and special-purpose hardware for disk access, faster screen display, *etc.*
- 
-

- Medical electronic systems measure bodily functions and perform complex processing algorithms to warn about unusual conditions. The availability of these complex systems, far from overwhelming consumers, only creates demand for even more complex systems.

The growing sophistication of applications continually pushes the design and manufacturing of integrated circuits and electronic systems to new levels of complexity. And perhaps the most amazing characteristic of this collection of systems is its variety—as systems become more complex, we build not a few general-purpose computers but an ever wider range of special-purpose systems. Our ability to do so is a testament to our growing mastery of both integrated circuit manufacturing and design, but the increasing demands of customers continue to test the limits of design and manufacturing.

#### *advantages of VLSI*

While we will concentrate on integrated circuits in this book, the properties of integrated circuits—what we can and cannot efficiently put in an integrated circuit—largely determine the architecture of the entire system. Integrated circuits improve system characteristics in several critical ways. ICs have three key advantages over digital circuits built from discrete components:

- **Size.** Integrated circuits are much smaller—both transistors and wires are shrunk to micrometer sizes, compared to the millimeter or centimeter scales of discrete components. Small size leads to advantages in speed and power consumption, since smaller components have smaller parasitic resistances, capacitances, and inductances.
- **Speed.** Signals can be switched between logic 0 and logic 1 much quicker within a chip than they can between chips. Communication within a chip can occur hundreds of times faster than communication between chips on a printed circuit board. The high speed of circuits on-chip is due to their small size—smaller components and wires have smaller parasitic capacitances to slow down the signal.
- **Power consumption.** Logic operations within a chip also take much less power. Once again, lower power consumption is largely due to the small size of circuits on the chip—smaller parasitic capacitances and resistances require less power to drive them.

#### *VLSI and systems*

These advantages of integrated circuits translate into advantages at the system level:

- **Smaller physical size.** Smallness is often an advantage in itself—consider portable televisions or handheld cellular telephones.

- **Lower power consumption.** Replacing a handful of standard parts with a single chip reduces total power consumption. Reducing power consumption has a ripple effect on the rest of the system: a smaller, cheaper power supply can be used; since less power consumption means less heat, a fan may no longer be necessary; a simpler cabinet with less shielding for electromagnetic shielding may be feasible, too.
- **Reduced cost.** Reducing the number of components, the power supply requirements, cabinet costs, and so on, will inevitably reduce system cost. The ripple effect of integration is such that the cost of a system built from custom ICs can be less, even though the individual ICs cost more than the standard parts they replace.

Understanding why integrated circuit technology has such profound influence on the design of digital systems requires understanding both the technology of IC manufacturing and the economics of ICs and digital systems.

---

## 1.2 Integrated Circuit Manufacturing

---

Integrated circuit technology is based on our ability to manufacture huge numbers of very small devices—today, more transistors are manufactured in California each year than raindrops fall on the state. In this section, we briefly survey VLSI manufacturing.

### 1.2.1 Technology

Most manufacturing processes are fairly tightly coupled to the item they are manufacturing. An assembly line built to produce Buicks, for example, would have to undergo moderate reorganization to build Chevys—tools like sheet metal molds would have to be replaced, and even some machines would have to be modified. And either assembly line would be far removed from what is required to produce electric drills.


*mask-driven  
manufacturing*

Integrated circuit manufacturing technology, on the other hand, is remarkably versatile. While there are several manufacturing processes for different circuit types—CMOS, bipolar, etc.—a manufacturing line can make any circuit of that type simply by changing a few basic tools called masks. For example, a single CMOS manufacturing plant can

---

---


make both microprocessors and microwave oven controllers by changing the masks that form the patterns of wires and transistors on the chips.

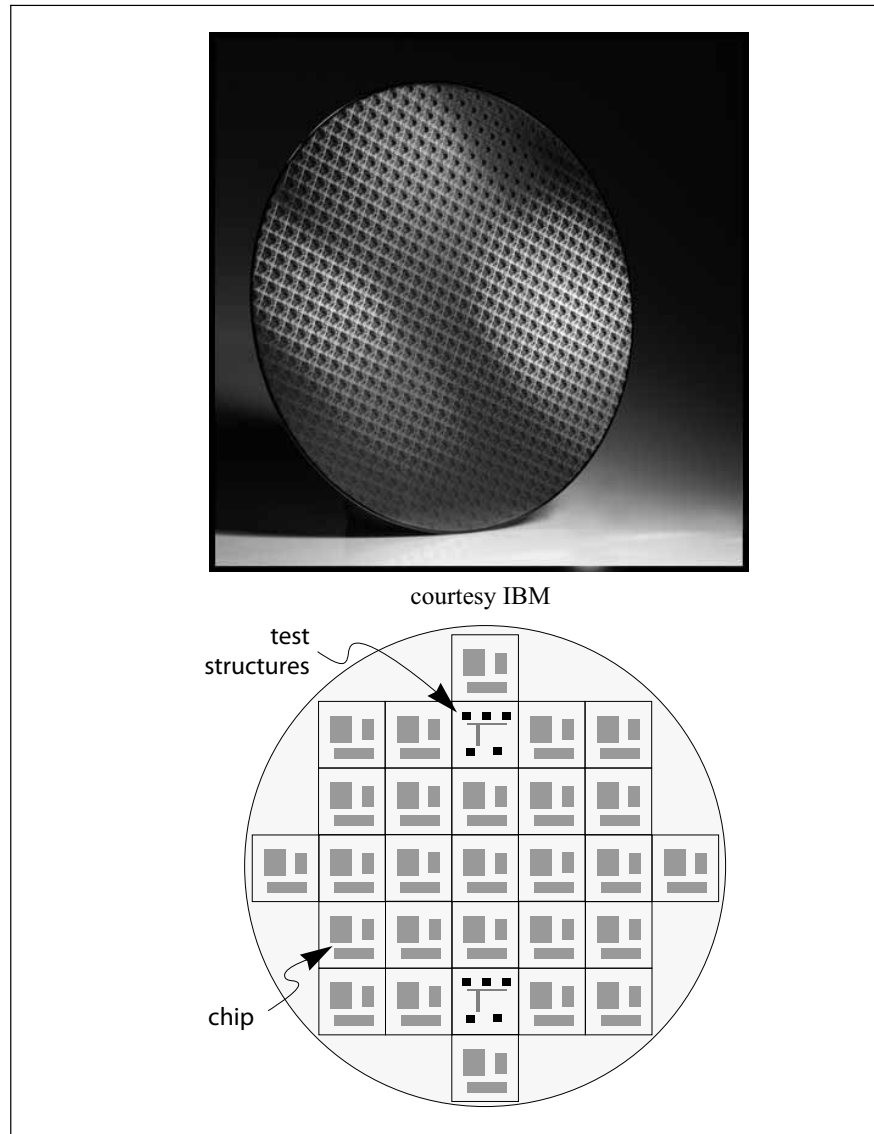

**Figure 1-1** A wafer divided into chips.

Silicon wafers are the raw material of IC manufacturing. The fabrication process forms patterns on the wafer that create wires and transistors. As shown in Figure 1-1, a series of identical chips are patterned onto the wafer (with some space reserved for test circuit structures which allow manufacturing to measure the results of the manufacturing process). The IC manufacturing process is efficient because we can produce many identical chips by processing a single wafer. By changing the masks that determine what patterns are laid down on the chip, we determine the digital circuit that will be created. The IC fabrication line is a generic manufacturing line—we can quickly retool the line to make large quantities of a new kind of chip, using the same processing steps used for the line's previous product.

**Figure 1-2** An inverter circuit and a sketch for its layout.

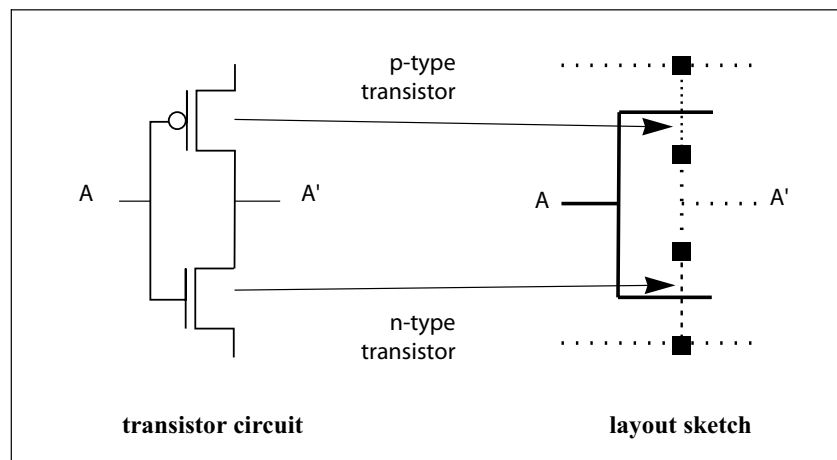

### *circuits and layouts*

Figure 1-2 shows the schematic for a simple digital circuit. From this description alone we could build a breadboard circuit out of standard parts. To build it on an IC fabrication line, we must go one step further and design the **layout**, or patterns on the masks. The rectangular shapes in the layout (shown here as a sketch called a stick diagram) form transistors and wires which conform to the circuit in the schematic. Creating layouts is very time-consuming and very important—the size of the layout determines the cost to manufacture the circuit, and the shapes of elements in the layout determine the speed of the circuit as well. During manufacturing, a **photolithographic** (photographic printing) process is used to transfer the layout patterns from the masks to the wafer. The patterns left by the mask are used to selectively change the wafer: impurities are added at selected locations in the wafer; insulating and

conducting materials are added on top of the wafer as well. These fabrication steps require high temperatures, small amounts of highly toxic chemicals, and extremely clean environments. At the end of processing, the wafer is divided into a number of chips.

#### *manufacturing defects*

Because no manufacturing process is perfect, some of the chips on the wafer may not work. Since at least one defect is almost sure to occur on each wafer, wafers are cut into smaller, working chips; the largest chip that can be reasonably manufactured today is 1.5 to 2 cm on a side, while a wafer is in moving from 30 to 45 cm. Each chip is individually tested; the ones that pass the test are saved after the wafer is diced into chips. The working chips are placed in the packages familiar to digital designers. In some packages, tiny wires connect the chip to the package's pins while the package body protects the chip from handling and the elements; in others, solder bumps directly connect the chip to the package.

Integrated circuit manufacturing is a powerful technology for two reasons: all circuits can be made out of a few types of transistors and wires; and any combination of wires and transistors can be built on a single fabrication line just by changing the masks that determine the pattern of components on the chip. Integrated circuits run very fast because the circuits are very small. Just as important, we are not stuck building a few standard chip types—we can build any function we want. The flexibility given by IC manufacturing lets us build faster, more complex digital systems in ever greater variety.

### 1.2.2 Economics

Because integrated circuit manufacturing has so much leverage—a great number of parts can be built with a few standard manufacturing procedures—a great deal of effort has gone into improving IC manufacturing. However, as chips become more complex, the cost of designing a chip goes up and becomes a major part of the overall cost of the chip.

#### *Moore's Law*

In the 1960s Gordon Moore predicted that the number of transistors that could be manufactured on a chip would grow exponentially. His prediction, now known as **Moore's Law**, was remarkably prescient. Moore's ultimate prediction was that transistor count would double every two years, an estimate that has held up remarkably well. Today, an industry group maintains the International Technology Roadmap for Semiconductors (ITRS), that maps out strategies to maintain the pace of Moore's Law. (The ITRS roadmap can be found at <http://www.itrs.net>.)

---

---

**Figure 1-3**  
Moore's Law.

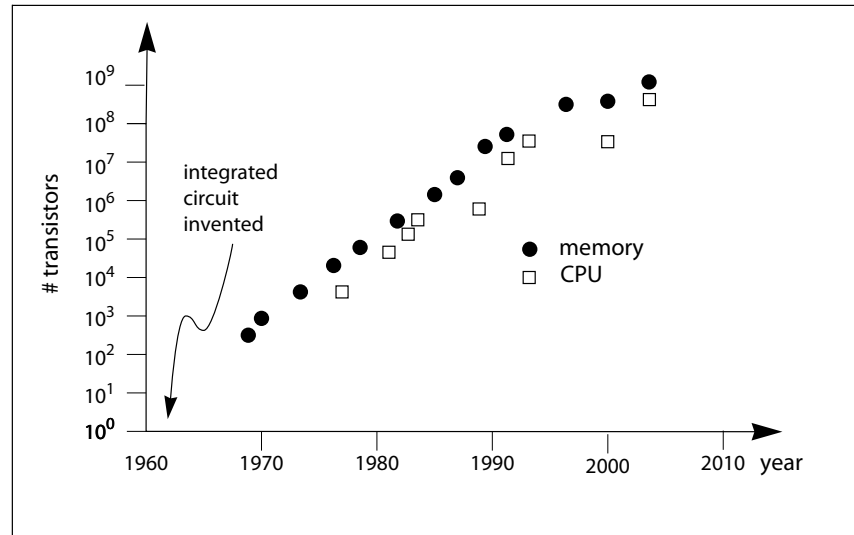


Figure 1-3 shows advances in manufacturing capability by charting the introduction dates of key products that pushed the state of the manufacturing art. The squares show various logic circuits, primarily central processing units (CPUs) and digital signal processors (DSPs), while the black dots show random-access memories, primarily dynamic RAMs or DRAMs. At any given time, memory chips have more transistors per unit area than logic chips, but both have obeyed Moore's Law.

#### *terminology*

The most basic parameter associated with a manufacturing process is the minimum channel length of a transistor. (In this book, for example, we will use as an example a technology that can manufacture 180 nm transistors.) A manufacturing technology at a particular channel length is called a **technology node**. We often refer to a family of technologies at similar feature sizes: **micron**, **submicron**, **deep submicron**, and now **nanometer** technologies. The term **nanometer technology** is generally used for technologies below 100 nm.

The next example shows how Moore's Law has held up in one family of microprocessors.



---

### **Example 1-1 Moore's Law and Intel microprocessors**

The Intel microprocessors are one good example in the growth in complexity of integrated circuits. Here are the sizes of several generations of the microprocessors descended from the Intel 8086 (data from the Intel Museum, available at <http://www.intel.com/museum>).

<b>microprocessor</b>	<b>date of introduction</b>	<b># transistors</b>
80286	2/82	134,000
80386	10/85	275,000
80486	4/89	1,200,000
Intel Pentium™	3/93	3,100,000
Intel Pentium Pro™	11/95	5,500,000
Intel Pentium II™	1997	7,500,000
Intel Pentium III™	1999	9,500,000
Intel Pentium 4™	2000	42,000,000
Intel Itanium™	2001	25,000,000
Intel Itanium 2™	2003	220,000,000
Intel Itanium 2™ (9 MB cache)	2004	592,000,000


The photomicrographs of these processors, all courtesy of Intel, vividly show the increase in design complexity implied by this exponential growth in transistor count.

---




---

1.2 Integrated Circuit Manufacturing

 


80286

 

80386


1.2 Integrated Circuit Manufacturing

13

 


80486



 

Pentium™

 

Pentium Pro™

---

*cost of manufacturing*

IC manufacturing plants are extremely expensive. A single plant costs as much as \$4 billion. Given that a new, state-of-the-art manufacturing process is developed every three years, that is a sizeable investment. The investment makes sense because a single plant can manufacture so many chips and can easily be switched to manufacture different types of chips. In the early years of the integrated circuits business, companies focused on building large quantities of a few standard parts. These parts are commodities—one 80 ns, 256Mb dynamic RAM is more or less the same as any other, regardless of the manufacturer. Companies concentrated on commodity parts in part because manufacturing processes

---

---

were less well understood and manufacturing variations are easier to keep track of when the same part is being fabricated day after day. Standard parts also made sense because designing integrated circuits was hard—not only the circuit, but the layout had to be designed, and there were few computer programs to help automate the design process.

#### *cost of design*

One of the less fortunate consequences of Moore's Law is that the time and money required to design a chip goes up steadily. The cost of designing a chip comes from several factors:

- Skilled designers are required to specify, architect, and implement the chip. A design team may range from a half-dozen people for a very small chip to 500 people for a large, high-performance microprocessor.
- These designers cannot work without access to a wide range of computer-aided design (CAD) tools. These tools synthesize logic, create layouts, simulate, and verify designs. CAD tools are generally licensed and you must pay a yearly fee to maintain the license. A license for a single copy of one tool, such as logic synthesis, may cost as much as \$50,000 US.
- The CAD tools require a large compute farm on which to run. During the most intensive part of the design process, the design team will keep dozens of computers running continuously for weeks or months.

A large ASIC, which contains millions of transistors but is not fabricated on the state-of-the-art process, can easily cost \$20 million US and as much as \$100 million. Designing a large microprocessor costs hundreds of millions of dollars.

#### *design costs and IP*

We can spread these design costs over more chips if we can reuse all or part of the design in other chips. The high cost of design is the primary motivation for the rise of IP-based design, which creates modules that can be reused in many different designs. We will discuss IP-based design in more detail in Section 1.5.

#### *types of chips*

The preponderance of standard parts pushed the problems of building customized systems back to the board-level designers who used the standard parts. Since a function built from standard parts usually requires more components than if the function were built with custom-designed ICs, designers tended to build smaller, simpler systems. The industrial trend, however, is to make available a wider variety of integrated circuits. The greater diversity of chips includes:

- **More specialized standard parts.** In the 1960s, standard parts were logic gates; in the 1970s they were LSI components. Today, standard parts include fairly specialized components: communication network interfaces, graphics accelerators, floating point processors. All these parts are more specialized than microprocessors but are used in enough volume that designing special-purpose chips is worth the effort. In fact, putting a complex, high-performance function on a single chip often makes other applications possible—for example, single-chip floating point processors make high-speed numeric computation available on even inexpensive personal computers.
- **Application-specific integrated circuits (ASICs).** Rather than build a system out of standard parts, designers can now create a single chip for their particular application. Because the chip is specialized, the functions of several standard parts can often be squeezed into a single chip, reducing system size, power, heat, and cost. Application-specific ICs are possible because of computer tools that help humans design chips much more quickly.
- **Systems-on-chips (SoCs).** Fabrication technology has advanced to the point that we can put a complete system on a single chip. For example, a single-chip computer can include a CPU, bus, I/O devices, and memory. SoCs allow systems to be made at much lower cost than the equivalent board-level system. SoCs can also be higher performance and lower power than board-level equivalents because on-chip connections are more efficient than chip-to-chip connections.

A wider variety of chips is now available in part because fabrication methods are better understood and more reliable. More importantly, as the number of transistors per chip grows, it becomes easier and cheaper to design special-purpose ICs. When only a few transistors could be put on a chip, careful design was required to ensure that even modest functions could be put on a single chip. Today's VLSI manufacturing processes, which can put millions of carefully-designed transistors on a chip, can also be used to put tens of thousands of less-carefully designed transistors on a chip. Even though the chip could be made smaller or faster with more design effort, the advantages of having a single-chip implementation of a function that can be quickly designed often outweighs the lost potential performance. The problem and the challenge of the ability to manufacture such large chips is design—the ability to make effective use of the millions of transistors on a chip to perform a useful function.

---

---



---

## 1.3 CMOS Technology

---

CMOS is the dominant integrated circuit technology. In this section we will introduce some basic concepts of CMOS to understand why it is so widespread and some of the challenges introduced by the inherent characteristics of CMOS.

### 1.3.1 Power Consumption

*power consumption  
constraints*

The huge chips that can be fabricated today are possible only because of the relatively tiny consumption of CMOS circuits. Power consumption is critical at the chip level because much of the power is dissipated as heat, and chips have limited heat dissipation capacity. Even if the system in which a chip is placed can supply large amounts of power, most chips are packaged to dissipate fewer than 10 to 15 Watts of power before they suffer permanent damage (though some chips dissipate well over 50 Watts thanks to special packaging). The power consumption of a logic circuit can, in the worst case, limit the number transistors we can effectively put on a single chip.

Limiting the number of transistors per chip changes system design in several ways. Most obviously, it increases the physical size of a system. Using high-powered circuits also increases power supply and cooling requirements. A more subtle effect is caused by the fact that the time required to transmit a signal between chips is much larger than the time required to send the same signal between two transistors on the same chip; as a result, some of the advantage of using a higher-speed circuit family is lost. Another subtle effect of decreasing the level of integration is that the electrical design of multi-chip systems is more complex: microscopic wires on-chip exhibit parasitic resistance and capacitance, while macroscopic wires between chips have capacitance and inductance, which can cause a number of ringing effects that are much harder to analyze.

The close relationship between power consumption and heat makes low-power design techniques important knowledge for every CMOS designer. Of course, low-energy design is especially important in battery-operated systems like cellular telephones. Energy, in contrast, must be saved by avoiding unnecessary work. We will see throughout the rest of this book that minimizing power and energy consumption requires careful attention to detail at every level of abstraction, from system architecture down to layout.

---

---

As CMOS features become smaller, additional power consumption mechanisms come into play. Traditional CMOS consumes power when signals change but consumes only negligible power when idle. In modern CMOS, leakage mechanisms start to drain current even when signals are idle. In the smallest geometry processes, leakage power consumption can be larger than dynamic power consumption. We must introduce new design techniques to combat leakage power.

### 1.3.2 Design and Testability

#### *design verification*

Our ability to build large chips of unlimited variety introduces the problem of checking whether those chips have been manufactured correctly. Designers accept the need to **verify** or **validate** their designs to make sure that the circuits perform the specified function. (Some people use the terms *verification* and *validation* interchangeably; a finer distinction reserves verification for formal proofs of correctness, leaving validation to mean any technique which increases confidence in correctness, such as simulation.) Chip designs are simulated to ensure that the chip's circuits compute the proper functions to a sequence of inputs chosen to exercise the chip.

#### *manufacturing test*

But each chip that comes off the manufacturing line must also undergo **manufacturing test**—the chip must be exercised to demonstrate that no manufacturing defects rendered the chip useless. Because IC manufacturing tends to introduce certain types of defects and because we want to minimize the time required to test each chip, we can't just use the input sequences created for design verification to perform manufacturing test. Each chip must be designed to be fully and easily testable. Finding out that a chip is bad only after you have plugged it into a system is annoying at best and dangerous at worst. Customers are unlikely to keep using manufacturers who regularly supply bad chips.

Defects introduced during manufacturing range from the catastrophic—contamination that destroys every transistor on the wafer—to the subtle—a single broken wire or a crystalline defect that kills only one transistor. While some bad chips can be found very easily, each chip must be thoroughly tested to find even subtle flaws that produce erroneous results only occasionally. Tests designed to exercise functionality and expose design bugs don't always uncover manufacturing defects. We use fault models to identify potential manufacturing problems and determine how they affect the chip's operation. The most common fault model is stuck-at-0/1: the defect causes a logic gate's output to be always 0 (or 1), independent of the gate's input values. We can often determine whether a logic gate's output is stuck even if we can't directly

observe its outputs or control its inputs. We can generate a good set of manufacturing tests for the chip by assuming each logic gate's output is stuck at 0 (then 1) and finding an input to the chip which causes different outputs when the fault is present or absent. (Both the stuck-at-0/1 fault model and the assumption that faults occur only one at a time are simplifications, but they often are good enough to give good rejection of faulty chips.)

*testability as a design process*

Unfortunately, not all chip designs are equally testable. Some faults may require long input sequences to expose; other faults may not be testable at all, even though they cause chip malfunctions that aren't covered by the fault model. Traditionally, chip designers have ignored testability problems, leaving them to a separate test engineer who must find a set of inputs to adequately test the chip. If the test engineer can't change the chip design to fix testability problems, his or her job becomes both difficult and unpleasant. The result is often poorly tested chips whose manufacturing problems are found only after the customer has plugged them into a system. Companies now recognize that the only way to deliver high-quality chips to customers is to make the chip designer responsible for testing, just as the designer is responsible for making the chip run at the required speed. Testability problems can often be fixed easily early in the design process at relatively little cost in area and performance. But modern designers must understand testability requirements, analysis techniques which identify hard-to-test sections of the design, and design techniques which improve testability.

### 1.3.3 Reliability

*reliability is a lifetime problem*

Earlier generations of VLSI technology were robust enough that testing chips at manufacturing time was sufficient to identify working parts—a chip either worked or it didn't. In today's nanometer-scale technologies, the problem of determining whether a chip works is more complex. A number of mechanisms can cause transient failures that cause occasional problems but are not repeatable. Some other failure mechanisms, like overheating, cause permanent failures but only after the chip has operated for some time. And more complex manufacturing problems cause problems that are harder to diagnose and may affect performance rather than functionality.

*design-for-manufacturability*

A number of techniques, referred to as **design-for-manufacturability** or **design-for-yield**, are in use today to improve the reliability of chips that come off the manufacturing line. We can make chips more reliable by designing circuits and architectures that reduce design stresses and check for problems. For example, heat is one major

cause of chip failure. Proper power management circuitry can reduce the chip's heat dissipation and reduce the damage caused by overheating. We also need to change the way we design chips. Some of the convenient levels of abstraction that served us well in earlier technologies are no longer entirely appropriate in nanometer technologies. We need to check more thoroughly and be willing to solve reliability problems by modifying design decisions made earlier.

---

## 1.4 Integrated Circuit Design Techniques

---

To make use of the flood of transistors given to us by Moore's Law, we must design large, complex chips quickly. The obstacle to making large chips work correctly is complexity—many interesting ideas for chips have died in the swamp of details that must be made correct before the chip actually works. Integrated circuit design is hard because designers must juggle several different problems:

- **Multiple levels of abstraction.** IC design requires refining an idea through many levels of detail. Starting from a specification of what the chip must do, the designer must create an architecture which performs the required function, expand the architecture into a logic design, and further expand the logic design into a layout like the one in Figure 1-2. As you will learn by the end of this book, the specification-to-layout design process is a lot of work.
  - **Multiple and conflicting costs.** In addition to drawing a design through many levels of detail, the designer must also take into account costs—not dollar costs, but criteria by which the quality of the design is judged. One critical cost is the speed at which the chip runs. Two architectures that execute the same function (multiplication, for example) may run at very different speeds. We will see that chip area is another critical design cost: the cost of manufacturing a chip is exponentially related to its area, and chips much larger than  $1 \text{ cm}^2$  cannot be manufactured at all. Furthermore, if multiple cost criteria—such as area and speed requirements—must be satisfied, many design decisions will improve one cost metric at the expense of the other. Design is dominated by the process of balancing conflicting constraints.
  - **Short design time.** In an ideal world, a designer would have time to contemplate the effect of a design decision. We do not, however, live in an ideal world. Chips which appear too late may make little or no
- 
-

money because competitors have snatched market share. Therefore, designers are under pressure to design chips as quickly as possible. Design time is especially tight in application-specific IC design, where only a few weeks may be available to turn a concept into a working ASIC.


Designers have developed two techniques to eliminate unnecessary detail: **hierarchical design** and **design abstraction**. Designers also make liberal use of computer-aided design tools to analyze and synthesize the design.

### 1.4.1 Hierarchical Design

*divide-and-conquer*


Hierarchical design is commonly used in programming: a procedure is written not as a huge list of primitive statements but as calls to simpler procedures. Each procedure breaks down the task into smaller operations until each step is refined into a procedure simple enough to be written directly. This technique is commonly known as **divide-and-conquer**—the procedure’s complexity is conquered by recursively breaking it down into manageable pieces.

**Figure 1-4** Pins on a component.

 


*components*

Chip designers divide and conquer by breaking the chip into a hierarchy of components. As shown in Figure 1-4, a component consists of a **body** and a number of **pins**—this full adder has pins **a**, **b**, **cin**, **cout**, and **sum**. If we consider this full adder the definition of a **type**, we can make many **instances** of this type. Repeating commonly used components is very useful, for example, in building an  $n$ -bit adder from  $n$  full adders. We typically give each component instance a **name**. Since all components of the same type have the same pins, we refer to the pins on a particular component by giving the component instance name and pin name together; separating the instance and pin names by a dot is common practice. If we have two full adders, *add1* and *add2*, we can refer to *add1.sum* and *add2.sum* as distinct **terminals** (where a terminal is a component-pin pair).

 

**Figure 1-5** A hierarchical logic design.

**Figure 1-6**  
A component hierarchy.

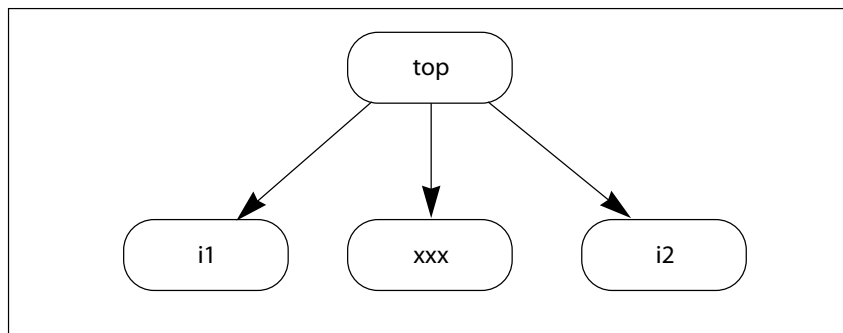

*net lists*

We can list the electrical connections which make up a circuit in either of two equivalent ways: a **net list** or a **component list**. A net list gives, for each net, the terminals connected to that net. Here is a net list for the top component of Figure 1-5:

```
net1: top.in1 i1.in
net2: i1.out xxx.B
topin1: top.n1 xxx.xin1
topin2: top.n2 xxx.xin2
botin1: top.n3 xxx.xin3
net3: xxx.out i2.in
outnet: i2.out top.out
```

A component list gives, for each component, the net attached to each pin. Here is a component list version of the same circuit:

```

top: in1=net1 n1=topin1 n2=topin2 n3=topin3 out=outnet
i1: in=net1 out=net2
xxx: xin1=topin1 xin2=topin2 xin3=botin1 B=net2
out=net3
i2: in=net3 out=outnet

```

Given one form of connectivity description, we can always transform it into the other form. Which format is used depends on the application—some searches are best performed net-by-net and others component-by-component. As an abuse of terminology, any file which describes electrical connectivity is usually called a **netlist file**, even if it is in component list format.

As shown in Figure 1-5, a logic design can be recursively broken into components, each of which is composed of smaller components until the design is described in terms of logic gates and transistors. In this figure, we have shown the type and instance as **instance(type)**; there are two components of type A. Component ownership forms a hierarchy. The component hierarchy of Figure 1-5 is shown in Figure 1-6. Each rounded box represents a component; an arrow from one box to another shows that the component pointed to is an element in the component which points to it. We may need to refer to several instance names to differentiate components. In this case, we may refer to either *top/i1* or *top/i2*, where we trace the component ownership from the most highest-level component and separate component names by slashes (/). (The resemblance of this naming scheme to UNIX file names is intentional—many design tools use files and directories to model component hierarchies.)

#### *components as black boxes*

Each component is used as a black box—to understand how the system works, we only have to know each component's input-output behavior, not how that behavior is implemented inside the box. To design each black box, we build it out of smaller, simpler black boxes. The internals of each type define its behavior in terms of the components used to build it. If we know the behavior of our primitive components, such as transistors, we can infer the behavior of any hierarchically-described component.

People can much more easily understand a 100,000,000-transistor hierarchical design than the same design expressed directly as ten million transistors wired together. The hierarchical design helps you organize your thinking—the hierarchy organizes the function of a large number of transistors into a particular, easy-to-summarize function. Hierarchical design also makes it easier to reuse pieces of chips, either by modifying an old design to perform added functions or by using one component for a new purpose.

### 1.4.2 Design Abstraction

#### *levels of modeling*

Design abstraction is critical to hardware system design. Hardware designers use multiple levels of design abstraction to manage the design process and ensure that they meet major design goals, such as speed and power consumption. The simplest example of a design abstraction is the logic gate. A logic gate is a simplification of the nonlinear circuit used to build the gate: the logic gate accepts binary Boolean values. Some design tasks, such as accurate delay calculation, are hard or impossible when cast in terms of logic gates. However, other design tasks, such as logic optimization, are too cumbersome to be done on the circuit. We choose the design abstraction that is best suited to the design task.

We may also use higher abstractions to make first-cut decisions that are later refined using more detailed models: we often, for example, optimize logic using simple delay calculations, then refine the logic design using detailed circuit information. Design abstraction and hierarchical design aren't the same thing. A design hierarchy uses components at the same level of abstraction—an architecture built from Boolean logic functions, for example—and each level of the hierarchy adds complexity by adding components. The number of components may not change as it is recast to a lower level of abstraction—the added complexity comes from the more sophisticated behavior of those components.

The next example illustrates the large number of abstractions we can create for a very simple circuit.




---

 **Example 1-2**  
**Layout and its**  
**abstractions**

Layout is the lowest level of design abstraction for VLSI. The layout is sent directly to manufacturing to guide the patterning of the circuits. The configuration of rectangles in the layout determines the circuit topology and the characteristics of the components. However, the layout of even a simple circuit is sufficiently complex that we want to introduce more abstract representations that help us concentrate on certain key details.

Here is a layout for a simple circuit known as a dynamic latch:




This layout contains rectangles that define the transistors, wires, and vias which connect the wires. The rectangles are drawn on several different layers corresponding to distinct layers of material or process steps in the integrated circuit.

---


---

 Here is an abstraction for that layout: a stick diagram, which is a sketch of a layout:




This stick diagram has the same basic structure as the layout, but the rectangles in the layout are abstracted here as lines. Different line styles represent different layers of material: metal, diffusion, etc. Transistors are formed at the intersection a line representing polysilicon with either a n-type or p-type diffusion line. The heavy dots represent vias, which connect material on two different layers. This abstraction conveys some physical information but not as much as the layout—the stick diagram reflects the relative positions of components, but not their absolute positions or their sizes.

 Going one more step up the abstraction hierarchy, we can draw a transistor-level schematic:



This formulation is not intended to describe the physical layout of the circuit at all—though the placement of transistors may resemble the organization of the transistors in the layout, that is a matter of convenience. The intent of the schematic is to describe the major electrical components and their interconnections.

 We can go one step higher in the abstraction hierarchy to draw a **mixed schematic**:




This is called mixed because it is built from components at different levels of abstraction: not only transistors, but also an inverter, which is in turn built from transistors. The added abstraction of the inverter helps to clarify the organization of the circuit.


The next example shows how a slightly more complex hardware design is built up from circuit to complex logic.
 
### Example 1-3 Digital logic abstractions

A transistor circuit for an inverter is relatively small. We can determine its behavior over time, representing input and output values as continuous voltages to accurately determine its delay:




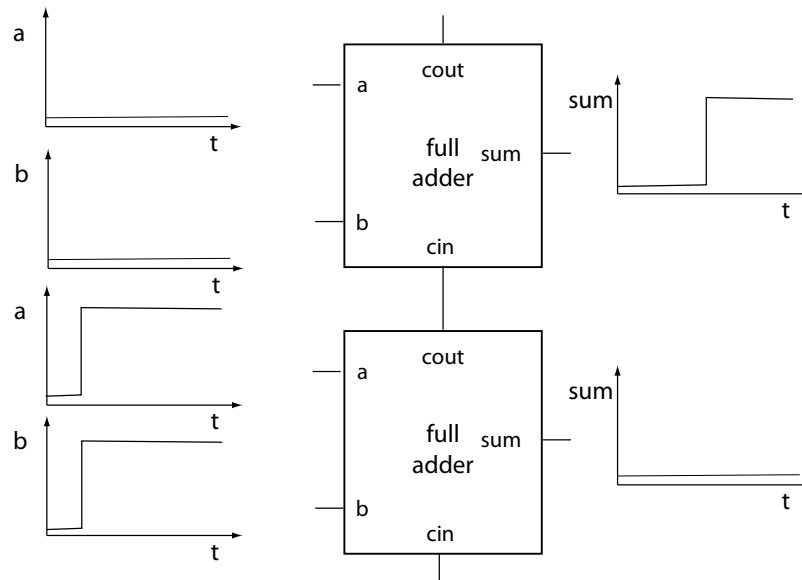We can use transistors to build more complex functions like the full adder. At this point, we often simplify the circuit behavior to 0 and 1 values which may be delayed in continuous time:



As circuits get bigger, it becomes harder to figure out their continuous time behavior. However, by making reasonable assumptions, we can determine approximate delays through circuits like adders. Since we are interested in the delay through adders, the ability to make simplifying assumptions and calculate reasonable delay estimates is very important.

 When designing large register-transfer systems, such as data paths, we may abstract one more level to generic adders:



At this point, since we don't know how the adders are built, we don't have any delay information. These components are pure combinational elements—they produce an output value given an input value. The

adder abstraction helps us concentrate on the proper function before we worry about the details of performance.


### *design abstractions*

Figure 1-7 shows a typical design abstraction ladder for digital systems:

- **Specification.** The customer specifies what the chip should do, how fast it should run, etc. A specification is almost always incomplete—it is a set of requirements, not a design.
- **Behavior.** The behavioral description is much more precise than the specification. Specifications are usually written in English, while behavior is generally modeled as some sort of executable program.
- **Register-transfer.** The system’s time behavior is fully-specified—we know the allowed input and output values on every clock cycle—but the logic isn’t specified as gates. The system is specified as Boolean functions stored in abstract memory elements. Only the vaguest delay and area estimates can be made from the Boolean logic functions.
- **Logic.** The system is designed in terms of Boolean logic gates, latches, and flip-flops. We know a lot about the structure of the system but still cannot make extremely accurate delay calculations.
- **Circuit.** The system is implemented as transistors.
- **Layout.** The final design for fabrication. Parasitic resistance and capacitance can be extracted from the layout to add to the circuit description for more accurate simulation.

### *top-down and bottom-up design*

Design always requires working down from the top of the abstraction hierarchy and up from the least abstract description. Obviously, work must begin by adding detail to the abstraction—**top-down** design adds functional detail. But top-down design decisions are made with limited information: there may be several alternative designs at each level of abstraction; we want to choose the candidate which best fits our speed, area, and power requirements. We often cannot accurately judge those costs until we have an initial design. **Bottom-up** analysis and design percolates cost information back to higher-levels of abstraction; for instance, we may use more accurate delay information from the circuit design to redesign the logic. Experience will help you judge costs before you complete the implementation, but most designs require cycles of top-down design followed by bottom-up redesign.

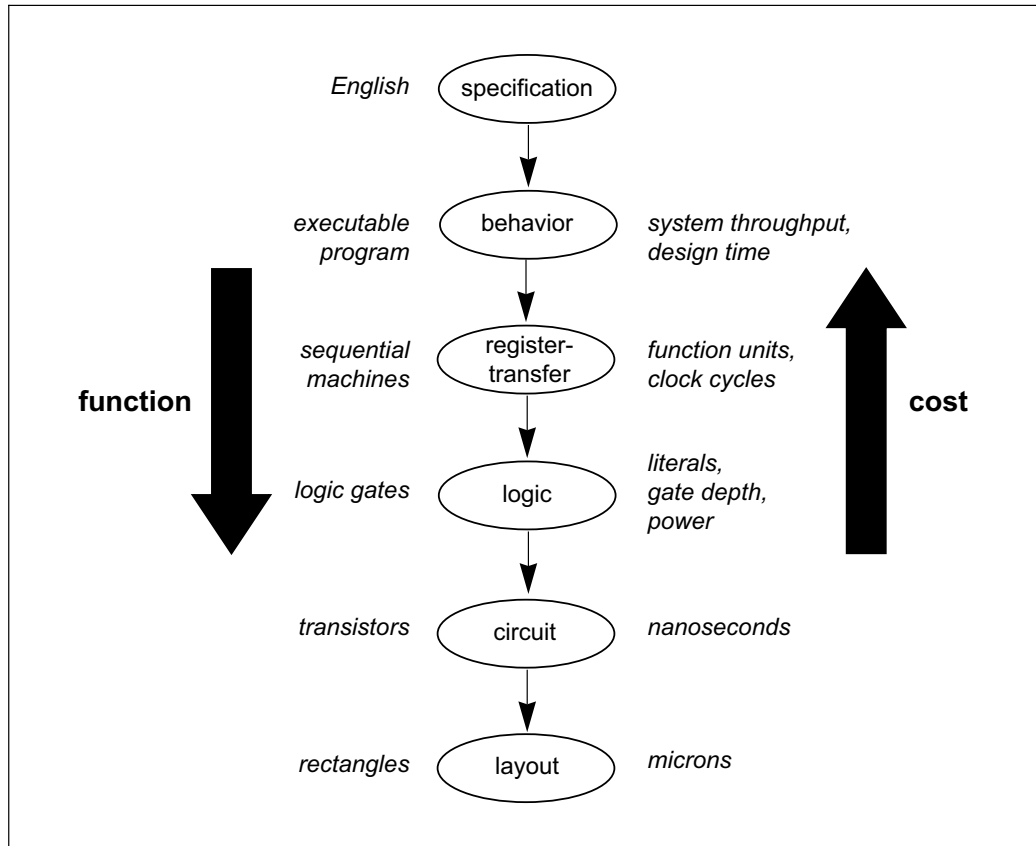

**Figure 1-7** A hierarchy of design abstractions for integrated circuits.

### 1.4.3 Computer-Aided Design

#### *CAD tools*

The only realistic way to design chips given performance and design time constraints is to automate the design process, using **computer-aided design (CAD)** tools which automate parts of the design process. Using computers to automate design, when done correctly, actually helps us solve all three problems: dealing with multiple levels of abstraction is easier when you are not absorbed in the details of a particular design step; computer programs, because they are more methodical, can do a better job of analyzing cost trade-offs; and, when given a well-defined task, computers can work much more quickly than humans.

<i>design entry</i>	Computer-aided design tools can be categorized by the design task they handle. The simplest of CAD tool handles design entry—for example, an interactive schematic drawing package. Design entry tools capture a design in machine-readable form for use by other programs, and they often allow easier modification of a design, but they don't do any real design work.
<i>analysis and verification</i>	Analysis and verification tools are more powerful. The Spice circuit simulator, for example, solves the differential equations which govern how the circuit responds to an input waveform over time. Such a program doesn't tell us how to change the circuit to make it do what we want, but many analysis tasks are too difficult to perform manually.
<i>synthesis</i>	Synthesis tools actually create a design at a lower level of abstraction from a higher level description. Some layout synthesis programs can synthesize a layout from a circuit description like that in Figure 1-2. Using computers for design is not a panacea. Computer programs cannot now, nor are they ever likely to be able to transform marketing brochures directly into finished IC designs. Designers will always be necessary to find creative designs and to perform design tasks which are too subtle to be left to algorithms.  Both hierarchical design and design abstraction are as important to CAD tools as they are to humans—the most powerful synthesis and analysis tools operate on a very restricted design model. CAD tools can help us immensely with pieces of the design task, but algorithms that have the detailed knowledge required to solve one design problem usually do not have the broad range of data required to balance broad requirements.
<i>tools as aids</i>	CAD tools must be used judiciously by a human designer to be most effective. Nonetheless, CAD tools are an essential part of the future of IC design because they are the only way to manage the complexity of designing large integrated circuits. Manual design of a hundred-million transistor chip, or even a 100,000 transistor chip, quickly overwhelms the designer with decisions. Not all decisions are equally important—some may have only a minor effect on chip size and speed while others may profoundly change the chip's costs. By concentrating on the wrong decisions, a designer may cause problems that are not easily correctable later. CAD tools, by automating parts of the design process, help the designer eliminate mundane decisions quickly and concentrate on the make-or-break problems posed by the chip.  For example, long wires can introduce excessive delay, increase power consumption, and create opportunities for crosstalk. Such problems can be found by a program that analyzes delays through the chip, but when designing a chip by hand, it may be easy to miss this single connection,

and the error will not be found until the chip comes back from fabrication. CAD tools are particularly important for evaluating complex situations in which solving one problem creates other problems—for example, making one wire shorter makes other wires longer. When two constraints compete, solutions to problems may not be so easy. Making one part of the design faster may, for example, make another part of the design unacceptably large and slow. CAD tools help us solve these problems with analytical methods to evaluate the cost of decisions and synthesis methods that let us quickly construct a candidate solution to a problem. Evaluation of candidate designs is critical to designing systems to satisfy multiple costs because optimizing a complete system cannot be done simply by optimizing all the parts individually—making each part in a chip run as fast as possible in isolation by no means ensures that the entire chip will run as fast as possible. Using CAD tools to propose and analyze solutions to problems lets us examine much larger problems than is possible by hand.

---

## 1.5 IP-Based Design

---

In this section, we will look at how **intellectual property** (IP) is used in chip design. All designers will either design IP for others or use IP in their own designs. IP-based design has different aspects, depending on the role of the designer and whether IP is being produced or used. We will start with the motivation for IP-based design, then look at some different types of IP, and then consider the IP-based design process.

### 1.5.1 Why IP?

Intellectual property is a dominant mode of chip design today simply because of the scale of chips that we can produce. Even modest chips contain millions of transistors and we can now design two billion transistor chips [Fil08]. We passed the point long ago when even a large team can design an entire chip from scratch.

#### *IP history*

An early form of IP was the standard cell, which dates back to the early 1970s. Standard cells are designed to abut together in a fixed-height row of cells and used by a placement-and-routing program. Standard cell design was created to automate the design of application-specific integrated circuits (ASICs) that were destined for low-volume manufacturing. In such cases, the cost of design exceeded the

---

---



cost of manufacturing, so a design technique that traded some area for lower design costs was acceptable. Standard cells are still used even in large custom designs for subsystems, like control, where human designers have a harder time finding optimizations.

Today, IP components include the entire range of modules, as we will see in the next section, ranging from standard cells through I/O devices and CPUs. Chip designers need complex IP components because modern levels of integration allow chips to be complete systems, not just components of systems. When designing a system-on-chip, much of the added value comes from the architect's ability to identify the right combination of components to put on the chip. Many of those components are standardized—either they are based on open standards or they are licensed from IP providers who own a standard (such as an instruction set). In some cases, the chip designers may not have the ability to design an equivalent for the IP component themselves without violating patents or other legal problems. One generation's chip often becomes the next technology generation's IP component as more and more elements are integrated onto a single chip. IP-based design is crucial even in the microprocessor world, where a chip consists entirely of one or more CPUs and cache. Several different versions of a processor family are needed to fill the product space; designing the processor as reusable IP makes much more sense than starting from scratch each time. And as multicore processors come to dominate the microprocessor world, processors must be replicated on the die.

### 1.5.2 Types of IP

*intellectual property as components*

A system-on-chip is not useful unless it can be designed in a reasonable amount of time. If all the subsystems of an SoC had to be designed by hand, most SoCs would not be ready in time to make use of the manufacturing process for which they were designed. SoC design teams often make use of **IP blocks** in order to improve their productivity. An IP block is a pre-designed component that can be used in a larger design. There are two major types of IP:

- **Hard IP** comes as a pre-designed layout. Because a full layout is available, the block's size, performance, and power consumption can be accurately measured.
- **Soft IP** comes as a synthesizable module in a hardware description language such as Verilog or VHDL. Soft IP can be more easily targeted to new technologies but it is harder to characterize and may not be as small or as fast as hard IP.

## 1.5 IP-Based Design

35

*hard IP*

The simplest and earliest example of a hard IP block is the standard cell, which is a gate-level IP component. Hard IP components are designed for a particular manufacturing process and its design rules. If the hard IP block is to be used in a different process, it must be redesigned.

Hard IP blocks must conform to a variety of standards relating to the physical and electrical characteristics of the process and of the other blocks designed in that process. A given process may dictate that certain types of signals appear on certain layers; an IP library may further dictate that certain types of signals appear at specific positions on the block. The block must also be defined to an electrical standard—it must be able to drive a certain load at some specified delay, for example.

Most important hard IP blocks that are sold by vendors are **qualified** for a given process. The qualification procedure consists of fabricating the IP block in the process and then testing the resulting chips. Qualification assures the customer that the block works functionally, that it meets its stated performance goals, etc.

*soft IP*

Soft IP is designed to be implemented using logic synthesis and place-and-route tools. As such, it is more easily targeted to a new manufacturing process, perhaps at some cost in performance, power, and area. A surprising number of large blocks, including CPUs, are delivered only as soft IP. The design time savings of soft IP often outweigh the cost and performance savings, even for such large IP blocks.

Although details of the physical interface to the IP block can be handled by the design flow, a soft IP block must still be designed to implement an interface that allows it to be connected to other blocks on the chip. In some cases, a block's interface may need to be changed—for example, if a different type of bus is used to connect the blocks. The logic used to adapt the interface is often called a **wrapper**.

Because a soft IP block is delivered in synthesizable form, it is more easily stolen than a hard IP block. Soft IP vendors may tag their blocks to more easily trace their source.

### 1.5.3 IP Across the Design Hierarchy

*standard cells*

The standard cell is one of the earliest examples of IP. A family of standard cells is designed together both to provide a useful set of logical functions and to have compatible layouts. The cells can be placed side-by-side in any order. The signals between the cells are then wired using computer-aided design tools. Standard cells are still widely used today.

---

---

*register-transfer modules*

Larger modules, like those used in register-transfer logic design, are also good candidates for encapsulation as IP. Many of these components are bit-oriented, which means that one bit of the function can be designed and then be replicated to create an  $n$ -bit component. Adders, ALUs, and even complete datapaths make good IP components.

*memories*

Memory is an important category of IP. Memory circuits are analog designs that must be carefully crafted. The memory cells themselves are necessarily delivered as hard IP for all but the simplest of memories. However, much of the complexity of memory IP comes from their use in systems. Memories may be needed in many different sizes and aspect ratios; generators are often used to generate a specific memory configuration. Memories also require a great deal of peripheral circuitry to be useful in systems. Memory controllers, bus interfaces, and other logic is also critical to the system interface to the memory core. Some of this associated logic may be delivered as soft IP.

*CPUs*

One critical type of IP for SoC design is the **embedded CPU**. An embedded processor can be programmed to perform certain functions on the chip, much as an embedded processor is used in a board design. Embedded CPUs have been used on chips for many years: early embedded processors were mostly 8-bit CPUs used for basic sequencing; today, powerful 32-bit CPUs can be embedded on a system-on-chip. The fact that not just the CPU but also its cache, main memory, and I/O devices can be integrated on the same chip make embedded processors especially attractive.

Embedded CPUs are increasingly popular on SoCs for several reasons. First, many sophisticated applications are best implemented in software. Multimedia applications like MP3 audio and MPEG video are examples of functions that are difficult to implement without some amount of embedded software. Second, many complex systems must run embedded software in order to implement their applications. For example, digital audio systems must run digital rights management software that is available only in binary form. Many systems-on-chips also use Linux, Windows CE, or some other OS to provide file management and networking. Third, embedded CPUs help decrease design time. Because the embedded processor is a relatively well-understood component, the design of the software can be somewhat decoupled from the hardware design.

Some CPUs are delivered as hard IP. However, the majority of CPUs are delivered as soft IP. The CPU's functionality may be fixed. A **configurable CPU** is one whose features are selected by the designer; a CPU is then created to match the specs, typically using a generator. A configu-

## 1.5 IP-Based Design

37

	vable CPU may provide options for custom instructions, registers, bus interfaces, or almost any aspect of the CPU.
<i>buses</i>	Buses (and other forms of system interconnect) are essential for CPU-oriented designs. The bus connects the processing elements, memories, and devices. The bus interface is a natural boundary for the interfaces to be implemented by IP components.  Because the bus connects to a large majority of the IP components on the SoC, many IP providers must be able to use the bus standard. One example of an open bus standard is the AMBA protocol ( <a href="http://www.amba.com">http://www.amba.com</a> ).
<i>I/O devices</i>	SoCs include many I/O devices. Because I/O devices are themselves usually defined by standards, they are natural candidates for embodiment as IP. I/O devices are often delivered as soft IP because they must be ported to many technologies and because they often don't require the fastest implementation.

## 1.5.4 The IP Life Cycle


	IP differs from custom chip design in that it is designed well before it is used. The life cycle of IP components may stretch over years from the time the IP modules are first created, through several generations of technology, to their final retirement.
<i>IP life cycle</i>	Figure 1-8 shows the IP life cycle in two stages: IP creation and IP use. Creation starts with a specification and goes through all the normal design processes, using hardware description languages and, in the case of hard IP, layout design tools. However, the IP modules go through more extensive testing since they will be used many times. IP creation results in the IP modules themselves, plus documentation and database descriptions. The database information is used by design tools for layout, performance analysis, <i>etc.</i> All this information feeds into standard chip design processes.

## 1.5.5 Creating IP

<i>specifying IP</i>	When we create intellectual property, we must first specify the module we want to design. Specification is a challenge because it must be done in cooperation with the potential users of the IP. If we do not start with a specification that is likely to attract enough users, then there is no point in designing the IP block.
----------------------	---

---

---

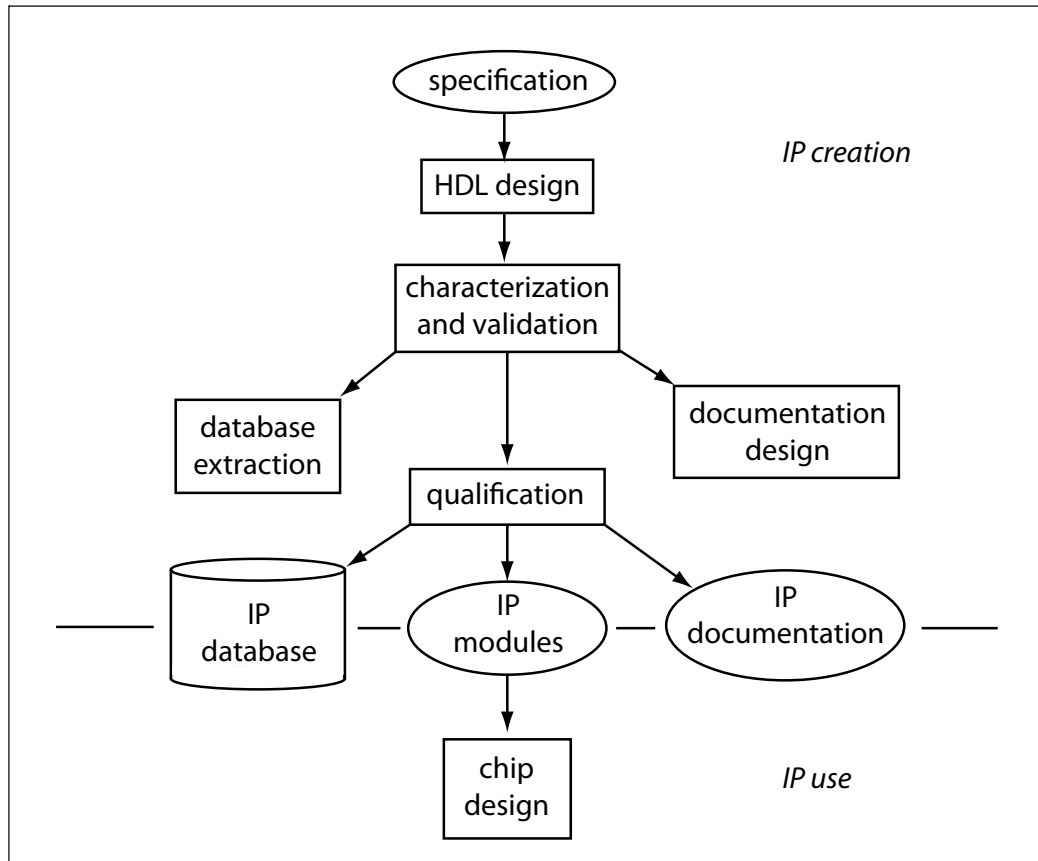

**Figure 1-8** The IP life cycle.

The specification must cover many aspects of the final design:

- whether the module will be hard or soft IP;
- function;
- performance, not just average case but at various combinations of process parameters;
- power consumption;
- what types of process features are required to support the module.

*design methodologies*

Once we have decided what to design, we need to follow design methodologies that ensure we will end up with an implementation that meets

## 1.5 IP-Based Design

39

our specification. Our design methodology must also support the extra work that we have to do in order to reuse our IP modules. In general, we need to test modules more thoroughly at each stage in the design process and run a rigorous set of tests. The basic form of the tests will be determined by the ways in which the IP module will be used.

*documentation*

Documentation is important in any design but critical to a design that will be widely disseminated. The IP block must be documented in sufficient detail that others can use it in a variety of circumstances; that documentation must go beyond functionality to circuit, *etc.* The nature of the documentation required for an IP module may be dictated by the organization that will distribute the IP.

*databases*

In order to be useful, the module must be entered into databases used by various tools: place-and-route, timing analysis, *etc.* A great deal of information is required to describe the module for all these tools. Specialized methodologies are generally used to generate the required database descriptions from the module implementations.

*characterization*

An IP module must be shown to provide a given performance and power level not just in the average case, but in a variety of conditions: variations in fabrication process parameters, temperature variations, *etc.* The process of determining the operational characteristics of a module over a range of parameters is known as **characterization**. Characterization requires extensive simulation at the circuit level and other levels. Each simulation is at one set of parameters; these parameter sets must be chosen to adequately cover the space of variations that must be verified.

*qualification*

A step beyond characterization is **qualification**, in which the module is fabricated and physically tested. This qualification exercise is used to show that the module works in one process—if you want to use the module in another process, then you must fabricate it again on the new process.

## 1.5.6 Using IP

*sources of IP*

IP blocks come from a variety of sources. A number of vendors sell IP blocks. Some IP vendors are large companies; in other cases, individuals may sell IP. The OpenCores Web site (<http://www.opencores.org>) provides a number of IP blocks that are available under open source licensing.

*identifying candidate IP modules*

In order to find IP modules that will be useful in your design, you should look at all the elements of the specification of the IP blocks. Functionality is certainly an easy filter to rule out many modules, but

you also have to check the power/performance trade-offs of the cells, what processes they are designed for, *etc.*

#### *acquiring IP*

IP modules can come from a variety of sources: foundries, independent IP vendors, or shareware. A foundry often provides basic IP—standard cells, I/O pads, *etc.*—that are optimized for their process. Some foundries may require payment for their IP, while others may not. (For example, a fab line may provide many cells for their process in order to attract customers.) Independent of whether the modules are paid for, the vendor may require the user to agree to certain terms of usage, such as whether they will reveal the design to others. Acquiring IP takes time, so the IP acquisition process should be factored into the total chip design time.

---

## 1.6 A Look into the Future

---

Moore's Law is likely to hold for quite some time to come. In a short amount of time from this writing, we will be able to design and fabricate in large quantities circuits with several hundred million transistors. We are already in the age of deep-submicron VLSI—the typical fabrication process constructs transistors that are much smaller than one micron in size. As we move toward even smaller transistors and even more transistors per chip, several types of challenges must be faced.

#### *interconnect*

The first challenge is interconnect. In the early days of the VLSI era, wires were recognized to be important because they occupied valuable chip area, but properly-designed wiring did not pose a bottleneck to performance. Today, wires cannot be ignored—the delay through a wire can easily be longer than the delay through the gate driving it. And because the parasitic components of wires are so significant, crosstalk between signals on wires can cause major problems as well. Proper design methodologies and careful analysis are keys to taming the problems introduced by interconnect.

Another challenge is power consumption. Power consumption is a concern on every large chip because of the large amount of activity generated by so many transistors. Excessive power consumption can make a chip so hot that it becomes unreliable. Careful analysis of power consumption at all stages of design is essential for keeping power consumption within acceptable limits.

---

---

## 1.7 Summary

41

*reliability*

As we move into nanometer-scale VLSI, transistors become less reliable. Traditionally, we have relied on manufacturing to deliver enough perfect components. (There are some exceptions—for example, memories have used spare cells for quite some time.) However, both permanent and transient failures are becoming frequent enough that we must design VLSI systems that can tolerate imperfection. We must apply reliability techniques at all levels of abstraction—circuit, logic, and architecture—if we are to cost-effectively manage the transition to nanometer-scale technology.

*complexity*

And we must certainly face the challenge of design complexity as we start to be able to create complete systems-on-silicon. In about ten years, we will be able to fabricate chips with a billion transistors—a huge design task at all levels of abstraction, ranging from layout and circuit to architecture. Over the long run, VLSI designers will have to become even more skilled at programming as some fraction of the system is implemented as on-chip software. We will look at systems-on-chips in more detail in Chapter 8.

---

## 1.7 Summary

---

Integrated circuit manufacturing is a key technology—it makes possible a host of important, useful new devices. ICs help us make better digital systems because they are small, stingy with power, and cheap. However, the temptation to build ever more complex systems by cramming more functions onto chips leads to an enormous design problem. Integrated circuits are so complex that the only way to effectively design them is to use computers to automate parts of the design process, a situation not unlike that in Isaac Asimov's robot stories, where positronic brains are employed to design the next, more advanced generation of robot brains. But humans are not out of control of the design process—by giving up control of some details, you can obtain a clearer view of the broad horizon and avoid problems that don't lie exactly at your feet.

---

---



---

## 1.8 References

---

The data points in the Moore's Law chart of Figure 1-3 were taken from articles in the *IEEE Journal of Solid State Circuits* (JSSC) and from a 1967 survey article by Petritz [Pet67]. The October issue of JSSC is devoted each year to logic and memory—those articles describe state-of-the-art integrated circuits. Business magazines and newspapers, such as *The Wall Street Journal*, *Business Week*, *Fortune*, and *Forbes* provide thorough coverage of the semiconductor industry. Following business developments in the industry provides valuable insight into the economic forces which shape technical decisions.

---

## 1.9 Problems

---

Q1-1. Name a product in your home that does not include an integrated circuit.

Q1-2. Use data from the ITRS Web site (<http://www.itrs.net>) to plot feature size as a function of time.

Q1-3. Draw a block diagram for a four-bit counter using one-bit counters. Each one-bit adder is a primitive represented by a box; it has one input  $a$  and one output  $s$ .

- a) Draw the four-bit counter using four one-bit counters.
- b) Draw the four-bit counter by first drawing a two-bit counter built from one-bit counters, then using the two-bit counter as a component in the one-bit counter.

Q1-4. Briefly describe the relationship between these design abstractions:

- a) Circuit waveforms vs. digital signals.
  - b) Digital signals vs. binary numbers.
  - c) Logic gates vs. adders.
- 
-

# 2

## Fabrication and Devices

### Highlights:

Fabrication methods.


Transistor structures.

Characteristics of transistors and wires.

Design rules.

Layout design.

Reliability.

 

Cross-section of an n-type transistor (Figure 2-5).

---

## 2.1 Introduction

---

We will start our study of VLSI design by learning about transistors and wires and how they are fabricated. The basic properties of transistors are clearly important for logic design. Going beyond a minimally-functional logic circuit to a high-performance design requires the consideration of **parasitic circuit elements**—capacitance and resistance. Those parasitics are created as necessary by-products of the fabrication process which creates the wires and transistors, which gives us a very good reason to understand the basics of how integrated circuits are fabricated. We will also study the rules which must be obeyed when designing the masks used to fabricate a chip and the basics of layout design.

Our first step is to understand the basic fabrication techniques, which we will cover in described in Section 2.2. This material will describe how the basic structures for transistors and wires are made. We will then study transistors and wires, both as integrated structures and as circuit elements, in Section 2.3 and Section 2.4, respectively. We will study design rules for layout in Section 2.5. We will discuss some physical sources of unreliable components in Section 2.6. Finally, we will introduce some basic concepts and tools for layout design in Section 2.7.

---

## 2.2 Fabrication Processes

---

### *example process*

We need to study fabrication processes and the design rules that govern layout. Examples are always helpful. We will use as our example the SCMOS rules, which have been defined by MOSIS, the MOS Implementation Service. (MOSIS is now an independent commercial service. Other organizations, such as EuroChip/EuroPractice in the European Community, VDEC in Japan, and CIC in Taiwan, serve educational VLSI needs in other countries.) SCMOS is unusual in that it is not a single fabrication process, but a collection of rules that hold for a family of processes. Using generic technology rules gives greater flexibility in choosing a manufacturer for your chips. It also means that the SCMOS technology is less aggressive than any particular fabrication process developed for some special purpose—some manufacturers may emphasize transistor switching speed, for example, while others emphasize the number of layers available for wiring.

---

---

Many important parameters depend on the particular technology. We will use as our example a 180 nm (0.18  $\mu\text{m}$ ) technology. We will also assume a power supply voltage of 1.2 V. This technology is advanced enough to be used for ASICs but does not introduce some of the complications of the most advanced processes.

### 2.2.1 Overview

#### *substrates*


A cross-section of an integrated circuit is shown in Figure 2-1. Integrated circuits are built on a silicon **substrate** provided by the wafer. Figure 2-2 shows a technician holding 300 mm a wafer. Wafer sizes have steadily increased over the years; larger wafers mean more chips per wafer and higher productivity.

#### *fabrication techniques*

Components are formed by a combination of processes:

- **doping** the substrate with impurities to create areas such as the n+ and p+ regions;
- adding or cutting away insulating glass (**silicon dioxide**, or  $\text{SiO}_2$ ) on top of the substrate;
- adding wires made of polycrystalline silicon (**polysilicon**, also known as **poly**) or metal, insulated from the substrate by  $\text{SiO}_2$ .

**Figure 2-1**  
Cross-section  
of an integrated  
circuit.

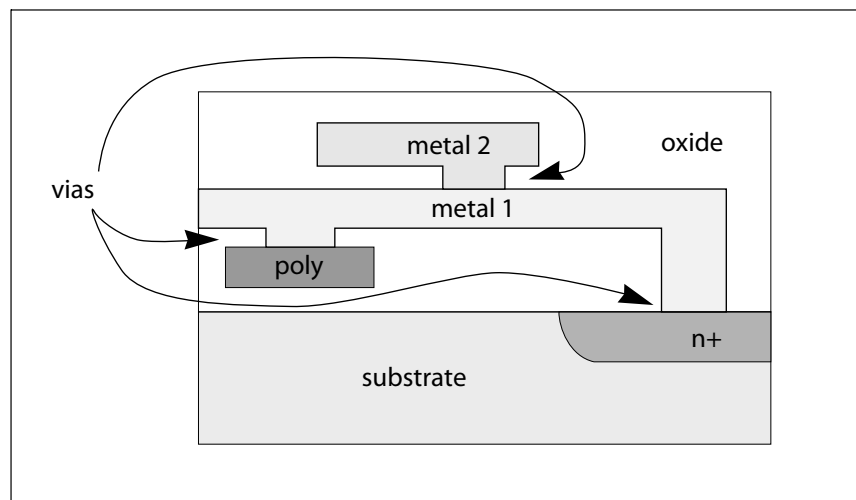

## 2.2 Fabrication Processes

47

*types of carriers*

A pure silicon substrate contains equal numbers of two types of electrical carriers: electrons and holes. While we cannot go into the details of device physics here, it is important to realize that the interplay between electrons and holes is what makes transistors work. The goal of doping is to create two types of regions in the substrate: an **n-type** region which contains primarily electrons and a **p-type** region which is dominated by holes. (Heavily doped regions are referred to as  $n^+$  and  $p^+$ .) Transistor action occurs at properly formed boundaries between n-type and p-type regions.



**Figure 2-2** A VLSI manufacturing line (courtesy IBM).

*other materials*

The n-type and p-type regions can be used to make wires as well as transistors, but polysilicon (which is also used to form transistor gates) and metal are the primary materials for wiring together transistors because of their superior electrical properties. There may be several levels of metal wiring to ensure that enough wires can be made to create all the

necessary connections. Several types of metal are used for interconnect. Aluminum, tungsten, and other metals are used for metal close to the silicon. Copper is a better conductor but it is a poison to semiconductors, so it is used only in higher layers. Glass insulation lets the wires be fabricated on top of the substrate using processes like those used to form transistors. The integration of wires with components, which eliminates the need to mechanically wire together components on the substrate, was one of the key inventions that made the integrated circuit feasible.

*size metrics*

The key figure of merit for a fabrication process is the size—more specifically, the channel length—of the smallest transistor it can manufacture. Transistor size helps determine both circuit speed and the amount of logic that can be put on a single chip. Fabrication technologies are usually identified by their minimum transistor length, so a process which can produce a transistor with a 180 nm minimum channel length is called a 180 nm process. When we discuss design rules, we will recast the on-chip dimensions to a scalable quantity  $\lambda$ . Our  $\lambda = 90$  nm CMOS process is also known as a 180 nm CMOS process; if  $\lambda$  is not referred to explicitly, the size of the process gives the minimum channel length.

### 2.2.2 Fabrication Steps


*patterning features*

Features are patterned on the wafer by a photolithographic process; the wafer is covered with light-sensitive material called **photoresist**, which is then exposed to light with the proper pattern. The patterns left by the photoresist after development can be used to control where  $\text{SiO}_2$  is grown or materials are placed on the surface of the wafer.

*masks*

A layout contains summary information about the patterns to be made on the wafer. Photolithographic processing steps are performed using **masks** which are created from the layout information supplied by the designer. In simple processes there is roughly one mask per layer in a layout, though in more complex processes some masks may be built from several layers while one layer in the layout may contribute to several masks. Figure 2-3 shows a simple layout and the mask used to form the polysilicon pattern.

**Figure 2-3** The relationship between layouts and fabrication masks.

 

*tubs*

Transistors are fabricated within regions called **tubs** or **wells**: an n-type transistor is built in a p-tub, and a p-type transistor is built in an n-tub. The wells prevent undesired conduction from the drain to the substrate. (Remember that the transistor type refers to the minority carrier which forms the inversion layer, so an n-type transistor pulls electrons out of a p-tub.)



There are three ways to form tubs in a substrate:

- start with a p-doped wafer and add n-tubs;
- start with an n-doped wafer and add p-tubs;
- start with an undoped wafer and add both n- and p-tubs.


CMOS processes were originally developed from nMOS processes, which use p-type wafers into which n-type transistors are added. However, the **twin-tub process**, which uses an undoped wafer, has become the most commonly used process because it produces tubs with better electrical characteristics. We will therefore use a twin-tub process as an example.

*fabrication steps*

Figure 2-4 illustrates important steps in a twin-tub process. Details can vary from process to process, but these steps are representative. The first step is to put tubs into the wafer at the appropriate places for the n-type and p-type wafers. Regions on the wafer are selectively doped by implanting ionized dopant atoms into the material, then heating the wafer to heal damage caused by ion implantation and further move the dopants by diffusion. The tub structure means that n-type and p-type wires cannot directly connect. Since the two diffusion wire types must exist in different type tubs, there is no way to build a via which can directly connect them. Connections must be made by a separate wire, usually metal, which runs over the tubs.

The next steps form an oxide covering of the wafer and the polysilicon wires. The oxide is formed in two steps: first, a thick field oxide is grown over the entire wafer. The field oxide is etched away in areas directly over transistors; a separate step grows a much thinner oxide which will form the insulator of the transistor gates. After the field and thin oxides have been grown, the polysilicon wires are formed by depositing polysilicon crystalline directly on the oxide.

Note that the polysilicon wires have been laid down before the diffusion wires were made—that order is critical to the success of MOS processing. Diffusion wires are laid down immediately after polysilicon deposition to create **self-aligned** transistors—the polysilicon masks the formation of diffusion wires in the transistor channel. For the transistor to work properly, there must be no gap between the ends of the source and drain diffusion regions and the start of the transistor gate. If the diffusion were laid down first with a hole left for the polysilicon to cover, it would be very difficult to hit the gap with a polysilicon wire unless the transistor were made very large. Self-aligned processing allows much smaller transistors to be built.

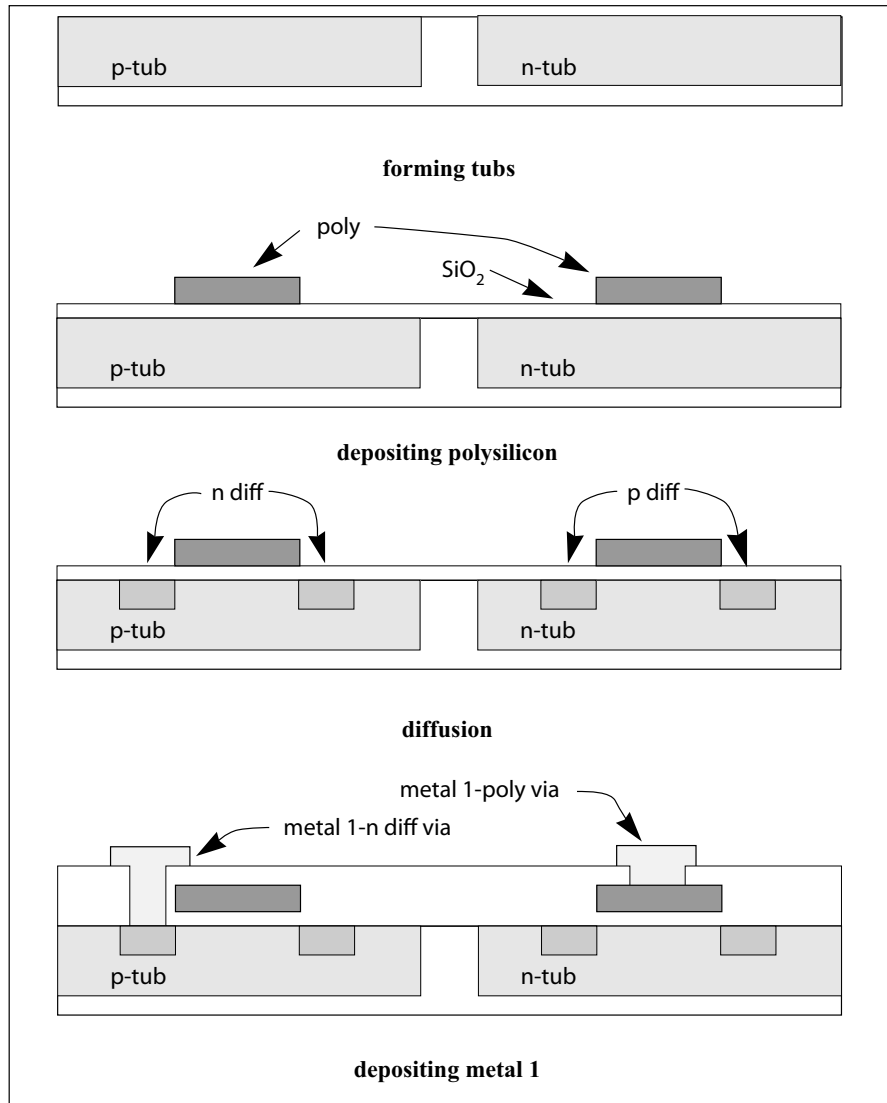

**Figure 2-4** Steps in processing a wafer.

After the diffusions are complete, another layer of oxide is deposited to insulate the polysilicon and metal wires. Aluminum has long been the dominant interconnect material, but copper has now moved into mass production. Copper is a much better conductor than aluminum, but even

trace amounts of it will destroy the properties of semiconductors. Chips with copper interconnect include a special protection layer between the substrate and the first layer of copper. That layer prevents the copper from entering the substrate during processing.

Holes are cut in the field oxide where vias to the substrate are desired. The metal 1 is then deposited where desired. The metal fills the cuts to make connections between layers. The metal 2 layer requires an additional oxidation/cut/deposition sequence. After all the important circuit features have been formed, the chip is covered with a final **passivation layer** of  $\text{SiO}_2$  to protect the chip from chemical contamination.

---

## 2.3 Transistors

---

In this section, we will consider transistors in detail. Based upon the structure of the transistor, we will develop electrical models for the transistor. Over the course of this section, we will start with a very simple model of a transistor and then add detail. We start in Section 2.3.1 with an introduction to the physical structure of a transistor and then develop a simple voltage-current model of the transistor in Section 2.3.2. We discuss transistor parasitics in Section 2.3.3. In Section 2.3.4 we consider latch-up, an important problem in transistor operation. Section 2.3.5 develops a more sophisticated model of the transistor. Section 2.3.6 looks at leakage currents, an important source of power dissipation, and Section 2.3.7 considers the thermal effects of leakage. Finally, Section 2.3.8 talks about Spice models of transistors used in circuit simulation.

### 2.3.1 Structure of the Transistor


*transistor cross-section*

Figure 2-5 shows the cross-section of an n-type MOS transistor. (The name MOS is an anachronism. The first such transistors, invented by Kahng and Atalla [Sze81] in 1960, used a metal wire for a gate, making the transistor a sandwich of metal, silicon dioxide, and the semiconductor substrate. Even though transistor gates are now made of polysilicon, the name MOS has stuck.) An n-type transistor is embedded in a p-type substrate; it is formed by the intersection of an n-type wire and a polysilicon wire. The region at the intersection, called the **channel**, is where the transistor action takes place. The channel connects to the two n-type wires which form the source and drain, but is itself doped to be p-type.

---

---

The insulating silicon dioxide at the channel (called the **gate oxide**) is much thinner than it is away from the channel (called the **field oxide**); having a thin oxide at the channel is critical to the successful operation of the transistor.

 

**Figure 2-5** Cross-section of an n-type transistor.

Figure 2-6 shows a photomicrograph of an MOS transistor's cross-section. The photograph makes clear just how thin and sensitive the gate oxide is. The gate of this transistor is made of a sandwich of polysilicon and silicide. The sandwich's resistance is much lower than that of straight polysilicon.


#### *transistor operation*

The transistor works as a switch because the gate-to-source voltage modulates the amount of current that can flow between the source and drain. When the gate voltage ( $V_{gs}$ ) is zero, the p-type channel is full of holes, while the n-type source and drain contain electrons. The p-n junction at the source terminal forms a diode, while the junction at the drain forms a second diode that conducts in the opposite direction. As a result, no current can flow from the source to the drain.

As  $V_{gs}$  rises above zero, the situation starts to change. While the channel region contains predominantly p-type carriers, it also has some n-type carriers. The positive voltage on the polysilicon which forms the gate attracts the electrons. Since they are stopped by the gate oxide, they collect at the top of the channel along the oxide boundary. At a critical voltage called the **threshold voltage** ( $V_t$ ), enough electrons have collected at the channel boundary to form an **inversion layer**—a layer of electrons dense enough to conduct current between the source and the drain.

#### *channel dimensions*

The size of the channel region is labeled relative to the direction of current flow: the channel **length** ( $L$ ) is along the direction of current flow between source and drain, while the **width** ( $W$ ) is perpendicular to cur-

 

**Figure 2-6** Photomicrograph of a submicron MOS transistor (courtesy Agere).

rent flow. The amount of current flow is a function of the  $W/L$  ratio, for the same reasons that bulk resistance changes with the object's width and length: widening the channel gives a larger cross-section for conduction, while lengthening the channel increases the distance current must flow through the channel. Since we can choose  $W$  and  $L$  when we draw the layout, we can very simply design the transistor current magnitude.


*p-type and n-type*

A p-type transistor has an identical structure but complementary materials: trade p's and n's in Figure 2-5 and you have a picture of a p-type transistor. The p-type transistor conducts by forming an inversion region of holes in the n-type channel; therefore, the gate-to-source voltage must be negative for the transistor to conduct current.

---

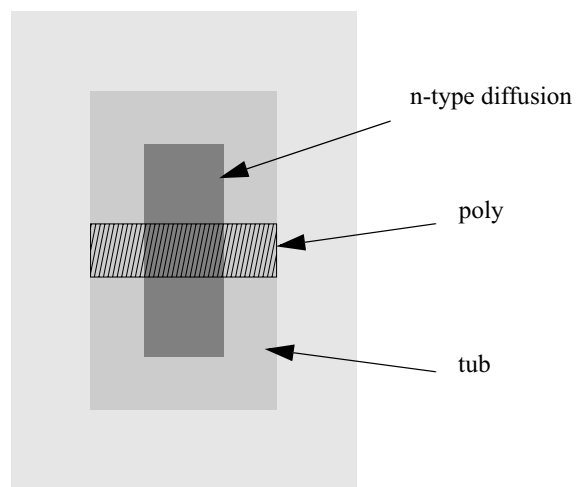**Example 2-1**  
**Layout of n-type**  
**and p-type**  
**transistors**

The basic layout of an n-type transistor is simple:




This layout is of a minimum-size transistor. Current flows through the channel vertically.

---

---

 
The layout of a p-type transistor is very similar:



In both cases, the tub rectangles are added as required. The details of which tub must be specified vary from process to process; many designers use simple programs to generate the tubs required around rectangles.

Fabrication engineers may sometimes refer to the **drawn length** of a transistor. Photolithography steps may affect the length of the channel. As a result, the actual channel length may not be the drawn length. The drawn length is usually the parameter of interest to the digital designer, since that is the size of rectangle that must be used to get a transistor of the desired size.

 We can also draw a wider n-type transistor, which delivers more current:



### 2.3.2 A Simple Transistor Model

*transistor model variables  
and constants*

The behavior of both n-type and p-type transistors is described by two equations and two physical constants; the sign of one of the constants distinguishes the two types of transistors. The variables that describe a transistor's behavior, some of which we have already encountered, are:

- $V_{gs}$ —the gate-to-source voltage;
- $V_{ds}$ —the drain-to-source voltage (remember that  $V_{ds} = -V_{sd}$ );
- $I_d$ —the current flowing between the drain and source.


The constants that determine the magnitude of source-to-drain current in the transistor are:

- $V_t$ —the transistor threshold voltage, which is positive for an n-type transistor and negative for a p-type transistor;
- $k'$ —the transistor transconductance, which is positive for both types of transistors;
- $W/L$ —the width-to-length ratio of the transistor.



Both  $V_t$  and  $k'$  are measured, either directly or indirectly, for a fabrication process.  $W/L$  is determined by the layout of the transistor, but since it does not change during operation, it is a constant of the device equations.

**Figure 2-7** The  $I_d$  curves of an n-type transistor.

 

*linear and saturated regions*

The equations that govern the transistor’s behavior are traditionally written to show the drain current as a function of the other parameters. A reasonably accurate model for the transistor’s behavior, written in terms of the drain current  $I_d$ , divides operation into **linear** and **saturated** [Yan78]. For an n-type transistor, we have:

- *Linear region*  $V_{ds} < V_{gs} - V_t$  :

$$I_d = k' \frac{W}{L} \left[ (V_{gs} - V_t) V_{ds} - \frac{1}{2} V_{ds}^2 \right] \tag{EQ 2-1}$$

- *Saturated region*  $V_{ds} \geq V_{gs} - V_t$  :

$$I_d = \frac{1}{2} k' \frac{W}{L} (V_{gs} - V_t)^2 \tag{EQ 2-2}$$

For a p-type transistor, the drain current is negative and the device is on when  $V_{gs}$  is below the device’s negative threshold voltage. Figure 2-7 plots these equations over some typical values for an n-type device.

*transistor behavior*

Each curve shows the transistor current as  $V_{gs}$  is held constant and  $V_{ds}$  is swept from 0 V to a large voltage.

The transistor's switch action occurs because the density of carriers in the channel depends strongly on the gate-to-substrate voltage. For  $|V_{gs}| < |V_t|$ , there are not enough carriers in the inversion layer to conduct an appreciable current. (To see how much current is conducted in the subthreshold region, check Section 2.3.5.) Beyond that point and until saturation, the number of carriers is directly related to  $V_{gs}$ : the greater the gate voltage applied, the more carriers are drawn to the inversion layer and the greater the transistor's conductivity.

The relationship between  $W/L$  and source-drain current is equally simple. As the channel width increases, more carriers are available to conduct current. As channel length increases, however, the drain-to-source voltage diminishes in effect.  $V_{ds}$  is the potential energy available to push carriers from drain to source; as the distance from drain to source increases, it takes longer to push carriers across the transistor for a fixed  $V_{ds}$ , reducing current flow.

**Table 2-1** Typical transistor parameters for our 180 nm process.

	$k'$	$V_t$
n-type	$k'_n = 170\mu A/V^2$	0.5V
p-type	$k'_p = -30\mu A/V^2$	-0.5V

Table 2-1 shows typical values of  $k'$  and  $V_t$  for a 180 nm process. The next example calculates the current through a transistor.

**Example 2-2**  
**Current through a transistor**

A minimum-size transistor in the SCMOS rules is of size  $L = 2\lambda$  and  $W = 3\lambda$ . Given this size of transistor and the 180 nm transistor characteristics, the current through a minimum-sized n-type transistor at the boundary between the linear and saturation regions when the gate is at the low voltage  $V_{gs} = 0.7V$  would be

$$I_d = \frac{1}{2} \left( 170 \frac{\mu A}{V^2} \right) \left( \frac{3\lambda}{2\lambda} \right) (0.7V - 0.5V)^2 = 5.1\mu A.$$


The saturation current when the transistor's gate is connected to a 1.2 V power supply would be

$$I_d = \frac{1}{2} \left( 170 \frac{\mu\text{A}}{\text{V}} \right) \left( \frac{3\lambda}{2\lambda} \right) (1.2\text{V} - 0.5\text{V})^2 = 62\mu\text{A}.$$

### 2.3.3 Transistor Parasitics

#### *gate capacitance*

Real devices have parasitic elements that are necessary artifacts of the device structure. The transistor itself introduces significant **gate capacitance**,  $C_g$ . This capacitance, which comes from the parallel plates formed by the poly gate and the substrate, forms the majority of the capacitive load in small logic circuits;  $C_g = 8.6\text{fF}/\mu\text{m}^2$  for both n-type and p-type transistors in a typical 180 nm process. The total gate capacitance for a transistor is computed by measuring the area of the active region (or  $W \times L$ ) and multiplying the area by the unit capacitance  $C_g$ .

 

**Figure 2-8** Parasitic capacitances from the gate to the source/drain overlap regions.

#### *source/drain capacitances*

We may, however, want to worry about the **source/drain overlap capacitances**. During fabrication, the dopants in the source/drain regions diffuse in all directions, including under the gate as shown in Figure 2-8. The source/drain overlap region tends to be a larger fraction of the channel area in deep submicron devices. The overlap region is independent of the transistor length, so it is usually given in units of Farads per unit gate width. Then the total source overlap capacitance for a transistor would be


$$C_{gs} = C_{ol}W. \quad (\text{EQ 2-3})$$

There is also a **gate/bulk overlap capacitance** due to the overhang of the gate past the channel and onto the bulk.

The source and drain regions also have a non-trivial capacitance to the substrate and a very large resistance. Circuit simulation may require the specification of source/drain capacitances and resistances. However, the techniques for measuring the source/drain parasitics at the transistor are the same as those used for measuring the parasitics of long diffusion wires. Therefore, we will defer the study of how to measure these parasitics to Section 2.4.1.

### 2.3.4 Tub Ties and Latchup

**Figure 2-9** Cross-section of an n-tub tie.

 


*tub ties connect tubs to power supply*

An MOS transistor is actually a four-terminal device, but we have up to now ignored the electrical connection to the substrate. The substrates underneath the transistors must be connected to a power supply: the p-tub (which contains n-type transistors) to  $V_{SS}$  and the n-tub to  $V_{DD}$ . These connections are made by special vias called **tub ties**.

Figure 2-9 shows the cross-section of a tub tie connecting to an n-tub and Figure 2-10 shows a tub tie next to a via and an n-type transistor. The tie connects a metal wire connected to the  $V_{DD}$  power supply directly to the substrate. The connection is made through a standard via cut. The substrate underneath the tub tie is heavily doped with n-type dopants (denoted as n<sup>+</sup>) to make a low-resistance connection to the tub. The SCMOS rules make the conservative suggestion that tub ties be placed every one to two transistors. Other processes may relax that rule to allow tub ties every four to five transistors. Why not place one tub tie

**Figure 2-10** A layout section featuring a tub tie.

 


in each tub—one tub tie for every 50 or 100 transistors? Using many tub ties in each tub makes a low-resistance connection between the tub and the power supply. If that connection has higher resistance, parasitic bipolar transistors can cause the chip to **latch-up**, inhibiting normal chip operation.


Figure 2-11 shows a chip cross-section which might be found in an inverter or other logic gate. The MOS transistor and tub structures form parasitic bipolar transistors: npn transistors are formed in the p-tub and pnp transistors in the n-tub. Since the tub regions are not physically isolated, current can flow between these parasitic transistors along the paths shown as wires. Since the tubs are not perfect conductors, some of these paths include parasitic resistors; the key resistances are those between the power supply terminals and the bases of the two bipolar transistors.

*parasitic elements and latch-up*

The parasitic bipolar transistors and resistors create a parasitic **silicon-controlled rectifier**, or SCR. The schematic for the SCR and its behavior are shown in Figure 2-12. The SCR has two modes of operation. When both bipolar transistors are off, the SCR conducts essentially no current between its two terminals. As the voltage across the SCR is raised, it may eventually turn on and conducts a great deal of current

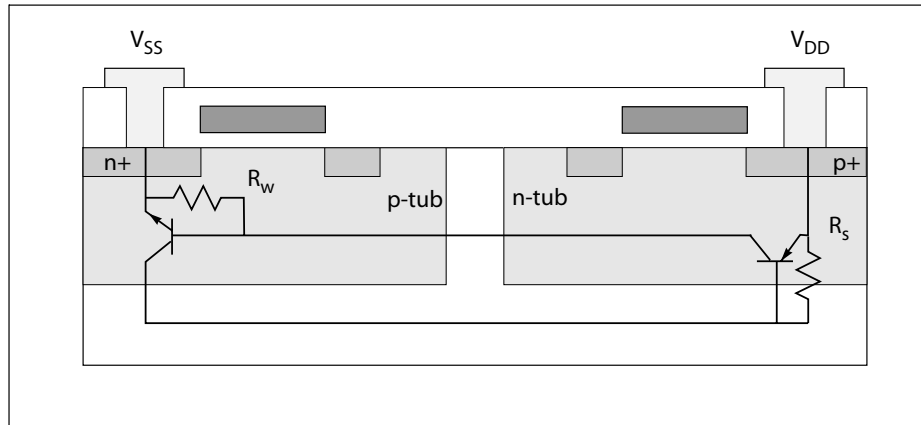

**Figure 2-11** Parasitics that cause latch-up.

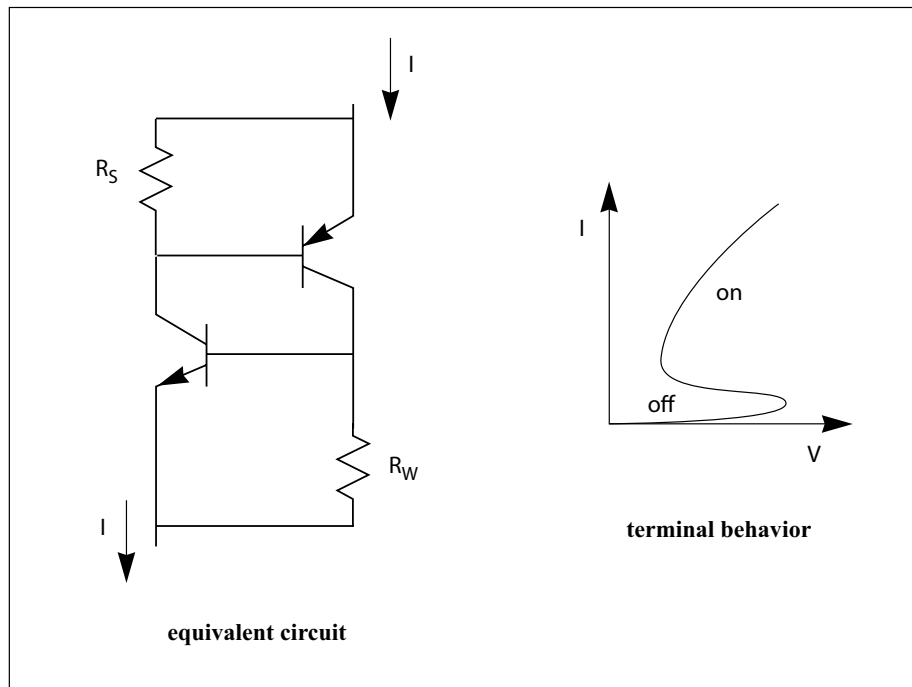

**Figure 2-12** Characteristics of a silicon-controlled rectifier.

with very little voltage drop. The SCR formed by the n- and p-tubs, when turned on, forms a high-current, low-voltage connection between  $V_{DD}$  and  $V_{SS}$ . Its effect is to short together the power supply terminals. When the SCR is on, the current flowing through it floods the tubs and prevents the transistors from operating properly. In some cases, the chip can be restored to normal operation by disconnecting and then reconnecting the power supply; in other cases the high currents cause permanent damage to the chip.

The switching point of the SCR is controlled by the values of the two power supply resistances  $R_s$  and  $R_w$ . Each bipolar transistor in the SCR turns on when its base-to-emitter voltage reaches 0.7 V; that voltage is controlled by the voltage across the two resistors. The higher the resistance, the less stray current through the tub is required to cause a voltage drop across the parasitic resistance that can turn on the associated transistor. Adding more tub ties reduces the values of  $R_s$  and  $R_w$ . The maximum distance between tub ties is chosen to ensure that the chip will not latch-up during normal operation.

### 2.3.5 Advanced Transistor Characteristics

In order to better understand the transistor, we will derive the basic device characteristics that were stated in Section 2.3.2. Along the way we will be able to identify some second-order effects that can become significant when we try to optimize a circuit design.

*gate capacitance*

The parallel plate capacitance of the gate determines the characteristics of the channel. We know from basic physics that the parallel-plate oxide capacitance per unit area (in units of Farads per  $\text{cm}^2$ ) is

$$C_{ox} = \epsilon_{ox}/x_{ox}, \quad \text{(EQ 2-4)}$$

where  $\epsilon_{ox}$  is the permittivity of silicon dioxide (about  $3.9\epsilon_0$ , where  $\epsilon_0$ , the permittivity of free space, is  $8.854 \times 10^{-14} \text{ F/cm}$ ) and  $x_{ox}$  is the oxide thickness in centimeters.

The intrinsic carrier concentration of silicon is denoted as  $n_i$ . N-type doping concentrations are written as  $N_d$  (donor) while p-type doping concentrations are written as  $N_a$  (acceptor). Table 2-2 gives the values of some important physical constants.

*threshold voltage*

Applying a voltage of the proper polarity between the gate and substrate pulls minority carriers to the lower plate of the capacitor, namely the channel region near the gate oxide. The threshold voltage is defined as

<b>charge of an electron</b>	$q$	$1.6 \times 10^{-19} C$
<b>Si intrinsic carrier concentration</b>	$n_i$	$1.45 \times 10^{10} C/cm^3$
<b>permittivity of free space</b>	$\epsilon_0$	$8.854 \times 10^{-14} F/cm^2$
<b>permittivity of Si</b>	$\epsilon_{Si}$	$11.9\epsilon_0$
<b>thermal voltage (300K)</b>	$kT/q$	$0.026V$

**Table 2-2** Values of some physical constants.

the voltage at which the number of minority carriers (electrons in an n-type transistor) in the channel region equals the number of majority carriers in the substrate. (This actually defines the **strong threshold condition**.) So the threshold voltage may be computed from the component voltages which determine the number of carriers in the channel. The threshold voltage (assuming that the source/substrate voltage is zero) has four major components:

$$V_{t0} = V_{fb} + \phi_s + \frac{Q_b}{C_{ox}} + V_{II} \quad \text{(EQ 2-5)}$$

Let us consider each of these terms.

- The first component,  $V_{fb}$ , is the **flatband voltage**, which in modern processes has two main components:

$$V_{fb} = \Phi_{gs} - (Q_f / C_{ox}) \quad \text{(EQ 2-6)}$$

$\Phi_{gs}$  is the difference in work functions between the gate and substrate material, while  $Q_f$  is the fixed surface charge. (Trapped charge used to be a significant problem in MOS processing which increased the flatband voltage and therefore the threshold voltage. However, modern processing techniques control the amount of trapped charge.)



If the gate polysilicon is n-doped at a concentration of  $N_{dp}$ , the formula for the work function difference is

$$\Phi_{gs} = -\frac{kT}{q} \ln\left(\frac{N_a N_{dp}}{n_i^2}\right). \quad (\text{EQ 2-7})$$

If the gate is p-doped at a concentration of  $N_{ap}$ , the work function difference is

$$\Phi_{gs} = \frac{kT}{q} \ln\left(\frac{N_{ap}}{N_a}\right). \quad (\text{EQ 2-8})$$

The second term is the surface potential. At the threshold voltage, the surface potential is twice the **Fermi potential** of the substrate:

$$\phi_s \approx 2|\phi_F| = 2\frac{kT}{q} \ln\frac{N_a}{n_i}. \quad (\text{EQ 2-9})$$

- The third component is the voltage across the parallel plate capacitor. The value of the charge on the capacitor  $Q_b$  is

$$\sqrt{2q\epsilon_{si}N_a\phi_s}. \quad (\text{EQ 2-10})$$

(We will not derive this value, but the square root comes from the value for the depth of the depletion region.)

- An additional ion implantation step is also performed to adjust the threshold voltage—the fixed charge of the ions provides a bias voltage on the gate. The voltage adjustment  $V_{II}$  has the value  $qD_I/C_{ox}$ , where  $D_I$  is the ion implantation concentration; the voltage adjustment may be positive or negative, depending on the type of ion implanted.

#### *body effect*

When the source/substrate voltage is not zero, we must add another term to the threshold voltage. Variation of threshold voltage with source/substrate voltage is called **body effect**, which can significantly affect the speed of complex logic gates. The amount by which the threshold voltage is increased is

$$\Delta V_t = \gamma_n(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s}) \quad (\text{EQ 2-11})$$

The term  $\gamma_n$  is the **body effect factor**, which depends on the gate oxide thickness and the substrate doping:

$$\gamma_n = \frac{\sqrt{2q\epsilon_{Si}N_A}}{C_{ox}}. \quad (\text{EQ 2-12})$$

(To compute  $\gamma_p$ , we substitute the n-tub doping  $N_D$  for  $N_A$ .) We will see how body effect must be taken into account when designing logic gates in Section 3.3.4.

### Example 2-3 Threshold voltage of a transistor

First, we will calculate the value of the threshold voltage of an n-type transistor at zero source/substrate bias. First, some reasonable values for the parameters:

- $x_{ox} = 4nm$  ;
- $\epsilon_{ox} = 3.5 \times 10^{-13} F/cm$  ;
- $\phi_s = 0.6V$  ;
- $Q_f = q \times 10^{11} = 1.6 \times 10^{-8} C/cm^2$  ;
- $\epsilon_{si} = 1.0 \times 10^{-12}$  ;
- $N_A = 10^{15} \text{ cm}^{-3}$  ;
- $N_{dp} = 10^{19} \text{ cm}^{-3}$  ;
- $N_{II} = 5 \times 10^{12}$  .

Let's compute each term of  $V_{t0}$  :

- $C_{ox} = \epsilon_{ox}/x_{ox}$ 

$$= 3.45 \times 10^{-13} / 4 \times 10^{-7} = 8.6 \times 10^{-7} C/cm^2 .$$
- $\Phi_{gs} = -\frac{kT}{q} \ln\left(\frac{N_a N_{dp}}{n_i^2}\right)$ 

$$= -0.026 \ln\left(\frac{10^{15} 10^{19}}{(1.45 \times 10^{10})^2}\right)$$

$$= -0.82V$$
- $V_{fb} = \Phi_{gs} - (Q_f/C_{ox})$ 

$$= -0.82 - (1.6 \times 10^{-8} / 8.6 \times 10^{-7})$$

$$= -0.83V .$$

- $$\begin{aligned}\phi_s &= 2 \frac{kT}{q} \ln \frac{N_a}{n_i} \\ &= 2 \times 0.026 \times \ln \left( \frac{10^{15}}{1.45 \times 10^{10}} \right) \\ &= 0.58 V\end{aligned}$$
- $$\begin{aligned}Q_b &= \sqrt{2q\epsilon_{s_i}N_a\phi_s} \\ &= \sqrt{2 \times (1.6 \times 10^{-19}) \times 1.0 \times 10^{-12} \times 10^{15} \times 0.58} \\ &= 1.4 \times 10^{-8}\end{aligned}$$
- $$\begin{aligned}V_{II} &= qD_I/C_{ox} \\ &= (1.6 \times 10^{-19}) \times (5 \times 10^{12}) / (8.6 \times 10^{-7}) \\ &= 0.93 V\end{aligned}$$

So,

$$\begin{aligned}V_{t0} &= V_{fb} + \phi_s + \frac{Q_b}{C_{ox}} + V_{II} \\ &= -0.83 V + 0.58 V + \frac{1.4 \times 10^{-8}}{8.6 \times 10^{-7}} + 0.93 V \\ &= 0.7 V .\end{aligned}$$

Note that it takes a significant ion implantation to give a threshold voltage that is reasonable for digital circuit design.

What is the value of the body effect at a source/substrate voltage of 0.5 V? First, we compute the body effect factor:

$$\begin{aligned}\gamma_n &= \frac{\sqrt{2q\epsilon_{s_i}N_A}}{C_{ox}} \\ &= \frac{\sqrt{2 \times (1.6 \times 10^{-19}) \times 1.0 \times 10^{-12} \times 10^{15}}}{8.6 \times 10^{-7}} \\ &= 0.02 .\end{aligned}$$

Then

$$\begin{aligned}\Delta V_t &= \gamma_n(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s}) \\ &= 0.02(\sqrt{0.58V + 0.5} - \sqrt{0.58V}) \\ &= 0.05V.\end{aligned}$$

This is a small fraction of the threshold voltage.

The drain current equation of Equation 2-1 can be found by integrating the charge over the channel. The charge at a point  $y$  is given simply by the definition of a parallel plate capacitance:

$$Q(y) = C_{ox}(V_{gs} - V_t - V(y)). \quad (\text{EQ 2-13})$$

The voltage differential over a differential distance in the channel is

$$dV = \frac{I_d dy}{\mu Q W}, \quad (\text{EQ 2-14})$$

where  $\mu$  is the (n- or p-) mobility at the surface and  $W$  is, of course, the channel width. Therefore, the total channel current is


$$I_d = \mu C_{ox} \frac{W}{L} \int_0^V (V_{gs} - V_t - V)(dV) ds. \quad (\text{EQ 2-15})$$

*device transconductance*

The factor  $\mu C_{ox}$  is given the name  $k'$  or **process transconductance**. We sometimes call  $k'W/L$  the **device transconductance**  $\beta$ . This integral gives us the linear-region drain current formula of Equation 2-1. At saturation, our first-order model assumes that the drain current becomes independent of the drain voltage and maintains that value as  $V_{ds}$  increases. As shown in Figure 2-13, the depth of the inversion layer varies with the voltage drop across the length of the channel and, at saturation, its height has been reduced to zero.

But this basic drain current equation ignores the small dependence of drain current on  $V_{ds}$  in saturation. Increasing  $V_{ds}$  while in saturation causes the channel to shorten slightly, which in turn slightly increases the drain current. This phenomenon can be modeled by multiplying Equation 2-2 by a factor  $(1 + \lambda V_{ds})$ . (Unfortunately, the **channel length modulation parameter**  $\lambda$  is given the same symbol as the scaling factor

**Figure 2-13** Shape of the inversion layer as a function of gate voltage.

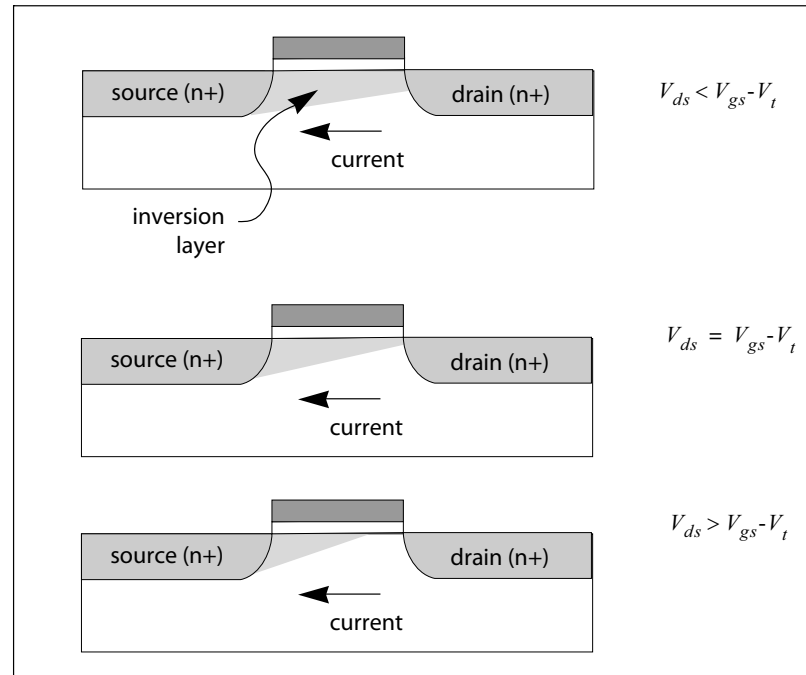

$\lambda$ .) The value of  $\lambda$  is measured empirically, not derived. This gives us the new drain current equation for the saturation region.

$$I_d = \frac{1}{2}k' \frac{W}{L} (V_{gs} - V_t)^2 (1 + \lambda V_{ds}). \quad (\text{EQ 2-16})$$

Unfortunately, the  $\lambda$  term causes a slight discontinuity between the drain current equations in the linear and saturation regions—at the transition point, the  $\lambda V_{ds}$  term introduces a small jump in  $I_d$ . A discontinuity in drain current is clearly not physically possible, but the discontinuity is small and usually can be ignored during manual analysis of the transistor's behavior. Circuit simulation, however, may require using a slightly different formulation that keeps drain current continuous.

### 2.3.6 Leakage and Subthreshold Currents

The drain current through the transistor does not drop to zero once the gate voltage goes below the threshold voltage. A variety of **leakage currents** continue to flow through various parts of the transistor, including a **subthreshold current** through the channel. Those currents are

## 2.3 Transistors

71

small, but they are becoming increasingly important in low-power applications. Not only do many circuits need to operate under very low current drains, but subthreshold currents are becoming relatively larger as transistor sizes shrink.

*sources of leakage*

Leakage currents come from a variety of effects within the transistor [Roy00]:

- **Reverse-biased pn junctions** in the transistor, such as the one between the drain and its well, carry small reverse bias currents.
- The **weak inversion current** (also known as the subthreshold current) is carried through the channel when the gate is below threshold.
- **Drain-induced barrier lowering** is an interaction between the drain's depletion region and the source that causes the source's potential barrier to be lowered.
- **Gate-induced drain leakage** current happens around the high electric field under the gate/drain overlap.
- **Punchthrough currents** flow when the source and drain depletion regions connect within the channel.
- **Gate oxide tunneling currents** are caused by high electric fields in the gate.
- **Hot carriers** can be injected into the channel.

Different mechanisms dominate at different drain voltages, with weak inversion dominating at low drain voltages.

*subthreshold current*

In nanometer technologies, subthreshold current is the largest source of leakage current. The subthreshold current can be written as [Roy00]:

$$I_{\text{sub}} = ke^{\left(\frac{V_{\text{gs}} - V_t}{S/\ln 10}\right)} [1 - e^{-qV_{\text{ds}}/kT}]. \quad (\text{EQ 2-17})$$

The **subthreshold slope**  $S$  characterizes the magnitude of the weak inversion current in the transistor. The subthreshold slope is determined by a plot of  $\log I_d$  vs.  $V_{\text{gs}}$ . An  $S$  value of 100 mV/decade indicates a very leaky transistor, with lower values indicating lower leakage currents.

The subthreshold current is a function of the threshold voltage  $V_t$ . The threshold voltage is primarily determined by the process. However, since the threshold voltage is measured relative to the substrate, we can adjust  $V_t$  by changing the substrate bias. We will take advantage of this effect in Section 3.6.

### 2.3.7 Thermal Effects

Modern VLSI systems generate large quantities of heat—enough that the chip must be designed with thermal effects in mind. Leakage currents are a prime cause of heat generation in nanometer devices, so it is worthwhile to consider the basic causes of heat generation here.

*leakage and temperature dependence*

Any current flow through the chip generates heat. In earlier CMOS technologies, leakage was negligible and power consumption was dominated by dynamic current flows. Today, leakage currents account for a large fraction of total power dissipation. Most important, some sources of leakage are temperature-dependent with higher temperatures causing more leakage current. This positive feedback between temperature and current is known as **thermal runaway** and can easily cause a chip to rapidly burn out.

*subthreshold leakage and temperature*

The most important source of temperature-dependent leakage current is the subthreshold leakage current, which is also the largest source of leakage current [Ped06]. The substrate current varies with temperature at the rate of 8x to 12x per  $100^{\circ}\text{C}$ , which means that threshold currents can increase drastically as the chip warms up. Furthermore, subthreshold leakage currents increase as we move to smaller technologies; these current increased by over 10x from 0.25  $\mu\text{m}$  to 90 nm.

### 2.3.8 Spice Models

*circuit simulation*

A circuit simulator, of which Spice [Nag75] is the prototypical example, provides the most accurate description of system behavior by solving for voltages and currents over time. The basis for circuit simulation is Kirchoff's laws, which describe the relationship between voltages and currents. Linear elements, like resistors and capacitors, have constant values in Kirchoff's laws, so the equations can be solved by standard linear algebra techniques.

However, transistors are non-linear, greatly complicating the solution of the circuit equations. The circuit simulator uses a model—an equivalent circuit whose parameters may vary with the values of other circuits voltages and currents—to represent a transistor. Unlike linear circuits, which can be solved analytically, numerical solution techniques must be used to solve non-linear circuits. The solution is generated as a sequence of points in time. Given the circuit solution at time  $t$ , the simulator chooses a new time  $t+\delta$  and solves for the new voltages and currents. The difficulty of finding the  $t+\delta$  solution increases when the circuit's voltages and currents are changing very rapidly, so the simulator chooses the time step  $\delta$  based on the derivatives of the  $I$ s and  $V$ s. The

**Table 2-3** Names of some Spice parameters.

parameter	symbol	Spice name
channel drawn length	<b>L</b>	L
channel width	<b>W</b>	W
source, drain areas		AS, AD
source, drain perimeters		PS, PD
source/drain resistances	$R_s, R_d$	RS, RD
source/drain sheet resistance		RSH
zero-bias bulk junction capacitance	$C_{j0}$	CJ
bulk junction grading coefficient	$m$	MJ
zero-bias sidewall capacitance	$C_{jsw0}$	CJSW
sidewall grading coefficient	$m_{sw}$	MJSW
gate-bulk/source/drain overlap capacitances	$C_{gb0}/C_{gs0}/C_{gd0}$	CGBO, CGSO, CGDO
bulk junction leakage current	$I_s$	IS
bulk junction leakage current density	$J_s$	JS
bulk junction potential	$\phi_0$	PB
zero-bias threshold voltage	$V_{t0}$	VT0
transconductance	$k'$	KP
body bias factor	$\gamma$	GAMMA
channel modulation	$\lambda$	LAMBDA
oxide thickness	$t_{ox}$	TOX
lateral diffusion	$x_d$	LD
metallurgical junction depth	$x_j$	XJ
surface inversion potential	$2 \phi_F $	PHI
substrate doping	$N_A, N_D$	NSUB
surface state density	$Q_{ss}/q$	NSS
surface mobility	$\mu_0$	U0
maximum drift velocity	$v_{max}$	VMAX
mobility critical field	$E_{crit}$	UCRIT
critical field exponent in mobility degradation		UEXP
type of gate material		TPG



resulting values can be plotted in a variety of ways using interactive tools.

#### *Spice models*


A circuit simulation is only as accurate as the model for the transistor. Spice supports a number of models of transistors (and other devices) that vary in their accuracy and computational expense [Gei90]. The level 1 Spice model is roughly the device equations of Section 2.3. We used the level 49 model for simulations described in this book. New models are regularly developed and incorporated into Spice as fabrication technology advances and device characteristics change. The model that you use in your simulations will generally be determined by your fabrication vendor, who will supply you with the model parameters in Spice format.

#### *Spice parameters*

Table 2-3 gives the Spice names for some common parameters of Spice models and their correspondence to names used in the literature. Process vendors typically supply customers with Spice model parameters directly. You should use these values rather than try to derive them from some other parameters.

## 2.4 Wires and Vias

**Figure 2-14** A cross-section of a chip showing wires and vias.

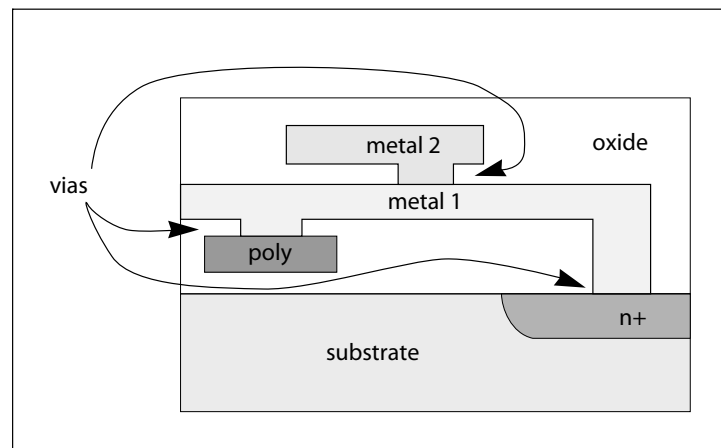


#### *layout cross section*

Figure 2-14 illustrates the cross-section of a nest of wires and vias. n-diffusion and p-diffusion wires are created by doping regions of the substrate. Polysilicon and metal wires are laid over the substrate, with silicon dioxide to insulate them from the substrate and each other. Wires are added in layers to the chip, alternating with  $\text{SiO}_2$ : a layer of wires is

added on top of the existing silicon dioxide, then the assembly is covered with an additional layer of  $\text{SiO}_2$  to insulate the new wires from the next layer. Vias are simply cuts in the insulating  $\text{SiO}_2$ ; the metal flows through the cut to make the connection on the desired layer below.

*copper interconnect*

As mentioned in Section 2.2, copper interconnect can now be produced in volume thanks to a special protection layer that keeps the copper from poisoning the semiconductors in the substrate. The fabrication methods, and therefore the design rules, for copper interconnect are similar to those used for aluminum wires. However, as we will see in Chapter 3, the circuit characteristics of copper differ radically from those of aluminum.

 

**Figure 2-15** Cross-section of twelve levels of metal interconnect (courtesy IBM).

*multi-layer interconnect*

Figure 2-15 shows a photomicrograph of a multi-level interconnect structure with twelve layers of metal. The bottom layer is tungsten, all layers above are copper. This photograph shows the huge variations in the sizes of wires—the levels closest to the transistors are small, while the wires at higher levels are both wider and taller. These widths are often referred to in  $nX$  terminology, where the bottom level of intercon-

nect is 1X and higher layers may be some factor larger. In this case, the first five copper layers are 1X with a width of 0.12  $\mu\text{m}$ , the next three are 2X scaled, and the next two are 6X scaled. (The top layer is made of a copper/aluminum alloy and is used for off-chip connections.)

#### *power distribution*

In addition to carrying signals, metal lines are used to supply power throughout the chip. On-chip metal wires have limited current-carrying capacity, as does any other wire. (Poly and diffusion wires also have current limitations, but since they are not used for power distribution those limitations do not affect design.) Electrons drifting through the voltage gradient on a metal line collide with the metal grains which form the wire. A sufficiently high-energy collision can appreciably move the metal grain. Under high currents, electron collisions with metal grains cause the metal to move; this process is called **metal migration** (also known as **electromigration**) [Mur93].

#### *mean time to failure*

The **mean time to failure (MTTF)** for metal wires—the time it takes for 50% of testing sites to fail—is a function of current density:

$$\text{MTF} \propto j^{-n} e^{Q/kT}, \quad (\text{EQ 2-18})$$

where  $j$  is the current density,  $n$  is a constant between 1 and 3, and  $Q$  is the diffusion activation energy. This equation is derived from the drift velocity relationship.

Metal wires can handle 1 mA of current per micron of wire width under the SCMOS rules. (Width is measured perpendicular to current flow.) A minimum width metal 1 wire can handle 0.54 mA of current. This is enough to handle several gates, but in larger designs, however, sizing power supply lines is critical to ensuring that the chip does not fail once it is installed in the field.


### 2.4.1 Wire Parasitics

Wires, vias and transistors all introduce parasitic elements into our circuits. We will concentrate here on resistance and capacitance analysis. It is important to understand the structural properties of our components that introduce parasitic elements, and how to measure parasitic element values from layouts.

#### *diffusion wire capacitance*

Diffusion wire capacitance is introduced by the p-n junctions at the boundaries between the diffusion and underlying tub or substrate. While these capacitances change with the voltage across the junction, which varies during circuit operation, we generally assume worst-case values. An accurate measurement of diffusion wire capacitance requires sepa-

**Figure 2-16** Sidewall and bottomwall capacitances of a diffusion region.

 

rate calculations for the bottom and sides of the wire—the doping density, and therefore the junction properties, vary with depth. To measure total capacitance, we measure the diffusion area, called **bottomwall capacitance**, and perimeter, called **sidewall capacitance**, as shown in Figure 2-16, and sum the contributions of each.

*diffusion capacitance derivation*

The **depletion region capacitance** value is given by

$$C_{j0} = \frac{\epsilon_{si}}{x_d} \tag{EQ 2-19}$$

This is the **zero-bias depletion capacitance**, assuming zero voltage and an abrupt change in doping density from  $N_a$  to  $N_d$ . The depletion region width  $x_{d0}$  is shown in Figure 2-16 as the dark region; the depletion region is split between the n+ and p+ sides of the junction. Its value is given by

$$x_{d0} = \sqrt{\left(\frac{1}{N_A} + \frac{1}{N_D}\right) \frac{2\epsilon_{si}V_{bi}}{q}} \tag{EQ 2-20}$$

where the built-in voltage  $V_{bi}$  is given by


$$V_{bi} = \frac{kT}{q} \ln\left(\frac{N_A N_D}{n_i^2}\right) \tag{EQ 2-21}$$

The junction capacitance is a function of the voltage across the junction  $V_r$ :

$$C_j(V_r) = \frac{C_{j0}}{\sqrt{1 + \frac{V_r}{V_{bi}}}} \quad (\text{EQ 2-22})$$

So the junction capacitance decreases as the reverse bias voltage increases.

**Figure 2-17** Plate and fringe capacitances of a parallel-plate capacitor.

 


*metal and poly capacitance*

The capacitance mechanism for poly and metal wires is, in contrast, the parallel plate capacitor from freshman physics. We must also measure area and perimeter on these layers to estimate capacitance, but for different reasons. The **plate capacitance** per unit area assumes infinite parallel plates. We take into account the changes in the electrical fields at the edges of the plate by adding in a **fringe capacitance** per unit perimeter. These two capacitances are illustrated in Figure 2-17. Capacitances can form between signal wires. In conservative technologies, the dominant parasitic capacitance is between the wire and the substrate, with the silicon dioxide layer forming the insulator between the two parallel plates.

*wire-to-wire parasitics*

At the higher levels of interconnect, wire-to-wire parasitics are becoming more important. Both capacitance between two different layers and between two wires on the same layer are basic parallel plate capacitances. The parasitic capacitance between two wires on different layers, such as  $C_{m1m2}$  in Figure 2-18, depends on the area of overlap between the two wires. In our typical 180 nm process, the plate capacitance between metal 1 and metal 2 is 14 aF/cm<sup>2</sup> and the metal 1-metal3 plate

**Figure 2-18** Capacitive coupling between signals on the same and different layers.

 


capacitance is  $14 \text{ aF/cm}^2$ . When two wires run together for a long distance, with one staying over the other, the layer-to-layer capacitance can be very large. The capacitance between two wires on the same layer,  $C_{w1w2}$  in the figure, is formed by the vertical sides of the metal wires. Metal wires can be very tall in relation to their width, so the vertical wall coupling is non-negligible. However, this capacitance depends on the distance between two wires. The values given in process specifications are for minimum-separation wires, and the capacitance decreases by a factor of  $1/x$  as distance increases. When two wires on the same layer run in parallel for a long distance, the coupling capacitance can become very large.

The following example illustrates how to measure parasitic capacitance from a layout.
 
### Example 2-4 Parasitic capacitance measurement

The n-diffusion wires in our typical 180 nm process have a bottomwall capacitance of  $940 \text{ aF}/\mu\text{m}^2$  and a sidewall capacitance of  $200 \text{ aF}/\mu\text{m}$ . The p-diffusion wires have bottomwall and sidewall capacitances of  $1000 \text{ aF}/\mu\text{m}^2$  and  $200 \text{ aF}/\mu\text{m}$ , respectively. The sidewall capacitance of a diffusion wire is typically as large or larger as its bottomwall capacitances because the well/substrate doping is highest near the surface. Typical metal 1 capacitances in a process are  $36 \text{ aF}/\mu\text{m}^2$  for plate and  $54 \text{ aF}/\mu\text{m}$  for fringe; typical poly values are  $63 \text{ aF}/\mu\text{m}^2$  plate and  $63 \text{ aF}/\mu\text{m}$  fringe. The fact that diffusion capacitance is an order of magnitude larger than metal or poly capacitance suggests that we should avoid using large amounts of diffusion.

Here is our example wire, made of n-diffusion and metal connected by a via:



To measure wire capacitance of a wire, simply measure the area and perimeter on each layer, compute the bottomwall and sidewall capacitances, and add them together. The only potential pitfall is that our layout measurements are probably, as in this example, in  $\lambda$  units, while unit capacitances are measured in units of  $\mu\text{m}$  (not nm). The n-diffusion section of the wire occupies

$$\left(12\lambda \times \frac{0.09\mu\text{m}}{\lambda}\right) \times \left(3\lambda \times \frac{0.09\mu\text{m}}{\lambda}\right) + \left(4\lambda \times \frac{0.09\mu\text{m}}{\lambda}\right)^2 = 0.42\text{fF}$$

of bottomwall capacitance. In this case, we count the n-diffusion which underlies the via, since it contributes capacitance to the substrate.


The n-diffusion's perimeter is, moving counterclockwise from the upper left-hand corner,

$$0.27\mu\text{m} + 1.08\mu\text{m} + 0.09\mu\text{m} + 0.36\mu\text{m} + 0.36\mu\text{m} + 1.44\mu\text{m} = 3.6\mu\text{m},$$

giving a total sidewall capacitance of  $0.72\text{fF}$ . Because the sidewall and bottomwall capacitances are in parallel, we add them to get the n-diffusion's contribution of  $1.1\text{fF}$ .

The metal 1 section has a total area of  $0.54\mu\text{m} \times 0.9\mu\text{m} = 1.44\mu\text{m}^2$ , giving a plate capacitance of  $0.051\text{fF}$ . The metal's perimeter is  $0.9\mu\text{m} \times 2 + 0.54\mu\text{m} \times 2 = 2.9\mu\text{m}$  for a fringe capacitance of  $0.156\text{fF}$  and a total metal contribution of  $0.16\text{fF}$ . A slightly more accurate measurement would count the metal area overlying the n-diffusion differently—strictly speaking, the metal forms a capacitance to the n-diffusion, not the substrate, since the diffusion is the closer material. However, since the via area is relatively small, approximating the metal 1-n-diffusion capacitance by a metal 1-substrate capacitance doesn't significantly change the result.

The total wire capacitance is the sum of the layer capacitances, since the layer capacitors are connected in parallel. The total wire capacitance is 1.3 fF; the n-diffusion capacitance dominates the wire capacitance, even though the metal 1 section of the wire is larger.

 

**Figure 2-19** Resistance per unit square is constant.

#### wire resistance


Wire resistance is also computed by measuring the size of the wire in the layout, but the unit of resistivity is **ohms per square** ( $\Omega/\square$ ), not ohms per square micron. The resistance of a square unit of material is the same for a square of any size; to understand, consider Figure 2-19. Assume that a unit square of material has a resistance of  $1\Omega$ . Two squares of material connected in parallel have a total resistance of  $1/2\Omega$ . Connecting two such rectangles in series creates a  $2 \times 2$  square with a resistance of  $1\Omega$ . We can therefore measure the resistance of a wire by measuring its aspect ratio.

Figure 2-20 shows two example wires. The upper wire is made of polysilicon, which has a resistivity of  $8\Omega/\square$  in our 180 nm process. Current flows in the direction shown; wire length is along the direction of current flow, while wire width is perpendicular to the current. The wire is composed of  $18/3$  squares connected in series, giving a total resistance of  $48\Omega$ .

The second wire is more interesting because it is bent. A  $90^\circ$  bend in a wire offers less resistance because electrons nearer the corner travel a shorter distance. A simple and common approximation is to count each square corner rectangle as  $1/2$  squares of resistance. The wire can be broken into three pieces:  $9/3 = 3$  squares,  $1/2$  squares, and  $6/3 = 2$  squares. P-diffusion resistivity is approximately  $2\Omega/\square$ , giving a total resistance of  $11\Omega$ .



**Figure 2-20** An example of resistance calculation.

 

*typical resistivity values*

In our typical 180 nm process, an n-diffusion wire has a resistivity of approximately  $7 \Omega/\square$ , with metal 1, metal 2, and metal 3 having resistivities of about 0.08, 0.08, and  $0.03 \Omega/\square$ , respectively. Note that p-diffusion wires in particular have higher resistivity than polysilicon wires, and that metal wires have low resistivities.

*source-drain parasitics*

The source and drain regions of a transistor have significant capacitance and resistance. These parasitics are, for example, entered into a Spice simulation as device characteristics rather than as separate wire models. However, we measure the parasitics in the same way we would measure the parasitics on an isolated wire, measuring area and perimeter up to the gate-source/drain boundary.

*via resistance*

Vias have added resistance because the cut between the layers is smaller than the wires it connects and because the materials interface introduces resistance. The resistance of the via is usually determined by the resistance of the materials: a metal 1-metal 2 via has a typical resistance of about  $5 \Omega$  while a metal1-poly contact has a resistance of  $10 \Omega$ . We rarely worry about the exact via resistance in layout design; instead, we try to avoid introducing unnecessary vias in current paths for which low resistance is critical.


## 2.4.2 Skin Effect in Copper Interconnect

*skin effect in copper*

Low-resistance conductors like copper not only exhibit inductance, they also display a more complex resistance relationship due to a phenomenon called **skin effect** [Ram65]. The skin effect causes a copper conduc-

tor's resistance to increase (and its inductance to decrease) at high frequencies.

**Figure 2-21** How current changes with frequency due to skin effect.

 

An ideal conductor would conduct currents only on its surface. The current at the surface is a boundary effect—any current within the conductor would set up an electromagnetic force that would induce an opposing and cancelling current. The copper wiring used on ICs is a non-ideal conductor; at low frequencies, the electromagnetic force is low enough and resistance is high enough that current is conducted throughout the wire's cross section. However, as the signal's frequency increases, the electromagnetic forces increase. As illustrated in Figure 2-21, the current through an isolated conductor migrates toward the edges as frequency increases; when the conductor is close to a ground, the current in both move toward each other.

Skin effect causes the conductor's resistance to increase with frequency. The **skin depth**  $\delta$  is the depth at which the conductor's current is reduced to  $1/e = 37\%$  of its surface value [Che00]:

$$\delta = \frac{1}{\sqrt{\pi f \mu \sigma}}, \quad (\text{EQ 2-23})$$

where  $f$  is the signal frequency,  $\mu$  is the magnetic permeability, and  $\sigma$  is the wire's conductivity. The skin depth goes down as the square root of frequency.

*skin effect and resistivity*

Cheng et al [Che00] provide an estimation of the delay per unit length of a wire suffering from skin effect. Two values,  $R_{dc}$  and  $R_{hf}$ , estimate the resistance at low and high frequencies:

$$\left( R_{dc} = \frac{1}{\sigma w t} \right), R_{hf} = \frac{1}{2 \sigma \delta (w + t)}, \quad (\text{EQ 2-24})$$

where  $w$  and  $t$  are the width and height of the conductor, respectively. The skin depth  $\delta$  ensures that  $R_{hf}$  depends on frequency. The resistance per unit length can be estimated as

$$R_{ac} = \sqrt{R_{dc}^2 + (\kappa R_{hf})^2}, \quad (\text{EQ 2-25})$$

where  $\kappa$  is a weighting factor typically valued at 1.2.

Skin effect typically becomes important at gigahertz frequencies in ICs. Some microprocessors already run at those frequencies and more chips will do so in the near future.

## 2.5 Fabrication Theory and Practice

---

*physical design and design rules*

Layouts are built from three basic component types: transistors, wires, and vias. We have seen the structures of these components created during fabrication. Now we will consider the design of the layouts which determine the circuit that is fabricated. **Design rules** govern the layout of individual components and the interactions—spacings and electrical connections—between those components. Design rules determine the low-level properties of chip designs: how small individual logic gates can be made; how small the wires connecting gates can be made, and therefore, the parasitic resistance and capacitance which determine delay.

*design rules and yield*

Design rules are determined by the conflicting demands of component packing and chip yield. On the one hand, we want to make the components as small as possible, to put as many functions as possible on-chip.

---

On the other hand, since the individual transistors and wires are about as small as the smallest feature that our manufacturing process can produce, errors during fabrication are inevitable: wires may short together or never connect, transistors may be faulty, etc. One common model for yield of a single type of structure is a Gamma distribution [Mur93]:

$$Y_i = \left( \frac{1}{1 + A\beta_i} \right)^{\alpha_i}. \quad (\text{EQ 2-26})$$

The total yield for the process is then the product of all the yield components:

$$Y = \prod_{i=1}^n Y_i. \quad (\text{EQ 2-27})$$

This formula suggests that low yield for even one of the process steps can cause serious final yield problems. But being too conservative about design rules leads to chips that are too large (which itself reduces yield) and too slow as well. We try to balance chip functionality and manufacturing yield by following rules for layout design which tell us what layout constructs are likely to cause the greatest problems during fabrication.

### 2.5.1 Fabrication Errors


*problems that motivate design rules*

The design rules for a particular process can be confusing unless you understand the motivation for the rules—the types of errors that are likely to occur while the chip is being manufactured. The design rules for a process are formulated to minimize the occurrence of common fabrication problems and bring the yield of correct chips to an acceptable level.

*metallization problems*

The most obvious type of fabrication problem is a wire or other feature being made too wide or too narrow. This problem can occur for a variety of reasons: photolithographic errors may leave an erroneous pattern for later steps; local materials variations may cause different rates of diffusion or deposition; processing steps at a nearby feature may cause harmful interactions. One important problem in fabrication is **planarization** [Gha94]—poly and metal wires leave hills in the oxide. The bumps in the oxide can be smoothed by several different chemical or mechanical methods; failure to do so causes **step coverage** problems which may lead to breaks in subsequent metallization layers. In any case, the result is a wire that is too narrow or too wide. As shown in Figure 2-22, a wire that is too narrow may never conduct current, or may burn out after

**Figure 2-22** Problems when wires are too wide or narrow.

 


some use. A too-wide wire may unintentionally short itself to another wire or, as in the case of a poly wire overlapping a parallel diffusion wire, cut into another element.

*spacing and minimum-width rules*

The simplest remedy for these problems is the introduction of **spacing** and **minimum-width** rules, which take a variety of forms in our design rules. Minimum-width rules give a minimum size for a layout element; they help ensure that even with minor variations in the position of the lines that form the element, the element will be of an acceptable size. Spacing rules give a minimum distance between the edges of layout elements, so that minor processing variations will not cause the element to overlap nearby layout elements.

**Figure 2-23** Potential problems in transistor fabrication.

 


*composition rules*

We also have a number of **composition** rules to ensure that components are well-formed. Consider the transistor layout in Figure 2-23—the transistor action itself takes place in the channel, at the intersection of the polysilicon and diffusion regions, but a valid transistor layout requires extensions of both the poly and diffusion regions beyond the

boundary. The poly extensions ensure that no strand of diffusion shorts together the source and drain. The diffusion extensions ensure that adequate contact can be made to the source and drain.

**Figure 2-24** Potential problems in via fabrication.

 

Vias have construction rules as well: the material on both layers to be connected must extend beyond the  $\text{SiO}_2$  cut itself; and the cut must be of a fixed size. As shown in Figure 2-24, the overlap requirement simply ensures that the cut will completely connect the desired layout elements and not mistakenly connect to the substrate or another wire. The key problem in via fabrication, however, is making the cuts. A large chip may contain millions of vias, all of which must be opened properly for the chip to work. The acid etching process which creates cuts must be very uniform—cuts may be neither too small and shallow nor too large. It isn't hard to mount a bookcase in a wall with an electric drill—it is easy to accurately size and position each hole required. Now imagine making those holes by covering the wall with acid at selected points, then wiping the wall clean after a few minutes, and you should empathize with the problems of manufacturing vias on ICs. The cut must also be filled with material without breaking as the material flows over the edge of the cut. The size, shape, and spacing of via cuts are all strictly regulated by modern fabrication processes to give maximum via yield.

### 2.5.2 Scaling Theory and Practice

#### *Moore's Law and design rules*

Manufacturing processes are constantly being improved. The ability to make ever-smaller devices is the driving force behind Moore's Law. But many characteristics of the fabrication process do not change as devices shrink—layouts do not have to be completely redesigned, simply shrunk in size. We can take best advantage of process scaling by formulating our design rules to be explicitly scalable.

We will scale our design rules by expressing them not in absolute physical distances, but in terms of  $\lambda$ , the size of the smallest feature in a layout. All features can be measured in integral multiples of  $\lambda$ . By choosing a value for  $\lambda$  we set all the dimensions in a scalable layout.

Scaling layouts makes sense because chips actually get faster as layouts shrink. As a result, we don't have to redesign our circuits for each new process to ensure that speed doesn't go down as packing density goes up. If circuits became slower with smaller transistors, then circuits and layouts would have to be redesigned for each process.

### scaling theory

Digital circuit designs scale because the capacitive loads that must be driven by logic gates shrink faster than the currents supplied by the transistors in the circuit [Den74]. To understand why, assume that all the basic physical parameters of the chip are shrunk by a factor  $1/x$ :

- lengths and widths:  $W \rightarrow W/x, L \rightarrow L/x$ ;
- vertical dimensions such as oxide thicknesses:  $t_{ox} \rightarrow t_{ox}/x$ ;
- doping concentrations:  $N_d \rightarrow N_d/x$ ;
- supply voltages:  $V_{DD} - V_{SS} \rightarrow (V_{DD} - V_{SS})/x$ .

We now want to compute the values of scaled physical parameters, which we will denote by variables with hat symbols. One result is that the transistor transconductance scales: since  $k' = (\mu_{eff}\epsilon_{ox})/t_{ox}$  [Mul77],  $\hat{k}'/k' = x$ . ( $\mu_{eff}$  is the carrier mobility and  $\epsilon_{ox}$  is the dielectric constant.) The threshold voltage scales with oxide thickness, so  $\hat{V}_t = V_t/x$ . Now compute the scaling of the saturation drain current  $W/L$ :

$$\begin{aligned} \frac{\hat{I}_d}{I_d} &= \left(\frac{\hat{k}'}{k'}\right) \left(\frac{\hat{W}/\hat{L}}{W/L}\right) \left[\frac{(\hat{V}_{gs} - \hat{V}_t)^2}{(V_{gs} - V_t)^2}\right] \\ &= x \left(\frac{1/x}{1/x}\right) \left(\frac{1}{x}\right)^2 \\ &= \frac{1}{x} \end{aligned} \quad \text{(EQ 2-28)}$$

The scaling of the gate capacitance is simple to compute:  $C_g = \epsilon_{ox}WL/t_{ox}$ , so  $\hat{C}_g/C_g = 1/x$ . The total delay of the logic circuit depends on the capacitance to be charged, the current available, and the voltage through which the capacitor must be charged; we will use  $CV/I$  as a measure of the speed of a circuit over scaling. The voltage through which the logic circuit swings is determined by the power supply, so the voltage scales as  $1/x$ . When we plug in all our values,

$$\frac{\hat{C}\hat{V}/\hat{I}}{CV/I} = \frac{1}{x}. \quad \text{(EQ 2-29)}$$

So, as the layout is scaled from  $\lambda$  to  $\hat{\lambda} = \lambda/x$ , the circuit is actually speeded up by a factor  $x$ .

In practice, few processes are perfectly  $\lambda$ -scalable. As process designers learn more, they inevitably improve some step in the process in a way that does not scale. High-performance designs generally require some modification when migrated to a smaller process as detailed timing properties change. However, the scalability of VLSI systems helps contain the required changes.

	<b>ideal scaling</b>	<b>constant dimension scaling</b>
<i>line width and spacing</i>	$S$	<b>1</b>
<i>wire thickness</i>	$S$	<b>1</b>
<i>interlevel dielectric thickness</i>	$S$	<b>1</b>
<i>wire length</i>	$1/\sqrt{S}$	$1/\sqrt{S}$
<i>resistance per unit length</i>	$1/S^2$	<b>1</b>
<i>capacitance per unit length</i>	<b>1</b>	<b>1</b>
<i>RC delay</i>	$1/S^3$	$1/S$
<i>current density</i>	$1/S$	$S$

**Table 2-4** Interconnect scaling methodologies for global wiring [Syl01].

#### *interconnect scaling*

Interconnect scales somewhat differently than do transistors because they present different fabrication problems. Sylvester and Hu presented several different methodologies for scaling global interconnect [Syl01]. Ideal scaling laws change the vertical and horizontal dimensions equally. Constant dimension scaling, in contrast, does not change the basic parameters of wiring. Under ideal scaling, resistance per unit length grows quickly as wires are scaled, while in constant dimension scaling, resistance per unit length stays the same. As Figure 2-15 shows, the higher levels of interconnect do in fact have larger dimensions, which essentially reflect interconnect that is unscaled from earlier generations of technology, which provides lower-resistance interconnect for global wiring.



*ITRS roadmap*

The **International Technology Roadmap for Semiconductors (ITRS)** (<http://www.itrs.net>) is a plan, written by the semiconductor industry, for the development of semiconductor manufacturing and the continuation of Moore's Law. The Roadmap is rewritten or updated every year. This document, which describes the practical side of scaling, gives goals for scaling and the challenges that must be met to meet those goals.

year	2005	2006	2007	2008	2009	2010	2011	2012
microprocessor metal 1 1/2 pitch (nm)	90	78	68	59	52	45	40	36
microprocessor physical gate length (nm)	32	28	25	23	20	18	16	14
ASIC/low power physical gate length (nm)	45	38	32	28	25	23	20	18

**Table 2-5** Goals from the 2005 ITRS Roadmap [Int05].


Table 2-5 shows some values for basic process parameters from the 2005 Roadmap. For each year, the target values for the 1/2 pitch (width of a wire) of metal 1, gate length for microprocessors, and gate length for low-power ASICs are given.

### 2.5.3 SCMOS Design Rules

*SCMOS*

Finally, we reach the SCMOS design rules themselves. The full SCMOS rules are on the Mosis Web site (<http://www.mosis.com/Technical/Designrules/scmos/scmos-main.html>). In this section, we will only summarize some of the basic rules. The full set of rules is complex and may change over time. The basic SCMOS rules define two layers of metal; options allow for up to six layers of metal. Two special set of rules, SCMOS Sub-micron and SCMOS Deep, have been added for submicron processes. We will start with the basic SCMOS rules and then move onto these special rules.

We will cast these rules in terms of  $\lambda$ . For the SCMOS rules, a 180 nm process, the nominal value for  $\lambda$  is 0.09  $\mu\text{m}$  90 nm. SCMOS layouts must be designed on a  $\frac{1}{2}\lambda$  grid.

 

**Figure 2-25** A summary of the SCMOS design rules.

*design rules as pictures plus text*

Design rules are generally specified as pictures illustrating basic situations, with notes to explain features not easily described graphically. While this presentation may be difficult to relate to a real layout, practice will teach you to identify potential design rule violations in a layout from the prototype situations in the rules. Many layout editor programs, such as Magic [Ost84], have built-in design-rule checkers which will identify design-rule violations on the screen for you. Using such a program is a big help in learning the process design rules.

*basic spacing and minimum size rules*

Figure 2-25 summarizes the basic spacing and minimum size design rules. Classifying the situations described in these pictures as separation, minimum size, or composition will help you distinguish and learn the rules. Many of these rules hold for any tub structure: n-tub, p-tub, or twin-tub. The rules regarding tubs and tub ties necessarily depend on the tub structure, however.

*separation and size rules*

The basic separation and minimum size rules are:

- **metal 1** Minimum width is  $3\lambda$ , minimum separation is  $3\lambda$ .
- **metal 2** Minimum width is  $3\lambda$ , minimum separation is  $4\lambda$ .
- **polysilicon** Minimum width is  $2\lambda$ , minimum poly–poly separation is  $2\lambda$ .
- **p-, n-diffusion** Minimum width is  $3\lambda$ , minimum separation between same-type diffusions is  $3\lambda$ , minimum p-diff–n-diff separation is  $10\lambda$ .
- **tubs** Tubs must be at least  $10\lambda$  wide. The minimum distance from the tub edge to source/drain active area is  $5\lambda$ .

*construction rules*

The basic construction rules are:

- **transistors** The smallest transistor is of width  $3\lambda$  and length  $2\lambda$ ; poly extends  $2\lambda$  beyond the active region and diffusion extends  $3\lambda$ . The active region must be at least  $1\lambda$  from a poly-metal via,  $2\lambda$  from another transistor, and  $3\lambda$  from a tub tie.
- **vias** Cuts are  $2\lambda \times 2\lambda$ ; the material on both layers to be connected extends  $1\lambda$  in all directions from the cut, making the total via size  $4\lambda \times 4\lambda$ . (MOSIS also suggests another via construction with  $1.5\lambda$  of material around the cut. This construction is safer but the fractional design rule may cause problems with some design tools.) Available via types are:

- n/p-diffusion–poly;
- poly–metal 1;
- n/p-diffusion–metal 1;
- metal 1–metal 2;

If several vias are placed in a row, successive cuts must be at least  $2\lambda$  apart. Spacing to a via refers to the complete  $4\lambda \times 4\lambda$  object, while spacing to a via cut refers to the  $2 \times 2\lambda$  cut.

- **tub ties** A p-tub tie is made of a  $2\lambda \times 2\lambda$  cut, a  $4\lambda \times 4\lambda$  metal element, and a  $4\lambda \times 4\lambda p^+$  diffusion. An n-tub tie is made with an  $n^+$  diffusion replacing the  $p^+$  diffusion. A tub tie must be at least  $2\lambda$  from a diffusion contact.

It is important to remember that different rules have different dependencies on electrical connectivity. Spacing rules for wires, for example, depend on whether the wires are on the same electrical node. Two wire segments on the same electrical node may touch. However, two via cuts must be at least  $2\lambda$  apart even if they are on the same electrical net. Similarly, two active regions must always be  $2\lambda$  apart, even if they are parallel transistors.

#### *higher-level metal rules*

The rules for metal 3 are:

- Minimum metal 3 width is  $6\lambda$ , minimum separation is  $4\lambda$ .
- Available via from metal 3 is to metal 2. Connections from metal 3 to other layers must be made by first connecting to metal 2.

#### *rules for submicron processes*

As mentioned above, the SCMOS Sub-micron and SCMOS Deep rules have been developed to support submicron processes. Table 2-6 describes some of the changes introduced by these rule sets; the full set of changes are on the MOSIS Web site. If you want to design for a particular process, you will need to determine which set of rules you need to follow.

#### *other rules*

There are some other rules that do not fit into the separation/minimum size/composition categorization.

- A cut to polysilicon must be at least  $3\lambda$  from other polysilicon.
- Polysilicon cuts and diffusion cuts must be at least  $2\lambda$  apart.
- A cut must be at least  $2\lambda$  from a transistor active region.
- A diffusion contact must be at least  $4\lambda$  away from other diffusion.
- A metal 2 via must not be directly over polysilicon.


	SCMOS	SCMOS Sub-micron	SCMOS Deep
<i>poly space</i>	2	3	3
<i>active extension beyond poly</i>	3	3	4
<i>contact space</i>	2	3	4
<i>via width</i>	2	2	3
<i>metal 1 space</i>	2	3	3
<i>metal 2 space</i>	3	3	4

**Table 2-6** Some differences between SCMOS, SCMOS Sub-micron, and SCMOS Deep rules.

*negative features*

Another rule is to avoid generating small **negative features**. Consider the layout of Figure 2-26: the two edges of the notch are  $1\lambda$  apart, but both sides of the notch are on the same electrical node. The two edges are not in danger of causing an inadvertent short due to a fabrication error, but the notch itself can cause processing errors. Some processing steps are, for convenience, done on the negative of the mask given, as shown in the figure. The notch in the positive mask forms a  $1\lambda$  wide protrusion on the negative mask. Such a small feature in the photoresist, called a **negative mask feature**, can break off during processing, float around the chip, and land elsewhere, causing an unwanted piece of material. We can minimize the chances of stray photoresist causing problems by requiring all negative features to be at least  $2\lambda$  in size.

**Figure 2-26** A negative mask feature.

 

*antenna rules*


Antenna rules help protect transistors against damage to their gate oxides. Polysilicon or metal wires that are connected to transistors may collect charge; the charge can then flow through the gate oxide using a mechanism known as Fowler-Nordheim tunneling [Sze81]. If the charge is large enough, this current will damage the gate oxide. Antenna rules restrict the ratio of poly or metal wiring to gate area—the wire-to-gate ratio must be no larger than a given amount.

### 2.5.4 Typical Process Parameters

Typical values of process parameters for a 180 nm fabrication process are given in Table 2-7. We use the term *typical* loosely here; these are approximate values that do not reflect a particular manufacturing process and the actual parameter values can vary widely. You should always request process parameters from your vendor when designing a circuit that you intend to fabricate.

### 2.5.5 Lithography for Nanometer Processes

We have so far treated design rules as a simple but complete abstraction of the manufacturing process—if we follow the design rules, our chips will be manufacturable with high yields. However, as we move to very fine feature sizes in the nanometer range, our simple view of lithography must change.

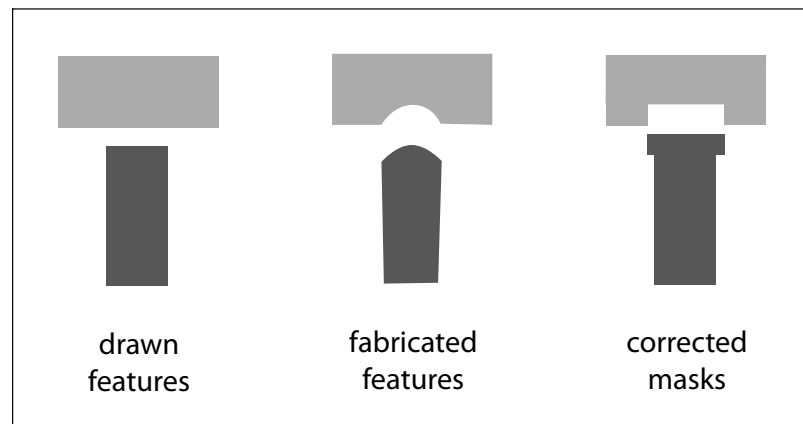

**Figure 2-27** Notching in nanometer-scale lithography.

n-type transconductance	$k'_n$	$170\mu\text{A}/\text{V}^2$
p-type transconductance	$k'_p$	$-30\mu\text{A}/\text{V}^2$
n-type threshold voltage	$V_{tn}$	0.5V
p-type threshold voltage	$V_{tp}$	-0.5V
n-diffusion bottomwall capacitance	$C_{ndiff,bot}$	$940\text{aF}/\mu\text{m}^2$
n-diffusion sidewall capacitance	$C_{ndiff,side}$	$200\text{aF}/\mu\text{m}$
p-diffusion bottomwall capacitance	$C_{pdiff,bot}$	$1000\text{aF}/\mu\text{m}^2$
p-diffusion sidewall capacitance	$C_{pdiff,side}$	$200\text{aF}/\mu\text{m}$
n-type source/drain resistivity	$R_{ndiff}$	$7\Omega/\square$
p-type source/drain resistivity	$R_{pdiff}$	$7\Omega/\square$
poly-substrate plate capacitance	$C_{poly,plate}$	$63\text{aF}/\mu\text{m}^2$
poly-substrate fringe capacitance	$C_{poly,fringe}$	$63\text{aF}/\mu\text{m}$
poly resistivity	$R_{poly}$	$8\Omega/\square$
metal 1-substrate plate capacitance	$C_{metal1,plate}$	$36\text{aF}/\mu\text{m}^2$
metal 1-substrate fringe capacitance	$C_{metal1,fringe}$	$54\text{aF}/\mu\text{m}$
metal 2-substrate capacitance	$C_{metal2,plate}$	$36\text{aF}/\mu\text{m}^2$
metal 2-substrate fringe capacitance	$C_{metal2,fringe}$	$51\text{aF}/\mu\text{m}$
metal 3-substrate capacitance	$C_{metal3,plate}$	$37\text{aF}/\mu\text{m}^2$
metal 3-substrate fringe capacitance	$C_{metal3,fringe}$	$54\text{aF}/\mu\text{m}$
metal 1 resistivity	$R_{metal1}$	$0.08\Omega/\square$
metal 2 resistivity	$R_{metal2}$	$0.08\Omega/\square$
metal 3 resistivity	$R_{metal3}$	$0.03\Omega/\square$
metal current limit	$I_{m,max}$	$1\text{mA}/\mu\text{m}$

**Table 2-7** Typical parameters for our 180 nm process.

## 2.5 Fabrication Theory and Practice

97

*lithographic limitations*

Lithography was chosen as a basic process for semiconductor manufacturing when the size of features was large compared to the wavelength of light. Today's features are small compared to the wavelengths of even invisible radiation. As a result, the features exposed on the chip by the mask do not exactly match the drawn features of the mask. As illustrated in Figure 2-27, the features that are drawn on the mask result in distorted features on the wafer. This effect is known as **optical proximity**. By modifying the masks, we can cause the fabricated features to appear as we want them, even though those fabricated features will differ from the shapes on the corrected mask.

*correction techniques*

**Optical proximity correction (OPC)** analyzes masks, determines where problems may occur, and modifies the masks to correct for optical proximity effects. Exact correction requires continuous curves on the masks, which we cannot fabricate. Some OPC tools allow the user to select the accuracy of the mask corrections and the allowable tolerance between the ideal and the actual correction.

### 2.5.6 3-D Integration

Traditional VLSI technology builds transistors on a single plane but several technologies have been developed to arrange and interconnect transistors in three dimensions. 3-D integration has several important benefits. First, it moves transistors closer together, which translates to shorter delays so long as the wires that can be built in the third dimension are of sufficient quality. Second, some 3-D technologies allow different fabrication techniques to be combined so that, for example, a digital process can be used for some of the transistors while a process optimized for analog devices can be used for other parts of the system.

*approaches to 3-D*

Several 3-D technologies have been developed that have very different characteristics [Dav05]. A commonly used technique is to stack chips and to use traditional wire bonding, such as we will describe in Section 7.5, to connect the chips. Stacked wire bonding is commonly used for cell phone systems-on-chips because it improves both physical size and power consumption. An alternative is **through-silicon-via (TSV) with die stacking**, in which inter-die vias are fabricated that go from one chip to another so that the chips can be stacked vertically. In this case, the TSV vias must exhibit low resistance and the chips must be carefully aligned. A third alternative is **multilayer buried structures (MLBS)**, in which several layers of devices are built upon a single substrate before interconnections are fabricated.



*die stacking applications*


One advantage of die stacking is that it requires relatively small changes to the basic fabrication technology as compared to MLBS approaches. Dies can be stacked in two different ways: face-to-back or face-to-face. 3-D die stacking is a promising technology for processors [Loh07].

## 2.6 Reliability

---

Reliability has always been a concern for integrated circuit designers due to the small size of the devices and the natural variations that occur in manufacturing processes. However, nanometer processes introduce new reliability problems, some of which must be handled at higher levels of abstraction. Modern design-for-manufacturability and design-for-yield techniques are based on a fundamental understanding of the failure mechanisms of integrated circuits.

**Figure 2-28** The bathtub curve for reliability.

 *bathtub curves*

Traditional VLSI manufacturing processes yielded chips that were remarkably reliable over a long period. Figure 2-28 illustrates the general form of failures vs. time for traditional processes. This curve is known as the **bathtub curve** because of its shape—many chips failed in the first few hours of operation, then few failures occurred for years, and finally chips started to fail at a higher rate as they wore out. Early chip failures are known as **infant mortality**; it may be caused by a variety of fabrication flaws that create marginal structures such as thin wires or malformed transistors. One commonly-used model for chip reliability is an exponential probability for failure [Mur93]:

$$R(t) = e^{-\lambda_0 t}. \quad (\text{EQ 2-30})$$

This model assumes that the failure rate starts high and rapidly decreases. Manufacturers generally **burn in** their chips for some period by running them with power so that marginal chips will fail at the factory rather than in the hands of the customer.

#### *types of failures*

The bathtub curve concerns itself with **hard failures**, meaning permanent functional failures of the chip. **Transient failures**, which cause errors on certain outputs, were not a major concern for quite some time in digital circuits, although they have long been a concern in memories. Transient failures can come from several causes, including bit flips and timing errors.

#### *failure rate measures*

The most common metric for failure rates is mean time to failure (MTTF). This metric defines the mean time to the next occurrence of a given failure mechanism. Based on MTTF, we can determine other interesting metrics, such as **lifetime**.

#### *reliability and nanometer processes*

As we move to nanometer processes, new sources of reliability become a concern. Many of these failure mechanisms promote transient failures. Unfortunately, we can't easily tell which chips in a fabrication lot will be more prone to transient failures; even if we could, throwing out all chips that may produce transient failures would drive yields to unacceptably low levels. The growing prominence of transient failures causes us to consider reliability throughout the design process.

In this section, we will first look at traditional sources of unreliability, then move on to the causes of unreliability in nanometer processes.

### 2.6.1 Traditional Sources of Unreliability

Semiconductor manufacturing processes are complex and build many different structures. As a result, several different important failure mechanisms have been identified for traditional VLSI processes [Ren06]:

- **diffusion and junctions** Crystal defects, impurity precipitation, mask misalignment, surface contamination.
- **oxides** Mobile ions, pinholes, interface states, hot carriers, time-dependent dielectric breakdown.
- **metallization** Scratches and voids, mechanical damage, non-ohmic contacts, step coverage, weak adhesion, improper thickness, corrosion, electromigration, stress migration.

- **passivation** Pinholes and cracks, thickness variations, contamination, surface inversion.

Several mechanisms stand out: **time-dependent dielectric breakdown (TDDB)**, **hot carriers**, **negative bias temperature instability (NTBI)**, electromigration, **stress migration** and **soft errors**. Some of these failure mechanisms target transistors while others come from interconnect.

*TDDB*

Time-dependent dielectric breakdown occurs because the electric fields across gate oxides induce stresses that damage the oxide. Small transistors require very thin oxides that are more susceptible to this form of damage. The traditional model for TDDB failure rates is known as Black's equation [Ren06]:

$$\text{MTTF} = A \times 10^{\beta E} e^{E_a/kT} \quad (\text{EQ 2-31})$$

In this formula,  $A$  is a constant,  $E_a$  is the activation energy in eV,  $E$  is the electric field intensity in MV/cm,  $\beta$  is the electric field intensity coefficient in cm/MV,  $k$  is Boltzmann's constant, and  $T$  is the absolute temperature.

*hot carriers*

A hot carrier is a carrier that gains enough energy to jump from the silicon substrate into the gate oxide. As these hot carriers accumulate, they create a space charge in the oxide that affects the transistor's threshold voltage and other parameters. Several factors, such as power supply voltage, channel length, and ambient temperature can affect the rate at which hot carriers are produced.

*NTBI*

Negative bias temperature instability is particular to pMOS devices. It refers to shifts in  $V_{th}/g_m$  due to stress that introduces interface states and space charge. Interestingly, this degradation can be reversed by applying a reverse bias to the transistor. As a result, it is not a significant failure mechanism for p-type transistors whose bias voltages change from forward to reverse regularly but is very important for DC-biased transistors.

*electromigration*

Electromigration is a degenerative failure mechanism for wires that we touched upon before. Aluminum wiring includes grains that carry many defects; these grain boundaries are the most important source of electromigration problems.

*stress migration*

Stress migration is caused by mechanical stress and can occur even when no current flows through the wire. These stresses are caused by the different thermal expansion coefficients of the wires and the materials in which they reside. Failures can be caused by long-term exposure

to moderate temperatures in the  $150^{\circ}\text{C} - 200^{\circ}\text{C}$  range. Failures can also occur due to short-term stresses at very high temperatures.


#### *soft errors*

Soft errors cause memory cells to change state. Soft errors can be caused by alpha particles that generate excess carriers as they travel through the substrate. The materials used in packages include small amounts of uranium and thorium, which is still enough to cause noticeable rates of soft errors.

### 2.6.2 Reliability in Nanometer Technologies

As we move to technologies beyond 90 nm, variations in many important parameters become very large. With so many parameters becoming more variable, we can no longer treat reliability as a deterministic problem—throwing out all potentially troublesome chips would drastically reduce yield, perhaps to zero. At nanometer geometries we must treat many design problems as probabilistic, not deterministic. Furthermore, other design parameters, such as power supply voltage and operating temperature, introduce additional factors that can cause significant numbers of transient failures.

**Figure 2-29** Leakage and frequency variations in manufactured chips [Bor0] © 2003 ACM.

 

#### *PVT challenges*

Borkar *et al.* [Bor03] identify variations in process, supply voltage, and temperature (PVT)—both systematic and random variations—as the key design challenge in nanometer technologies. Here, we will consider the nature of these challenges. In later sections, we will look at design techniques that can be used to mitigate these problems.

#### *process variations*

Both channel length and threshold voltage vary significantly in nanometer-scale transistors. One result of this is that leakage current can vary by huge amounts. Figure 2-29 shows variations in leakage current and maximum operating frequency measured from manufactured chips. The plot shows that leakage current can vary by 20x. Furthermore, the wid-

est variations occur in chips that operate at the highest frequencies. Chips that can operate at higher frequencies command higher premiums, but high-frequency chips with high leakage currents are less valuable and, if they leak enough, may be unusable.

*supply voltage variations*

The interconnect used to distribute power across the chip is not an ideal conductor and introduces its own transient behavior. The activity across the chip also changes as a function of space and time, causing variations in the current demanded from the power supply network. As the power supply voltage delivered at each point on the chip varies, the subthreshold leakage of transistors varies. Lower power supply voltages also result in slower switching speeds of gates. The minimum acceptable power supply voltage is determined by the required performance while the maximum acceptable power supply voltage is determined by the required reliability.

*temperature variations*

As chips operate at higher frequencies, the temperatures of the die change. Higher operating temperatures degrade the performance of both transistors and interconnect. Variations in temperature across the chip can cause communicating subsystems to run at different operating points, which can cause failures.

*thermal bounds*

Sato *et al.* [Sat05] define a headroom coefficient for current densities allowed for worst-case heat consumption:

$$\gamma_j = \frac{J_{max}(T_{junc})}{J_{max}(T_{spec})}. \quad (\text{EQ 2-32})$$

$J_{max}(T_{spec})$  is the maximum current density defined at the reference temperature of  $120^\circ\text{C}$ .  $J_{max}(T_{junc})$  is a current limit that gives the same mean time to failure as that given by Black's equation of Section (EQ 2-31). Since the temperatures at some junctions may be substantially higher than others due to variations in activity and current, Sato *et al.* report that  $J_{max}(T_{junc})$  may be as low as 30% of  $J_{max}(T_{spec})$ .

*on-chip temperature sensors*

Since semiconductor devices are temperature-sensitive, we can use them as sensors to measure on-chip temperature; these measurements can be used to drive thermal management hardware or software. Embedded temperature sensors may measure absolute or differential temperature [Alt06]. An absolute sensor is made from a pn junction that is found in one of the parasitic bipolar transistors shown in Figure 2-11. An MOS transistor can also be used as a sensor. Circuits around the sensor device convert the device behavior into a form useful for thermal management systems. Differential temperature sensors depend on thermocouple effects that relate voltage and temperature differences.

## 2.7 Layout Design and Tools


---

Layouts are very detailed and designing them can be very tedious and difficult. In this section, we will introduce some abstractions and methodologies to help us design layouts.

### 2.7.1 Layouts for Circuits

We ultimately want to design layouts for circuits. Layout design requires not only a knowledge of the components and rules of layout, but also strategies for designing layouts which fit together with other circuits and which have good electrical properties.

**Figure 2-30** Wires and wire segments.

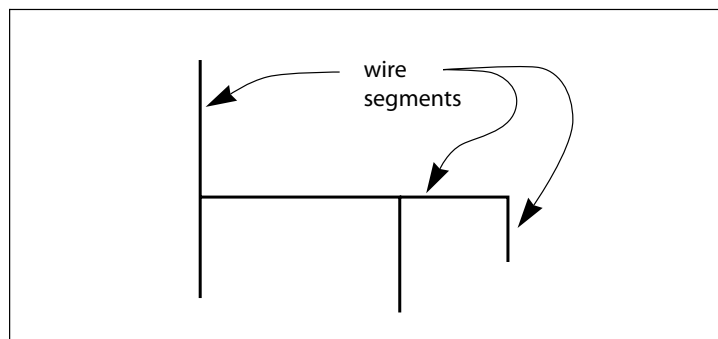


#### *terminology*

Since layouts have more physical structure than schematics, we need to augment our terminology. Chapter 1 introduced the term *net* to describe a set of electrical connections; a net corresponds to a variable in the voltage equations, but since it may connect many pins, it is hard to draw. A **wire** is a set of point-to-point connections; as shown in Figure 2-30, a wire may contain many branches. The straight sections are called **wire segments**.

#### *schematic diagrams*


The starting point for layout is a **circuit schematic**. The schematic symbols for n- and p-type transistors are shown in Figure 2-31. The schematic shows all electrical connections between transistors (except for tub ties, which are often omitted to simplify the diagram); it must also be annotated with the W/L of each transistor. We will discuss the design of logic circuits from transistors in detail in Chapter 3. At this point, we will treat the circuit schematic as a specification for which we must

 **Figure 2-31** Schematic symbols for transistors.

implement the transistors and connections in layout. (Most professional layout designers, in fact, have no training in electrical engineering and treat layout design strictly as an artwork design problem.) The next example walks through the design of an inverter's layout.

 
### Example 2-5 Design of an inverter layout

The inverter circuit is simple (+ is  $V_{DD}$  and the triangle is  $V_{SS}$ ):



In thinking about how the layout will look, a few problems become clear. First, we cannot directly connect the p-type and n-type transistors with pdiff and ndiff wires. We must use vias to go from ndiff to metal and then to pdiff. Second, the *in* signal is naturally in polysilicon, but the *out* signal is naturally in metal, since we must use a metal strap to connect the transistors' source and drain. Third, we must use metal for the power and ground connections. We probably want to place several layouts side-by-side, so we will run the power/ground signals from left to right across the layout.

 Assuming that both transistors are minimum size, here is one layout for the inverter:




We chose to put a metal-poly via at the inverter's input so the signal would be on the same layer at input and output; we might want to con-



nect the output of one inverter directly to the input of another. We ran power and ground along the top and bottom of the cell, respectively, placing the p-type transistor in the top half and the n-type in the bottom half. Larger layouts with many transistors follow this basic convention: p-type on the top, n-type on the bottom. The large tub spacing required between p-type and n-type devices makes it difficult to mix them more imaginatively. We also included a tub tie for both the n-tub and p-tub.

## 2.7.2 Stick Diagrams

**Figure 2-32** A stick diagram for an inverter.

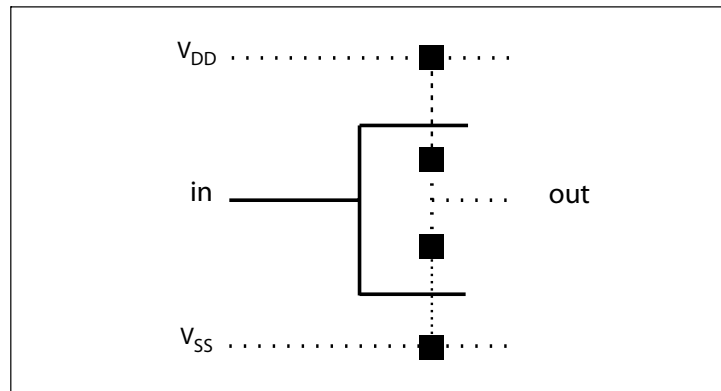


*sticks as abstract layout*

We must design a complete layout at some point, but designing a complex system directly in terms of rectangles can be overwhelming. We need an abstraction between the traditional transistor schematic and the full layout to help us organize the layout design. A **stick diagram** is a cartoon of a chip layout. Figure 2-32 shows a stick diagram for an inverter. The stick diagram represents the rectangles with lines which represent wires and component symbols. While the stick diagram does not represent all the details of a layout, it makes some relationships much clearer and it is simpler to draw.


Layouts are constructed from rectangles, but stick diagrams are built from cartoon symbols for components and wires. The symbols for wires used on various layers are shown in Figure 2-33. You probably want to draw your own stick diagrams in color: red for poly, green for n-diffusion, yellow for p-diffusion, and shades of blue for metal are typical colors. A few simple rules for constructing wires from straight-line segments ensure that the stick diagram corresponds to a feasible layout. First, wires cannot be drawn at arbitrary angles—only horizontal and

vertical wire segments are allowed. Second, two wire segments on the same layer which cross are electrically connected. Vias to connect wires that do not normally interact are drawn as black dots. Figure 2-34 shows the stick figures for transistors—each type of transistor is represented as poly and diffusion crossings, much as in the layout.

**Figure 2-33** Stick diagram symbols for wires.

 

**Figure 2-34** Symbols for components in stick diagrams.

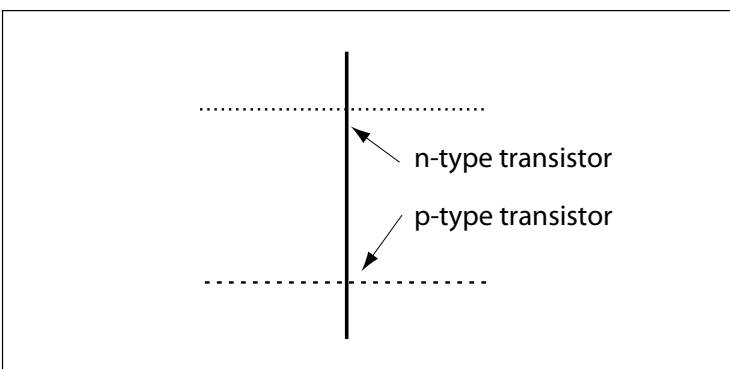

The complete rules which govern how wires on different layers interact are shown in Table 2-8; they tell whether two wires on given layers are allowed to cross and, if so, the electrical properties of the new construct. This table is derived from the manufacturing design rules.

*sticks vs. layout*

Stick diagrams are not exact models of layouts. Most of the differences are caused by the use of zero-width lines and zero-area transistors in stick diagrams. When you draw a layout using a stick diagram as a guide, you may find it necessary to move transistors and vias and to reroute wires. Area and aspect ratio are also difficult to estimate from

metal3	metal2	metal1	poly	ndiff	pdiff	
short	open	open	open	open	open	metal3
	short	open	open	open	open	metal2
		short	open	open	open	metal1
			short	n-type	p-type	poly
				short	illegal	ndiff
					short	pdiff

**Table 2-8** Rules for possible interactions between layers.

stick diagrams. But a stick diagram can be drawn much faster than a full-fledged layout and lets you evaluate a candidate design with relatively little effort. Stick diagrams are especially important tools for layouts built from large cells and for testing the connections between cells—tangled wiring within and between cells quickly becomes apparent when you sketch the stick diagram of a cell.


### 2.7.3 Hierarchical Stick Diagrams

*cell hierarchies*

Drawing a large chip as a single stick diagram—covering a huge sheet of butcher paper with arcane symbols—usually leads to a spaghetti layout. We can make use of hierarchy to organize stick diagrams and layouts just as with schematics. Components in a layout or hierarchical stick diagram are traditionally called **cells**. In schematics, we either invent a symbol for a type (e.g., logic gate symbols) or we use a box; however, the shape of the component symbol has no physical significance. Layouts and stick diagrams have physical extent. The simplest representation for a cell is its **bounding box**: a rectangle which just encloses all the elements of the cell. Bounding boxes are easy to generate; some layout tools require that cells be represented by rectangular bounding boxes. However, in some cases, we use non-rectangular **cell boundaries** to represent cells with very non-rectangular shapes.

Figure 2-35 shows a hierarchical stick diagram built from two copies of an inverter cell. The top-level cell in the hierarchy, *pair1*, includes some wires used to connect the cells together and to make external connections. Note that *pair1*'s wiring implies that the *inv1* stick diagram has


**Figure 2-35** A hierarchical stick diagram.

 

been redesigned so that, unlike the stick diagram of Figure 2-32, its input and output are both on the polysilicon layer. We sometimes want to show sticks cells in their entirety, and sometimes as outlines—some relationships between cells are apparent only when detail within a cell is suppressed. Hierarchical design is particularly useful in layout and sticks design because we can reuse sections of layout. Many circuits are designed by repeating the same elements over and over. Repeating cells saves work and makes it easier to correct mistakes in the design of cells.

 **Example 2-6**  
**Sticks design of a**  
**multiplexer**


A more interesting example of a stick diagram which takes advantage of hierarchy is a multiplexer (also known as a mux):




A two-input,  $n$ -bit multiplexer (in this case,  $n = 3$ ) has two  $n$ -bit data inputs and a select input, along with an  $n$ -bit data output. When **select** = 0, the data output's value is equal to the **a** data input's value; if **select** = 1, the data output's value is equal to **b**.

The multiplexer can be designed as a one-bit slice which can be replicated to create an  $n$ -bit system. The Boolean logic formula which determines the output value of one bit is  $o_i = (a_i \text{ select}) + (b_i \text{ select}')$ ; the value of  $o_i$  depends only on  $a_i$ ,  $b_i$ , and  $\text{select}$ . We can rewrite this formula in terms of two-input NAND gates:  $o_i = \text{NAND}(\text{NAND}(a_i, \text{select}), \text{NAND}(b_i, \text{select}'))$ . Since we know how to design the stick diagram for a NAND gate, we can easily design the one-bit multiplexer out of NAND cells.

 
Here is the transistor schematic for a two-input NAND gate:



 And here is a stick diagram for the two-input NAND:




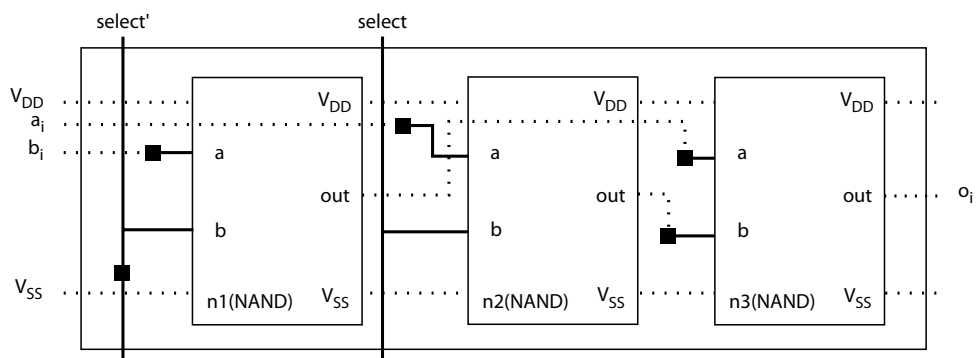We can use the NAND cell to build a one-bit multiplexer cell:



In this case we've drawn the hierarchical stick diagram using bounding boxes; to design the complete layout we would have to look into the cells. The connections designed between NAND cells were designed to avoid creating unwanted shorts with wires inside the NANDs; to be completely sure the intercell wires do not create problems, you must expand the view of the bit slice to include the internals of the NAND cells. However, making an initial wiring design using the NANDs as boxes, remembering the details of their internals as you work, makes it easier to see the relationships between wires that go between the cells.

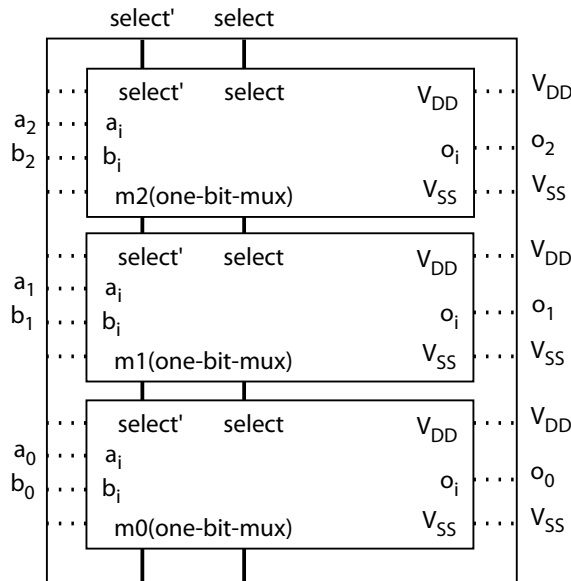We can build a three-bit multiplexer from our bit slice by stacking three instances of the slice cell along with a few wires:



The *select* signal was designed to run vertically through the cell so vertical connections could easily be made between stacked cells. The multiplexer inputs arrive at the left edge of the stack, while the multiplexer’s outputs leave at the right edge.

Constructing this three-bit multiplexer required very little labor—given a NAND cell, we were able to construct the bit slice with only a few extra wires; and given the bit slice building the complete multiplexer was almost trivial. Changing  $n$ , the width of the data word, is very simple. And last but not least, building large stick diagrams out of previously-designed smaller cells means the complete design is more likely to be correct: cells we have used before are likely to have been previously checked, and repeating cells gives us fewer opportunities to make simple mistakes while copying simple constructs.

### 2.7.4 Layout Design and Analysis Tools

#### *varieties of tools*

A variety of CAD tools help us design and verify layouts. The most important tools are **layout editors**, **design rule checkers**, and **circuit extractors**.

#### *layout editors*

A layout editor is an interactive graphic program that lets you create and delete layout elements. Most layout editors work on hierarchical layouts, organizing the layout into cells which may include both primitive layout elements and other cells. Some layout editing programs, such as Magic, work on **symbolic layouts**, which include somewhat more detail than do stick diagrams but are still more abstract than pure layouts. A via, for example, may be represented as a single rectangle while you edit the symbolic layout; when a final physical layout is requested, the symbolic via is fleshed out into all the rectangles required for your process. Symbolic layout has several advantages: the layout is easier to specify because it is composed of fewer elements; the layout editor ensures that the layouts for the symbolic elements are properly constructed; and the same symbolic layout can be used to generate several variations, such as n-tub, p-tub, and twin-tub versions of a symbolic design.

#### *design rule checking*

A design rule checker (often called a **DRC** program), as the name implies, looks for design rule violations in the layout. It checks for minimum spacing and minimum size and ensures that combinations of layers form legal components. The results of the DRC are usually shown as highlights on top of the layout. Some layout editors, including Magic, provide on-line design rule checking.

#### *circuit extraction*


**Circuit extraction** is an extension of design rule checking and uses similar algorithms. A design rule checker must identify transistors and vias to ensure proper checks—otherwise, it might highlight a transistor as a poly-diffusion spacing error. A circuit extractor performs a complete job of component and wire extraction. It produces a net list which lists the transistors in the layout and the electrical nets which connect their terminals. Vias do not appear in the net list—a via simply merges two nets into a single larger net. The circuit extractor usually measures parasitic resistance and capacitance on the wires and annotates the net list with those parasitic values. The next example describes how we can extract a circuit from a layout.


 
### Example 2-7 Circuit extraction

We will extract the circuit by successively identifying, then deleting components. After all component types have been extracted, only the wires will remain.

Identifying components from the layout requires manipulating masks singly and in combination. **Grow** and **shrink** are two important operations:



The grow operation increases the extent of each polygon in the mask by a fixed amount in every direction; the shrink operation does the converse. We will also need to form Boolean combinations of masks: the NOT of a mask covers all the area not covered by the mask itself; the AND of two masks covers only the area under both masks; and the OR includes the area covered by either mask. Boolean and grow/shrink operations generate new masks.

When we extract the circuit, we will assume the layout has no design-rule errors; we can always DRC the layout before extraction. We can identify all the transistors in the layout very easily: the n-type transistors' active areas are exactly the AND of the poly and the n-diff masks, with analogous definition for the p-type transistors. After identifying the transistors, we can remove them from the layout of the active-area mask, which leaves the gate, source, and drain connections hanging. We will mark and remember the locations of the transistors' terminals for the final step of extraction.

Identifying vias requires a little more effort. To identify poly-metal vias, we first grow the cut mask by  $2\lambda$ , then we form the AND of the grown-cut, metal, and poly masks. The result is one  $4\lambda$ -by- $4\lambda$  square for each poly-metal vias. After identifying all the vias, we remove them while marking their place. We can identify tub ties, but we won't need them for the later stages of analysis, since they don't make new electrical connections.

At this point, only the wires are left in the layout. A polygon on one layer forms an electrically connected region. However, we're not quite done, because connections may have been made by vias or by wires through transistors. To take account of all connections, we must first identify where each wire touches a connection point to a via or transistor. We then form the transitive closure of all the connection points: if one wire connects points A and B, and another wire connects B and C, then A, B, and C are all electrically connected.

Once we have traced through all the connections, we have a basic circuit description. We have not yet taken parasitics into account. To do so, we must count parasitics for each wire, via, and transistor, then mark each electrical node appropriately. However, for simple functional analysis, extracting parasitics may not be necessary. Here is a fragment of an extracted circuit written in Magic's *ext* format:

```
node "6_38_29#" 122 55 19 -14 green 0 0 0 0 54 34 0 0 92 62 0 0 0 0 0
node "6_50_15#" 120 10 25 -7 green 0 0 0 0 12 16 0 0 0 0 0 0 0 0 0
node "6_50_7#" 521 92 25 -3 green 0 0 60 44 30 22 0 0 80 64 0 0 0 0 0
node "6_36_19#" 825 12 18 -9 p 110 114 0 0 0 0 0 0 0 0 0 0 0 0 0
node "6_36_11#" 690 9 18 -5 p 92 96 0 0 0 0 0 0 0 0 0 0 0 0 0
node "6_40_40#" 559 83 20 20 brown 0 0 80 54 0 0 0 0 68 58 0 0 0 0 0
cap "6_36_19#" "6_50_7#" 1
fet nfet 25 -9 26 -8 12 16 "GND!" "6_36_19#" 4 0 "6_38_29#" 6 0 "6_50_15#" 6 0
fet nfet 25 -5 26 -4 12 16 "GND!" "6_36_11#" 4 0 "6_50_15#" 6 0 "6_50_7#" 6 0
fet pfet 39 17 40 18 12 16 "Vdd!" "6_36_19#" 4 0 "6_50_7#" 6 0 "6_40_40#" 6 0
fet pfet 25 17 26 18 12 16 "Vdd!" "6_36_11#" 4 0 "6_50_7#" 6 0 "6_40_40#" 6 0
```

The exact format of this file isn't important, but a few details should help make this information less forbidding. A *node* record defines an electrical node in the circuit—explicit declaration of the nodes simplifies the program which reads the file. The record gives total resistance and capacitance for the node, an *x, y* position which can be used to identify the node in the layout, and area and perimeter information for resistance extraction. A *cap* record gives two nodes and the capacitance between them. A *fet* record describes the type of transistor, the corners of its channel, and the electrical nodes to which the source, drain, and gate are connected.

---

The simplest extraction algorithm works on a layout without cells—this is often called flat circuit extraction because the component hierarchy is flattened to a single level before extraction. However, a flattened layout is very large: a layout built of one 100-rectangle cell repeated 100 times


---

will have 100 rectangles plus 100 (small) cell records; the same layout flattened to a single cell will have 10,000 rectangles. The largest chips today need over one billion rectangles to describe their mask sets. That added size claims penalties in disk storage, main memory, and CPU time.

*hierarchical circuit  
extraction*

**Hierarchical circuit extraction** extracts circuits directly on the hierarchical layout description. Dealing with cell hierarchies requires more sophisticated algorithms which are beyond our scope. Hierarchical extraction may also require design restrictions, such as eliminating overlaps between cells. However, one problem which must be solved illustrates the kinds of problems introduced by component hierarchies.

**Figure 2-36** Tracing nets for hierarchical circuit extraction.

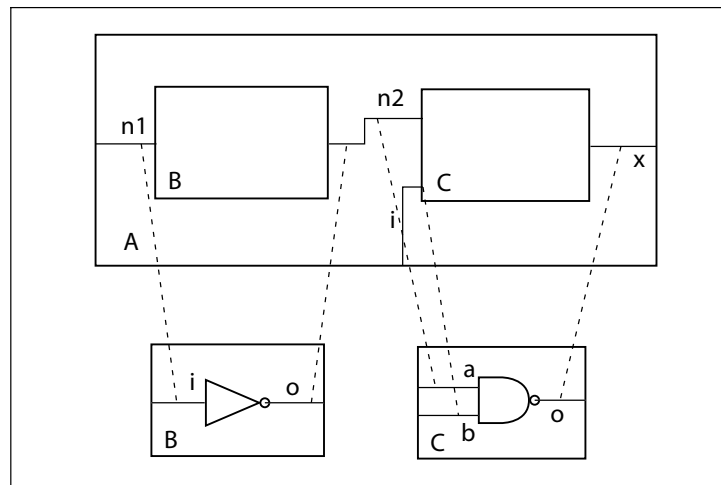

Consider the example of Figure 2-36. Each cell has its own net list. The net lists of leaf cells make sense on their own, but A's net list is written in terms of its components. We often want to generate a flattened net list—flattening the net list after extraction makes sense because the net list is much smaller than the layout. To create the flattened net list, we must make correspondences between nets in the cells and nets in the top-level component. Once again, we use transitive closure: if net *o* in cell *B* is connected to *n2* in *A*, which in turn is connected to net *a* in *C*, then *B.o*, *A.n2*, and *C.a* are all connected. Flattening algorithms can be very annoying if they choose the wrong names for combined elements. In this case, *n2*, the top-level component's name for the net, is probably the name most recognizable to the designer.

*verification from extracted circuits*

A circuit extracted from layout has two important uses. First, the extracted circuit can be simulated and the results compared to the specified circuit design. Serious layout errors, such as a missing transistor or wire, should show up as a difference in the specified and extracted circuits. Second, extracted parasitics can be used to calculate actual delays. Circuit performance may have been estimated using standard parasitic values or parasitics may have been ignored entirely, but long wires can slow down logic gates. Comparing the actual performance of the extracted layout to the predicted performance tells you whether the logic and circuits need to be modified and, if so, where critical delay problems exist.

### 2.7.5 Automatic Layout

Hierarchical stick diagrams are a good way to design large custom cells. But you will probably design large cells from scratch infrequently. You are much more likely to use layouts generated by one of two automated methods: **cell generators** (also known **macrocell generators**), which create optimized layouts for specialized functions such as ALUs; or **standard cell placement and routing**, which use algorithms to build layouts from gate-level cells.

*cell generators*


A cell generator is a parameterized layout—it is a program written by a person to generate the layout for a particular cell or a families of cells. The generator program is usually written textually, though some graphical layout editors provide commands to create parameterized layouts. If the generator creates only one layout, it may as well have been created with a graphical layout editor. But designers often want to create variations on a basic cell: changing the sizes of transistors, choosing the number of busses which run through a cell, perhaps adding simple logic functions. Specialized functions like ALUs, register files, and RAMs often require careful layout and circuit design to operate at high speed. Generator languages let skilled designers create parameterized layouts for such cells which can be used by chip designers whose expertise is in system design, not circuit and layout design.

*placement and routing*


Place-and-route programs take a very different approach to layout synthesis: they break the problem into placing components on the plane, then routing wires to make the necessary connections. Placement and routing algorithms may not be able to match the quality of hand-designed layouts for some specialized functions, but they often do better than people on large random logic blocks because they have greater patience to search through large, unstructured problems to find good solutions.

The most common placement-and-routing systems use **standard cells**, which are logic gates, latches, flip-flops, or occasionally slightly larger functions like full adders. Figure 2-37 shows the architecture of a standard cell layout: the component cells, which are of standard height but of varying width, are arranged in rows; wires are run in **routing channels** between the cell rows, along the sides, and occasionally through **feedthroughs** (spaces left open for wires in the component cells). The layout is designed in two stages: components are placed using approximations to estimate the amount of wire required to make the connections; then the wires are routed. Figure 2-38 shows a small standard cell layout generated by the *wolfe* program [San84, Sec85].

**Figure 2-37**  
Architecture of  
a standard cell  
layout.

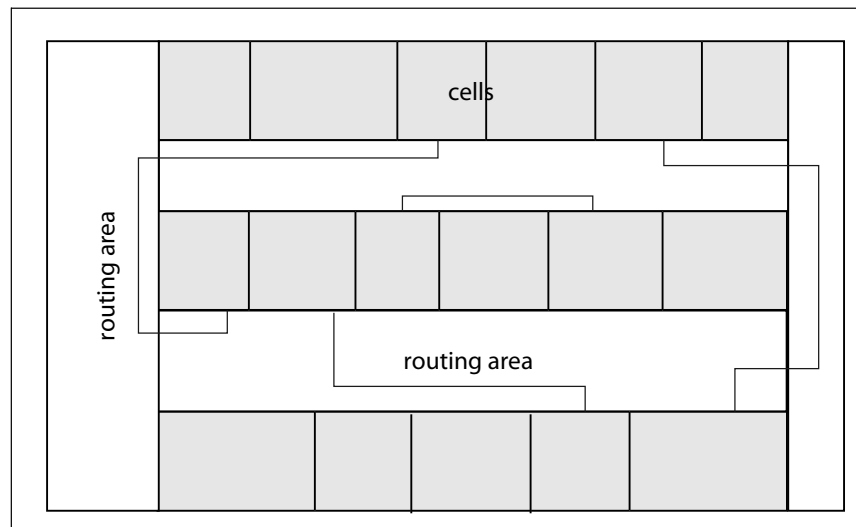

**Figure 2-38** An example of standard cell layout.

 

## 2.8 References

---

Dennard *et al.* [Den74] first explained why shrinking IC feature sizes led to higher performance as well as smaller chips. That observation led to the development of scalable design rules, which were first introduced by Mead and Conway [Mea80]. The specifications for the MOSIS SCMOS process were derived from MOSIS data. Complete documentation on the SCMOS rules is available on the World Wide Web at <http://www.mosis.edu>. The MOSIS SCMOS rules do occasionally change, so it is always best to consult MOSIS for the latest design rules before starting a design. Cheng *et al.* [Che00] survey modeling techniques for interconnect.

---

---

## 2.9 Problems

---

Use process parameters from Table 2-7 as required.

Q2-1. Draw the cross section of:

- a) A metal 1-metal 2 via.
- b) A poly-n-diffusion via.
- c) A p-type transistor.

Q2-2. What W/L is required to make the saturation drain current of a p-type transistor approximately equal to the saturation drain current of a minimum-width n-type transistor?

Q2-3. Plot  $I_d$  vs.  $V_{ds}$  through a minimum-size n-type transistor for a range of  $V_{ds}$  from 0V through the power supply voltage of 1.2 V. Plot for three values of  $V_{gs}$  : 0.6 V, 0.9 V, 1.2 V.

Q2-4. Plot  $I_d$  vs.  $V_{ds}$  through a minimum-size p-type transistor for a range of  $V_{ds}$  from 0V through the power supply voltage of 1.2 V. Plot for three values of  $V_{gs}$  : 0.6 V, 0.9 V, 1.2 V.

Q2-5. Redraw Figure 2-11 to show how tub ties modify the parasitic circuit in a way that reduces the occurrence of latch-up.

Q2-6. Replot the drain current curves of Q2-3 to include a channel length modulation factor  $\lambda = 0.05$ .

Q2-7. Give the reasoning behind each of these design rules:

- a) Overhang of poly at transistor gate.
- b) Metal 1 surround of via cut.
- c) Tub overhang.
- d) Poly-diffusion spacing.
- e) Via cut-via cut spacing.

Q2-8. Predict how metal 1 and metal 2 resistance would change for a 90 nm ( $\lambda = 45$  nm) process using:

- a) Ideal scaling.
  - b) Constant dimension scaling.
- 
-

Q2-9. Draw layouts for:

- a) A metal 1-n-diffusion via.
- b) A minimum width,  $25 \lambda$  poly wire.
- c) A  $4/3$  n-type transistor.
- d) A  $6/2$  p-type transistor.

Q2-10. Compute the parasitic resistance of:

- a) A minimum-width  $20 \lambda$  n-diffusion wire.
- b) A minimum-width  $20 \lambda$  p-diffusion wire.
- c) A minimum-width  $100 \lambda$  poly wire.
- d) A minimum-width  $1000 \lambda$  metal 1 wire.

Q2-11. Compute the parasitic capacitance of:

- a) A minimum-width  $20 \lambda$  n-diffusion wire.
- b) A minimum-width  $20 \lambda$  p-diffusion wire.
- c) A minimum-width  $100 \lambda$  poly wire.
- d) A minimum-width  $1000 \lambda$  metal 1 wire.

Q2-12. For each of these failure mechanisms, identify whether the mechanism pertains to a transistor or a wire:

- a) TDDB.
- b) Hot carriers.
- c) NTBI.
- d) Electromigration.
- e) Stress migration.

Q2-13. Draw a stick diagram for:

- a) An n-type transistor.
- b) A p-type transistor.
- c) A metal 1 wire connected to a poly wire.
- d) A metal 1 wire connected to an n-diffusion wire.

Q2-14. How should tub ties be treated during circuit extraction?

Q2-15. Write a netlist for the two-input NAND gate of Example 2-6.

---

---





# 3

## Logic Gates

### **Highlights:**

Combinational logic.

Static logic gates.


Delay and power.

Alternate gate structures: switch, domino, etc.

Wire delay models.

Design-for-yield.

Gates as IP.

 

An AOI-21 gate (Figure 3-7).

---

## 3.1 Introduction

---

This chapter concentrates on the design of combinational logic gates. The knowledge gained in the last chapter on fabrication is important for combinational logic design—technology-dependent parameters for minimum size, spacing, and parasitic values largely determine how big a gate circuit must be and how fast it can run.

We will start by reviewing some important facts about combinational logic functions. The first family of logic gate circuits we will consider in Section 3.3 are **static, fully complementary** gates, which are the mainstay of CMOS design. We will analyze the properties of these gates in detail: speed, power consumption, layout design, testability. Section 3.4 studies switch logic. Section 3.5 considers other circuits that can be used to build logic gates. Section 3.6 considers power consumption in gates. We will also study the delays through wires: resistive interconnect in Section 3.7 and inductive interconnect in Section 3.8. Section 3.9 studies design-for-yield. Section 3.10 looks at IP-based design at the gate level.

---

## 3.2 Combinational Logic Functions

---

*Boolean algebra and combinational logic*

We use Boolean algebra to represent the logical functions of digital circuits. Boolean algebra represents **combinational** (not combinatorial) **logic** functions. The Boolean functions describe combinations of inputs; we do not use functions with existential ( $\exists x f(x)$ ) or universal ( $\forall x g(x)$ ) quantification.

It is important to distinguish between *combinational logic expressions* and *logic gate networks*. A combinational logic expression is a mathematical formula which is to be interpreted using the laws of Boolean algebra: given the expression  $a + b$ , for example, we can compute its truth value for any given values of  $a$  and  $b$ ; we can also evaluate relationships such as  $a + b = c$ . A logic gate computes a specific Boolean function, such as  $(a + b)'$ .

*why we optimize logic*

The goal of logic design or optimization is to find a network of logic gates that together compute the combinational logic function we want. Logic optimization is interesting and difficult for several reasons:


---



---

- We may not have a logic gate for every possible function, or even for every function of  $n$  inputs. Lookup tables can represent any function of  $n$  inputs, but multiplexer-based logic elements are much more stylized. It therefore may be a challenge to rewrite our combinational logic expression so that each term represents a gate.
- Not all gate networks that compute a given function are alike—networks may differ greatly in their area and speed. For example, we may want to take advantage of the specialized adder circuitry in a logic element. We want to find a network that satisfies our area and speed requirements, which may require drastic restructuring of our original logic expression.

**Figure 3-1** Two logic gate implementations of a Boolean function.

 

*logic and gates*

Figure 3-1 illustrates the relationship between logic expressions and gate networks. The two expressions are logically equivalent:  $(a + b)'c = a'b'c$ . We have shown a logic gate network for each expression which directly implements each function—each term in the expression becomes a gate in the network. The two logic networks have very different structures. Which is best depends on the requirements—the relative importance of area and delay—and the characteristics of the technology. But we must work with both logic expressions and gate networks to find the best implementation of a function, keeping in mind:

- combinational logic expressions are the specification;
- logic gate networks are the implementation;
- area, delay, and power are the costs.

## 3.2 Combinational Logic Functions

127

*notation*

We will use fairly standard notation for logic expressions: if  $a$  and  $b$  are variables, then  $a'$  (or  $\bar{a}$ ) is the complement of  $a$ ,  $a \cdot b$  (or  $ab$ ) is the AND of the variables, and  $a + b$  is the OR of the variables. In addition, for the NAND function  $(ab)'$  we will use the  $|$  symbol<sup>1</sup>, for the NOR function  $(a + b)'$  we will use  $a \text{ NOR } b$ , and for exclusive-or ( $a \text{ XOR } b = ab' + a'b$ ) we will use the  $\oplus$  symbol. (Students of algebra know that XOR and AND form a ring.) We use the term **literal** for either the true form ( $a$ ) or complemented form ( $a'$ ) of a variable. Understanding the relationship between logical expressions and gates lets us study problems in the model that is simplest for that problem, then transfer the results. Two problems that are of importance to logic design but easiest to understand in terms of logical expressions are **completeness** and **irredundancy**.

*completeness*

A set of logical functions is complete if we can generate every possible Boolean expression using that set of functions—that is, if for every possible function built from arbitrary combinations of  $+$ ,  $\cdot$ , and  $'$ , an equivalent formula exists written in terms of the functions we are trying to test. We generally test whether a set of functions is complete by inductively testing whether those functions can be used to generate all logic formulas. It is easy to show that the NAND function is complete, starting with the most basic formulas:

- 1:  $a|(a|a) = a|a' = 1$ .
- 0:  $\{a|(a|a)\}|\{a|(a|a)\} = 1|1 = 0$ .
- $a'$ :  $a|a = a'$ .
- $ab$ :  $(a|b)|(a|b) = ab$ .
- $a + b$ :  $(a|a)|(b|b) = a'|b' = a + b$ .

From these basic formulas we can generate all the formulas. So the set of functions  $\{|, |\}$  can be used to generate any logic function. Similarly, any formula can be written solely in terms of NORs.

The combination of AND and OR functions, however, is not complete. That is fairly easy to show: there is no way to generate either 1 or 0 directly from any combination of AND and OR. If NOT is added to the set, then we can once again generate all the formulas:  $a + a' = 1$ , etc. In fact, both  $\{', \cdot\}$  and  $\{', +\}$  are complete sets.

---

1. The Scheffer stroke is a dot with a negation line through it. C programmers should note that this character is used as OR in the C language.

*redundancy  
and minimality*

Any circuit technology we choose to implement our logic functions must be able to implement a complete set of functions. Static, complementary circuits naturally implement NAND or NOR functions, but some other circuit families do not implement a complete set of functions. Incomplete logic families place extra burdens on the logic designer to ensure that the logic function is specified in the correct form.

A logic expression is irredundant if no literal can be removed from the expression without changing its truth value; otherwise, the expression is called **redundant**. For example,  $ab + ab'$  is redundant, because it can be reduced to  $a$ . An irredundant formula and its associated logic network have some important properties: the formula is smaller than a logically equivalent redundant formula; and the logic network is guaranteed to be testable for certain kinds of manufacturing defects. However, irredundancy is not a panacea. Irredundancy is not the same as **minimality**—there are many irredundant forms of an expression, some of which may be smaller than others, so finding one irredundant expression may not guarantee you will get the smallest design. Irredundancy often introduces added delay, which may be difficult to remove without making the logic network redundant. However, simplifying logic expressions before designing the gate network is important for both area and delay. Some obvious simplifications can be done by hand; CAD tools can perform more difficult simplifications on larger expressions.

### 3.3 Static Complementary Gates

---

This section concentrates on one family of logic gate circuits: the static complementary gate. These gates are static because they do not depend on stored charge for their operation. They are complementary because they are built from complementary (dual) networks of p-type and n-type transistors. The important characteristics of a logic gate circuit are its layout area, delay, and power consumption. We will concentrate our analysis on the inverter because it is the simplest gate to analyze and its analysis extends straightforwardly to more complex gates.

#### 3.3.1 Gate Structures

*pullups and pulldowns*

A static complementary gate is divided into a **pullup network** made of p-type transistors and a **pulldown network** made of n-type transistors. The gate's output can be connected to  $V_{DD}$  by the pullup network or


---



---

$V_{SS}$  by the pulldown network. The two networks are complementary to ensure that the output is always connected to exactly one of the two power supply terminals at any time: connecting the output to neither would cause an indeterminate logic value at the output, while connecting it to both would cause not only an indeterminate output value, but also a low-resistance path from  $V_{DD}$  to  $V_{SS}$ .

**Figure 3-2** Transistor schematic of a static complementary inverter.

 

*inverter*

The structure of an inverter is shown in Figure 3-2. The + stands for  $V_{DD}$  and the triangle stands for  $V_{SS}$ . In this case, a single transistor is sufficient in both the pullup and pulldown networks, since the inverter has only one input.

*NAND gate*

Figure 3-3 shows the structure of a two-input NAND gate. The pullup network is a parallel combination of p-type transistors while the pulldown network is a series combination of n-type transistors. This ensures that the output is 0 only when both inputs are 1.

*NOR gate*


Figure 3-4 shows the NOR gate. In this case, the pullup network is a series connection and the pulldown transistors are in parallel. Inspection shows that the inverter, NAND gate, and NOR gate all satisfy the complementarity requirement: for any combination of input values, the output value is connected to exactly one of  $V_{DD}$  or  $V_{SS}$ .

*other gate functions*


Gates can be designed for functions other than NAND and NOR by designing the proper pullup and pulldown networks. Networks that are series-parallel combinations of transistors can be designed directly from the logic expression the gate is to implement. In the pulldown network, series-connected transistors or subnetworks implement AND functions



**Figure 3-3** A static complementary NAND gate.

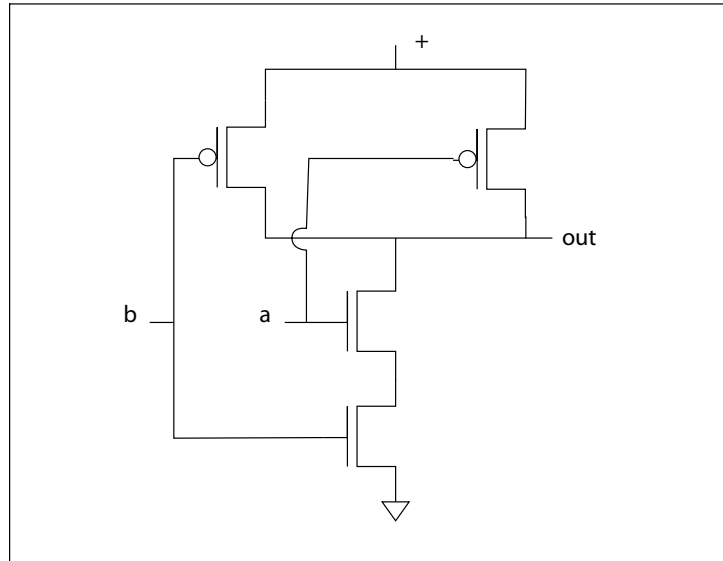


**Figure 3-4** A static complementary NOR gate.

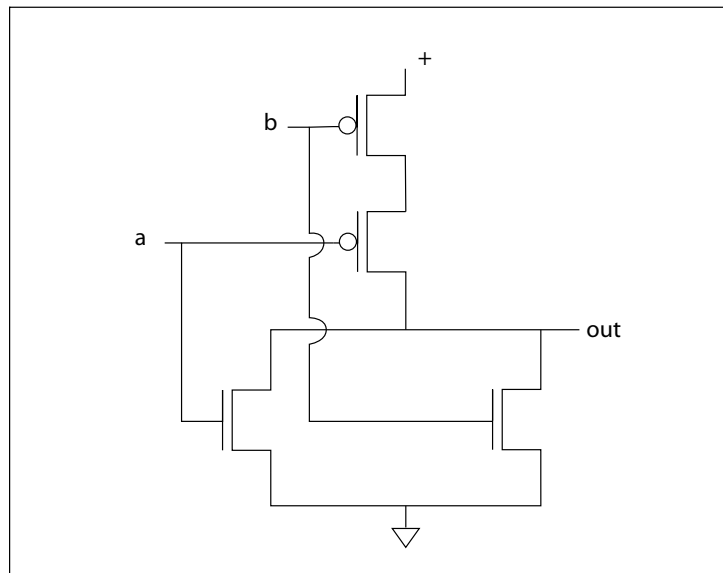

in the expression and parallel transistors or subnetworks implement OR functions. The converse is true in the pullup network because p-type transistors are off when their gates are high. Consider the design of a two-input NAND gate as an example. To design the pulldown network,

write the gate's logic expression to have negation at the outermost level:  $(ab)'$  in the case of the NAND. This expression specifies a series-connected pair of n-type transistors. To design the pullup network, rewrite the expression to have the inversion pushed down to the innermost literals:  $a' + b'$  for the NAND. This expression specifies a parallel pair of p-type transistors, completing the NAND gate design of Figure 3-3. Figure 3-5 shows the topology of a gate which computes  $[a(b+c)]'$ : the pulldown network is given by the expression, while the rewritten expression  $a' + (b'c')$  determines the pullup network.


**Figure 3-5** A static complementary gate that computes  $[a(b+c)]'$ .

 

*duality*

You can also construct the pullup network of an arbitrary logic gate from its pulldown network, or vice versa, because they are **duals**. Figure 3-6 illustrates the dual construction process using the pulldown network of Figure 3-5. First, add a dummy component between the output and the  $V_{SS}$  (or  $V_{DD}$ ) terminals. Assign a node in the dual network for each region, including the area not enclosed by wires, in the non-dual graph. Finally, for each component in the non-dual network, draw a dual component THAT is connected to the nodes in the regions separated by the non-dual component. The dual component of an n-type transistor is a p-type, and the dual of the dummy is the

**Figure 3-6** Constructing the pullup network from the pulldown network.

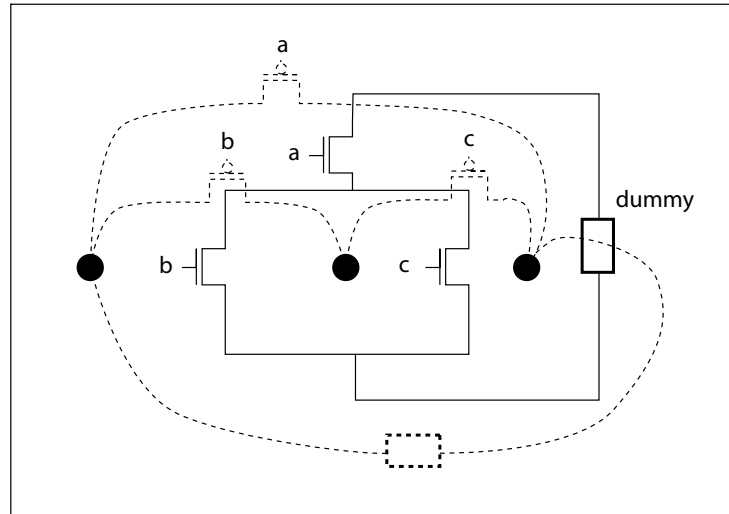


dummy. You can check your work by noting that the dual of the dual of a network is the original network.

#### *AOI and OAI gates*

Common forms of complex logic gates are **and-or-invert** (AOI) and **or-and-invert** (OAI) gates, both of which implement sum-of-products/product-of-sums expressions. The function computed by an AOI gate is best illustrated by its logic symbol, shown in Figure 3-7: groups of inputs are ANDed together, then all products are ORed together and inverted for output. An AOI-21 gate, like that shown in the figure, has two inputs to its first product and one input (effectively eliminating the AND gate) to its second product; an AOI-121 gate would have two one-input products and one two-input product.

It is possible to construct large libraries of complex gates with different input combinations. An OAI gate computes an expression in product-of-sums form: it generates sums in the first stage which are then ANDed together and inverted. An AOI or OAI function can compute a sum-of-products or product-of-sums expression faster and using less area than an equivalent network of NAND and NOR gates. Human designers rarely make extensive use of AOI and OAI gates, however, because people have difficulty juggling a large number of gate types in their heads. Logic optimization programs, however, can make very efficient use of AOI, OAI, and other complex gates to produce very efficient layouts.

**Figure 3-7** An and-or-invert-21 (AOI-21) gate.

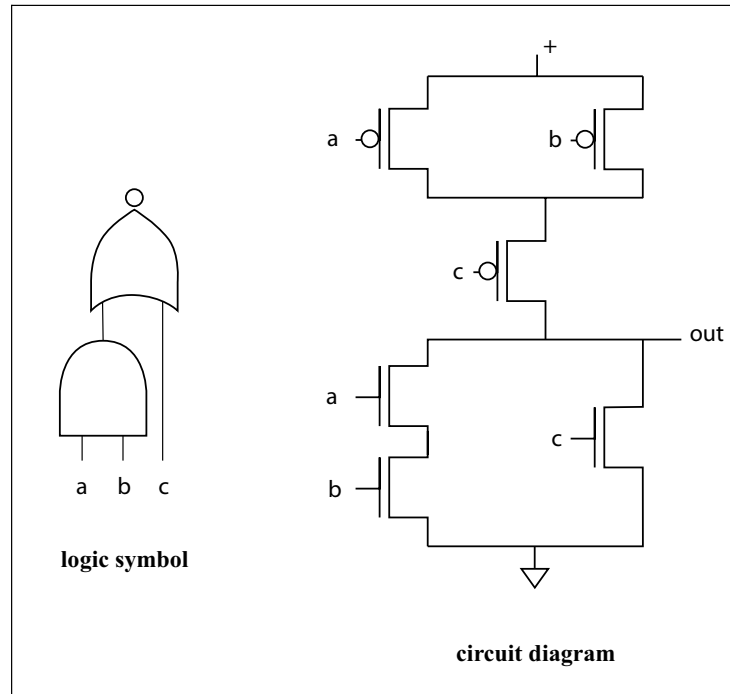

### 3.3.2 Basic Gate Layouts


*inverter layout*

Figure 3-8 shows a layout of an inverter. CMOS technology allows for relatively few major variations of the basic cell organization:  $V_{DD}$  and  $V_{SS}$  lines run in metal along the cell, with n-type transistors along the  $V_{SS}$  rail and p-types along the  $V_{DD}$  rail. In this case, the pullup and pull-down transistors are the same size; we will see that this is not ideal for optimizing delay.


*NAND gate layout*

Figure 3-9 shows a layout of a static NAND gate. Transistors in a gate can be densely packed—the NAND gate is not much larger than the inverter. The input and output signals of the NAND are presented at the cell's edge on different layers: the inputs are in poly while the output is in metal 1. If we want to cascade two cells, with the output of one feeding an input of another, we will have to add a via to switch layers; we will also have to add the space between the cells required for the via and make sure that the gaps in the  $V_{DD}$  and  $V_{SS}$  caused by the gap are bridged. The p-type transistors in the NAND gate were made wide to

**Figure 3-8**  
A layout of an inverter.

 


compensate for their lower current capability. The n-type transistors were also made wider because they are connected in series. We routed both input wires of the NAND to the transistor gates entirely in poly.

 

**Figure 3-9** A layout of a NAND gate.

*NOR gate layout*


Figure 3-10 shows a layout of a static NOR gate. We made the pullups wide because they are connected in series. We used minimum-sized pulldowns since they are connected in parallel. We used a metal 1 jumper to connect one of the inputs to all of the proper transistors.

 

**Figure 3-10** A layout of a NOR gate.

*splitting wide transistors*

If you are truly concerned with cell size, many variations are possible. Figure 3-11 shows a very wide transistor. A very wide transistor can create too much white space in the layout, especially if the nearby transis-

 

**Figure 3-11** A wide transistor split into two sections.

tors are smaller. We have split this transistor into two pieces, each half as wide, and turned one piece 180 degrees, so that the outer two sections of diffusions are used as drains and the inner sections become sources.


### 3.3.3 Logic Levels

*voltages and logic levels*

Since we must use voltages to represent logic values, we must define the relationship between the two. As Figure 3-12 shows, a range of voltages near  $V_{DD}$  corresponds to logic 1 and a band around  $V_{SS}$  corresponds to logic 0. The range in between is X, the unknown value. Although sig-



**Figure 3-12** How voltages correspond to logic levels.

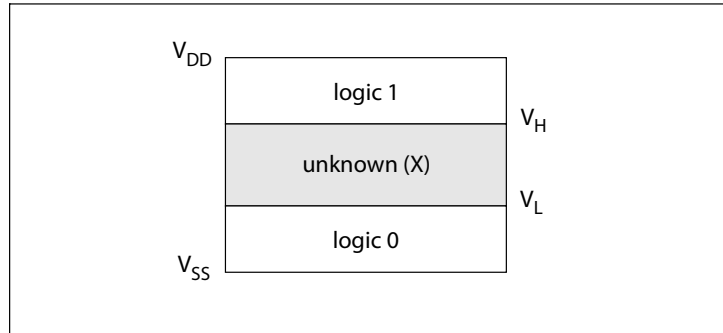


nals must swing through the X region while the chip is operating, no node should ever achieve X as its final value.

*ranges of legal voltages*

We want to calculate the upper boundary of the logic 0 region and the lower boundary of the logic 1 region. In fact, the situation is slightly more complex, as shown in Figure 3-13, because we must consider the logic levels produced at outputs and required at inputs. Given our logic gate design and process parameters, we can guarantee that the maximum voltage produced for a logic 0 will be some value  $V_{OL}$  and that the minimum voltage produced for a logic 1 will be  $V_{OH}$ . These same constraints place limitations on the input voltages which will be interpreted as a logic 0 ( $V_{IL}$ ) and logic 1 ( $V_{IH}$ ). If the gates are to work together, we must ensure that  $V_{OL} < V_{IL}$  and  $V_{OH} > V_{IH}$ .


**Figure 3-13** Logic levels on cascaded gates.

 


The output voltages produced by a static, complementary gate are  $V_{DD}$  and  $V_{SS}$ , so we know that the output voltages will be acceptable. (That isn't true of all gate circuits; the pseudo-nMOS circuit of Section 3.5.1 produces a logic 0 level well above  $V_{SS}$ .) We need to compute the values of  $V_{IL}$  and  $V_{IH}$  and to do the computation, we need to define those values. A standard definition is based on the **transfer characteristic** of the inverter—its output voltage as a function of its input voltage, assum-

3.3 Static Complementary Gates

**Figure 3-14** The inverter circuit used to measure transfer characteristics.

 

**Figure 3-15** Voltage transfer curve of an inverter.

 

ing that the input voltage and all internal voltages and currents are at equilibrium. Figure 3-14 shows the circuit we will use to measure an inverter's transfer characteristic. We the input voltage through its allowable range and measure the voltage at the output. Alternatively, we can solve the circuit's voltage and current equations to find  $V_{out}$  as a function of  $V_{in}$ ; we equate the drain currents of the two transistors and set their gate voltages to be complements of each other (since the n-type's gate voltage is measured relative to  $V_{SS}$  and the p-type's to  $V_{DD}$ ).

*transfer curve*

Figure 3-15 shows a transfer characteristic (simulated using Spice) of an inverter with minimum-size pulldown and pullup transistors. We define  $V_{IL}$  and  $V_{IH}$  as the points at which the curve's tangent has a slope of -1. Between these two points, the inverter has high gain—a small change in the input voltage causes a large change in the output voltage. Outside that range, the inverter has a gain less than 1, so that even a large change at the input causes only a small change at the output, attenuating the noise at the gate's input.


*noise margin*

The difference between  $V_{OL}$  and  $V_{IL}$  (or between  $V_{OH}$  and  $V_{IH}$ ) is called the **noise margin**—the size of the safety zone that prevents production of an illegal X output value. Since real circuits function under less-than-ideal conditions, adequate noise margins are essential for ensuring that the chip operates reliably. Noise may be introduced by a number of factors: it may be introduced by off-chip connections; it may be generated by capacitive coupling to other electrical nodes; or it may come from variations in the power supply voltage.

### 3.3.4 Delay and Transition Time

Delay is one of the most important properties of a logic gate—the majority of chip designs are limited more by speed than by area. An analysis of logic gate delay not only tells us how to compute the speed of a gate, it also points to parasitics that must be controlled during layout design to minimize delay. Later, in Section 3.3.7, we will apply what we have learned from delay analysis to the design of logic gate layouts.

**Figure 3-16** The inverter circuit used for delay analysis.

 

## 3.3 Static Complementary Gates

141

*delay metrics*

There are two interesting but different measures of combinational logic effort:

- **Delay** is generally used to mean the time it takes for a gate's output to arrive at 50% of its final value.
- **Transition time** is generally used to mean the time it takes for a gate to arrive at 10% (for a logic 0) or 90% (for a logic 1) of its final value; both **fall time**  $t_f$  and **rise time**  $t_r$  are transition times.

*inverters as delay models*

We will analyze delay and transition time on the simple inverter circuit shown in Figure 3-16; our analysis easily extends to more complex gates as well as more complex loads. We will assume that the inverter's input changes voltage instantaneously; since the input signal to a logic gate is always supplied by another gate, that assumption is optimistic, but it simplifies analysis without completely misleading us.

*load capacitance is important*

It is important to recognize that we are analyzing not just the gate delay but delay of the combination of the gate and the load it drives. CMOS gates have low enough gain to be quite sensitive to their load, which makes it necessary to take the load into account in even the simplest delay analysis. The load on the inverter is a single resistor-capacitor (RC) circuit; the resistance and capacitance come from the logic gate connected to the inverter's output and the wire connecting the two. We will see in Section 4.4.1 that other models of the wire's load are possible. There are two cases to analyze: the output voltage  $V_{out}$  is pulled down (due to a logic 1 input to the inverter); and  $V_{out}$  is pulled up. Once we have analyzed the 1  $\rightarrow$  0 output case, modifying the result for the 0  $\rightarrow$  1 case is easy.


*model for inverter delay*

While the circuit of Figure 3-16 has only a few components, a detailed analysis of it is difficult due to the complexity of the transistor's behavior. We need to further simplify the circuit. A detailed circuit analysis would require us to consider the effects of both pullup and pulldown transistors. However, our assumption that the inverter's input changes instantaneously between the lowest and highest possible values lets us assume that one of the transistors turns off instantaneously. Thus, when  $V_{out}$  is pulled low, the p-type transistor is off and out of the circuit; when  $V_{out}$  is pulled high, the n-type transistor can be ignored.

 *$\tau$  model*


There are several different models that people use to compute delay and transition time. The first is the  $\tau$  **model**, which was introduced by Mead and Conway [Mea80] as a simple model for basic analysis of digital circuits. This model reduces the delay of the gate to an RC time constant which is given the name  $\tau$ . As the sizes of the transistors in the gate are increased, the delay scales as well.

**Figure 3-17** Current through the pulldown during a  $1 \rightarrow 0$  transition.

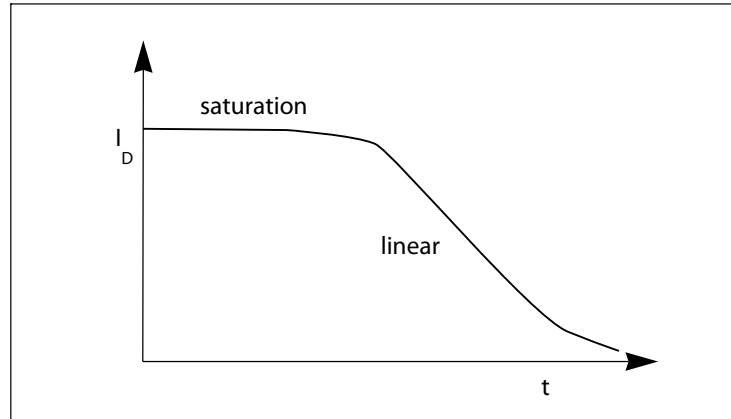

At the heart of the  $\tau$  model is the assumption that the pullup or pulldown transistor can be modeled as a resistor. The transistor does not obey Ohm's law as it drives the gate's output, of course. As Figure 3-17 shows, the pulldown spends the first part of the  $1 \rightarrow 0$  transition in the saturation region, then moves into the linear region. But the resistive model will give sufficiently accurate results to both estimate gate delay and to understand the sources of delay in a logic circuit.

**Figure 3-18** Test circuit for measuring load capacitance.

 

*capacitive load*

We also need to know the capacitive load that the inverter must drive. Gate-to-substrate capacitance is a large component of load capacitance, but as we move to smaller geometries, other capacitances have become important as well. We saw some of these capacitances in Chapter 2: gate-to-source and gate-to-drain, for example, as well as the capacitance of the wires connecting the transistors. The most effective way to determine the load capacitance is to use Spice to sum together all the capacitances that it models. (In our version of Spice, the statement `.option captab` post prints the total capacitance on all nodes.)

## 3.3 Static Complementary Gates

143

*unit load capacitance*

We define a **unit load capacitance**  $C_l$  as 1/2 of the load capacitance of a minimum-size inverter driving another minimum-size inverter. As shown in Figure 3-18, we can give Spice a test circuit that includes two minimum-size inverters and ask it to compute the capacitance of the node that connects the output of the first to the input of the second. The capacitance of that node is equal to  $2C_l$ . This technique captures more than just the parallel plate gate capacitance—it includes all the capacitances of the load transistors as well as the capacitances of the driving transistors that affect that node.

**Table 3-1** Unit load capacitance of an n-type or p-type transistor.

	capacitance per transistor
$C_l$	0.89 fF

Table 3-1 shows the unit load capacitance of an n-type or p-type transistor in our 180 nm process. Note that this value is per transistor, not per unit area. If we want to estimate the load capacitance  $C_L$  presented by another gate with different function and transistor sizes, we scale each transistor in the gate appropriately based on the transistor sizes:

$$C_L = \sum_{1 \leq i \leq n} \frac{W}{L_i} C_l. \quad (\text{EQ 3-1})$$

For the most accurate estimate of load capacitance, we should use Spice to analyze the full circuit.

*effective resistance*

How do we choose a resistor value to represent the transistor over its entire operating range? In older technologies, we can model the transistor's effective resistance by taking the average voltage/current at two points [Hod83]: the inverter's maximum output voltage,  $V_{DS} = V_{DD} - V_{SS}$ , where the transistor is in the saturation region; and the middle of the linear region,  $V_{DS} = (V_{DD} - V_{SS} - V_t)/2$ .

However, as we move to nanometer technologies, simple models become less and less accurate. A more accurate approach is to simply fit the resistance to the delay data obtained from Spice simulation. We must choose the delay metric to be used: delay or transition time. We then solve for the resistance that makes the RC model give the same timing as the Spice simulation's delay  $t_s$  at the required voltage  $V_f$  starting from an initial voltage  $V_0$ :

**Table 3-2** Effective resistance values (transition time) for minimum-size transistors in our 180 nm process.

type	$V_{DD}-V_{SS} = 1.2V$
$R_n$	<b>6.47 kΩ</b>
$R_p$	<b>29.6 kΩ</b>

$$R_{eff} = \frac{t_s}{C \ln\left(\frac{V_f}{V_0}\right)} \tag{EQ 3-2}$$

Table 3-2 shows the effective resistance values for transition time delay for our 180 nm process. The resistance values for minimum-size n-type and p-type transistors are shown in Table 3-2. The effective resistance of a transistor is scaled by  $L/W$ :


$$R_t = \frac{W}{L} R_{n,p} \tag{EQ 3-3}$$

The p-type transistor has about 4.5 times the effective resistance of an n-type transistor for this set of process parameters. If we used the 50% point delay as our metric, then we would need to fit the curves to different points, giving us different values for  $R$ .

*delay calculation*

Given these resistance and capacitance values, we can then analyze the delay and transition time of the gate.

**Figure 3-19** The circuit model for the  $\tau$  model delay.

 

*$\tau$  model calculation*

We can now develop the  $\tau$  model that helps us compute delay and transition time. Figure 3-19 shows the circuit model we use:  $R_n$  is the transistor's effective resistance while  $R_L$  and  $C_L$  are the load. The capacitor has an initial voltage of  $V_{DD}$ . The transistor discharges the load capacitor from  $V_{DD}$  to  $V_{SS}$ ; the output voltage as a function of time is

$$V_{\text{out}}(t) = V_{\text{DD}} e^{-t/[(R_n + R_L)C_L]} \quad (\text{EQ 3-4})$$

We typically use  $R_L$  to represent the resistance of the wire which connects the inverter to the next gate; in this case, we'll assume that  $R_L = 0$ , simplifying the total resistance to  $R = R_n$ .

#### 50% point calculation

For our example, we will use transition time, since that is the metric we used to find our  $R$  values; a similar analysis will give us delay. To measure fall time, we must calculate the time required to reach the 10% point. Then

$$0.1 = e^{-t_d/[(R_n + R_L)C_L]} \quad (\text{EQ 3-5})$$

$$t_d = -(R_n + R_L)C_L \ln 0.1 = 2.30(R_n + R_L)C_L \quad (\text{EQ 3-6})$$

The next example illustrates fall time in our manufacturing process.

### Example 3-1 Inverter transition time using the $\tau$ model

Once the effective resistance of a transistor is known, calculating transition time is easy. What is a minimum inverter delay and fall time with our 180 nm process parameters? Assume a minimum-size pulldown, no wire resistance, and a capacitive load equal to  $2C_L$ . First, the  $\tau$  model parameters:

$$\begin{aligned} R_n &= 6.47k\Omega \\ C_L &= 0.89 \frac{fF}{\mu m^2} \times 2 \\ &= 1.78fF \end{aligned}$$

Then fall time is

$$t_d = 2.3 \cdot 6.47k\Omega \cdot 1.78 \times 10^{-15} = 26.4ps .$$

If the transistors are not minimum size, their effective resistance is scaled by  $L/W$ . To compute the delay through a more complex gate, such as a NAND or an AOI, compute the effective resistance of the pullup/pulldown network using the standard Ohm's law simplifications, then plug the effective  $R$  into the delay formula.



*observations on transition time*

This simple RC analysis tells us two important facts about transition time. First, if the pullup and pulldown transistor sizes are equal, the  $0 \rightarrow 1$  transition will be slower than the  $1 \rightarrow 0$  transition, in proportion to  $R_p/R_n$ . That observation follows directly from the ratio of the p-type and n-type effective resistances. Put another way, to make the high-going and low-going transition times equal, the pullup transistor must be twice to three times as wide as the pulldown. Second, complex gates like NANDs and NORs require wider transistors where those transistors are connected in series. A NAND's pulldowns are in series, giving an effective pulldown resistance of  $2R_n$ . To give the same delay as an inverter, the NAND's pulldowns must be twice as wide as the inverter's pulldown. The NOR gate has two p-type transistors in series for the pullup network. Since a p-type transistor must be two to three times wider than an n-type transistor to provide equivalent resistance, the pullup network of a NOR can take up quite a bit of area.

*current source model*

A second model for delay is the **current source model**, which is sometimes used in power/delay studies because of its tractability. If we assume that the transistor acts as a current source whose  $V_{gs}$  is always at the maximum value, then the delay can be approximated as

$$t_f = \frac{C_L(V_{DD}-V_{SS})}{I_d} = \frac{C_L(V_{DD}-V_{SS})}{0.5k'(W/L)(V_{DD}-V_{SS}-V_t)^2}. \quad (\text{EQ 3-7})$$

*fitted model*


A third type of model is the **fitted model**. This approach measures circuit characteristics and fits the observed characteristics to the parameters in a delay formula. Fitted models use more sophisticated models than our simple  $\tau$  model. This technique is not well-suited to hand analysis but it is easily used by programs that analyze large numbers of gates.

*accuracy*

Figure 3-20 shows the results of Spice simulation of an inverter and the  $\tau$  RC model. The  $\tau$  model meets the inverter output at the 10% point, which is to be expected since we fitted the resistance value to achieve that goal. However, the RC waveform is not close to the inverter response at other points. You should always remember that the RC delay model is meant as only a rough approximation.

*accuracy vs. utility*

The fundamental reason for developing an RC model of delay is that we often can't afford to use anything more complex. Full circuit simulation of even a modest-size chip is infeasible: we can't afford to simulate even one waveform, and even if we could, we would have to simulate all possible inputs to be sure we found the worst-case delay. The RC model lets us identify sections of the circuit which probably limit circuit

 

**Figure 3-20** Comparison of inverter transition time to the  $\tau$  model.


performance; we can then, if necessary, use more accurate tools to more closely analyze the delay problems of that section.

#### *body effect*

Body effect, as we saw in Section 2.3.5, is the modulation of threshold voltage by a difference between the voltage of the transistor's source and the substrate—as the source's voltage rises, the threshold voltage also rises. This effect can be modeled by a capacitor from the source to the substrate's ground as shown in Figure 3-21. To eliminate body effect, we want to drive that capacitor to 0 voltage as soon as possible. If there is one transistor between the gate's output and the power supply, body effect is not a problem, but series transistors in a gate pose a challenge. Not all of the gate's input signals may reach their values at the same time—some signals may arrive earlier than others. If we connect early-arriving signals to the transistors nearest the power supply and late-arriving signals to transistors nearest the gate output, the early-arriving signals will discharge the body effect capacitance of the signals closer to the output. This simple optimization can have a significant effect on gate delay [Hil89].

#### *temperature dependence of delay*

Thermal effects also play a role in delay. Gate delays change at a rate of 4% per  $40^{\circ}\text{C}$  in a 130 nm process [Sat05, Ped06].

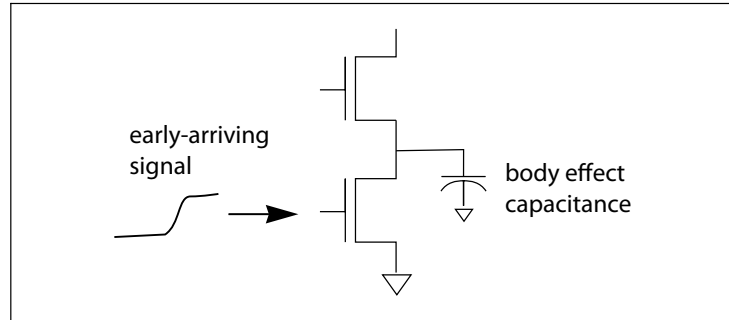**Figure 3-21** Body effect and signal ordering.

### 3.3.5 Power Consumption

Analyzing the power consumption of an inverter provides an alternate window into the cost and performance of a logic gate. Circuits can be made to go faster—up to a point—by causing them to burn more power. Power consumption always comes at the cost of heat which must be dissipated out of the chip. Static, complementary CMOS gates are remarkably efficient in their use of power to perform computation.

*static and dynamic power consumption*

Power is consumed by gates in two different ways:

- **dynamic** power is consumed when gates drive their outputs to new values;
- **static** power is consumed even when the gate is quiet and its output is not changing.

We can summarize this observation in a formula:


$$P = P_D + P_S. \quad (\text{EQ 3-8})$$

In earlier CMOS technologies, static power was negligible. However, in nanometer technologies, static power is very important. In today's most advanced technologies, static power consumption exceeds dynamic power consumption. CMOS gates consume dynamic power because they are charging and discharging their load capacitances. Static power is consumed because non-idealities in the transistors cause them to conduct current even when off. Static power consumption is best analyzed using Spice simulation. In this section, we will analyze dynamic power consumption to better understand its nature.

*circuit model for dynamic power*

Once again we will analyze an inverter with a capacitor connected to its output. However, to analyze power consumption we must consider both the pullup and pulldown phases of operation. The model circuit is

**Figure 3-22** Circuit used for power consumption analysis.

 

shown in Figure 3-22. The first thing to note about the circuit is that it has almost no steady-state power consumption. After the output capacitance has been fully charged or discharged, only one of the pullup and pulldown transistors is on. The following analysis ignores the leakage current; we will look at techniques to combat leakage current in Section 3.6.

*power and transistor size*

Power is consumed when gates drive their outputs to new values. Surprisingly, the power consumed by the inverter is independent of the sizes/resistances of its pullup and pulldown transistors—power consumption depends only on the size of the capacitive load at the output and the rate at which the inverter’s output switches. To understand why, consider the energy required to drive the inverter’s output high calculated two ways: by the current through the load capacitor  $C_L$  and by the current through the pullup transistor, represented by its effective resistance  $R_p$ .

*dynamic power calculation*

The current through the capacitor and the voltage across it are:

$$i_{CL}(t) = \frac{V_{DD}-V_{SS}}{R_p} e^{-(t/R_p C_L)}, \tag{EQ 3-9}$$

$$v_{CL}(t) = (V_{DD}-V_{SS})[1-e^{-(t/R_p C_L)}]. \tag{EQ 3-10}$$

So, the energy required to charge the capacitor is:

$$\begin{aligned}
 E_C &= \int_0^{\infty} i_{C_L}(t)v_{C_L}(t)dt && \text{(EQ 3-11)} \\
 &= C_L(V_{DD}-V_{SS})^2 \left( e^{-t/R_p C_L} - \frac{1}{2} e^{-2t/R_p C_L} \right) \Big|_0^{\infty} \\
 &= \frac{1}{2} C_L (V_{DD}-V_{SS})^2
 \end{aligned}$$

This formula depends on the size of the load capacitance but not the resistance of the pullup transistor. The current through and voltage across the pullup are:

$$i_p(t) = i_{C_L}(t), \quad \text{(EQ 3-12)}$$

$$v_p(t) = V e^{-(t/R_p C_L)}. \quad \text{(EQ 3-13)}$$

The energy required to charge the capacitor, as computed from the resistor's point of view, is

$$\begin{aligned}
 E_R &= \int_0^{\infty} i_p(t)v_p(t)dt && \text{(EQ 3-14)} \\
 &= C_L(V_{DD}-V_{SS})^2 \left( e^{-2t/R_p C_L} \right) \Big|_0^{\infty} \\
 &= \frac{1}{2} C_L (V_{DD}-V_{SS})^2
 \end{aligned}$$

Once again, even though the circuit's energy consumption is computed through the pullup, the value of the pullup resistance drops from the energy formula. (That holds true even if the pullup is a nonlinear resistor.) The two energies have the same value because the currents through the resistor and capacitor are equal.

*energy per cycle*

The energy consumed in discharging the capacitor can be calculated the same way. The discharging energy consumption is equal to the charging power consumption:  $1/2 C_L(V_{DD}-V_{SS})^2$ . A single cycle requires the capacitor to both charge and discharge, so the total energy consumption is  $C_L(V_{DD}-V_{SS})^2$ .

## 3.3 Static Complementary Gates

151

*power as a function of clock frequency*

Power is energy per unit time, so the power consumed by the circuit depends on how frequently the inverter's output changes. The worst case is that the inverter alternately charges and discharges its output capacitance. This sequence takes two clock cycles. The clock frequency is  $f = 1/t$ . The total power consumption is

$$fC_L(V_{DD}-V_{SS})^2. \quad (\text{EQ 3-15})$$

Dynamic power consumption in CMOS circuits depends on the frequency at which they operate, which is very different from nMOS or bipolar logic circuits. Power consumption depends on clock frequency because most power is consumed while the outputs are changing; most other circuit technologies burn most of their power while the circuit is idle. Dynamic power consumption depends on the sizes of the transistors in the circuit only in that the transistors largely determine  $C_L$ . The current through the transistors, which is determined by the transistor  $W/L$ , doesn't determine power consumption, though the available transistor current does determine the maximum speed at which the circuit can run, which indirectly determines power consumption.

*analysis*

Does it make sense that CMOS dynamic power consumption should be independent of the effective resistances of the transistors? It does, when you remember that CMOS circuits consume only dynamic power. Most power calculations are made on static circuits—the capacitors in the circuit have been fully charged or discharged, and power consumption is determined by the current flowing through resistive paths between  $V_{DD}$  and  $V_{SS}$  in steady state. Dynamic power calculations, like those for our CMOS circuit, depend on the current flowing through capacitors; the resistors determine only maximum operating speed, not power consumption.

*power supply voltage*

Static complementary gates can operate over a wide range of voltages, allowing us to trade delay for power consumption. To see how performance and power consumption are related, let's consider changing the power supply voltage from its original value  $V$  to a new  $V'$ . It follows directly from Equation 3-15 that the ratio of power consumptions  $P'/P$  is proportional to  $V'^2/V^2$ . When we compute the ratio of rise times  $t'_r/t_r$ , the only factor to change with voltage is the transistor's equivalent resistance  $R$ , so the change in delay depends only on  $R'/R$ . If we use the technique of Section 3.3.4 to compute the new effective resistance, we find that  $t'_r/t_r \propto V/V'$ . So as we reduce power supply voltage, power consumption goes down faster than does delay.

### 3.3.6 The Speed-Power Product

*power-delay product*

The **speed-power product**, also known as the **power-delay product**, is an important measure of the quality of a logic circuit family. Since delay can in general be reduced by increasing power consumption, looking at either power or delay in isolation gives an incomplete picture.

The speed-power product for ideal static CMOS is easy to calculate. If we ignore leakage current and consider the speed and power for a single inverter transition, then we find that the speed-power product  $SP$  is

$$SP = \frac{1}{f}P = CV^2. \quad (\text{EQ 3-16})$$

The speed-power product for static CMOS is independent of the operating frequency of the circuit. It is, however, a quadratic function of the power supply voltage. This result suggests an important method for power consumption reduction known as **voltage scaling**: we can often reduce power consumption by reducing the power supply voltage and adding parallel logic gates to make up for the lower performance. Since the power consumption shrinks more quickly than the circuit delay when the voltage is scaled, voltage scaling is a powerful technique. We will study techniques for low-power gate design in Section 3.6.


### 3.3.7 Layout and Parasitics

How do parasitics affect the performance of a single gate? As shown in the next example, answering this question tells us how to design the layout of a gate to maximize performance and minimize area.

---

 **Example 3-2**  
**Parasitics and**  
**performance**


To answer the question, we will consider the effects of adding resistance and capacitance to each of the labeled points of this layout:



- **a**  
Adding capacitance to point **a** (or its conjugate point on the  $V_{SS}$  wire) adds capacitance to the power supply wiring. Capacitance on this node doesn't slow down the gate's output.
- 
-



 Resistance at **a** can cause problems. Resistance in the  $V_{SS}$  line can be modeled by this equivalent circuit:



The power supply resistance is in series with the pulldown. That differential isn't a serious problem in static, complementary gates. The resistance slows down the gate, but since both the transistor gates of the pullup and pulldown are connected to the same electrical node, we can be sure that only one of them will be on in steady state. However, the dynamic logic circuits we will discuss in Section 3.5 may not work if the series power supply resistance is too high, because the voltages supplied by the gate with resistance may not properly turn on succeeding transistor gates.

The layout around point **a** should be designed to minimize resistance. A small length of diffusion is required to connect the transistors to the power lines, but power lines should be kept in metal as long as possible. If the diffusion wire is wider than a via (to connect to a wide transistor), several parallel vias should be used to connect the metal and diffusion lines.


- **b**

Capacitance at **b** adds to the load of the gate driving this node. However, the transistor capacitances are much larger than the capacitance added by the short wire feeding the transistor gates. Resistance at **b** actually helps isolate the previous gate from the load capacitance, as we will see when we discuss the  $\pi$  model in Section 4.4.1. Gate layouts should avoid making big mistakes by using large sections of diffusion wire or a single via to connect high-current wires.

- c

Capacitance and resistance at c are companions to parasitics at b—they form part of the load that this gate must drive, along with the parasitics of the b zone of the next gate. But if we consider a more accurate model of the parasitics, we will see that not all positions for parasitic  $R$  and  $C$  are equally bad.

 Up to now we have modeled the resistance and capacitance of a wire as one lump. Now let's consider the inverter's load as two RC sections:



One  $RC$  section is contributed by the wires at point c, near the output; the  $RC$  section comes from the long wire connecting this gate to the next one. How does the voltage at point x—the input to the next gate—depend on the relative values of the  $R$ 's? The simplified circuit shows how a large value for  $R_x$ , which is supplied by the parasitics at point c, steals current from  $R_L C_L$ . As  $R_x$  grows relative to  $R_L$ , the voltage drop across  $R_x$  increases, increasing the current through  $R_x$  while decreasing the current through  $R_L$ . As a result, more of the current supplied by the gate will go through  $C_x$ ; only after it is fully charged will  $C_L$  get the full current supplied by the gate.  $C_L$  is almost certainly significantly larger than  $C_x$  because it includes both the transistor capacitances and the long-wire capacitance, it is more important to charge  $C_L$  to switch the next gate as quickly as possible. But charging/discharging of  $C_L$  has been delayed while  $R_x$  diverts current into  $C_x$ .

The moral is that resistance close to the gate output is worse than resistance farther away—close-in resistance must charge more capacitors, slowing down the signal swing at the far end of the wire. Therefore, the layout around c should be designed to minimize resistance by:

- using as little diffusion as possible—diffusion should be connected to metal (or perhaps poly) as close to the channel as possible;
  - using parallel vias at the diffusion/metal interface to minimize resistance.
-


### 3.3.8 Driving Large Loads

#### *sources of large loads*

Logic delay increases as the capacitance attached to the logic's output becomes larger. In many cases, one small logic gate is driving an equally small logic gate, roughly matching drive capability to load. However, there are several situations in which the capacitive load can be much larger than that presented by a typical gate:

- driving a signal connected off-chip;
- driving a long signal wire;
- driving a clock wire that goes to many points on the chip.

The obvious answer to driving large capacitive loads is to increase current by making wider transistors. However, this solution begs the question—those large transistors simply present a large capacitive load to the gate that drives them, pushing the problem back one level of logic. It is inevitable that we must eventually use large transistors to drive the load, but we can minimize delay along the path by using a sequence of successively larger drivers.

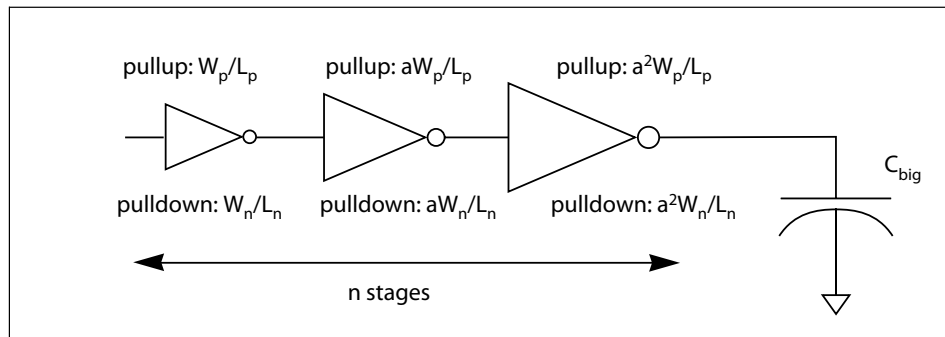

**Figure 3-23** Cascaded inverters driving a large capacitive load.

#### *exponentially tapered driver chains*

The driver chain with the smallest delay to drive a given load is exponentially tapered—each stage supplies  $e$  times more current than the last [Jae75]. In the chain of inverters of Figure 3-23, each inverter can produce  $\alpha$  times more current than the previous stage (implying that its pullup and pulldown are each  $\alpha$  times larger). If  $C_L$  is the load capacitance of a minimum-size inverter, the number of stages  $n$  is related to  $\alpha$  by the formula  $\alpha = (C_{big}/C_L)^{1/n}$ . The time to drive a minimum-size load is  $t_{min}$ . We want to minimize the total delay through the driver chain:

$$t_{tot} = n \left( \frac{C_{big}}{C_L} \right)^{1/n} t_{min}. \quad (\text{EQ 3-17})$$

To find the minimum, we set  $\frac{dt_{tot}}{dn} = 0$ , which gives

$$n_{opt} = \ln \left( \frac{C_{big}}{C_L} \right). \quad (\text{EQ 3-18})$$

When we substitute the optimal number of stages back into the definition of  $\alpha$ , we find that the optimum value is at  $\alpha = e$ . Of course,  $n$  must be an integer, so we will not in practice be able to implement the exact optimal circuit. However, delay changes slowly with  $n$  near the optimal value, so rounding  $n$  to the floor of  $n_{opt}$  gives reasonable results.


### 3.4 Switch Logic

We can use switches to implement Boolean functions. However, there is more than one way to build a switch from transistors.

*transmission gate*

One way is the **transmission gate** shown in Figure 3-24, built from parallel n-type and p-type transistors. This switch is built from both types of transistors so that it transmits logic 0 and 1 from drain to source equally well: when you put a  $V_{DD}$  or  $V_{SS}$  at the drain, you get  $V_{DD}$  or  $V_{SS}$  at the source. But it requires two transistors and their associated tubs; equally damning, it requires both true and complement forms of the gate signal.

**Figure 3-24**  
A complementary transmission gate.

 


*n-type switch*

An alternative is the **n-type switch**—a solitary n-type transistor. It requires only one transistor and one gate signal, but it is not as forgiving electrically: it transmits a logic 0 well, but when  $V_{DD}$  is applied to the

drain, the voltage at the source is  $V_{DD} - V_{in}$ . When switch logic drives gate logic, n-type switches can cause electrical problems. An n-type switch driving a complementary gate causes the complementary gate to run slower when the switch input is 1: since the n-type pulldown current is weaker when a lower gate voltage is applied, the complementary gate's pulldown will not suck current off the output capacitance as fast. When the n-type switch drives a pseudo-nMOS gate, disaster may occur. A pseudo-nMOS gate's ratioed transistors depend on logic 0 and 1 inputs to occur within a prescribed voltage range. If the n-type switch doesn't turn on the pseudo-nMOS pulldown strongly enough, the pull-down may not divert enough current from the pullup to force the output to a logic 0, even if we wait forever. Ratioed logic driven by n-type switches must be designed to produce valid outputs for both polarities of input.

**Figure 3-25** Circuit model for switch delay.

 

*switch logic delay*

When we calculate the delay through either an n-type or complementary switch, we need to properly account for the circuit capacitances [Bak05]. The transistor resistance can be modeled the same way as for static gates. The gate capacitance of the transistor used as the switch is divided between the source and drain. This gives a total load capacitance as

$$C_{tot} = \frac{C_g}{2} + C_L. \tag{EQ 3-19}$$

The delay through the switch is then

$$t_d = 0.7R_n\left(\frac{C_g}{2} + C_L\right), \tag{EQ 3-20}$$

*switch logic and noise*

Both types of switch logic are sensitive to noise—pulling the source beyond the power supply (above  $V_{DD}$  or below  $V_{SS}$ ) causes the transistor to start conducting. We will see in Section 4.6 that logic networks made of switch logic are prone to errors introduced by parasitic capacitance.

---

## 3.5 Alternative Gate Circuits

---

*gate design trade-offs*

The static complementary gate has several advantages: it is reliable, easy to use in large combinational logic networks, and does not require any separate precharging steps. It is not, however, the only way to design a logic gate with p-type and n-type transistors. Other circuit topologies have been created that are smaller or faster (or both) than static complementary gates. Still others use less power.

In this section we will review the design of several important alternative CMOS gate topologies. Each has important uses in chip design. But it is important to remember that they all have their limitations and caveats. Specialized logic gate designs often require more attention to the details of circuit design—while the details of circuit and layout design affect only the speed at which a static CMOS gate runs, circuit and layout problems can cause a fancier gate design to fail to function correctly. Particular care must be taken when mixing logic gates designed with different circuit topologies to ensure that one's output meets the requirements of the next's inputs. A good, conservative chip design strategy is to start out using only static complementary gates, then to use specialized gate designs in critical sections of the chip to meet the project's speed or area requirements.

### 3.5.1 Pseudo-nMOS Logic


*pseudo-nMOS*

The simplest non-standard gate topology is **pseudo-nMOS**, so called because it mimics the design of an nMOS logic gate. Figure 3-26 shows a pseudo-nMOS NOR gate. The pulldown network of the gate is the same as for a fully complementary gate. The pullup network is replaced by a single p-type transistor whose gate is connected to  $V_{SS}$ , leaving the transistor permanently on. The p-type transistor is used as a resistor: when the gate's inputs are  $ab = 00$ , both n-type transistors are off and the p-type transistor pulls the gate's output up to  $V_{DD}$ . When either a or

---

---

**Figure 3-26** A pseudo-nMOS NOR gate.

 

b is 1, both the p-type and n-type transistor are on and both are fighting to determine the gate's output voltage.

*transistor sizing*

We need to determine the relationship between the  $W/L$  ratios of the pullup and the pulldowns that provide reasonable output voltages for the gate. For simplicity, assume that only one of the pulldown transistors is on; then the gate circuit's output voltage depends on the ratio of the effective resistances of the pullup and the operating pulldown. The high output voltage of the gate is  $V_{DD}$ , but the output low voltage  $V_{OL}$  will be some voltage above  $V_{SS}$ . The chosen  $V_{OL}$  must be low enough to activate the next logic gate in the chain. For pseudo-nMOS gates that feed static or pseudo-nMOS gates, a value of  $V_{OL} = 0.15(V_{DD} - V_{SS})$  is a reasonable value, though others could be chosen. To find the transistor sizes that give appropriate output voltages, we must consider the simultaneous operation of the pullup and pulldown. When the gate's output has just switched to a logic 0, the n-type pulldown is in saturation with  $V_{gs,n} = V_{in}$ . The p-type pullup is in its linear region: its  $V_{gs,p} = V_{DD} - V_{SS}$  and its  $V_{ds,p} = V_{out} - (V_{DD} - V_{SS})$ . We need to find  $V_{out}$  in terms of the  $W/L$ s of the pullup and pulldown. To solve this problem, we set the currents through the saturated pulldown and the linear pullup to be equal:


$$\frac{1}{2}k'_n \frac{W_n}{L_n} (V_{gs,n} - V_{tn})^2 = \frac{1}{2}k'_p [2(V_{gs,p} - V_{tp})V_{ds,p} - V_{ds,p}^2] \quad \text{(EQ 3-21)}$$

The simplest way to solve this equation is to substitute the technology and circuit values. Using the 0.5 μm values and assuming a 3.3V power supply and a full-swing input ( $V_{gs,n} = V_{DD} - V_{SS}$ ), we find that

$$\frac{W_p/L_p}{W_n/L_n} \approx 3.9 \quad . \quad \text{(EQ 3-22)}$$

The pulldown network must exhibit this effective resistance in the worst case combination of inputs. Therefore, if the network contains series pulldowns, they must be made larger to provide the required effective resistance.

**Figure 3-27** Currents in a pseudo-nMOS gate during low-to-high transition.

 

*power consumption*

The pseudo-nMOS gate consumes static power. When both the pullup and pulldown are on, the gate forms a conducting path from  $V_{DD}$  to  $V_{SS}$ , which must be kept on to maintain the gate's logic output value. The choice of  $V_{OL}$  determines whether the gate consumes static power when its output is logic 1. If pseudo-nMOS feeds pseudo-nMOS and  $V_{OL}$  is chosen to be greater than  $V_{t,n}$ , then the pulldown will remain on. Whether the pulldown is in the linear or saturation region depends on the exact transistor characteristics, but in either case, its drain current will be low since  $V_{gs,n}$  is low. As shown in Figure 3-27, so long as the pulldown drain current is significantly less than the pullup drain current, there will be enough current to charge the output capacitance and bring the gate output to the desired level.

The ratio of the pullup and pulldown sizes also ensures that the times for  $0 \rightarrow 1$  and  $1 \rightarrow 0$  transitions are asymmetric. Since the pullup transistor has about three times the effective resistance of the pulldown, the  $0 \rightarrow 1$  transition occurs much more slowly than the  $1 \rightarrow 0$  transition and domi-



nates the gate’s delay. The long pullup time makes the pseudo-nMOS gate slower than the static complementary gate.

*uses of pseudo-nMOS*


Why use a pseudo-nMOS gate? The main advantage of the pseudo-nMOS gate is the small size of the pullup network, both in terms of number of devices and wiring complexity. The pullup network of a static complementary gate can be large for a complex function. Furthermore, the input signals do not have to be routed to the pullup, as in a static complementary gate. The pseudo-nMOS gate is used for circuits where the size and wiring complexity of the pullup network are major concerns but speed and power are less important. We will see two examples of uses of pseudo-nMOS circuits in Chapter 6: busses and PLAs. In both cases, we are building **distributed NOR gates**—we use pulldowns spread over a large physical area to compute the output, and we do not want to have to run the signals that control the pulldowns around this large area. Pseudo-nMOS circuits allow us to concentrate the logic gate’s functionality in the pulldown network.

3.5.2 DCVS Logic

*latching structures in gates*

**Differential cascode voltage switch logic** (DCVSL) is a static logic family that, like pseudo-nMOS logic, does not have a complementary pullup network, but it has a very different structure. It uses a latch structure for the pullup which both eliminates non-leakage static power consumption and provides true and complement outputs.

**Figure 3-28**  
Structure of a DCVSL gate.

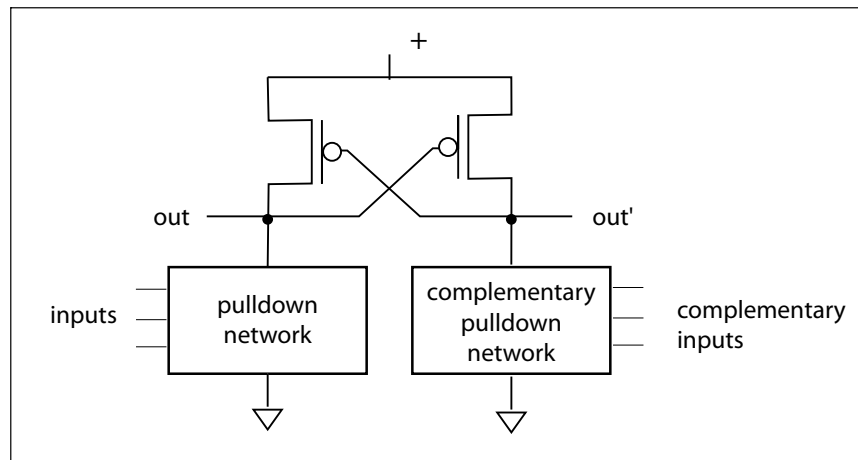

*DCVSL structure*

The structure of a generic DCVSL gate is shown in Figure 3-28. There are two pulldown networks which are the duals of each other, one for each true/complement output. Each pulldown network has a single p-type pullup, but the pullups are cross-coupled. Exactly one of the pulldown networks will create a path to ground when the gate's inputs change, causing the output nodes to switch to the required values. The cross-coupling of the pullups helps speed up the transition—if, for example, the complementary network forms a path to ground, the complementary output goes toward  $V_{SS}$ , which turns on the true output's pullup, raising the true output, which in turn lowers the gate voltage on the complementary output's pullup. This gate consumes no DC power (except due to leakage current), since neither side of the gate will ever have both its pullup and pulldown network on at once.

**Figure 3-29** An example DCVSL gate circuit.

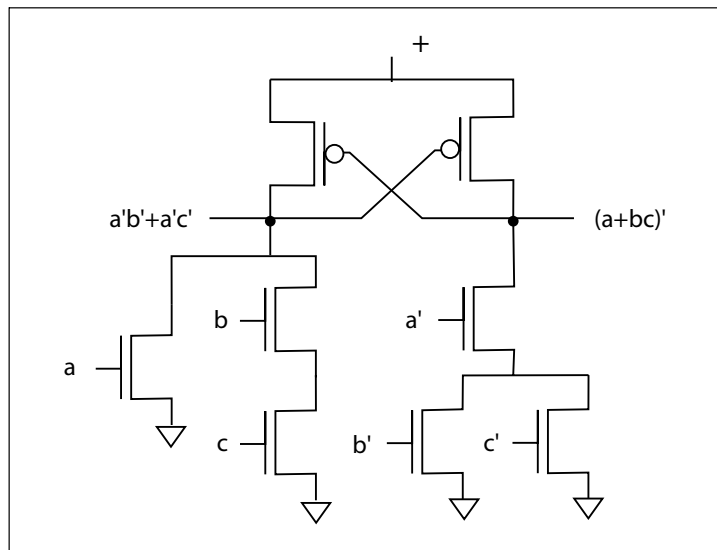


Figure 3-29 shows the circuit for a particular DCVSL gate. This gate computes  $a+bc$  on one output and  $(a+bc)' = a'b'+a'c'$  on its other output.


### 3.5.3 Domino Logic

*precharged logic*

**Precharged** circuits offer both low area and higher speed than static complementary gates. Precharged gates introduce functional complexity because they must be operated in two distinct phases, requiring intro-

duction of a clock signal. They are also more sensitive to noise; their clocking signals also consume power and are difficult to turn off to save power.

**Figure 3-30**  
A domino OR gate and its operation.

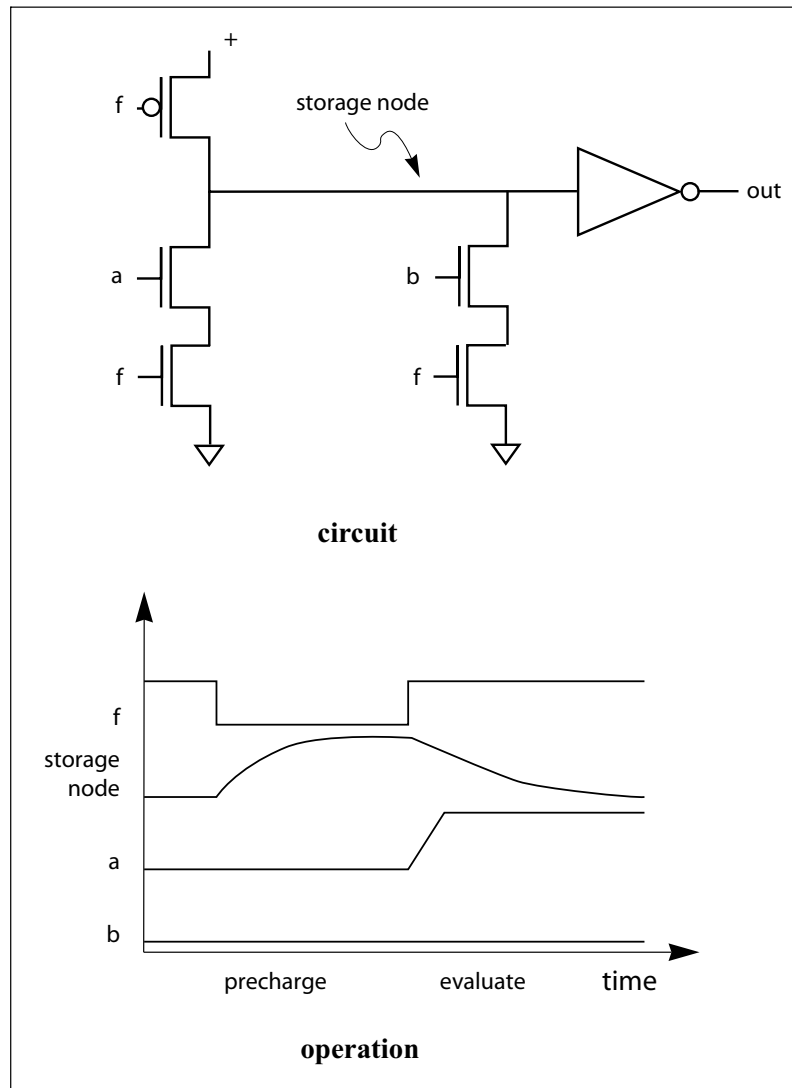

*domino logic*


The canonical precharged logic gate circuit is the **domino** circuit [Kra82]. A domino gate is shown in Figure 3-30, along with a sketch of its operation over one cycle. The gate works in two phases, first to pre-

charge the storage node, then to selectively discharge it. The phases are controlled by the clock signal  $\phi$ :

- **Precharge.** When  $\phi$  goes low, the p-type transistor starts charging the precharge capacitance. The pulldown transistors controlled by the clock keep that precharge node from being drained. The length of the  $\phi = 0$  phase is adjusted to ensure that the storage node is charged to a solid logic 1.
- **Evaluate.** When  $\phi$  goes high, precharging stops (the p-type pullup turns off) and the evaluation phase begins (the n-type pulldowns at the bottom of the circuit turn on). The logic inputs *a* and *b* can now assume their desired value of 0 or 1. The input signals must monotonically rise—if an input goes from 0 to 1 and back to 0, it will inadvertently discharge the precharge capacitance. If the inputs create a conducting path through the pulldown network, the precharge capacitance is discharged, forcing its value to 0 and the gate's output (through the inverter) to 1. If neither *a* nor *b* is 1, then the storage node would be left charged at logic 1 and the gate's output would be 0.

The gate's logic value is valid at the end of the evaluation phase, after enough time has been allowed for the pulldown transistors to fully discharge the storage node. If the gate is to be used to compute another value, it must go through the precharge-evaluate cycle again.


**Figure 3-31**  
Successive evaluations in a domino logic network.

 

*domino logic networks*

Figure 3-31 illustrates the phenomenon which gave the domino gate its name. Since each gate is precharged to a low output level before evaluation, the changes at the primary inputs ripple through the domino network from one end to another. Signals at the far end of the network

change last, with each change to a gate output causing a change to the next output. This sequential evaluation resembles a string of falling dominos.

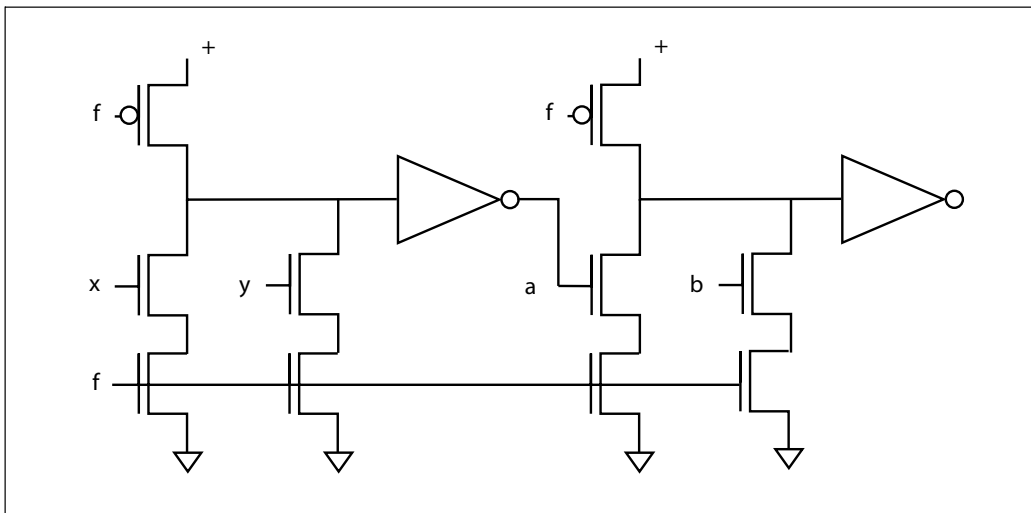


**Figure 3-32** Why domino gate input values must monotonically increase.

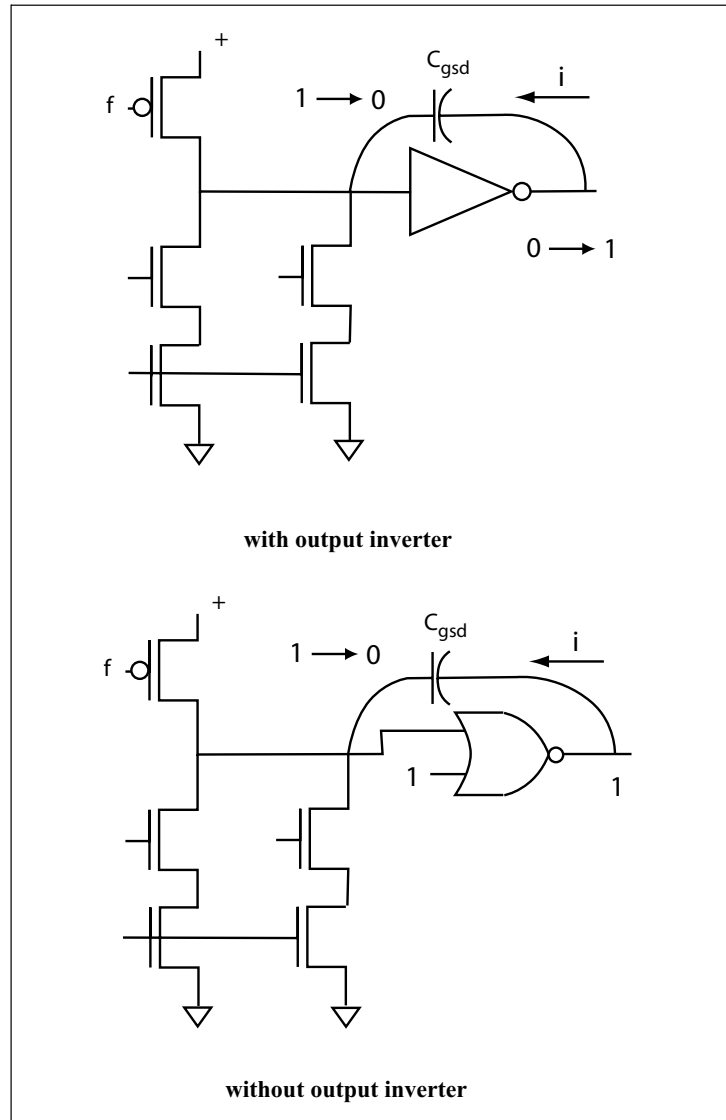Why is there an inverter at the output of the domino gate? There are two reasons: logical operation and circuit behavior. To understand the logical need for an output inverter, consider the circuit of Figure 3-32, in which the output of one domino gate is fed into an input of another domino gate. During the precharge phase, if the inverter were not present, the intermediate signal would rise to 1, violating the requirement that all inputs to the second gate be 0 during precharging.

However, the more compelling reason for the output inverter is to increase the reliability of the gate. Figure 3-33 shows two circuit variations: one with the output inverter and one without. In both cases, the storage node is coupled to the output of the following gate by the gate-to-source/drain capacitances of the transistors in that gate. This coupling can cause current to flow into the storage node, disturbing its value. Since the coupling capacitance is across the transistor, the Miller effect magnifies its value. When the storage node is connected to the output inverter, the inverter's output is at least correlated to the voltage on the storage node and we can design the circuit to withstand the effects of the coupling capacitance. However, when the storage node is connected to an arbitrary gate, that gate's output is not necessarily correlated to the


**Figure 3-33** Capacitive coupling in domino gates.



storage node's behavior, making it more difficult to ensure that the storage node is not corrupted. The fact that the wire connecting the domino gate's pull-down network to the next gate (and the bulk of the storage node capacitance) may be long and subject to crosstalk

generated by wire-to-wire coupling capacitances only makes this circuit less attractive.

**Figure 3-34** Charge sharing in a domino circuit.

 

*charge sharing*

Domino gates are also vulnerable to errors caused by **charge sharing**. Charge sharing is a problem in any network of switches, and we will cover it in more detail in Section 4.6. However, we need to understand the phenomenon in the relatively simple form in which it occurs in domino gates. Consider the example of Figure 3-34.  $C_{sd}$ , the stray capacitance on the source and drain of the two pulldown transistors, can store enough charge to cause problems. In the case when the **a** input is 1 and the **b** input is 0, the precharge node should not be discharged. However, since **a** is one, the pulldown connected to the storage node is turned on, draining charge from the storage node into the parasitic capacitance between the two pulldowns. In a static gate, charge stored in the intermediate pulldown capacitances does not matter because the power supply drives the output, but in the case of a dynamic gate that charge is lost to the storage node. If the gate has several pulldown transistors, the charge loss is that much more severe. The problem can be averted by precharging the internal pulldown network nodes along with the precharge node itself, although at the cost of area and complexity.

*charge leakage*

Because dynamic gates rely on stored charge, they are vulnerable to charge leakage through the substrate. The primary threat comes from

designs that do not evaluate some dynamic gates on every clock cycle; in these cases, the designer must verify that the gates are always re-evaluated frequently enough to ensure that the charge stored in the gates has not leaked away in sufficient quantities to destroy the gate's value.

*domino is not complete* Domino gates cannot invert, and so this logic family does not form a complete logic, as defined in Section 3.2. A domino logic network consists only of AND, OR, and complex AND/OR gates. However, any such function can be rewritten using De Morgan's laws to push all the inverters to the forward outputs or backward to the inputs; the bulk of the function can be implemented in domino gates with the inverters implemented as standard static gates. However, pushing back the inversions to the primary inputs may greatly increase the number of gates in the network.

---

### 3.6 Low-Power Gates

---

There are several different strategies for building low-power gates. Which one is appropriate for a given design depends on the required performance and power as well as the fabrication technology. In very deep submicron technologies leakage current has become a major consumer of power.

*power supply voltage* Of course, the simplest way to reduce the operating voltage of a gate is to connect it to a lower power supply. We saw the relationship between power supply voltage and power consumption in Section 3.3.5:

- For large  $V_p$ , Equation 3-7 tells us that delay changes linearly with power supply voltage.
- Equation 3-15 tells us that power consumption varies quadratically with power supply voltage.

This simple analysis tells us that reducing the power supply saves us much more in power consumption than it costs us in gate delay. Of course, the performance penalty incurred by reducing the power supply voltage must be taken care of somewhere in the system. One possible solution is architecture-driven voltage scaling, which we will study in Section 8.6, which replicates logic to make up for slower operating speeds.

*multiple-voltage logic* It is also possible to operate different gates in the circuit at different voltages: gates on the critical delay path can be run at higher voltages


---



---



while gates that are not delay-critical can be run at lower voltages. However, such circuits must be designed very carefully since passing logic values between gates running at different voltages may run into noise limits. The transistors used to transfer from low to high voltages also create a source of static power dissipation. In addition, the layout must include multiple power supply grids to provide the different voltage domains.

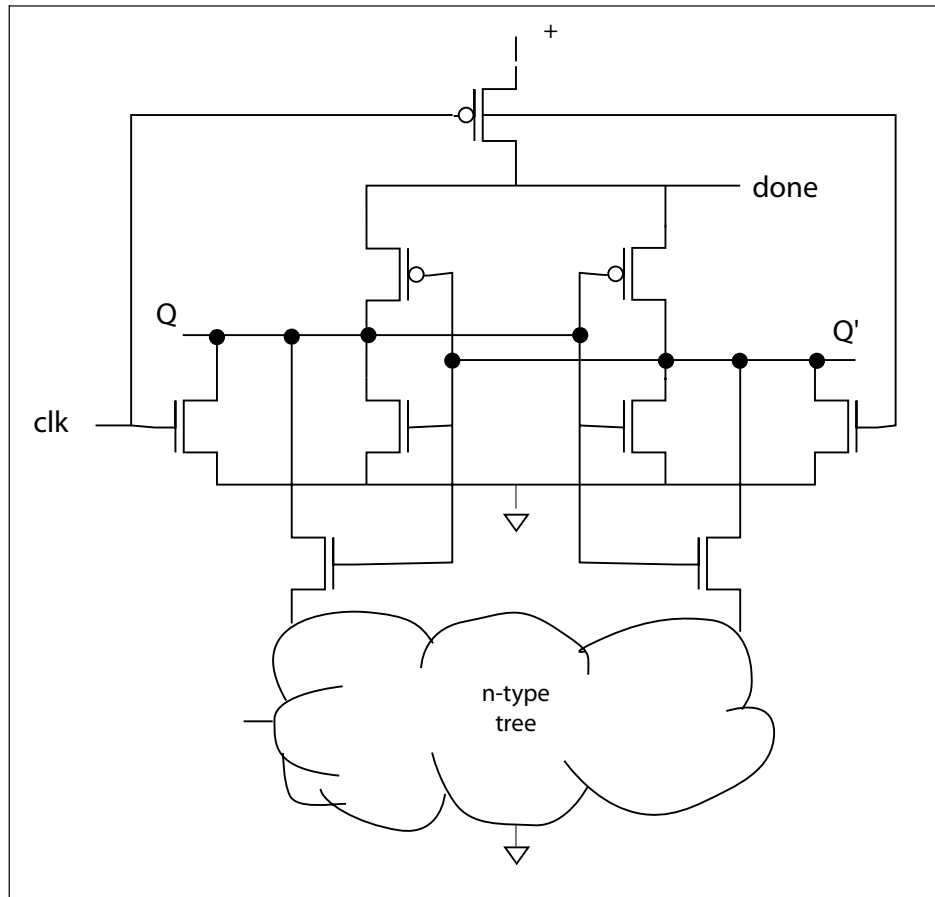

**Figure 3-35** A DCSL gate.

*gate circuits*

After changing power supply voltages, the next step is to use different logic gate topologies. An example of this strategy is the differential current switch logic (DCSL) gate [Roy00] shown in Figure 3-35, which is

## 3.6 Low-Power Gates

171

related to the DCVS gate of Section 3.5.2. Both use nMOS pulldown networks for both logic 0 and logic 1. However, the DCSL gate disconnects the n-type networks to reduce their power consumption. This gate is precharged with Q and Q' low. When the clock goes high, one of Q or Q' will be pulled low by the n-type evaluation tree and that value will be latched by the cross-coupled inverters.

*leakage and power supply control*

After these techniques have been tried, two techniques can be used: reducing leakage current and turning off gates when they are not in use. Leakage current is becoming increasingly important in very deep submicron technologies. We studied leakage currents in Section 2.3.6. One simple approach to reducing leakage currents in gates is to choose, whenever possible, don't-care conditions on the inputs to reduce leakage currents. Series chains of transistors pass much lower leakage currents when both are off than when one is off and the other is on. If don't-care conditions can be used to turn off series combinations of transistors in a gate, the gate's leakage current can be greatly reduced.

*leakage and threshold voltage*

The key to low leakage current is low threshold voltage. Unfortunately, there is an essential tension between low leakage and high performance. Remember from Equation 2-17 that leakage current is an exponential function of  $V_{gs} - V_t$ . As a result, increasing  $V_t$  decreases the subthreshold current when the transistor is off. However, a high threshold voltage increases the gate's delay since the transistor turns on later in the input signal's transition. One solution to this dilemma is to use transistors with different thresholds at different points in the circuit.


*turning off gates*

Turning off gates when they are not used saves even more power, particularly in technologies that exhibit significant leakage currents. Care must be used in choosing which gates to turn off, since it often takes 100  $\mu$ s for the power supply to stabilize after it is turned on. We will discuss the implications of power-down modes in Section 8.6. However, turning off gates is a very useful technique that becomes increasingly important in very deep submicron technologies with high leakage currents.

*leakage in transistor chains*


The leakage current through a chain of transistors in a pulldown or pullup network is lower than the leakage current through a single transistor [De01]. It also depends on whether some transistors in the stack are also on. Consider the pulldown network of a NAND gate shown in Figure 3-36. If both the  $a$  and  $b$  inputs are 0, then both transistors are off. Because a small leakage current flows through transistor  $M_a$ , the parasitic capacitance between the two transistors is charged, which in turn holds the voltage at that node above ground. This means that  $V_{gs}$  for  $M_a$  is negative, thus reducing the total leakage current. The leakage current is found by simultaneously solving for the currents through the two tran-

**Figure 3-36** Leakage through transistor stacks.

 

sistors. The leakage current through the chain can be an order of magnitude lower than the leakage current through a single transistor. But the total leakage current clearly depends on the gate voltages of the transistors in the chain; if some of the gate's inputs are logic 1, then there may not be chains of transistors that are turned off and thus have reduced input voltages. Algorithms can be used to find the lowest-leakage input values for a set of gates; latches can be used to hold the gates' inputs at those values in standby mode to reduce leakage.

**Figure 3-37** A multiple-threshold (MTCMOS) inverter.

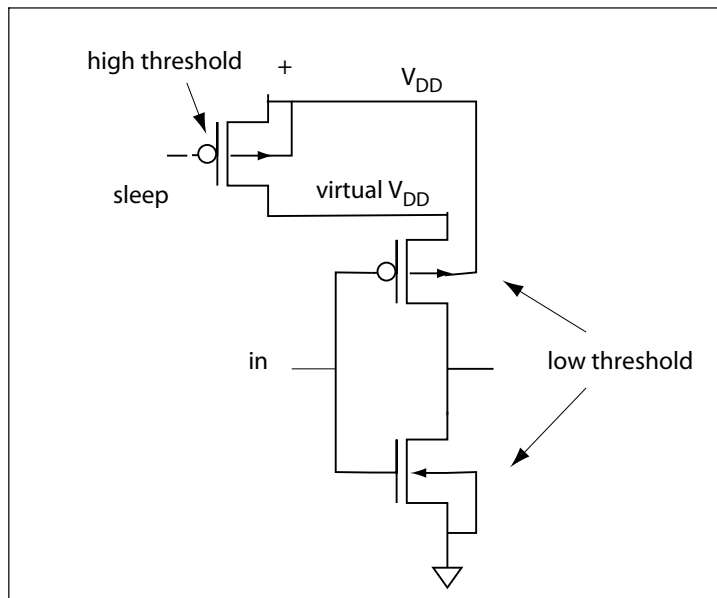


*multi-threshold logic*

Figure 3-37 shows a **multiple-threshold logic (MTCMOS)** [Mut98] gate that can be powered down. This circuit family uses low-leakage transistors to turn off gates when they are not in use. A **sleep transistor** is used to control the gate's access to the power supply; the gated power supply is known as a **virtual  $V_{DD}$** . The gate uses low-threshold transistors to increase the gate's delay time. However, lowering the threshold voltage also increases the transistors' leakage current, which causes us to introduce the sleep transistor. The sleep transistor has a high threshold to minimize its leakage. The fabrication process must be able to build transistors with low and high threshold voltages.


The layout of this gate must include both  $V_{DD}$  and virtual  $V_{DD}$ : virtual  $V_{DD}$  is used to power the gate but  $V_{DD}$  connects to the pullup's substrate. The sleep transistor must be properly sized. If the sleep transistor is too small, its impedance would cause virtual  $V_{DD}$  to bounce. If the sleep transistor is too large, the sleep transistor would occupy too much area and it would use more energy when switched.

**Figure 3-38** A variable-threshold CMOS (VTCMOS) gate.

 

It is important to remember that some other logic must be used to determine when a gate is not used and control the gate's power supply. This logic must watch the state of the chip's inputs and memory elements to know when logic can safely be turned off. It may also take more than one cycle to safely turn on a block of logic.

Figure 3-39 shows an MTCMOS flip-flop. The storage path is made of high  $V_t$  transistors and is always on. The signal is propagated from input to output through low  $V_t$  transistors. The sleep control transistors on the

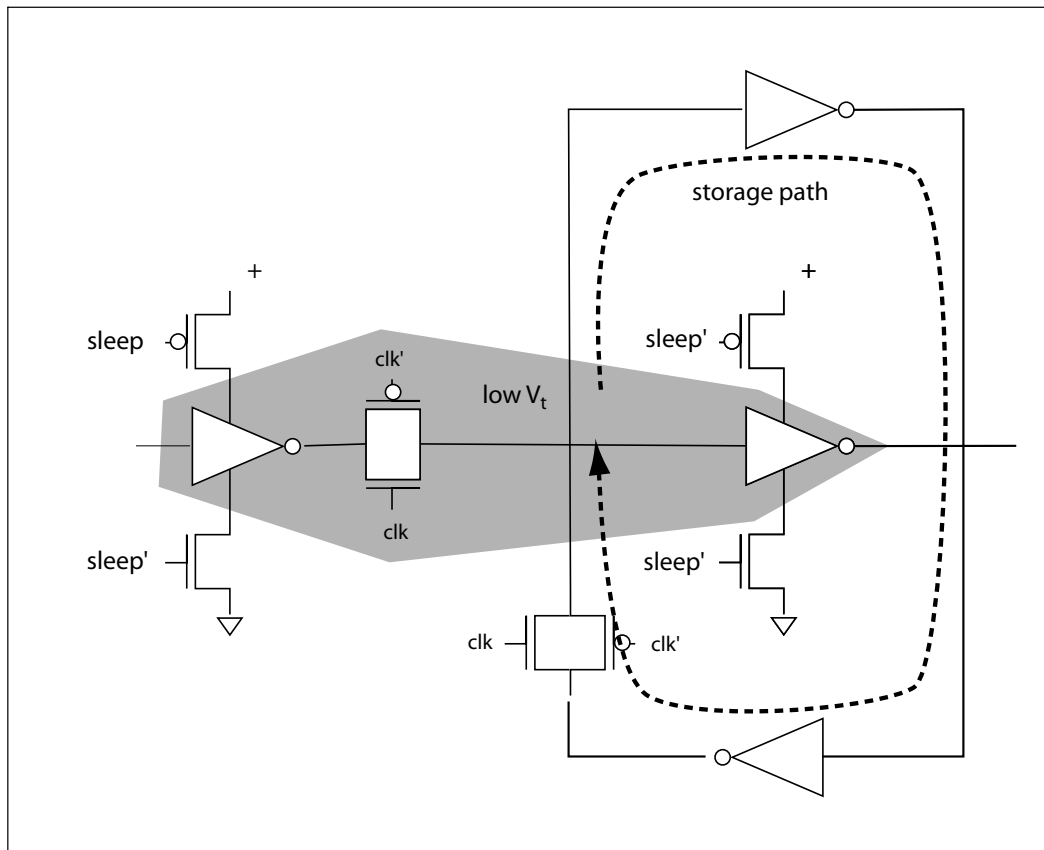

**Figure 3-39** An MTCMOS flip-flop.

second inverter in the forward path are used to prevent a short-circuit path between  $V_{DD}$  and virtual  $V_{DD}$  that could flow through the storage inverter's pullup and the forward chain inverter's pullup.

*variable threshold CMOS*

A more aggressive method is **variable threshold CMOS (VTCMOS)** [Kur96], which actually can be implemented in several ways. Rather than fabricating fixed-threshold voltage transistors, the threshold voltages of the transistors in the gate are controlled by changing the voltages on the substrates. Figure 3-38 shows the structure of a VTCMOS gate. The substrates for the p- and n-type transistors are each connected to their own threshold supply voltages,  $V_{BB,p}$  and  $V_{BB,n}$ .  $V_{BB}$  is

raised to put the transistor in standby mode and lowered to put it into active mode. Rather sophisticated circuitry is used to control the substrate voltages.

VTCMOS logic comes alive faster than it falls asleep. The transition time to sleep mode depends on how quickly current can be pulled out of the substrate, which typically ranges from tens to hundreds of microseconds. Returning the gate to active mode requires injecting current back into the substrate, which can be done 100 to 1000 times faster than pulling that current out of the substrate. In most applications, a short wake-up time is important—the user generally gives little warning that the system is needed.

---

## 3.7 Delay through Resistive Interconnect

---

In this section, we analyze the delay through resistive (non-inductive) interconnect. In many modern chips, the delay through wires is larger than the delay through gates, so studying the delay through wires is as important as studying delay through gates. We will build a suite of analytical models, starting from the relatively straightforward Elmore model for an RC transmission line through more complex wire shapes. We will also consider the problem of where to insert buffers along wires to minimize delay.

### 3.7.1 Delay through an RC Transmission Line

#### *RC transmission lines*

An **RC transmission line** models a wire as infinitesimal RC sections, each representing a differential resistance and capacitance. Since we are primarily concerned with RC transmission lines, we can use the transmission line model to compute the delay through very long wires. We can model the transmission line as having unit resistance  $r$  and unit capacitance  $c$ . The standard schematic for the RC transmission line is shown in Figure 3-40. The transmission line's voltage response is modeled by a differential equation:

$$\frac{1}{r} \frac{d^2 V}{dx^2} = c \frac{dV}{dt}. \quad (\text{EQ 3-23})$$


This model gives the voltage as a function of both  $x$  position along the wire and of time.

---



---


**Figure 3-40** Symbol for a distributed RC transmission line.

 

*Elmore delay*

The raw differential equation, however, is unwieldy for many circuit design tasks. **Elmore delay** [Elm48] is the most widely used metric for RC wire delay and has been shown to sufficiently accurately model the results of simulating RC wires on integrated circuits [Boe93]. Elmore defined the delay through a linear network as the first moment of the impulse response of the network:

$$\delta_E = \int_0^\infty tV_{out}(t)dt \quad . \quad \text{(EQ 3-24)}$$

 

**Figure 3-41** An RC transmission line for Elmore delay calculations.

Because only the first moment is used as the delay metric, Elmore delay is not sufficiently accurate for inductive interconnect. However, in overdamped RC networks, the first moment is sufficiently accurate.

*transmission line as RC sections*

Elmore modeled the transmission line as a sequence of  $n$  sections of RC, as shown in Figure 3-41. In the case of a general RC network, the Elmore delay can be computed by taking the sum of RC products, where each resistance  $R$  is multiplied by the sum of all the downstream capacitors (a special case of the RC tree formulas we will introduce in Section 3.7.2).

## 3.7 Delay through Resistive Interconnect

177

Since all the transmission line section resistances and capacitances in an  $n$ -section are identical, this reduces to

$$\delta_E = \sum_{i=1}^n r(n-i)c = \frac{1}{2}rc \times n(n-1). \quad (\text{EQ 3-25})$$

One consequence of this formula is that wire delay grows as the square of wire length, since  $n$  is proportional to wire length. Since the wire's delay also depends on its unit resistance and capacitance, it is imperative to use the material with the lowest RC product (which will almost always be metal) to minimize the constant factor attached to the  $n^2$  growth rate.

*more complex models*

Although the Elmore delay formula is widely used, we will need some results from the analysis of continuous transmission lines for our later discussion of crosstalk. The normalized voltage step response of the transmission line can be written as

$$V(t) = 1 + \sum_{k=1}^{\infty} K_k e^{-\sigma_k t/RC} \approx 1 + K_1 e^{-\sigma_1 t/RC}, \quad (\text{EQ 3-26})$$

where  $R$  and  $C$  are the total resistance and capacitance of the line. We will define  $R_i$  as the internal resistance of the driving gate and  $C_i$  as the load capacitance at the opposite end of the transmission line.

Sakurai [Sak93] estimated the required values for the first-order estimate of the step response as:

$$K_1 = \frac{-1.01(R_T + C_T + 1)}{R_T + C_T + \pi/4}, \quad (\text{EQ 3-27})$$

$$\sigma_1 = \frac{1.04}{R_T C_T + R_T + C_T + (2/\pi)^2}, \quad (\text{EQ 3-28})$$

where  $R_T$  and  $C_T$  are  $R_i/R$  and  $C_i/C$ , respectively.

*tapered wires*

So far, we have assumed that the wire has constant width. In fact, tapered wires provide lower delay. Consider the first resistance element in the transmission line—the current required to charge all the capacitance of the wire must flow through this resistance. In contrast, the resistance at the end of the wire handles only the capacitance at the end. Therefore, if we can decrease the resistance at the head of the wire, we can decrease the delay through the wire. Unfortunately, increasing the




resistance by widening the wire also increases its capacitance, making this a non-trivial problem to solve.

Fishburn and Schevon [Fis95] proved that the optimum-shaped wire has an exponential taper. If the source resistance is  $R_0$ , the sink capacitance is  $C_0$ , and the unit resistance and capacitance are  $R_s$  and  $C_s$ , the width of the wire as a function of distance is

$$w(x) = \frac{2C_0}{C_s L} W \left( \frac{L}{2} \sqrt{\frac{R_s C_s}{R_0 C_0}} \right) e^{2W \left( \frac{L}{2} \sqrt{\frac{R_s C_s}{R_0 C_0}} \right) \frac{x}{L}}, \quad \text{(EQ 3-29)}$$

where  $W$  is the function that satisfies the equality  $W(x)e^{W(x)} = x$ . The advantage of optimal tapering is noticeable. Fishburn and Schevon calculate that, for one example, the optimally tapered wire has a delay of 3.72 ns while the constant-width wire with minimum delay has a delay of 4.04 ns. In this example, the optimally tapered wire shrinks from 30.7  $\mu\text{m}$  at the source to 7.8  $\mu\text{m}$  at the sink.

Of course, exponentially-tapered wires are impossible to fabricate exactly, but it turns out that we can do nearly as well by dividing the wire into a few constant width sections. Figure 3-42 shows that a few segments of wire can be used to approximate the exponential taper reasonably well. This result also suggests that long wires which can be run on several layers should run on the lowest-resistance layer near the driver and can move to the higher-resistance layers as they move toward the signal sink.

 

**Figure 3-42** A step-tapered wire.


*thermal effects*

Temperature affects wire properties: wire resistance increased by 12% for 40°C around the nominal temperature in the same process. This resulted in a delay change of about 5% per 40°C.

### 3.7.2 Delay through RC Trees

#### *RC tree model*

While analyzing a straight transmission line is straightforward, analyzing more complex networks is harder. We may not always need an exact answer, either—a good approximation is often enough considering the other uncertainties in IC design and manufacturing. In the case of RC trees, as shown in Figure 3-43, we can quickly compute accurate bounds on the delay through the wire [Rub83]. The wiring can be broken into an RC tree either by representing each branch by one RC lump or by breaking a branch into several lumps.

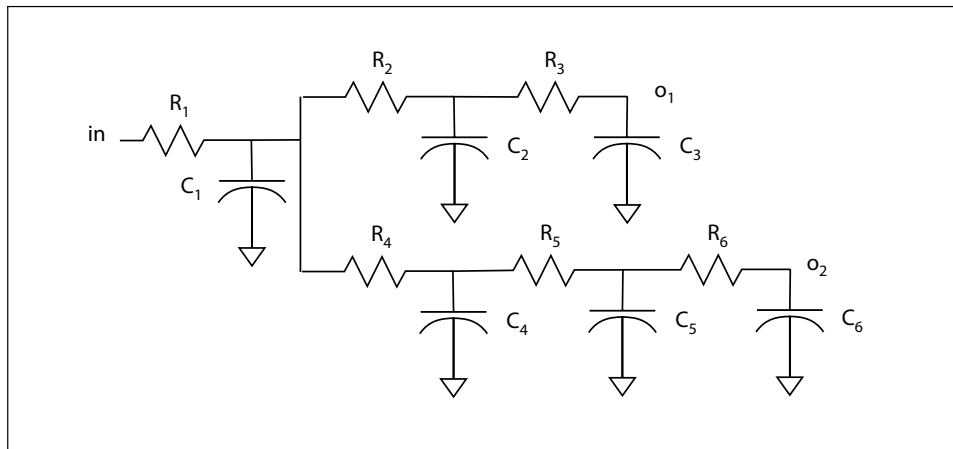

**Figure 3-43** An RC tree.

When analyzing the RC tree, we assume the network has one input, which provides a voltage step, and several outputs. We can find the transition time through the wire by analyzing the voltages at the output nodes and measuring the time between the 10% and 90% points. While an exact solution for the output voltages for an arbitrary RC network is complex, we can find accurate upper and lower bounds on the output voltage, and from those voltage bounds we can compute delay bounds. We won't perform a detailed derivation of the bounds formulas, but will only try to provide an intuitive explanation of their form.

#### *R and C along paths*

The capacitance at a node  $k$  is called  $C_k$ . We are primarily concerned with resistances along paths, notably the resistances along shared paths. If  $o$  is an output node and  $k$  is an internal node, the resistance along the intersection of the paths from the input to  $o$  and to  $k$  is called  $R_{ko}$ . In

Figure 3-43,  $R_{1O_1} = R_1$  because  $R_1$  is the only resistor shared by the paths to 1 and  $O_1$ .  $R_{o0}$  is the total resistance from input to the output  $o$  and similarly,  $R_{kk}$  is the total resistance from input to the internal node  $k$ . The simplest time constant for the tree is

$$T_P = \sum_k R_{kk} C_k. \quad (\text{EQ 3-30})$$

Each term in the summation is the time constant of the simple  $RC$  circuit built from the capacitance at  $k$  and all the resistance from the input to  $k$ .

Two other time constants relative to the output  $o$  are important to the bounds:

$$T_{Do} = \sum_k R_{ko} C_k; \quad (\text{EQ 3-31})$$

$$T_{Ro} = \left( \sum_k R_{ko}^2 C_k \right) / R_{oo}. \quad (\text{EQ 3-32})$$

The terms of  $T_{Do}$  compute the time constant of the capacitance at each node and the resistance shared by the paths to  $k$  and  $o$  available to charge  $C_k$ . The terms of  $T_{Ro}$  weight the terms of  $T_{Do}$  against the total resistance along the path to the output, squaring  $R_{ko}$  to ensure the value has units of time. Although we won't prove it here, these inequalities relate the voltage at each output,  $v_o(t)$ , and the voltage at an interior node,  $v_k(t)$ , using the path resistances:

$$R_{oo} [1 - v_k(t)] \geq R_{ko} [1 - v_o(t)] \quad (\text{EQ 3-33})$$

$$R_{ko} [1 - v_k(t)] \leq R_{kk} [1 - v_o(t)] \quad (\text{EQ 3-34})$$

Some intermediate steps are required to find the  $v_o(t)$ 's; we will skip to the resulting bounds, shown in Table 3-3. The bounds are expressed both as the voltage at a given time and as the time required for the output to assume a specified voltage; the two formulas are, of course, equivalent.

#### accuracy

Do these bounds match our intuition about the circuit's behavior? At  $t=0$ , the upper bound for the output voltage is  $v_o(0) = 1 - T_{Do} / T_{Do}$ .  $T_{Do}$  is formed by the time constants of  $RC$  sections formed by all the resistance along the path to  $o$  that are also connected to the  $k^{\text{th}}$  capacitor, such as the highlighted resistors at **a** in the figure. Some of the current through those resistors will go to outputs other than  $o$ , and so are not available to

3.7 Delay through Resistive Interconnect

	validity	bound
lower	$t \leq T_{Do} - T_{Ro}$ $T_{Do} - T_{Ro} \leq t \leq T_p - T_{Ro}$ $t \geq T_p - T_{Ro}$	$v_o(t) \geq 0$ $v_o(t) \geq 1 - [T_{Do} / (t + T_{Ro})]$ $v_o(t) \geq 1 - \frac{T_{Do}}{T_p} e^{(T_p - T_{Ro}) / T_p} e^{-(t / T_p)}$
upper	$t \leq T_{Do} - T_{Ro}$ $t \geq T_{Do} - T_{Ro}$	$v_o(t) \leq 1 - ((T_{Do} - t) / T_p)$ $v_o(t) \leq 1 - \frac{T_{Ro}}{T_p} e^{(T_{Do} - T_{Ro}) / T_{Ro}} e^{-(t / T_p)}$

**voltage**

	validity	bound
lower	$v_o(t) \leq 1 - (T_{Ro} / T_p)$ $v_o(t) \geq 1 - (T_{Ro} / T_p)$	$t \geq T_{Do} - T_p [1 - v_o(t)]$ $t \geq T_{Do} - T_{Ro} + T_{Ro} \ln\left(\frac{T_{Ro}}{T_p [1 - v_o(t)]}\right)$
upper	$v_o(t) \leq 1 - (T_{Do} / T_p)$ $v_o(t) \geq 1 - (T_{Do} / T_p)$	$t \leq [T_{Do} / (1 - v_o(t))] - T_{Ro}$ $t \leq T_p - T_{Ro} + T_p \ln\left(\frac{T_{Do}}{T_p [1 - v_o(t)]}\right)$

**time**

**Table 3-3** Rubinstein-Penfield-Horowitz voltage and time bounds for RC trees.


charge the capacitors closest to  $o$ ; the upper bound assumes that *all* their current will be used to charge capacitors along the path from input to  $o$ . The lower bound is dominated by  $T_{Ro}$ , which compares  $R_{k0}$  to the total

resistance from the input to  $o$ ; the ratio  $R_{k0}/R_{00}$  gives a minimum resistance available to charge the capacitor  $C_k$ .

### 3.7.3 Buffer Insertion in RC Transmission Lines

*optimum buffer insertion*

We do not obtain the minimum delay through an RC transmission line by putting a single large driver at the transmission line's source. Rather, we must put a series of buffers equally spaced through the line to restore the signal. Bakoglu [Bak90] derived the optimal number of repeaters and repeater size for an RC transmission line. As shown in Figure 3-44, we want to divide the line into  $k$  sections, each of length  $l$ . Each buffer will be of size  $h$ .

 

**Figure 3-44** An RC transmission line with repeaters.

*unit-sized buffers*

Let's first consider the case in which  $h=1$  and the line is broken into  $k$  sections.  $R_{int}$  and  $C_{int}$  are the total resistance and capacitance of the transmission line.  $R_0$  is the driver's equivalent resistance and  $C_0$  its input capacitance. Then the 50% delay formula is

$$T_{50\%} = k \left[ 0.7R_0 \left( \frac{C_{int}}{k} + C_0 \right) + \frac{R_{int}}{k} \left( 0.4 \frac{C_{int}}{k} + 0.7C_0 \right) \right] \quad \text{(EQ 3-35)}$$

The various coefficients are due to the distributed nature of the transmission line. We find the minimum delay by setting  $dT/dk = 0$ . This gives the number of repeaters as

$$k = \sqrt{\frac{0.4R_{int}C_{int}}{0.7R_0C_0}} \quad \text{(EQ 3-36)}$$

## 3.7 Delay through Resistive Interconnect

183

*arbitrary buffer sizes*

When we free the size of the repeater to be an arbitrary value  $h$ , the delay equation becomes

$$T_{50\%} = k \left[ 0.7 \frac{R_0}{h} \left( \frac{C_{\text{int}}}{k} + h C_0 \right) + \frac{R_{\text{int}}}{k} \left( 0.4 \frac{C_{\text{int}}}{k} + 0.7 h C_0 \right) \right]. \quad (\text{EQ 3-37})$$

We solve for minimum delay by setting  $\frac{dT}{dk} = 0$  and  $\frac{dT}{dh} = 0$ . This gives the optimal values for  $k$  and  $h$  as

$$k = \sqrt{\frac{0.4 R_{\text{int}} C_{\text{int}}}{0.7 R_0 C_0}}, \quad (\text{EQ 3-38})$$

$$h = \sqrt{\frac{R_0 C_{\text{int}}}{R_{\text{int}} C_0}}. \quad (\text{EQ 3-39})$$

The total delay at these values is

$$T_{50\%} = 2.5 \sqrt{R_0 C_0 R_{\text{int}} C_{\text{int}}}. \quad (\text{EQ 3-40})$$

### Example 3-3 Buffer insertion in an RC line

Let's calculate the buffers required when a minimum-size inverter drives a metal 1 wire that is  $20,000\lambda \times 3\lambda$ . In this case,  $R_0 = 6.47 \text{ k}\Omega$  and  $C_0 = 1.78 \text{ fF}$  while  $R_{\text{int}} = 533 \text{ }\Omega$  and  $C_{\text{int}} = 17.5 \text{ fF} + 194 \text{ fF} = 212 \text{ fF}$ . The optimal number of buffers is

$$k = \sqrt{\frac{0.4 \times 533 \times 212 \times 10^{-15}}{0.7 \times 6470 \times 1.78 \times 10^{-15}}} = 2.37.$$

The optimal buffer size is

$$h = \sqrt{\frac{6470 \times 212 \times 10^{-15}}{533 \times 1.78 \times 10^{-15}}} = 38.0.$$

The 50% delay is


$$T_{50\%} = 2.5 \sqrt{6470 \times 1.78 \times 10^{-15} \times 533 \times 212 \times 10^{-15}} = 90.2 \text{ ps}.$$

If we increase the size of the driver by a factor of 4, reducing its resistance by 4X and increasing its capacitance by 4X, what happens?  $k$  and  $T_{50\%}$  remain unchanged, but the buffer size drops by a factor of 4.

### 3.7.4 Crosstalk between RC Wires

*aggressors and victims*

**Crosstalk** is important to analyze because it slows down signals—the crosstalk noise increases the signal's settling time. Crosstalk can become a major component of delay if wiring is not carefully designed.

 


**Figure 3-45** Aggressor and victim nets.

Figure 3-45 shows the basic situation in which crosstalk occurs. Two nets are coupled by parasitic capacitance. One net is the **aggressor net** that interferes with a **victim net** through that coupling capacitance. A transition in the aggressor net is transmitted to the victim net causing the victim to glitch. The glitch causes the victim net to take longer to settle to its final value. In static combinational logic, crosstalk increases the delay across a net; in dynamic logic, crosstalk can cause the state of a node to flip, causing a permanent error.

*crosstalk models*

In this section we will develop basic analytical models for crosstalk; in Section 4.4.4 we will learn how to minimize crosstalk through routing techniques. The simplest case to consider is a set of three wires [Sak93],

**Figure 3-46** A simple crosstalk model (after Sakurai [Sak93], © 1993 IEEE).

 

as shown in Figure 3-46. The middle wire carries the signal of interest, while the other two capacitively inject crosstalk noise. Each wire is of height  $T$  and width  $W$ , giving an aspect ratio of  $W/T$ . Each wire is height  $H$  above the substrate and the wires are spaced a distance  $S$  apart. We must consider three capacitances:  $C_{20}$  between the signal wire and the substrate, and two capacitances of equal value,  $C_{21}$ , to the two interfering wires. We denote the sum of these three capacitances as  $C_3$ . Sakurai estimates the RC delay through the signal wire in arbitrary time units as

$$t_r = \frac{(C_{20} + 4C_{21})}{W/H}. \tag{EQ 3-41}$$


Using this simple model, Figure 3-47 shows Sakurai’s calculation of relative RC delay in arbitrary units for a  $0.5\ \mu\text{m}$  technology for the signal wire. This plot assumes that  $T/H = 1$  and that the aspect ratio varies from near 0 through 4; the delay is shown for four different spacings between the wires, as given by the  $P/H$  ratio. This plot clearly shows two important results. First, there is an optimum wire width for any given wire spacing, as shown by the U shape of each curve. Second, the optimum width increases as the spacing between wires increases.

*multiple transitions*

That analysis assumes that the signals on the surrounding wires are stable, which is the best case. In general, we must assume that the surrounding wires are in transition. Consider the model of Figure 3-48, in which we have two RC transmission lines with a coupling capacitance  $C_c$  between them. A step is applied to each wire at  $t=0$ , resulting in response waveforms at the opposite ends of the transmission lines [Sak93]. We assume that the unit resistances and capacitances of the two transmission lines are equal.



**Figure 3-47** Delay vs. wire aspect ratio and spacing (after Sakurai [Sak93] © 1993 IEEE).

 

Defining differential voltages between the two wires helps simplify the voltage response equations:


$$V_+ = \frac{V_1 + V_2}{\sqrt{2}}, V_- = \frac{V_1 - V_2}{\sqrt{2}}. \tag{EQ 3-42}$$

The voltage responses of the transmission lines can then be written as

$$\frac{d^2 V_+}{dx^2} = rc \frac{dV_+}{dt}, \tag{EQ 3-43}$$

$$\frac{d^2 V_-}{dx^2} = r(c + 2c_c) \frac{dV_-}{dt}. \tag{EQ 3-44}$$

**Figure 3-48** Two coupled RC transmission lines.

 

If we let  $R = rl$ ,  $C = cl$ , and  $C_c = c_c l$ , then the voltage responses  $V_1$  and  $V_2$  at the ends of the transmission lines can be written as:

$$V_1(t) \approx E_1 + \frac{K_1}{2} [(E_1 + E_2)e^{-\sigma_1 t/RC} + (E_1 - E_2)e^{-\sigma_1 t/RC + 2RC_c}], \text{ (EQ 3-45)}$$

$$V_2(t) \approx E_2 + \frac{K_1}{2} [(E_1 + E_2)e^{-\sigma_1 t/RC} - (E_1 - E_2)e^{-\sigma_1 t/(RC + 2RC_c)}]. \text{ (EQ 3-46)}$$

### 3.8 Delay through Inductive Interconnect

Copper wiring provides much better performance, particularly for long wires. However, copper wires have significant inductance. Analyzing inductive wiring is more complicated than is analyzing RC transmission lines. RLC transmission lines have a more complex response that requires more subtle interpretation as well as more effort.

#### 3.8.1 RLC Basics

*overdamped and underdamped circuits*

First, let's review the basics of RLC circuits. A single RLC section is shown in Figure 3-49. The poles of the RLC section are at


$$\omega_0 [\xi \pm \sqrt{\xi^2 - 1}] \text{ (EQ 3-47)}$$

where the damping factor  $\xi$  is defined as

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}. \quad (\text{EQ 3-48})$$

If the damping factor is greater than 1, the circuit is **overdamped** and responds to an impulse or step by monotonically approaching the final voltage. If the damping factor is less than 1, the circuit is **underdamped** and oscillates as it converges to the steady-state voltage. Underdamped circuits create a new challenge for digital circuit analysis because it is harder to find their rise times. For an underdamped circuit, we simply have to find the first time the waveform crosses the desired voltage threshold, knowing that it will always remain above that level. To determine the rise time of an underdamped circuit, we must find the last time at which the waveform falls below the threshold.

**Figure 3-49** An RLC circuit and its behavior.

 

The simplest form of an RLC transmission line is the lossless LC line with zero resistance. A signal propagates along an LC transmission line [Ram65] with velocity

$$v = \frac{1}{\sqrt{LC}}. \quad (\text{EQ 3-49})$$

Therefore, the propagation delay through an LC transmission line of length  $l$  is  $t_p = l\sqrt{LC}$ . This value is a lower bound on the delay introduced by an RLC transmission line.

### 3.8.2 RLC Transmission Line Delay

#### *analytical delay model*

Kahng and Muddu [Kah97] developed an analytical model for inductive delay that is only somewhat more difficult to calculate than the Elmore delay for RC delay. Let  $R_S$  and  $L_S$  be the source impedance,  $R_{int}$ ,  $C_{int}$ ,

and  $L_{int}$  be the transmission line unit impedances, and  $C_L$  be the load capacitance. They define two coefficients  $b_1$  and  $b_2$ :

$$b_1 = R_S C_{int} + R_S C_L + \frac{R_{int} C_{int}}{2} + R_{int} C_L, \quad (\text{EQ 3-50})$$

$$b_2 = \frac{R_S R_{int} C_{int}^2}{6} + \frac{R_S R_{int} C_{int}}{2} + \frac{(R_{int} C_{int})^2}{24} + \frac{R_{int}^2 C_{int} C_L}{6} + L_S C_{int} + L_S C_L + \frac{L_{int} C_{int}}{2} + L_{int} C_L. \quad (\text{EQ 3-51})$$

They approximated the transfer function of the network as

$$H(s) \approx \frac{1}{1 + s b_1 + s^2 b_2}. \quad (\text{EQ 3-52})$$

For an underdamped transmission line, they estimate delay as

$$\tau_C = K_C \frac{2b_2}{\sqrt{4b_2 - b_1^2}}, \quad (\text{EQ 3-53})$$

where  $K_C = 1.66$  for most technologies.

*analytical/numerical  
model*

Ismail and Friedman used analytical and numerical techniques to model RLC delay [Ism00]. We will model the driving gate as a resistance  $R_{tr}$  and the load gate as a capacitance  $C_L$ . We will use  $R$ ,  $L$  and  $C$  for the unit resistance, inductance, and capacitance and  $R_t$ ,  $L_t$  and  $C_t$  for the total resistance, inductance, and capacitance of the line. The complete system is shown in Figure 3-50.

We can simplify our analysis by scaling time using the factor

$$\omega_n = \frac{1}{\sqrt{L_t(C_t + C_L)}}. \quad (\text{EQ 3-54})$$

We normalize time by substituting  $t = t'/\omega_n$ . We also need two additional values:

$$R_T = \frac{R_{tr}}{R_t}, \quad (\text{EQ 3-55})$$

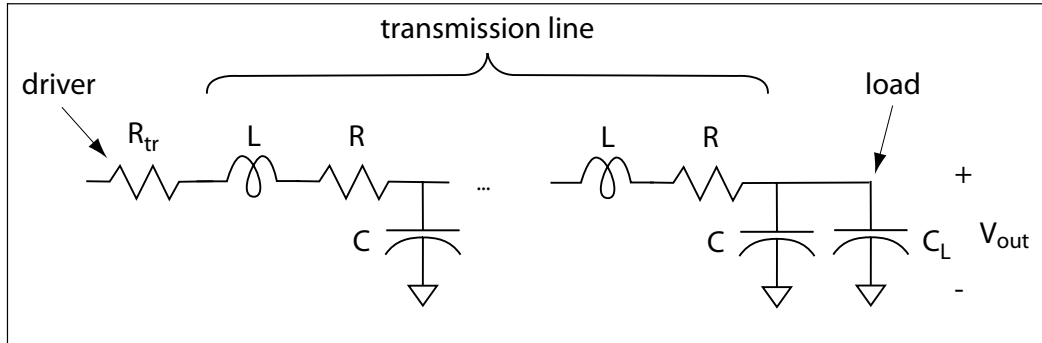


Figure 3-50 An RLC transmission line with a driver and load.

$$C_T = \frac{C_L}{C_t} \tag{EQ 3-56}$$

where  $l$  is once again the length of the transmission line.

The complete derivation of the transmission line's response is rather complex, but we are most interested in the propagation delay through the wire to the load capacitance. Ismail and Friedman showed that propagation delay is primarily a function of  $\xi$ , which is defined as

$$\xi = \frac{R_t}{2} \sqrt{\frac{C_t}{L_t} \left( \frac{Rl + Cl + RCt^2 + 0.5}{\sqrt{1 + Cl}} \right)} \tag{EQ 3-57}$$

They used numerical techniques to approximate the 50% propagation delay of our RLC transmission line as


$$t_{pd} = (e^{-2.9\xi^{1.35}} + 1.48\xi) / \omega_n \tag{EQ 3-58}$$

Figure 3-51 compares the response of RLC and RC wires for different values of  $\xi$ . These plots show that ignoring inductance results in very poor results for small values of  $\xi$ .

*RC vs. RLC delay*

Figure 3-52 compares RC and RLC models for wires driven by inverters in a 0.25  $\mu\text{m}$  technology. This figure shows that ignoring inductance results in serious errors in estimating delay for a variety of wire and driver configurations.


3.8 Delay through Inductive Interconnect

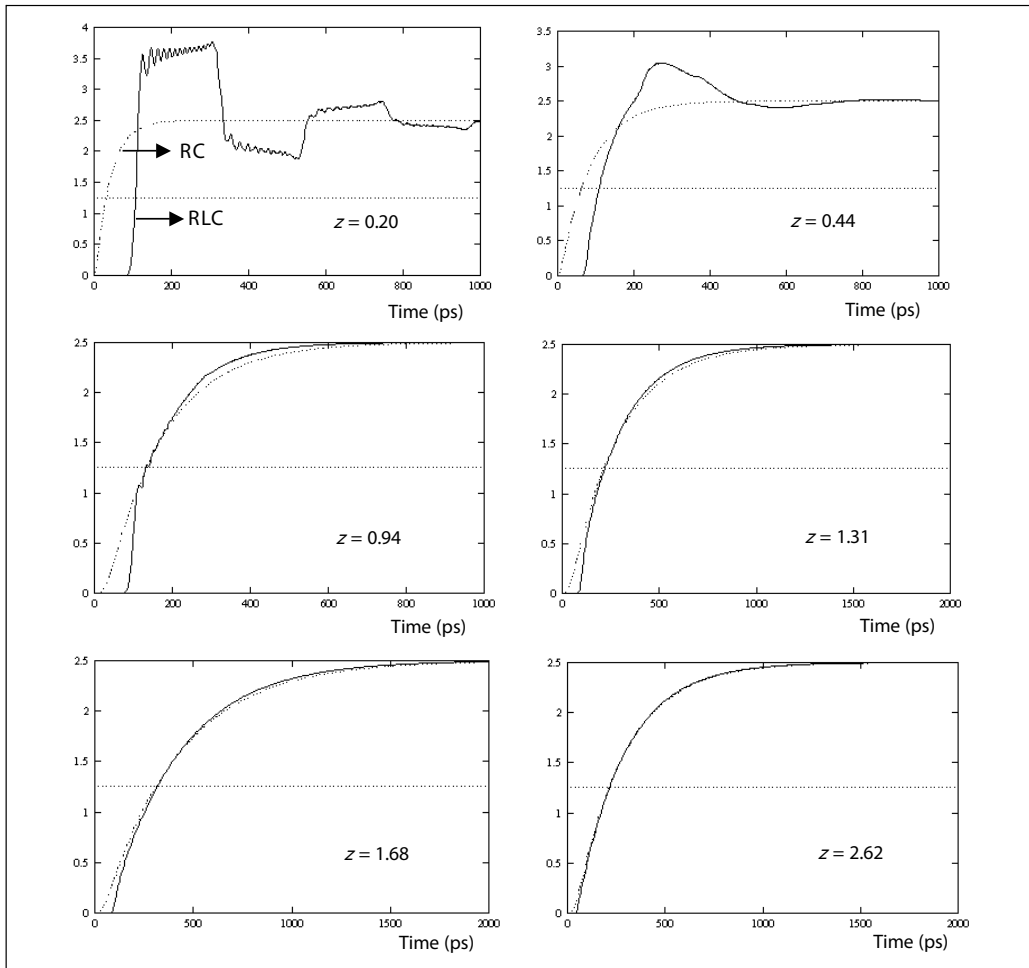

**Figure 3-51** RC vs. RLC models for interconnect for various values of  $\xi$  (from Ismail and Friedman [Ism00]). © 2000 IEEE.

### 3.8.3 Buffer Insertion in RLC Transmission Lines

Ismail and Friedman also showed where to place buffers in an RLC transmission line [Ism00]. The circuit is shown in Figure 3-53. The transmission line is divided into  $k$  sections, each of length  $l/k$ . All the buffers are of the same size and are  $h$  times larger than a minimum-size

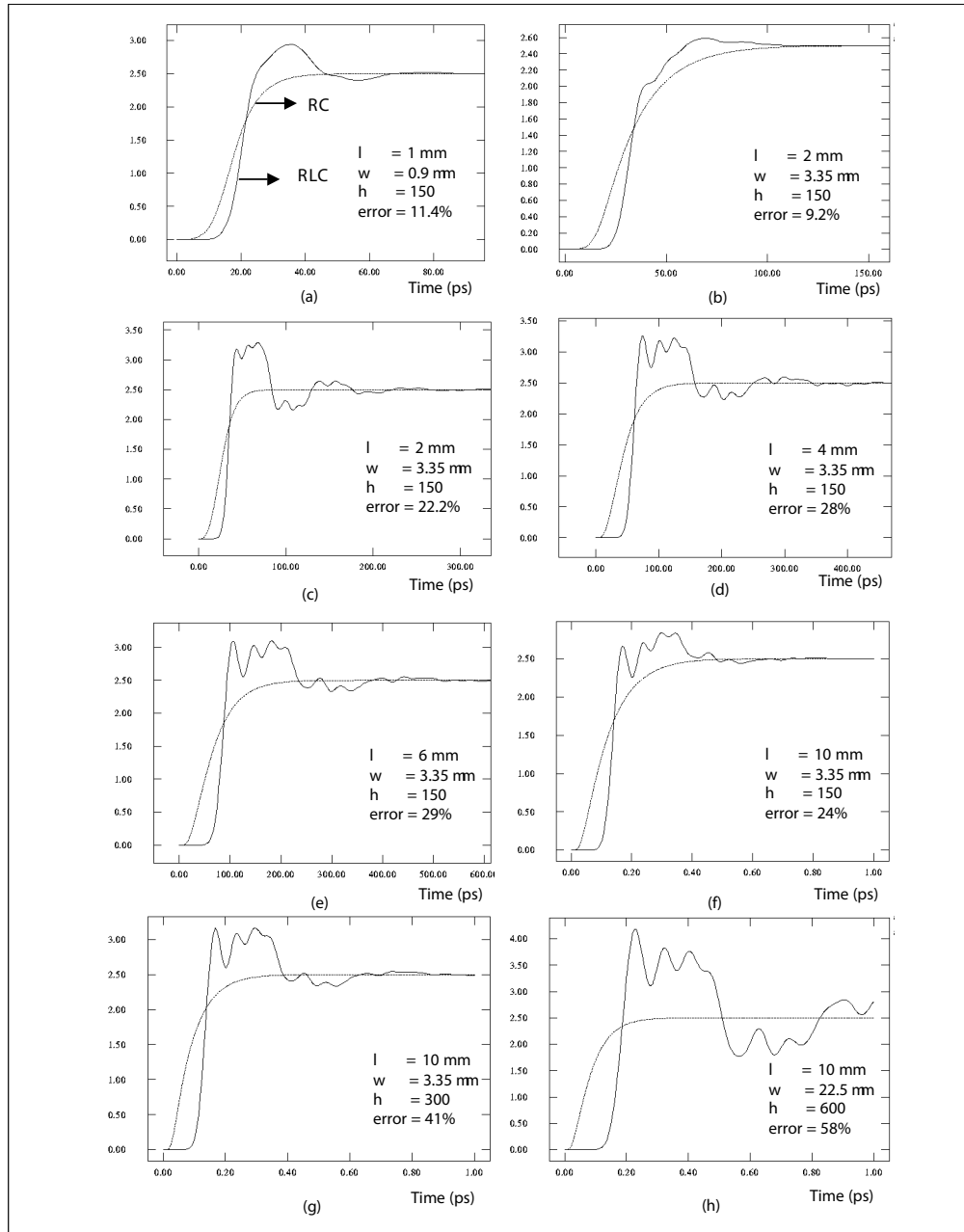

**Figure 3-52** CMOS gate driving a copper wire, using RC and RLC models (from Ismail and Friedman [Ism00]). © 2000 IEEE.

buffer; we use  $R_0$  and  $C_0$  to represent the source resistance and load capacitance of a minimum-size buffer.

 


Figure 3-53 Repeaters in an RLC transmission line.

We can define

$$T_{L/R} = \sqrt{\frac{L_t/R_t}{R_0 C_0}} \tag{EQ 3-59}$$

As in the RC case, we are interested in determining the optimum drive per stage  $h_{opt}$  and the optimum length of each stage's wire  $k_{opt}$ . This optimization problem cannot be solved analytically, but Ismail and Friedman fitted curves to the functions to provide these formula:

$$h_{opt} = \sqrt{\frac{R_0 C_t}{R_t C_0} \frac{1}{[1 + 0.16(T_{L/R})^3]^{0.3}}} \tag{EQ 3-60}$$

$$k_{opt} = \sqrt{\frac{R_t C_t}{2R_0 C_0} \frac{1}{[1 + 0.18(T_{L/R})^3]^{0.3}}} \tag{EQ 3-61}$$

### 3.9 Design-for-Yield

Design-for-yield is a relatively new term for a set of design processes that aim to improve chip yield in advanced processes. Traditionally, design and manufacturing have been maintained as separate tasks, with the interface between them described by the design rules. As we move to



nanometer processes, design rules prove to be inadequate to describe all the procedures that must be followed to obtain a high yield of chips that work at the design speed. Design-for-yield bridges the design/manufacturing boundary to improve yields without imposing extreme burdens on designers.

*causes of variations*

Variations in chips come from three major sources [Aga07]: systematic variations, random variations, and environmental variations. The chip designer does not have direct control over the environment in which the chip will operate, but the chip must be designed to be able to handle the expected range of environmental conditions. Random variations in electrical characteristics vary from chip to chip. Systematic variations can be predicted based on the design and mask information along with information about the manufacturing equipment. Systematic variations are known as either cross-field, which depend on position on the reticle, or layout-dependent, which is caused by a particular combination of layout features.

A variety of trends make it harder to manufacture chips at high yields:

- larger variations in process and circuit parameters;
- higher leakage currents;
- patterning problems caused by specific combinations of geometric features;
- metal width and thickness variations;
- stress in vias.

All these trends mean that manufacturing errors are harder to predict. Traditionally, we have used worst-case design rules for spacing and minimum width to abstract the manufacturing process and worst-case circuit design to handle device and interconnect variations. However, there are too many possible problems to be described in worst-case rules without suffering huge losses in yield.

*design-for-yield techniques*

The exact design-for-yield techniques to be used depend in part on the manufacturing process being targeted. However, some examples illustrate how we can bridge the manufacturing/design gap [Pet04]:

- Some lithography features depend on the exact configuration of mask features in ways that are too complex to be captured in design rules. Modern DRC closure techniques simulate the lithographic process to determine the on-chip features that will be created from a set of masks. These features are then checked for correctness. If an

error is found, such as an open or a short, the corresponding features on the mask can be identified and modified to prevent the problem from occurring on the fab line.

- Interconnect variations, either due to lithography or metal deposition, may cause a via to be partially uncovered. Adding an extra via can ensure that the connection is properly made. Some extra vias may not be acceptable because they require the layout to be come larger, increasing die size. An alternative is to change the metal configuration to avoid the coverage problem. If the extra via is added, it must be checked to be sure that it does not cause performance problems.
- Metal variations cause complex effects in circuit timing: thinner metal increases resistance but reduces coupling capacitance. Timing analysis can take advantage of statistical methods to determine whether metal variations may cause significant problems on a given circuit.

---

## 3.10 Gates as IP

---

A **standard cell library** is a set of cells designed to work together in a standard cell layout. Although some standard cells provide larger functions, such as adders, the logic gate is the principal component of standard cell libraries. The logical function of a standard cell is easy to describe. However, the layout of the cell must be carefully designed. The gate layouts of Section 3.3.2 are designed simply to pack the logical function into a small space. No concern was given to how the gate would fit into a larger layout and we did not seriously consider the different load capacitances that the gate might see at its output. If we want to design a gate layout to be used over and over in a variety of contexts, such as in the standard cell systems we saw in Section 2.7.5, we need to be much more careful.


### *standard cell organization*

A standard cell layout is standardized in several important respects, removing some degrees of freedom. The cell is designed to be placed in a row with other cells; some connections, like  $V_{DD}$  and  $V_{SS}$ , must match up from cell to cell. Furthermore, we must design cells to be electrically compatible. The cells in a standard cell library must be compatible at several levels of abstraction:

---

---

**Figure 3-54** Layout organization of a standard cell.

 

- **layout** Cell size, pin placement.
- **delay** Ability to drive a specified load with a given delay.
- **power** Power consumption as well as circuit topology.

Standard cell layout systems read in the basic library parameters from a database. This allows different libraries to be designed to different specifications, such as cell heights. But the cells in each library need to work together with each other.

*standard cell physical design*

The physical design of a standard cell is dictated by the placement and routing algorithms used. All cells are the same height and are designed to be abutted horizontally, with the left-hand  $V_{DD}$  and  $V_{SS}$  wires of one cell connecting to the right-hand  $V_{DD}$  and  $V_{SS}$  wires of the adjacent cell. The signal inputs and outputs are on the top and bottom of the cell. These pins must be placed on one of the layers used by the place-and-route system for connections into cells. Cells may be of differing widths, but the width of the cell has to be a multiple of the grid pitch to keep the pins on the grid. Many place-and-route systems allow over-the-cell routing. In this case, the cell designer must keep a certain part of the cell free of wires on the layer used for over-the-cell wires.

*standard cell logical design*

A standard cell library is designed to have a set of logical functions that cover an adequate range. Libraries generally have enough gates types so that functions can be implemented in more than one way. The complexity of a cell's function is determined largely by the size of the cell. Some typical functions for cells include:

<i>standard cell power options</i>	<ul style="list-style-type: none"> <li>• NAND, NOR, NOT.</li> <li>• AOI<sub>nm</sub>, OAI<sub>nm</sub>.</li> <li>• Adders, multiplexers, other register-transfer functions.</li> </ul> <p>Standard cell libraries should provide different versions of functions at different points on the power/delay curve. The simplest way to provide low-power and high-speed versions of a gate is to change the transistor sizes. However, the library may also provide more sophisticated versions of cells, such as sleep transistors. In this case, the tools that generate the logic given to the standard cell system must ensure that the circuits of gates along a path are compatible.</p>
<i>cell verification and qualification</i>	<p>Standard cell verification leans heavily on circuit simulation. The logical function of a gate, or even a 1-bit adder, is not too difficult to verify. Most of the CPU time in the verification process goes to extracting the circuit parameters, including parasitics, from the layouts and simulating the circuit behavior of the cells at many different combination of device and parasitic parameter values. The library specifications determine the worst-case delay and power consumption values that are acceptable. The cells must also be qualified on each fabrication process using a test chip. The test chip's logic should be designed to make it easy to determine the proper functioning of all types of cells. If several different libraries are allowed to be mixed together, such as low-power and high-performance libraries, the test chip should include circuits that test the proper functioning of combinations of these different cell types.</p> <p>The next example describes some widely used libraries.</p>

---

### **Example 3-4**

#### **The ARM Artisan™ Physical IP Libraries**

ARM provides the Artisan Physical IP library [ARM08], which in turn is distributed by MOSIS for use in MOSIS-fabricated projects. This family of cells includes several different libraries, each optimized for a different point in the design space:

- Advantage and SAGE-X includes cells up to arithmetic operations and register file cells. They are optimized for speed and density.
  - Advantage-HS and SAGE-HS are designed for high speed.
  - Metro cells provide high density and low power.
  - The Power Management Kit provides dynamic and leakage power management function. It provides several options for threshold voltage implants, including mixtures of implants in a cell. It also provides level shifters, retention flip-flops, and other circuits.
-

Cells from different libraries can be mixed-and-matched to provide high performance for part of the logic and high density for other parts.

---

### 3.11 References

---

Claude Shannon first showed how to model switch networks with Boolean functions for his Master's thesis which was later published in the *Transactions of the AIEE* [Sha38]. Keep in mind, however, that his paper didn't say that he was switching digital values and that switch networks were commonly used to route analog telephone signals at that time. Hodges and Jackson [Hod83] give an excellent introduction to device characteristics and digital circuit design, showing how to analyze CMOS logic gates as well as design more complex digital circuits. Books by Rabaey *et al.* [Rab03] and Uyemura [Uye92] are detailed presentations of digital logic circuits. Geiger, Allen, and Strader [Gei90] give a good introduction to circuit simulation as well as a number of important topics in circuit and logic design. Shoji [Sho88] gives a very thorough analysis of delay through CMOS gates. Domino logic was introduced by Krambeck, Lee, and Law [Kra82]. De *et al* [De01] concentrate on leakage currents in CMOS logic. Kursun and Friedman [Kur06] discuss multi-voltage CMOS logic in detail.

---

---

---

## 3.12 Problems

---

Use the parameters for the 180 nm process of Table 2-7 whenever process parameters are required and the transistor equivalent resistances of Table 3-2, unless otherwise noted.

Q3-1. Design the static complementary gates for these logic expressions. If the complementary form of the variable is given, assume that it is available.

- a)  $a'b'$ .
- b)  $a' + b'c'$ .
- c)  $a'b'c'$ .
- d)  $a'b' + c'd'$ .

Q3-2. Design stick diagrams for static complementary gates for each of these functions:

- a)  $a'b'$ .
- b)  $a'+b'c'$ .
- c)  $a'b'c'$ .
- d)  $a'b'+c'd'$ .

Q3-3. Write the defining logic equation and draw the transistor topology for each complex gate below:

- a) OAI-21.
  - b) AOI-21.
  - c) AOI-221.
  - d) OAI-222.
- 
-

Q3-4. Design stick diagrams for these complex gates:

- a) AOI-12.
- b) OAI-12.
- c) AOI-212.

Q3-5. Compare transistor sizes in NAND and NOR gates:

- a) Size the transistors in a three-input, static complementary NAND gate so that the gate's rise and fall times are approximately equal.
- b) Size the transistors in a three-input, static complementary NOR gate so that the gate's rise and fall times are approximately equal.
- c) Find the ratio of total transistor area in the NAND gate vs. the NOR gate.

Q3-6. Size the transistors in each of these gates so that its pullup and pulldown times are approximately equal:

- a)  $a'b'$ .
- b)  $a' + b'c'$ .
- c)  $a'b'c'$ .
- d)  $a'b' + c'd'$ .

Q3-7. What are the best-case and worst-case transition time for a two-input NAND gate with minimum-size transistors assuming a load equal to one minimum-size inverter?

Q3-8. What are the best-case and worst-case transition time for a two-input NOR gate with minimum-size transistors assuming a load equal to one minimum-size inverter?

Q3-9. Compute the capacitive load presented by these gates:

- a) Inverter with  $3/2$  pulldown and  $6/2$  pullup.
- b) 2-input NAND with  $6/2$  pulldown and  $6/2$  pullup.
- c) 2-input NOR with  $6/2$  pulldown and  $12/2$  pullup.

Q3-10. Compute transition times for an inverter with  $3/2$  pulldown and  $6/2$  pullup that drives an identically-sized inverter:

- a) Rise time.
  - b) Fall time.
- 
-

Q3-11. An inverter that drives a load equal to  $4C_1$  reaches its 50% output value at 12 ps. Compute the value of  $R_n$  required to model this behavior.

Q3-12. Compute transition time for a two-input NAND gate with  $6/2$  pulldown and  $6/2$  pullup that drives an identically-sized NAND gate:

- a) Rise time.
- b) Fall time.

Q3-13. Compute transition times for a two-input NOR gate with  $6/2$  pulldown and  $6/2$  pullup that drives an identically-sized NOR gate:

- a) Rise time.
- b) Fall time.

Q3-14. Compute transition times for a two-input NOR gate with  $6/2$  pulldown and  $12/2$  pullup that drives an identically-sized inverter:

- a) Rise time.
- b) Fall time.

Q3-15. Compute rise time for an inverter with  $3/2$  pulldown and  $6/2$  pullup that drives these wires (assume that the wire impedance is modeled as a single lump):

- a) Poly wire of width  $2\lambda$ , length  $1,000\lambda$ .
- b) Metal 1 wire of width  $3\lambda$ , length  $1,000\lambda$ .
- c) Metal 1 wire of width  $3\lambda$ , length  $10,000\lambda$ .

Q3-16. Compute fall time for a two-input NAND gate with  $6/2$  pulldown and  $6/2$  pullup that drives these wires (assume that the wire impedance is modeled as a single lump):

- a) Poly wire of width  $2\lambda$ , length  $1,000\lambda$ .
- b) Metal 1 wire of width  $3\lambda$ , length  $1,000\lambda$ .
- c) Metal 1 wire of width  $3\lambda$ , length  $10,000\lambda$ .

Q3-17. Compute fall time for a two-input NOR gate with  $6/2$  pulldown and  $12/2$  pullup that drives these wires (assume that the wire impedance is modeled as a single lump):

- a) Poly wire of width  $2\lambda$ , length  $1,000\lambda$ .
  - b) Metal 1 wire of width  $3\lambda$ , length  $1,000\lambda$ .
  - c) Metal 1 wire of width  $3\lambda$ , length  $10,000\lambda$ .
- 
-



Q3-18. Plot the rise time for a two-input NAND gate with  $6/2$  pulldown and  $6/2$  pullup as its load varies from one minimum-size inverter through 20 minimum-size inverters.

Q3-19. Plot the fall time for a two-input NAND gate with  $6/2$  pulldown and  $6/2$  pullup as its load varies from one minimum-size inverter through 20 minimum-size inverters.

Q3-20. Plot the rise time for a two-input NOR gate with  $6/2$  pulldown and  $12/2$  pullup as its load varies from one minimum-size inverter through 20 minimum-size inverters.

Q3-21. Plot the fall time for a two-input NOR gate with  $6/2$  pulldown and  $12/2$  pullup as its load varies from one minimum-size inverter through 20 minimum-size inverters.

Q3-22. Draw transistor-level schematics for domino gates that implement these functions:

- a) Three-input OR.
- b) Three-input AND.
- c)  $ab + c$ .
- d)  $ab + cd$ .

Q3-23. Draw stick diagrams for domino gates that implement these functions:

- a) Three-input OR.
- b) Three-input AND.
- c)  $ab+c$ .
- d)  $ab+cd$ .

Q3-24. Design a transistor-level schematic for a two-input NOR gate in MTCMOS logic.

Q3-25. Design a transistor-level schematic for a two-input NAND gate in MTCMOS logic.

---

---

Q3-26. Compute the Elmore delay for these wires assuming each wire is divided into 100 sections:

- a) Poly wire of width  $2\lambda$ , length  $1,000\lambda$ .
- b) Metal 1 wire of width  $3\lambda$ , length  $1,000\lambda$ .
- c) Metal 1 wire of width  $3\lambda$ , length  $10,000\lambda$ .
- d) Metal 2 wire of width  $3\lambda$ , length  $1,000\lambda$ .
- e) Metal 2 wire of width  $3\lambda$ , length  $10,000\lambda$ .
- f) Metal 3 wire of width  $3\lambda$ , length  $1,000\lambda$ .
- g) Metal 3 wire of width  $3\lambda$ , length  $10,000\lambda$ .

Q3-27. Plot the Elmore delay for these wires when calculated using 2 sections, 4 sections, and 10 sections:

- a) Metal 1 wire of width  $3\lambda$ , length  $1,000\lambda$ .
- b) Metal 2 wire of width  $3\lambda$ , length  $10,000\lambda$ .

Q3-28. Compute the optimal number of buffers and buffer sizes for these RC wires when driven by a minimum-size inverter:

- a) Metal 1 wire of width  $3\lambda$ , length  $1,000\lambda$ .
  - b) Metal 1 wire of width  $3\lambda$ , length  $10,000\lambda$ .
  - c) Metal 2 wire of width  $3\lambda$ , length  $1,000\lambda$ .
  - d) Metal 2 wire of width  $3\lambda$ , length  $10,000\lambda$ .
  - e) Metal 3 wire of width  $3\lambda$ , length  $1,000\lambda$ .
  - f) Metal 3 wire of width  $3\lambda$ , length  $10,000\lambda$ .
- 
-





**4**

# Combinational Logic Networks

## Highlights:


Layouts for logic networks.

Delay through networks.

Power consumption.

Switch logic networks.

Combinational logic testing.

 

A cutset through a critical timing path (Figure 4-12).



---

## 4.1 Introduction

---

This chapter concentrates on the design of combinational logic functions. Building a single inverter doesn't justify a multi-billion VLSI fabrication line. We want to build complex systems of many combinational gates. To do so, we will study basic aspects of hierarchical design and analysis, especially delay and power analysis. The knowledge gained about fabrication is important for combinational logic design—technology-dependent parameters for minimum size, spacing, and parasitic values largely determine how big a gate circuit must be and how fast it can run. We will use our knowledge of logic gates, developed in the last chapter, to analyze the delay and testability properties of combinational logic networks, including both the interconnect and the gates.

The next section talks about standard cells, a design technique at the intersection of logic and layout design. Section 4.3 builds models for analyzing delay in combinational logic networks. Section 4.4 describes design techniques for networks of gates. Section 4.5 analyzes the power consumption of logic networks. Section 4.6 introduces switch logic. Section 4.7 introduces methods for testing of logic networks.

---

## 4.2 Standard Cell-Based Layout

---

Many layout design methods are common to most subsystems. In this section we will cover general-purpose layout design methods for use in the rest of the chapter, largely by amplifying the lessons learned in Chapter 3.

*CMOS layouts are structured*

CMOS layouts are pleasantly tedious, thanks to the segregation of pullups and pulldowns into separate tubs. The tub separation rules force a small layout into a row of p-type transistors stacked on top of a row of n-type transistors. On a larger scale, they force the design into rows of gates, each composed of their own p-type and n-type rows. That style makes layout design easier because it clearly marks the boundaries of the design space.

*cell layout as placement and routing*

As has been mentioned before, a good way to attack the design of a layout is to divide the problem into placement, which positions components, and routing, which runs wires between the components. These two phases clearly interact: we can't route the wires until components

---

---


are placed, but the quality of a placement is judged solely by the quality of the routing it allows. We separate layout design into these two phases to make each part more tractable. We generally perform placement using simple estimates of the quality of the final routing, then route the wires using that fixed placement; occasionally we modify the placement and patch up the routing to fix problems that weren't apparent until all the wires were routed. The primitives in placement are almost always logic gates, memory elements, and occasionally larger components like full adders. Transistors are too small to be useful as placement primitives—the transistors in a logic gate move as a clump since spreading them out would introduce huge parasitics within the gate. We generally place logic gates in single-row layouts and either gates or larger register-transfer components in multi-row layouts.

#### 4.2.1 Single-Row Layout Design

*rows of gates + wiring channels*


We can design a one-row layout as a one-dimensional array of gates connected by wires. Changing the placement of logic gates (and as a result changing the wiring between the gates) has both area and delay effects. By sketching the wiring organization during placement, we can judge the feasibility of wiring, the size of the layout, and the wiring parasitics which will limit performance.

**Figure 4-1** Structure of a one-row layout.

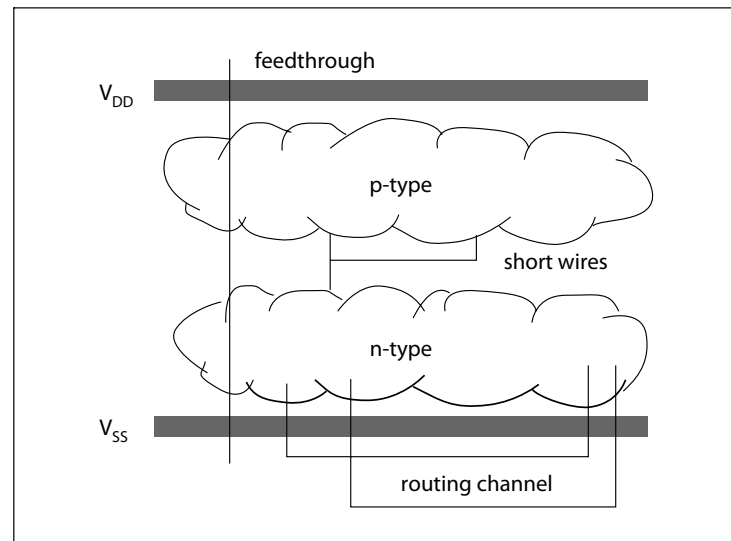

The basic structure of a one-row layout is shown in Figure 4-1. The transistors are all between the **power rails** formed by the  $V_{DD}$  and  $V_{SS}$  lines. The major routing **channel** runs below the power rails (there is another channel above the row, of course, that can also be used by these transistors). The gate inputs and outputs are near the center of the row, so vertical wires connect the gates to the routing channel and the outside world. Sometimes space is left in the transistor area for a feedthrough to allow a wire to be routed through the middle of the cell. Smaller areas within the transistor area—above the  $V_{SS}$  line, below the  $V_{DD}$  line, and between the n-type and p-type rows—are also available for routing wires.

**Figure 4-2** Intra-row wiring.

 


*intra-row wiring*

We usually want to avoid routing wires between the p-type and n-type rows because stretching apart the logic gates adds harmful parasitics, as discussed in Section 3.3.7. However, useful routing areas can be created when transistor sizes in the row vary widely, leaving extra room around the smaller transistors, as shown in Figure 4-2. The intra-row wiring areas are useful for short wires between logic gates in the same row—not only is a routing track saved, but the wire has significantly less capacitance since it need not run down to the routing channel and back up. Intra-row routing is a method of last resort, but if it becomes



necessary, the best way to take advantage of the available space is to first design the basic gate layout first, then look for interstitial space around the small transistors where short wires can be routed, and finally to route the remaining wires through the channel.

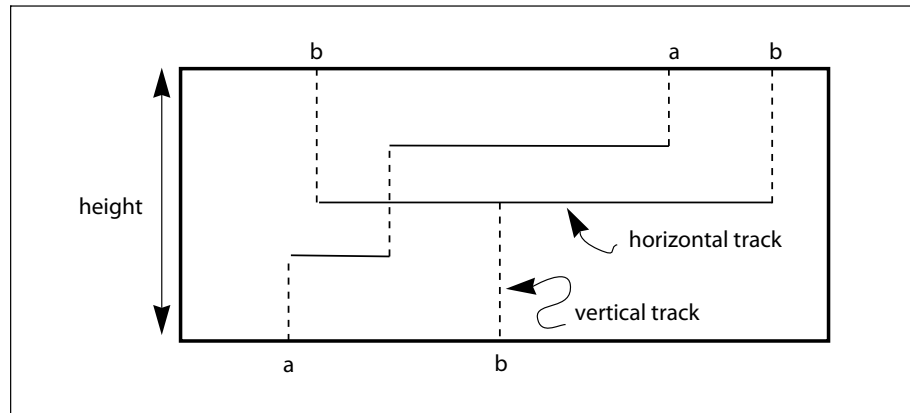

**Figure 4-3** Structure of a routing channel.


#### *channel structure*

The wiring channel's structure is shown in Figure 4-3. A channel has pins only along its top and bottom walls. The channel is divided into **horizontal tracks**, more typically called **tracks**, and **vertical tracks**. The horizontal and vertical tracks form a grid on which wire segments are placed. The distance between tracks is equal to the minimum spacing between a wire and a via. Using a standard grid greatly simplifies wiring design with little penalty—human or algorithmic routers need only place wires in the tracks to ensure there will be no design rule violations. Wire segments on horizontal and vertical tracks are on separate layers—some advanced routing programs occasionally violate this rule to improve the routing, but keeping vertical and horizontal wire segments separate greatly simplifies wiring design. Segregation ensures that vertical wires are in danger of shorting horizontal wires only at corners, where vias connect the horizontal and vertical layers. If we consider each horizontal segment to be terminated at both ends by vias, with longer connections formed by multiple segments, then the routing is completely determined by the endpoints of the horizontal segments.

The width of the routing channel is determined by the placement of pins along its top and bottom edges. The major variable in area devoted to signal routing is the height of the channel, which is determined by the **density**—the maximum number of horizontal tracks occupied on any

vertical cut through the channel. Good routing algorithms work hard to minimize the number of tracks required to route all the signals in a channel, but they can do no better than the density: if three signals must go from one side of the channel to the other at a vertical cut, at least three tracks are required to accommodate those wires.

**Figure 4-4**  
Channel density  
changes with pin  
placement.

 

*pin placement*

Changing the placement of pins can change both the density and the difficulty of the routing problem. Consider the example of Figure 4-4. The position of a pin along the top or bottom edge is determined by the position of the incoming vertical wire that connects the channel to the appropriate logic gate input or output; the transistor rows above and below the wiring channel can both connect to the channel, though at opposite edges. In this case, swapping the *a* and *b* pins reduces the channel density from three to two.


*density and wirability*

Density is a measure that can be used to evaluate the wirability of a channel before we have actually completed the wiring. It is very important to be able to estimate the results of routing so that we can provide for adequate space in the design. It is sometimes valuable to leave extra space in the channel to make it easier to route the wires, as well as to be able to change the wiring to accommodate logic design changes. Not all blocks of logic are equally performance-critical, and it may be worth spending some area to make a logic block easier to layout and to modify.


The next example walks through the design process for a one-row layout.
 
### Example 4-1 Layout of a full adder

A full adder illustrates the techniques used to design single-row layouts. The full adder computes two functions:  $s_i = a_i \oplus b_i \oplus c_i$  and  $c_{i+1} = a_i \cdot b_i + a_i \cdot c_i + b_i \cdot c_i$ . We will compute  $s_i$  using two two-input XORs:



 We will use a two-level NAND network to compute  $c_{i+1}$ :




(An AOI gate is a better choice for the carry computation, but we have more cells to use to illustrate placement options by choosing this implementation.) We have a total of six gates to place and route. In this case, we won't use intra-row wiring—all of the wires will go into the wiring channel below the gates. Our layout job is to place the gates such that the wiring channel below the row of gates has as few tracks as possible.

We can use a three-step process to generate and evaluate a candidate layout for the adder:

 1. Place the gates in a row by any method.
2. Draw the wires between the gates and the primary inputs and outputs.
3. Measure the density of the channel.

Once we have evaluated a placement, we can decide how to improve it. We can generate the first placement by almost any means; after that, we use the results of the last routing to suggest changes to the placement.

The full adder has four gates to place, two for each function. We will start by keeping together the gates for each function:



Though the final layout will have its wires in the wiring channel below the cell, we have drawn the wires over the gates here for clarity—drawing the paths of the wires down to the channel and then back up to the gate inputs is too confusing. The channel density for this placement is five.

We can try to reduce the channel density by interchanging gates. Two opportunities suggest themselves:

- **Swap the gates within each function.** A simple test shows that this doesn't reduce the density.
- **Swap the XOR pair with the NAND network.** This doesn't help either, because we must still drag  $a_i$ ,  $b_i$ , and  $c_i$  to the XORs and send  $c_{i+1}$  to the right edge of the cell.

This placement seems to give the minimum-height routing channel, which means that the channel's area will be as small as possible. Gate placement can affect transistor size in larger layouts—we may be able to reduce the sizes of the transistors in some critical gates by placing those gates closer together. But in a layout this small, if we use metal wiring as much as possible, the sizes of the gate cells are fixed. So minimizing wiring channel density minimizes total layout area.

Systems with more than six gates provide more opportunities for placement optimization. If we are more concerned about parasitics on some critical wires (such as the carry), we can choose a placement to make those wires as short as possible. If those wires are sufficiently critical,

we may even want to increase density beyond the minimum required to make those critical wires shorter.


*routing algorithms*

We also need to know how to route the wires in the channel. Channel routing is NP-complete [Szy85], but simple algorithms exist for special cases, and effective heuristics exist that can solve many problems. Here, we will identify what makes each problem difficult and identify some simple algorithms and heuristics that can be applied by hand.


The **left-edge algorithm** is a simple channel routing algorithm that uses only one horizontal wire segment per net. The algorithm sweeps the channel from left to right; imagine holding a ruler vertically over the channel and stopping at each pin, whether it is on the top or bottom of the channel. If the pin is the first pin on a net, that net is assigned its lone horizontal wire segment immediately. The track assignment is greedy—the bottommost empty track is assigned to the net. When the last pin on a net is encountered, the net’s track is marked as empty and it can be reused by another net farther to the right. The vertical wire segments that connect the pins to the horizontal segment, along with the necessary vias, can be added separately, after assignment of horizontal segments is complete. The next example shows how to use this algorithm to route a channel.

**Example 4-2**  
**Left-edge channel routing**


This channel has three nets:

 

 
The left-most net is *A*; we route it in the first empty track, which is track 1. We run a wire segment from *A*'s left-most pin to its right-most:



 Moving to the right, the next pin is *B*. Track 1 is occupied, so we route *B* in track 2:




 The third and final net is *C*. At this position, *A* no longer occupies track 1, so we can reuse it to route *C*:



Once the horizontal wire segments have all been placed, we can add the vertical wire segments to connect the tracks to the pins and, of course, the vias needed to connect the horizontal and vertical segments. Since the channel needs only two tracks, its height can be reduced appropriately.


**Figure 4-5** A channel that cannot be routed by the left-edge algorithm.

 

*vertical constraints and routability*

The left-edge algorithm is exact for the problems we have encountered so far—it always gives a channel with the smallest possible height. But it fails in an important class of problems illustrated in Figure 4-5. Both ends of nets **A** and **B** are on the same vertical tracks. As a result, we can't route both nets using only one horizontal track each. If only one of the pins were moved—for instance, the right pin of **B**—we could route **A** in the first track and **B** in the second track. But pins along the top and bottom of the track are fixed and can't be moved by the router—the router controls only the placement of horizontal segments in tracks. Vertically aligned pins form a **vertical constraint** on the routing problem: on the left-hand side of this channel, the placement of **A**'s pin above **B**'s constrains **A**'s horizontal segment to be above **B**'s at that point; on the right-hand side, **B**'s horizontal segment must be above **A**'s at that point in the channel. We obviously can't satisfy both constraints simultaneously if we restrict each net to one horizontal segment.

**Figure 4-6** A dogleg wire.

 

*dogleg wires*

The natural solution is to allow a net to move from track to track as it travels along the channel [Deu76]. Figure 4-6 shows a **dogleg**—those who can see Greek gods in the constellations should also be able to identify this wire as a dog's outstretched hind leg. We can use one single-track net and one dogleg to route the channel of Figure 4-5. Dogleg channel routing algorithms are much more sophisticated than the

left-edge algorithm. If you want to route a channel with a few cyclic constraints by hand, a good strategy is to route the nets that require dog-legs first, then route the remaining nets using the left-edge algorithm, avoiding the regions occupied by the previously routed nets.

### 4.2.2 Standard Cell Layout Design

#### *multi-row layouts*


Large layouts are composed of several rows. We introduced standard cell layout in Chapter 2; we are now in a position to investigate standard cell layout design in more detail. A standard cell layout is composed of cells taken from a library. Cells include combinational logic gates and memory elements, and perhaps cells as complex as full adders and multiplexers. A good standard cell library includes many variations on logic gates: NANDs, NORs, AOIs, OAI, etc., all with varying number of inputs. The more complete the library, the less that is wasted when mapping your logic function onto the available components.

Figure 4-7 shows how the layout of a typical standard cell is organized. All cells in the library must have the same **pitch** (the distance between two points, in this case height) because they will be connected by abutment and their  $V_{DD}$  and  $V_{SS}$  lines must match up. Wires that must be connected to other cells are pulled to the top and bottom edges of the cell and placed to match the grid of the routing channel. The wire must be presented at the cell's edge on the layer used to make vertical connections in the channel. Most of the cell's area cannot be used for wiring, but some cells can be designed with a feedthrough area. Without feedthroughs, any wire going from one channel to another would have to be run to the end of the channel and around the end of the cell row; feedthroughs provide shortcuts through which delay-critical wires can be routed.

#### *driving standard cell loads*

Transistors in standard cells are typically much larger than those in custom layouts. The designer of a library cell doesn't know how it will be used. In the worst case, a cell may have to drive a wire from one corner of a large chip to the other. To ensure that even worst-case delays are acceptable, the cells are designed with large transistors. Some libraries give two varieties of cells: high-power cells can be used to drive long wires, while low-power cells can be used to drive nodes with lower capacitive loads. Of course, the final selection cannot be made until after placement; we usually make an initial selection of low- or high-power based on the critical path of the gate network, then adjust the selection after layout. Furthermore, both low-power and high-power



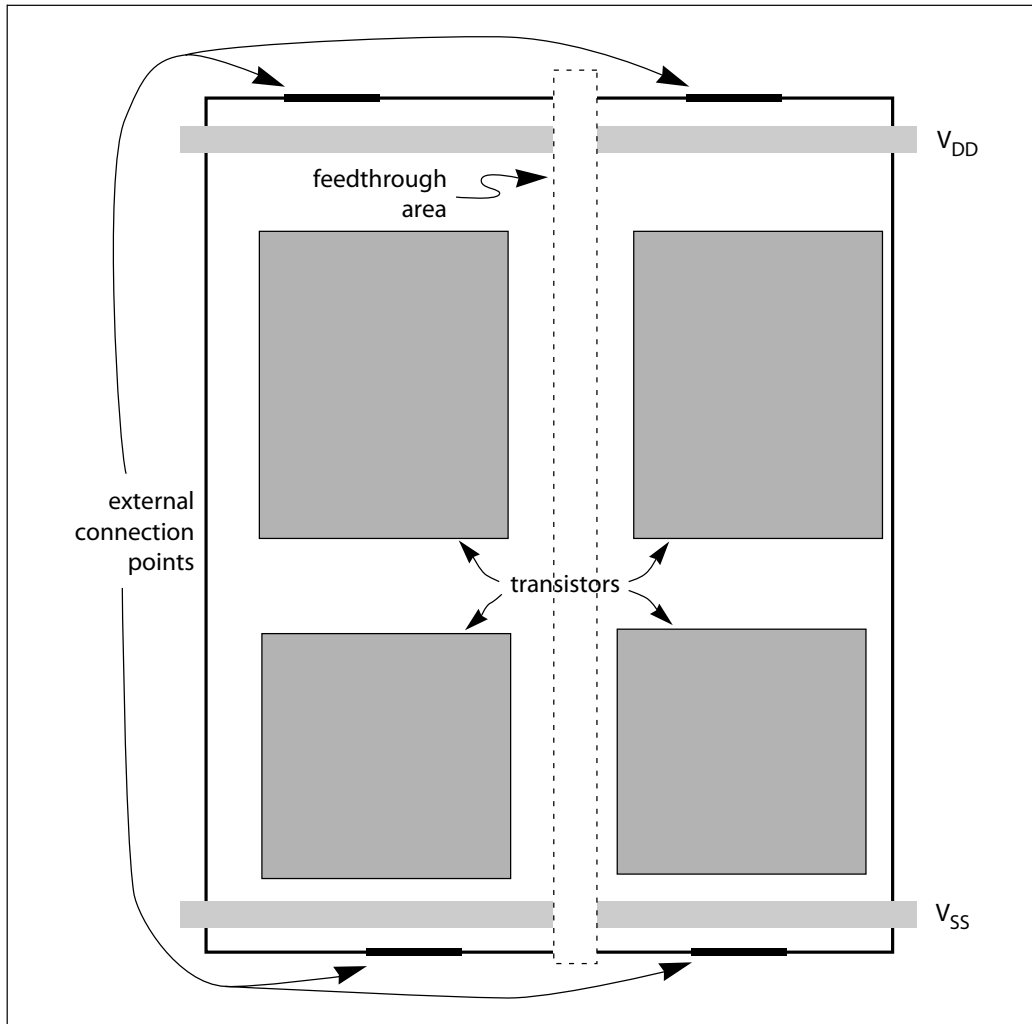


**Figure 4-7** Configuration of a typical standard cell.

cells must be the same height so that they can be mixed; the smaller transistor sizes of low-power cells may result in narrower cells.

*area and delay*

The interaction between area and delay in a multi-row layout can be complex. Generally we are interested in minimizing area while satisfying a maximum delay through the combinational logic. One good way

**Figure 4-8** A rat's nest plot of wires.

 

to judge the wirability of a placement is to write a program to generate a **rat's nest** plot. (Use a program to generate the plot—it is too tedious to construct by hand for examples of interesting size.) An example is shown in Figure 4-8. The plot shows the position of each component, usually as a point or a small box, and straight lines between components connected by a wire. The straight line is a grossly simplified cartoon of the wire's actual path in the final routing, but for medium-sized layouts it is sufficient to identify congested areas. If many lines run through a small section, either the routing channel in that area will be very tall, or wires will have to be routed around that region, filling up other channels. Individual wires also point to delay problems—a long line from one end of the layout to the other indicates a long wire. If that wire is on the critical delay path, the capacitance of the wire will seriously affect performance.

## 4.3 Combinational Network Delay

---


We know how to analyze the speed of a single logic gate, but that isn't sufficient to know the delay through a complex network of logic gates. The delay through one or two gates may in fact limit a system's clock rate—transistors that are too small to drive the gate's load, particularly if the gate fans out to a number of other gates, may cause one gate to run

---

---

much more slowly than all the other gates in the system. However, the clock rate may be limited by delay on a path through a number of gates. The delay through a combinational network depends in part on the number of gates the signal must go through; if some paths are significantly longer than others, the long paths will determine the maximum clock rate. The two problems must be solved in different ways: speeding up a single gate requires modifying the transistor sizes or perhaps the layout to reduce parasitics; cutting down excessively long paths requires redesigning the logic at the gate level. We must consider both to obtain maximum system performance.

**Figure 4-9** Sources of delay through a single gate.

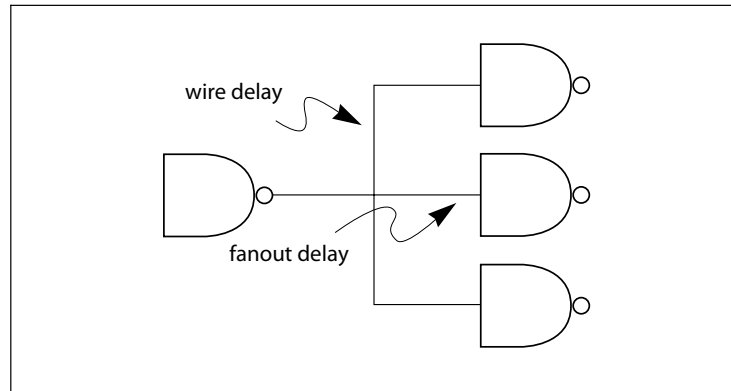

In this section, we'll assume that the wires between the gates are ideal. In the next section we will extend our techniques to take into account the characteristics of real interconnect.

### 4.3.1 Fanout


#### *sources of gate delay*

Let's first consider the problems that can cause a single gate to run too slowly. A gate runs slowly when its pullup and pulldown transistors have  $W/L$ s too small to drive the capacitance attached to the gate's output. As shown in Figure 4-9, that capacitance may come from the transistor gates or from the wires to those gates. The gate can be sped up by increasing the sizes of its transistors or reducing the capacitance attached to it.

#### *fanout capacitance*

Logic gates that have large **fanout** (many gates attached to the output) are prime candidates for slow operation. Even if all the fanout gates use minimum-size transistors, presenting the smallest possible load, they may add up to a large load capacitance. Some of the fanout gates may use transistors that are larger than they need, in which case those transi-

**Figure 4-10** Fanout reduction by buffer insertion.

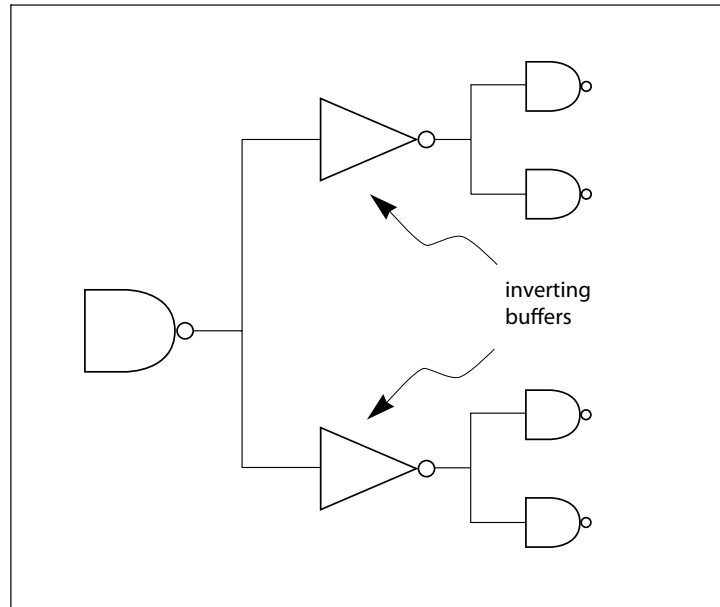

tors can be reduced in size to speed up the previous gate. In many cases this fortuitous situation does not occur, leaving two possible solutions:


- The transistors of the driving gate can be enlarged, in severe cases using the buffer chains of Section 3.3.8.
- The logic can be redesigned to reduce the gate's fanout.

An example of logic redesign is shown in Figure 4-10. The driver gate now drives two inverters, each of which drives two other gates. Since inverters were used, the fanout gates must be reversed in sense to absorb the inversion; alternatively, non-inverting buffers can be used. The inverters/buffers add delay themselves but cut down the load capacitance on the driver gate. In the case shown in the figure, adding the inverters probably slowed down the circuit because they added too much delay; a gate which drives more fanout gates can benefit from buffer insertion.

#### *wire capacitance*

Excess load capacitance can also come from the wires between the gate output and its fanout gates. We saw in Section 3.7.3 how to optimally add buffers in RC transmission lines.

**Figure 4-11** A graph model for delay through combinational logic.

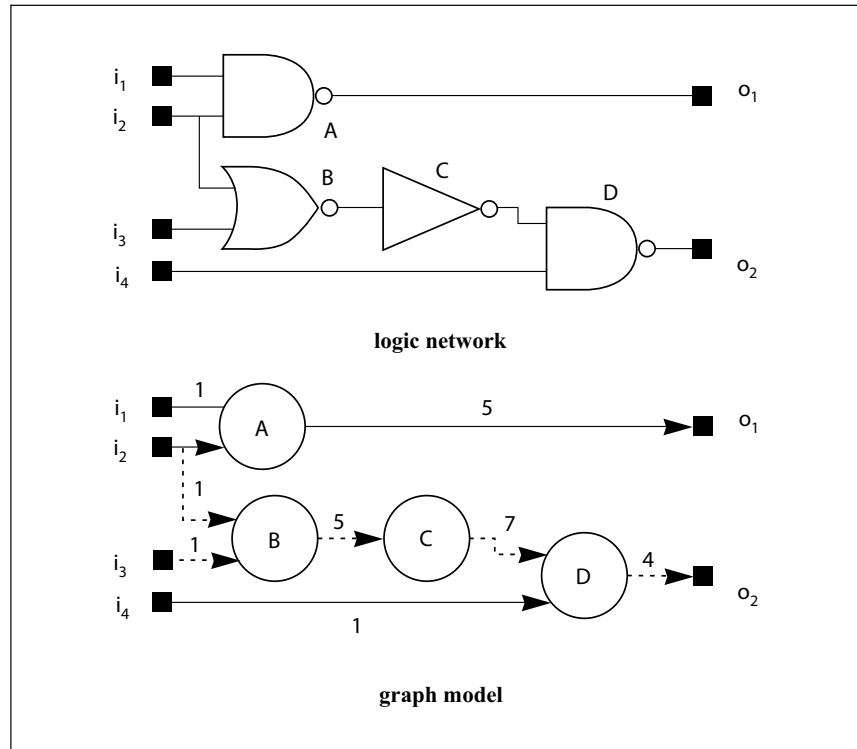

### 4.3.2 Path Delay

*paths and delay*

In other cases, performance may be limited not by a single gate, but by a **path** through a number of gates. To understand how this can happen and what we can do about it, we need a concise model of the combinational logic that considers only delays. As shown in Figure 4-11, we can model the logic network and its delays as a directed graph. Each logic gate and each primary input or output is assigned its own node in the graph. When one gate drives another, an edge is added from the driving gate's node to the driven gate's node; the number assigned to the edge is the delay required for a signal value to propagate from the driver to the input of the driven gate. (The delay for 0→1 and 1→0 transitions will in general be different; since the wires in the network may be changing arbitrarily, we will choose the worst delay to represent the delay along a path.)

In building the graph of Figure 4-11, need to know the gate along each edge in the graph. We use a **delay calculator** to estimate the delay from one gate's input through the gate and its interconnect to the next gate's input. The delay calculator may use a variety of models ranging from simple to complex. We will consider the problem of calculating the delay between one pair of gates in more detail in Section 4.4.1.

*propagating a single event*

The simplest delay problem to analyze is to change the value at only one input and determine how long it takes for the effect to be propagated to a single output. (Of course, there must be a path from the selected input to the output.) That delay can be found by summing the delays along all the edges on the path from the input to the output. In Figure 4-11, the path from *i4* to *o2* has two edges with a total delay of 5 ns.


We could use a logic simulator that models delays to compute the delays through various paths in the logic. However, system performance is determined by the *maximum* delay through the logic—the longest delay from any input to any output for any possible set of input values. To determine the maximum delay by simulation, we would have to simulate all  $2^n$  possible input values to the combinational logic. It is possible, however, to find the logic network's maximum delay without exhaustive simulation. **Timing analysis** [McW80,Ost83] builds a graph that models delays through the network and identifies the longest delay path. Timing analysis is also known as *static timing analysis* because it determines delays statically, independent of the values input to the logic gates.

*critical path*

The longest delay path is known as the **critical path** since that path limits system performance. We know that the graph has no cycles, or paths from a node back to itself—a cycle in the graph would correspond to feedback in the logic network. As a result, finding the critical path isn't too difficult. In Figure 4-11, there are two paths of equal length: *i2* → *B* → *C* → *D* → *o2* and *i3* → *B* → *C* → *D* → *o2* both have total delays of 17 ns. Any sequential system built from this logic must have a total delay of 17 ns, plus the setup time of the latches attached to the outputs, plus the time required for the driving latches to switch the logic's inputs (a term which was ignored in labeling the graph's delays).

The critical path not only tells us the system cycle time, it points out what part of the combinational logic must be changed to improve system performance. Speeding up a gate off the critical path, such as *A* in the example, won't speed up the combinational logic. The only way to reduce the longest delay is to speed up a gate on the critical path. That can be done by increasing transistor sizes or reducing wiring capaci-

**Figure 4-12**  
A cutset through a critical timing path.

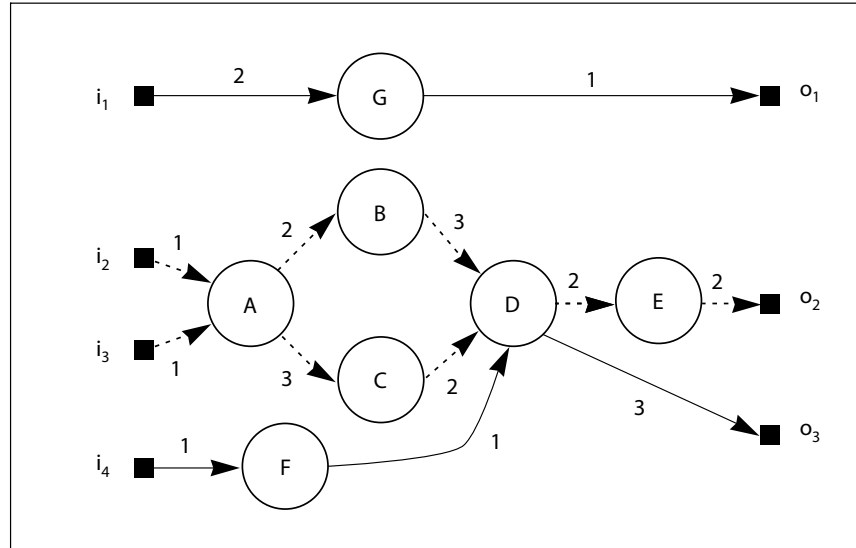

tance. It can also be done by redesigning the logic along the critical path to use a faster gate configuration.

*cutsets and timing optimization*


Speeding up the system may require modifying several sections of logic since the critical path can have multiple branches. The circuit in Figure 4-12 has a critical path with a split and a join in it. Speeding up the path from B to D will not speed up the system—when that branch is removed from the critical path, the parallel branch remains to maintain its length. The system can be improved only by speeding up both branches [Sin88]. A **cutset** is a set of edges in a graph that, when removed, break the graph into two unconnected pieces. Any cutset that separates the primary inputs and primary outputs identifies a set of speedups sufficient to reduce the critical delay path. The set b-d and c-d is one such cutset; the single edge d-e is another. We probably want to speed up the circuit by making as few changes to the network as possible. It may not be possible, however, to speed up every connection on the critical path. After selecting a set of optimization locations identified by a cutset, you must analyze them to be sure they can be sped up, and possibly alter the cutset to find better optimization points.

*false paths*


However, not all paths in the timing analysis graph represent changes propagating through the circuit that limit combinational delay. Because logic gates compute Boolean functions, some paths through the logic network are cut short. Consider the example of Figure 4-14—the upper input of the NAND gate goes low first, followed by the lower input.

4.3 Combinational Network Delay

**Figure 4-13**  
Using Boolean identities to reduce delay.

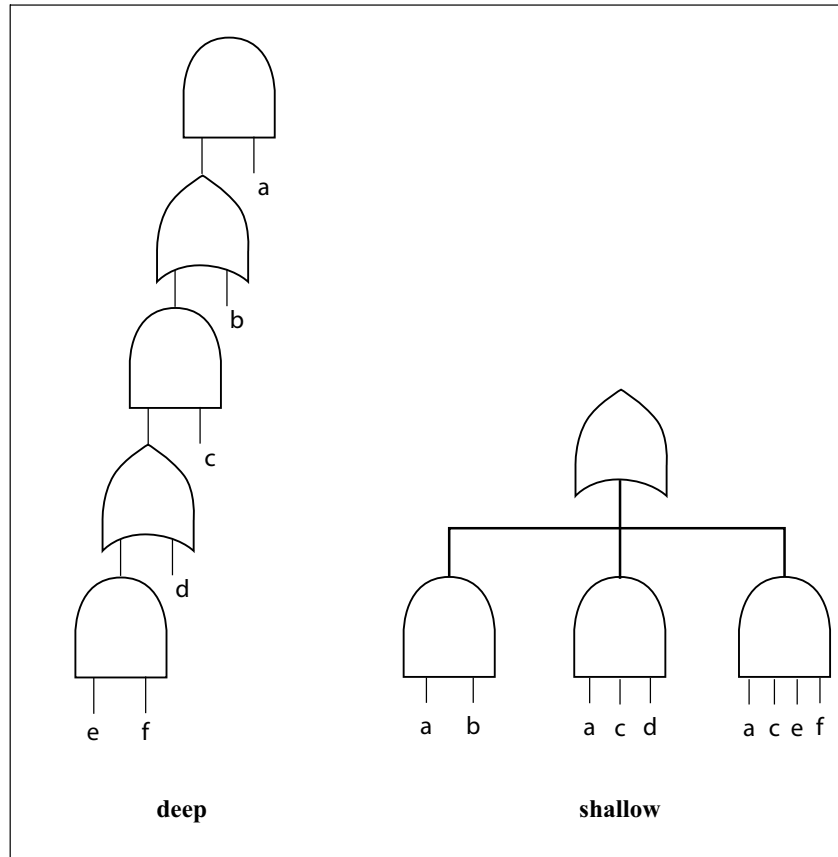

**Figure 4-14** Boolean gates create false delay paths.

 

Either input going low causes the NAND's output to go low, but after one has changed, the high-to-low transition of the other input doesn't affect the gate's output. If we know that the upper input changes first,



we can declare the path through the lower input a **false path** for the combination of primary input values which cause these internal transitions. Even if the false path is longer than any true path, it won't determine the network's combinational delay because the transitions along that path don't cause the primary outputs to change. Note, however, that to identify false paths we must throw away our previous, simplifying assumption that the delay between two gates is equal to the worst of the rise and fall times.

Redesigning logic to reduce the critical path length requires rewriting the function to reduce the number of logic levels. Consider the logic of Figure 4-13. The critical path is clearly from e and f to the primary output. Writing the Boolean expression for this network both illustrates its depth and suggests a solution. The function is  $a(b + c(d + ef))$ ; by eliminating parentheses we can reduce the depth of the equivalent logic network. The logic corresponding to  $ab + acd + acef$  has only two levels. Care must be taken, however—flattening logic leads to gates with higher fanin. Since adding inputs to a gate slows it down (due to the delay through series transistors), all of the delay gained by flattening may be eaten up in the gates.


### 4.3.3 Transistor Sizing

One of the most powerful tools available to the integrated circuit designer is transistor sizing. By varying the sizes of transistors at strategic points, a circuit can be made to run much faster than when all its transistors have the same size. Transistor sizing can be chosen arbitrarily in full-custom layout, though it will take extra time to construct the layout. But transistor sizing can also be used to a limited extent in standard cells if logic gates come in several versions with variously-sized transistors.

The next example illustrates the effects of transistor sizing on one of the most important circuits, the adder.
 
### Example 4-3 Transistor sizing in an adder carry chain


We will concentrate on the carry chain of the adder, since the longest delay follows that path. We will use a ripple-carry adder made of full adders (the full adder is described in more detail in Section 6.3). For this adder, we will use an AOI gate to implement the carry computation because it is faster and more compact than a NAND-NAND network. The AOI must compute the function  $c_{i+1} = a_i b_i + (a_i + b_i) c_i$ . Here is the schematic for the AOI gate:



We arranged the order of transistors to put the early-arriving signals,  $a_i$  and  $b_i$ , closer to the power supplies, as was discussed in Section 3.3.4. We will build a four-bit carry chain using four of these AOI gates, with the four outputs being  $c_1$ ,  $c_2$ ,  $c_3$ , and  $c_4$ .

The worst case for delay is that the  $a$  or  $b$  are 1 and the carry-in to the zero-th stage  $c_0$  is 1. We will make the simplifying assumption that  $a_i=1$  and  $b_i=0$  for all bits, since other combinations only add a small delay which is independent of the stage. The carry of the  $i^{\text{th}}$  stage, on the other hand, must wait for the  $i-1^{\text{th}}$  stage to complete.

 The simplest circuit uses small transistors all of the same size. Using the 180 nm technology, we have made all n-type transistors with  $W/L = 270\text{nm}/180\text{nm}$  and all p-type transistors with  $W/L = 540\text{nm}/180\text{nm}$ . Here are the waveforms for the four carry outputs in this case:




You can verify for yourself that uniformly increasing the sizes of all the transistors in the carry chain does not decrease delay—all the gates have larger loads to drive, negating the effect of higher drive.
 
## 4.3 Combinational Network Delay

229


The worst-case delay scenario for the pulldown network is the same in every stage:  $c_i$  is the latest-arriving signal and is rising. We can therefore widen these highlighted transistors in the AND-OR pulldown network:



These transistors include the pulldown controlled by  $c_i$  and the  $a_i$  and  $b_i$  transistors on the same path, which also must be widened to ensure that they do not become a bottleneck. We must also increase the size of the output inverter.

We will first try making the  $a$ ,  $b$ , and  $c$  pulldowns with  $W/L = 540nm/180nm$ , the first-stage inverter pullup with  $W/L = 1620nm/180nm$  and the pulldown with  $W/L = 540nm/180nm$ .

 
The inverters in the subsequent stages have pullups and pulldowns of size  $W/L = 540nm/180nm$ . Here is the result:



The adder is now somewhat faster. The slope of  $c_1$  is now steeper and all the  $c$ 's are spaced closer together.

We can try increasing the sizes of the transistors in the second and third stages, also increasing the first-stage transistors somewhat. In this case, the first-stage  $a$  and  $b$  pulldowns in the first stage have  $W/L = 270nm/180nm$ , the first stage  $c$  pulldown have  $W/L = 1080nm/180nm$ , and the first-stage inverter with a  $W/L = 1620nm/180nm$  pullup and  $W/L = 540nm/180nm$  pulldown. The second- and third-stage  $a$ ,  $b$ , and  $c$  pulldowns have been increased in size to  $W/L = 1080nm/180nm$ . The inverter pullup is  $W/L = 1080nm/180nm$  and pulldown is  $W/L = 540nm/180nm$  as in the last case.

Here are the results:

 

This is much faster than our previous efforts. The total carry propagation takes less time and the four carry outputs are about equally spaced.

#### *logical effort*

The theory of **logical effort** [Sut99] provides a clear and useful foundation for transistor sizing. Logical effort uses relatively simple models to analyze the behavior of chains of gates in order to optimally size all the transistors in the gates. Logical effort works best on tree networks and less well on circuits with reconvergent fanout, but the theory is both widely useful and intuitively appealing. Logical effort not only lets us easily calculate delay, it shows us how to size transistors to optimize delay along a path.

Logical effort computes  $d$ , the delay of a gate, in units of  $\tau$ , the delay of a minimum-size inverter. We start with a model for a single gate. A gate's delay consists of two components:

$$d = f + p. \quad (\text{EQ 4-1})$$

The **effort delay**  $f$  is related to the gate's load, while the **parasitic delay**  $p$  is fixed by the gate's structure. We can express the effort delay in terms of its components:

$$f = gh. \quad (\text{EQ 4-2})$$

The **electrical effort**  $h$  is determined by the gate's load while the logical effort  $g$  is determined by the gate's structure. Electrical effort is given by

the relationship between the gate’s capacitive load and the capacitance of its own drivers (which is related to the drivers’ current capability):

$$h = \frac{C_{out}}{C_{in}}. \tag{EQ 4-3}$$

**Table 4-1** Logical effort for several types of static CMOS gates.

	1 input	2 inputs	3 inputs	4 inputs	n inputs
<b>inverter</b>	1				
<b>NAND</b>		4/3	5/3	6/3	(n+2)/3
<b>NOR</b>		5/3	7/3	9/3	(2n+1)/3
<b>mux</b>		2	2	2	2
<b>XOR</b>		4	12	32	

The **logical effort**  $g$  for several different gates is given in Table 4-1. The logical effort can be computed by a few simple rules.

We can rewrite Equation 3-1 using our definition of  $f$  to give

$$d = gh + p. \tag{EQ 4-4}$$

We are now ready to consider the logical effort along a path of logic gates. The path logical effort of a chain of gates is

$$G = \prod_{i=1}^n g_i. \tag{EQ 4-5}$$

The electrical effort along a path is the ratio of the last stage’s load to the first stage’s input capacitance:

$$H = \frac{C_{out}}{C_{in}}. \tag{EQ 4-6}$$

**Branching effort** takes fanout into account. We define the branching effort  $b$  at a gate as

$$b = \frac{C_{onpath} + C_{offpath}}{C_{onpath}}. \tag{EQ 4-7}$$

The branching effort along an entire path is

$$B = \prod_{i=1}^n b_i. \quad (\text{EQ 4-8})$$

The path effort is defined as

$$F = GBH. \quad (\text{EQ 4-9})$$

The path delay is the sum of the delays of the gates along the path:

$$D = \sum_{i=1}^N d_i = \sum_{i=1}^N g_i h_i + \sum_{i=1}^N p_i = D_F + P. \quad (\text{EQ 4-10})$$

We can use these results to choose the transistor sizes that minimize the delay along that path. We know from Section 3.3.8 that optimal buffer chains are exponentially tapered. When recast in the logical effort framework, this means that each stage exerts the same effort. Therefore, the optimal stage effort is

$$\hat{f} = F^{1/N}. \quad (\text{EQ 4-11})$$

We can determine the ratios of each of the gates along the path by starting from the last gate and working back to the first gate. Each gate  $i$  has a ratio of

$$C_{\text{in},i} = \frac{g_i C_{\text{out},i}}{\hat{f}}. \quad (\text{EQ 4-12})$$

The delay along the path is

$$\hat{D} = NF^{1/N} + P. \quad (\text{EQ 4-13})$$

Example 4-4 illustrates the use of logical effort in transistor sizing.



---

### Example 4-4 Sizing transistors with logical effort

Let us apply logical effort to a chain of three two-input NAND gates. The first NAND gate is driven by a minimum-size inverter and the output of the last NAND gate is connected to an inverter that is 4X the minimum size.

The logical effort for the chain of three NAND gates is

$$G = \prod_{i=1}^3 \frac{4}{3}.$$

The branching effort along the path is  $B = 1$  since there is no fanout. The electrical effort is the ratio of input to output capacitances, which was given as 4. Then

$$F = GBH = \left(\frac{4}{3}\right)^3 \times 1 \times 4 = 9.5.$$

The optimum effort per stage is

$$\hat{f} = \sqrt[3]{9.5} = 2.1.$$

Since all the stages have the same type of gate, we can compute the output-to-input capacitance ratio for the stages as

$$\frac{C_{\text{in},i}}{C_{\text{out},i}} = \frac{g_i}{h} = \frac{4/3}{2.1} = 0.6.$$


---

#### 4.3.4 Logic Synthesis

Logic design—turning a logic function into a network of gates—is tedious and time-consuming. While we may use specialized logic designs for ALUs, **logic optimization** or **logic synthesis** programs are often used to design random logic. Logic optimization programs have two goals: area minimization and delay satisfaction. Logic optimizers typically minimize area subject to meeting the designer's specified maximum delay. These tools can generate multi-level logic using a variety of methods: simplification, which takes advantage of don't-cares; common factor extraction; and structure collapsing, which eliminates common factors by reducing logic depth.

---

Finding good common factors is one of the most important steps in multi-level logic optimization. There are two particularly useful types of common factors: a cube is a product of literals; a kernel is a sum-of-products expression. A factor for a function  $f$  must be made of literals found in  $f$ . One way to factorize logic is to generate potential common factors and test each factor  $k$  to see whether it divides  $f$ —that is, whether there is some function  $g$  such that  $g = f/k$ . Once we have found a set of candidate factors for  $f$ , we can evaluate how they will affect the network's costs. A factor that can be used in more than one place (a common factor) can help save gate area, though at the cost of some additional wiring area. But factors increase the delay and power consumption of the logic network. The effects of introducing a factor can be evaluated in several ways with varying levels of accuracy.

The important point to remember at this point is that logic optimization along with place-and-route algorithms give us an automated path from Boolean logic equations to a complete layout.

---

## 4.4 Logic and Interconnect Design

---

In this section, we will consider how to design logic networks using realistic interconnect models. Interconnect comes in all shapes and sizes. Not only do nets vary in the number of gates they connect, but they can be laid out in a number of different topologies as well.

### *wiring trees*

Figure 4-15 shows the two basic forms of interconnection trees. Think of the gate inputs and outputs as nodes in a graph and the wires connecting them as edges in the graph. A **spanning tree** uses wire segments to directly connect the gate inputs and outputs. A **Steiner tree** adds nodes to the graph so that wires can join at a **Steiner point** rather than meeting at a gate input or output.

### *wiring optimizations*

In order to make the problem tractable, we will generally assume that the logic structure is fixed. This still leaves us many degrees of freedom:


- we can change the topology of the wires connecting the gates;
- we can change the sizes of the wires;
- we can add buffers;
- we can size transistors.

We would like to solve all these problems simultaneously; in practice we solve either one at a time or a few in combination. Even this careful

---



---

 **Figure 4-15** Varieties of wiring trees.

approach leaves us with quite a few opportunities for optimizing the implementation of our combinational network.

#### 4.4.1 Delay Modeling


##### *accurate and fast models*

We saw in Section 4.3.2 that timing analysis consists of two phases: using a delay calculator to determine the delay to each gate's output; and using a path analyzer to determine the worst-case critical timing path. The delay calculator's model should take into account the wiring delay as well as the driving and driven gates. When analyzing large networks, we want to use a model that is accurate but that also can be evaluated quickly. Quick evaluation is important in timing analysis but even more important when you are optimizing the design of a wiring network. Fast analysis lets you try more wiring combinations to determine the best topology.

The Elmore model is well-known because it is computationally tractable. However, it works only for single RC sections. In some problems,

such as when we are designing wiring tree topologies, we can break the wiring tree into a set of RC sections and use the Elmore model to evaluate each one independently. In other cases, we want to evaluate the entire wiring tree, which generally requires numerical techniques.


**Figure 4-16** The effective capacitance model.

 

*effective capacitance model*

One model often used is the effective capacitance model shown in Figure 4-16. This model considers the interconnect as a single capacitance. While this is a simplified model, it allows us to separate the calculation of gate and interconnect delay. We then model the total delay as the sum of the gate and interconnect delays. The gate delay is determined using the total load capacitance and numerically fitting a set of parameters that characterize the delay. Qian *et al.* developed methods for determining an effective capacitance value [Qia94]. **Asymptotic waveform evaluation (AWE)** [Pil90] is a well-known numerical technique that can be used to evaluate the interconnect delay. AWE uses numerical techniques to find the dominant poles in the response of the network; those poles can be used to characterize the network's response.

**Figure 4-17** A  $\pi$  model for RC interconnect.

 

*$\pi$  model*


The  $\pi$  model, shown in Figure 4-17, is often used to model RC interconnect. The  $\pi$  model consists of two capacitors connected by a resistor. The values of these components are determined numerically by analyzing the characteristics of the RC network. The waveform at the output of the  $\pi$  model (the node at the second capacitor) does not reflect the wire's output waveform—this model is intended only to capture the effect of the wire's load on the gate. This model is chosen to be simple yet capture the way that resistance in an RC line shields downstream capaci-

tance. Capacitance near the driver has relatively little resistance between it and the driver, while wire capacitance farther from the driver is partially shielded from the driver by the wire's resistance. The  $\pi$  model divides the wire's total capacitance into shielded and unshielded components.

#### 4.4.2 Wire Sizing

We saw in Section 3.7.1 that the delay through an RC line can be reduced by tapering it. The formulas in that section assumed a single RC section. Since many wires connect more than two gates, we need methods to determine how to size wires in more complex wiring trees.

**Figure 4-18** A tree with sized segments.

 

Cong and Leung [Con93] developed CAD algorithms for sizing wires in wiring trees. In a tree, the sizing problem is to assign wire widths to each segment in the wire, with each segment having constant width; since most paths require several turns to reach their destinations, most trees have ample opportunities for tapering. Their algorithm also puts wider wires near the source and narrower wires near the sinks to minimize delay, as illustrated in Figure 4-18.

#### 4.4.3 Buffer Insertion

We saw in Section 3.7.3 how to insert buffers in a single RC transmission line. However, in practice we must be able to handle RC trees. Not only do the RC trees have more complex topologies, but different subtrees may have differing sizes and arrival time requirements.

*buffering RC trees*


van Ginneken [van90] developed an algorithm for placing buffers in RC trees. The algorithm is given the placement of the sources and sinks and the routing of the wiring tree. It places buffers within the tree to mini-

mize the departure time required at the source that meets the delay requirements at the sinks:

$$T_{\text{source}} = \min_i(T_i - D_i) \quad (\text{EQ 4-14})$$

where  $T_i$  is the arrival time at node  $i$  and  $D_i$  is the required delay between the source and sink  $i$ . This ensures that even the longest delay in the tree satisfies its arrival time requirement.

**Figure 4-19**  
Recursively  
computing  
delay in the  
van Ginneken  
algorithm.

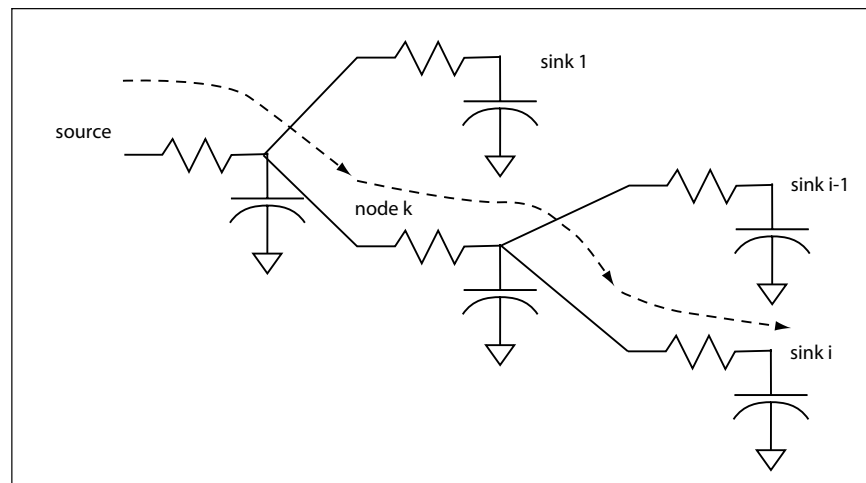

This algorithm uses the Elmore model to compute the delay through the RC network. As shown in Figure 4-19, when we want to compute the delay from the source to sink  $i$ , we apply the R and C values along that path to the Elmore formula. If we want to compute the delay from some interior node  $k$  to sink  $i$ , we can use the same approach, counting only the resistance and capacitance on the path from  $k$  to  $i$ .

This formulation allows us to recursively compute the Elmore delay through the tree starting from the sinks and working back to the source. Let  $r$  and  $c$  be the unit resistance and capacitance of the wire and  $L_k$  be the total capacitive load of the subtree rooted at node  $k$ . As we walk the tree, we need to compute the required time  $T_k$  of the signal at node  $k$  assuming the tree is driven by a zero-impedance buffer.

When we add a wire of length  $l$  at node  $k$ , then the new delay at node  $k$  is

$$T_k' = T_k - r l L_k - \frac{1}{2} r c l^2, \quad (\text{EQ 4-15})$$

$$L_k' = L_k + c l. \quad (\text{EQ 4-16})$$

When node  $k$  is buffered the required time becomes

$$T_k' = T_k - D_{\text{buf}} - R_{\text{buf}} L_k, \quad (\text{EQ 4-17})$$

$$L_k' = C_{\text{buf}}, \quad (\text{EQ 4-18})$$

where  $D_{\text{buf}}$ ,  $R_{\text{buf}}$ , and  $C_{\text{buf}}$  are the delay, resistance, and capacitance of the buffer, respectively.

When we join two subtrees  $m$  and  $n$  at node  $k$ , the new values become

$$T_k = \min(T_m, T_n), \quad (\text{EQ 4-19})$$

$$L_k = L_m + L_n. \quad (\text{EQ 4-20})$$


We can then use these formulas to recursively evaluate buffering options in the tree. The algorithm's first phase moves bottom-up to calculate all the buffering options at each node in the tree. The second phase chooses the best buffering strategy at each node in the tree.

#### 4.4.4 Crosstalk Minimization

Coupling capacitances between wires can introduce crosstalk between signals. Crosstalk at best increases the delay required for combinational networks to settle down; at worst, it causes errors in dynamic circuits and memory elements. We can, however, design logic networks to minimize the crosstalk generated between signals.

##### *circuit techniques*

We can use basic circuit techniques as a first line of defense against crosstalk. One way to minimize crosstalk is to introduce a larger capacitance to ground (or to  $V_{DD}$ , which is also a stable voltage). Since ground is at a stable voltage, it will not introduce noise into a signal. The larger the capacitance to ground relative to the coupling capacitance, the smaller the effect of the coupling capacitance, since the amount of charge on each capacitance is proportional to the value of the capacitance. In that case, the ground capacitance is said to *swamp out* the coupling capacitance. One way to add capacitance to ground is to interleave

 

**Figure 4-20** Interleaved ground signals for crosstalk minimization.

$V_{SS}$  or  $V_{DD}$  wires between the signal wires as shown in Figure 4-20. This method is particularly well-suited to signals that must run together for long distances. Adding ground wires works best for groups of signals which travel together for long distances.


If we cannot provide shielding, minimizing coupling capacitance will help to reduce the effects of crosstalk. A simple example shows how we can redesign wire routes to reduce crosstalk.



---

 **Example 4-5**  
**Crosstalk**  
**minimization**

We need to route these signals in a channel:




Let us assume for the moment that we can measure the total crosstalk in the wiring by examining only the horizontal wires. The vertical wires can introduce coupling, but they are generally shorter and we can also arrange to put them on a layer with lower coupling capacitance.

---

---

 Here is one routing for these wires which minimizes channel height (assuming one horizontal segment per wire) but which has significant capacitive coupling:




If we assume that non-adjacent wires have no coupling, then the total coupling capacitance for this route is:

- a-b 5**
- b-c 6**
- c-d 5**

for a total coupling capacitance of 16 units.

 By rearranging the track assignments, we can significantly reduce the total coupling without changing the channel height or total wire length:



This routing has less coupling:


- a-b 5
- a-d 2
- c-d 5

for a total coupling capacitance of 12 units.

*twizzling*

One technique for reducing the correlation between two wires is **twizzling**. As illustrated in Figure 4-21, after running together for a certain length, wires change tracks so that they are adjacent to different wires. (The track-switching segments of the wires are shown schematically for simplicity.) The total coupling capacitance on each wire does not change. However, that capacitance no longer goes to a single wire, but to several different wires. If the signals on the twizzled wires are not correlated, then each wire will on average receive a smaller aggressor signal.

**Figure 4-21** Twizzling wires to randomize crosstalk.

 

*estimating crosstalk delay*

However, in practice, minimizing crosstalk requires estimating the delays induced by crosstalk, not just minimizing coupling capacitance. Routing problems are sufficiently complex that it may not be obvious how to balance coupling capacitance against other criteria in the absence of information about how much critical path delay that coupling capacitance actually induces. Detailed analytical models are too complex and slow to be used in the inner loop of a routing algorithm. Sapatnekar [Sap00] developed an efficient crosstalk model that can be used during routing.

The effect of the coupling capacitance depends on the relative transitions of the aggressor and victim nets:

- When the aggressor changes and the victim does not, the coupling capacitance takes its nominal value  $C_c$ .
- When the aggressor and victim switch in opposite directions, the coupling capacitance is modeled as  $2C_c$ .
- When the aggressor and victim switch in the same direction, the coupling capacitance is modeled as 0.

The major problem in modeling the effect of coupling is that those effects depend on the relative switching times of the two nets. If the driver inputs of two nets switch in the intervals  $[T_{\min,1}, T_{\max,1}]$  and  $[T_{\min,2}, T_{\max,2}]$  and the propagation delays for those two signals are  $[d_{1,\min}, d_{1,\max}]$  and  $[d_{2,\min}, d_{2,\max}]$ , then the lines can switch during the intervals  $[T_{\min,1} + d_{1,\min}, T_{\max,1} + d_{1,\max}]$  and  $[T_{\min,2} + d_{2,\min}, T_{\max,2} + d_{2,\max}]$ . We can write the above observations on the coupling capacitance more precisely in terms of these intervals:

- $\max(T_{\min,1} + d_{1,\min}, T_{\min,2} + d_{2,\min}) < t < \min(T_{\max,1} + d_{1,\max}, T_{\max,2} + d_{2,\max})$   
Coupling capacitance is 0 or  $2C_c$ , depending on whether the aggressor and victim nets switch in the same or opposite directions.

- $\min(T_{\min,1} + d_{1,\min}, T_{\min,2} + d_{2,\min}) < t < \max(T_{\min,1} + d_{1,\min}, T_{\min,2} + d_{2,\min})$   
Coupling capacitance is  $C_c$ .
- $\min(T_{\max,1} + d_{1,\max}, T_{\max,2} + d_{2,\max}) < t < \max(T_{\max,1} + d_{1,\max}, T_{\max,2} + d_{2,\max})$   
Coupling capacitance is  $C_c$ .

Furthermore, the values for the  $d$ s depend on the values chosen for the coupling capacitance, which of course depends on the  $d$ s. As a result, an iterative algorithm must be used to solve for the transition times and coupling capacitances. The effective coupling capacitance's value changes over the course of the signal propagation and the order in which the transition times and coupling capacitances are updated affect the speed at which the solution converges.

Sapatnekar's algorithm iteratively finds the delays through the signals; since only a few iterations are generally required, the algorithm can be used in the inner loop of a router. This allows the router to exchange nets to reduce the actual crosstalk between the wires, not just their coupling capacitance.

There are several other ways to redesign the layout to reduce the amount of coupling capacitance between wires. One method is to increase the spacing between critical signals [Cha93]. Since the coupling capacitance decreases with distance, this technique can reduce the coupling capacitance to an acceptable level. However, this may require significant space when applied to signals that are coupled over a long distance. Alternatively, signals may be swapped in their tracks [Gao94] or a more global view may be taken to assign signals to tracks to minimize total crosstalk risk [Kir94]. Xue *et al.* [Xue96] developed an algorithm that tries to minimize the total crosstalk risk across the chip. It starts with crosstalk risk values for signal pairs, based on an assessment of the criticality of a signal, etc. It then selects nets for rip-up and reroute in order to minimize the total crosstalk risk.

## 4.5 Power Optimization

---

Power consumption is an important metric in VLSI system design. In this section, we will look at estimating power in logic networks and optimizing those networks to minimize their power consumption.

---




---

### 4.5.1 Power Analysis

#### *glitches and power*

We saw in Section 3.3.5 how to optimize the power consumption of an isolated logic gate. One important way to reduce a gate's power consumption is to make it change its output as few times as possible. While the gate would not be useful if it never changed its output value, it is possible to design the logic network to reduce the number of *unnecessary* changes to a gate's output as it works to compute the desired value.

 


**Figure 4-22** Glitching in a simple logic network.

Figure 4-22 shows an example of power-consuming glitching in a logic network. Glitches are more likely to occur in multi-level logic networks because the signals arrive at gates at different times. In this example, the NOR gate at the output starts at 0 and ends at 0, but differences in arrival times between the gate input connected to the primary input and the output of the NAND gate cause the NOR gate's output to glitch to 1.

#### *sources of glitching*

Some sources of glitches are more systematic and easier to eliminate. Consider the logic networks of Figure 4-23, both of which compute the sum  $a+b+c+d$ . The network on the left-hand side of the figure is configured as a long chain. The effects of a change in any signal—either a primary input or an intermediate value—propagate through the successive stages. As a result, the output of each adder assumes multiple values as values reach its inputs. For example, the last adder first takes on the value of the  $d$  input (assuming, for simplicity, that all the signals start at 0), then computes  $c+d$  as the initial value of the middle adder arrives, and finally settles at  $a+b+c+d$ . The right-hand network, on the other hand, is more balanced. Intermediate results from various subnetworks reach the next level of adder at roughly the same time. As a result, the adders glitch much less while settling to their final values.

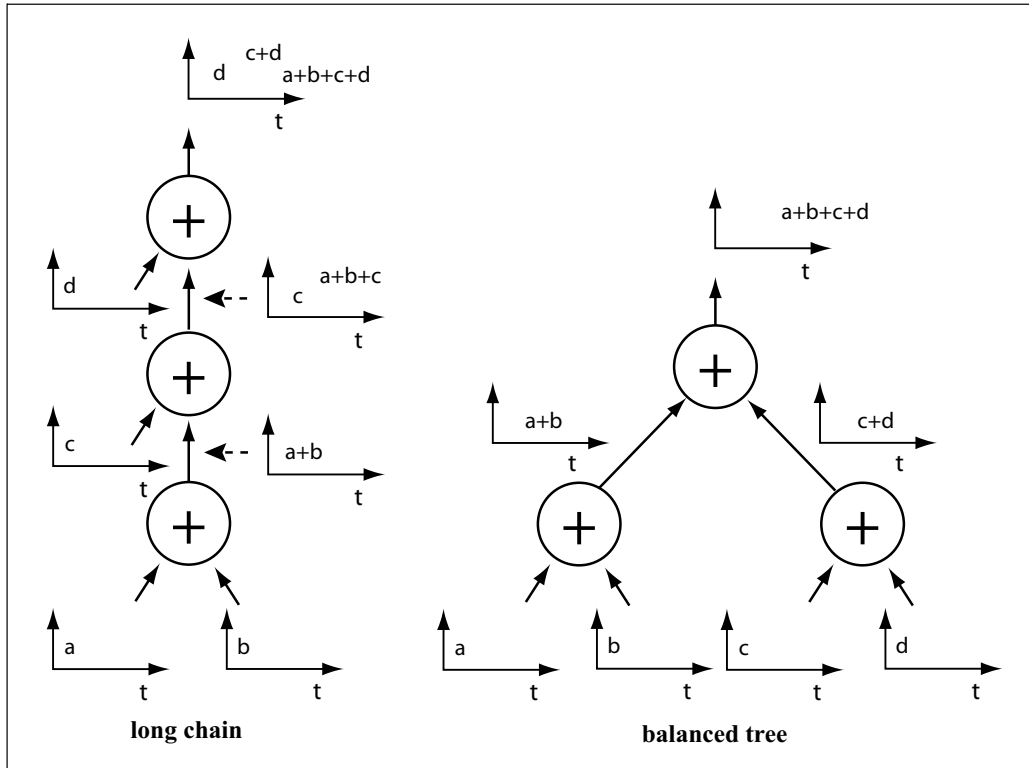

**Figure 4-23** Glitching in a chain of adders.

*signal probabilities*

We cannot in general eliminate glitches in all cases. We may, however, be able to eliminate the most common kinds of glitches. To do so, we need to be able to estimate the **signal probabilities** in the network. The signal probability  $P_s$  is the probability that signal  $s$  is 1. The probability of a transition  $P_{tr,s}$  can be derived from the signal probability, assuming that the signal's values on clock cycles are independent:

$$P_{tr,s} = 2P_s(1-P_s). \tag{EQ 4-21}$$

The first matter to consider is the probability distribution of values on primary inputs. The simplest model is that a signal is equally likely to be 0 or 1. We may, however, have some specialized knowledge about signal probabilities. Some control signals may, for example, assume one value most of the time and only occasionally take on the opposite value

## 4.5 Power Optimization

249

*delay-independent and delay-dependent power estimation*

to signal an operation. Some sets of signals may also have correlated values, which will in turn affect the signal probabilities of logic gate outputs connected to those sets of signals.

Signal probabilities are generally computed by **power estimation tools** which take in a logic network, primary input signal probabilities, and perhaps some wiring capacitance values and estimate the power consumption of the network. There are two major ways to compute signal probabilities and power consumption: **delay-independent** and **delay-dependent**. Analysis based on delay-independent signal probabilities is less accurate than delay-dependent analysis but delay-independent values can be computed much more quickly. The signal probabilities of primitive Boolean functions can be computed from the signal probabilities of their inputs. Here are the formulas for NOT, OR, and AND:

$$P_{NOT} = 1 - P_{in}; \quad (\text{EQ 4-22})$$

$$P_{OR} = 1 - \prod_{i \in \text{in}} (1 - P_i); \quad (\text{EQ 4-23})$$

$$P_{AND} = \prod_{i \in \text{in}} P_i. \quad (\text{EQ 4-24})$$


When simple gates are combined in networks without reconvergent fanout, the signal probabilities of the network outputs can easily be computed exactly. More sophisticated algorithms are required for networks that include reconvergent fanout.

*power estimation tools*

Delay-independent power estimation, although useful, is subject to errors because it cannot predict delay-dependent glitching. The designer can manually assess power consumption using a simulator. This technique, however, suffers the same limitation as does simulation for delay in that the user must manually evaluate the combinations of inputs that produce the worst-case behavior. Power estimation tools may rely either directly on simulation results or on extended techniques that use simulation-style algorithms to compute signal probabilities. The time/accuracy trade-offs for power estimation track those for delay estimation: circuit-level methods are the most accurate and costly; switch-level simulation is somewhat less accurate but more efficient; logic-based simulation is less powerful but can handle larger networks.

Given the power estimates from a tool, the designer can choose to redesign the logic network to reduce power consumption as required. Logic synthesis algorithms designed to minimize power can take advantage of



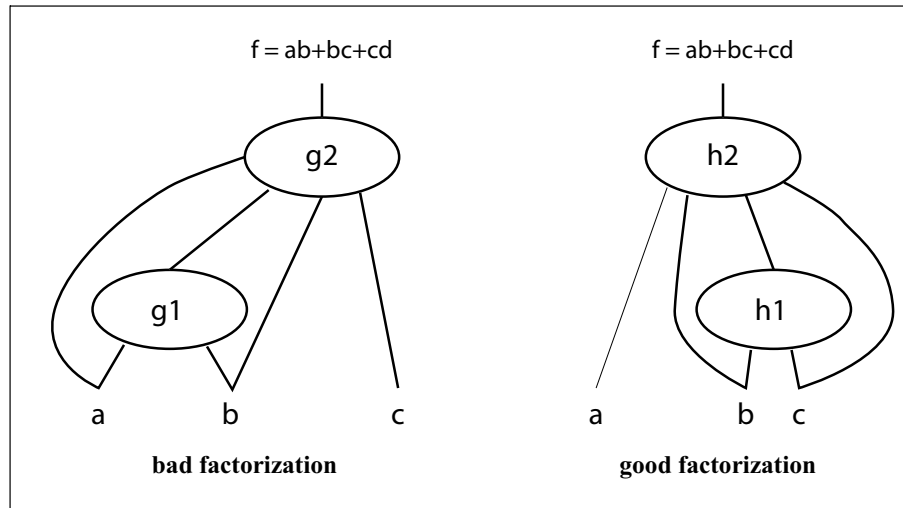

**Figure 4-24** Logic factorization for power.

signal probabilities to redesign the network [Roy93]. Figure 4-24 shows two factorizations of the function  $f = ab + bc + cd$  [Ped96]. If  $a$  glitches much more frequently than  $b$  and  $c$ , then the right-hand network exhibits lower total glitching: in the left-hand network, both  $g1$  and  $g2$  glitch when  $a$  changes; in the right-hand network, glitches in  $a$  cause only  $h2$  to glitch.

Glitch analysis can also be used to optimize placement and routing. Nodes that suffer from high glitching should be laid out to minimize their routing capacitance. The capacitance estimates from placement and routing can be fed back to power estimation to improve the results of that analysis.


Of course, the best way to make sure that signals in a logic block do not glitch is to not change the inputs to the logic. Of course, logic that is never used should not be included in the design, but when a block of logic is not used on a particular clock cycle, it may be simple to ensure that the inputs to that block are not changed unnecessarily. In some cases, eliminating unnecessary register loads can eliminate unnecessary changes to the inputs. In other cases, logic gates at the start of the logic block can be used to stop the propagation of logic signals based on a disable signal.

## 4.6 Switch Logic Networks

### *switches as Boolean operators*

We have used MOS transistors to build logic gates, which we use to construct combinational logic functions. But MOS transistors are good switches—a switch being a device that makes or breaks an electrical connection—and switches can themselves be used to directly implement Boolean function [Sha38]. Switch logic isn't universally useful: large switch circuits are slow and switches introduce hard-to-trace electrical problems; and the lack of drive current presents particular problems when faced with the relatively high parasitics of deep-submicron processes. But building logic directly from switches can help save area and parasitics in some specialized cases.


**Figure 4-25** Boolean functions built from switches.

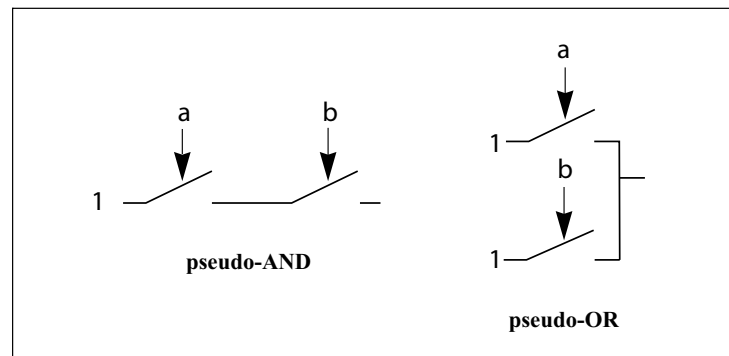

### *ANDs and ORs in switches*

Figure 4-25 shows how to build AND and OR functions from switches. The control inputs control the switches—a switch is closed when its control input is 1. The switch drains are connected to constants ( $V_{DD}$  or  $V_{SS}$ ). A pseudo-AND is computed by series switches: the output is logic 1 if and only if both inputs are 1. Similarly, a pseudo-OR is computed by parallel switches: the output is logic 1 if either input is 1. We call these functions *pseudo* because when none of the switches is turned on by the input variables, the output is not connected to any constant source and its value is not defined. As we will see shortly, this property causes havoc in real circuits with parasitic capacitance. Switch logic is not complete—we can compute AND and OR but we cannot invert an input signal. If, however, we supply both the true and complement forms of the input variables, we can compute any function of the variables by combining true and complement forms with AND and OR switch networks.

**Figure 4-26** A switch network with non-constant source inputs.

 


*variables as inputs*

We can reduce the size of a switch network by applying some of the input variables to the switches' gate inputs. The network of Figure 4-26, for example, computes the function  $ab' + a'b$  using two switches by using one variable to select another. This network's output is also defined for all input combinations. Switch networks that apply the inputs to both the switch gate and drain are especially useful because some functions can be computed with a very small number of switches.
 
### Example 4-6 Switch implementation of a multiplexer


We want to design a multiplexer (commonly called a mux) with four data inputs and four select inputs—the two select bits  $s_1$ ,  $s_0$  and their complements are all fed into the switch network. The network's structure is simple:



In practice, the number of select lines limits the useful size of the multiplexer.


#### *delay of switches*

Computing delay through a switch network is similar to computing pullup or pulldown delay through a logic gate—the switch transistor is in series with the pullup or pulldown network. However, the resistive approximation to the transistor becomes less accurate as more transistors are placed in series. For accurate delay analysis, you should perform a more accurate circuit or timing simulation. Switch networks with long paths from input to output may be slow. Just as no more than four transistors should be in series in a logic gate, switch logic should contain no paths with more than four switches for minimum delay (though long chains of pass transistors may be useful in some situations, as in the Manchester carry chain of Section 6.3).

 **Figure 4-27** Charge sharing.*charge sharing*

The most insidious electrical problem in switch networks is **charge sharing**. Switches built from MOS transistors have parasitic capacitances at their sources and drains thanks to the source/drain diffusion; capacitance can be added by wires between switches. While this capacitance is too small to be of much use (such as building a memory element), it is enough to cause trouble.

Consider the circuit of Figure 4-27. Initially,  $a = b = c = i = 1$  and the output  $o$  is driven to 1. Now set  $a = b = c = i = 0$ —the output remains one, at least until substrate resistance drains the parasitic capacitance, because the parasitic capacitance at the output stores the value. The network's output should be undefined, but instead it gives us an erroneous 1.

 **Figure 4-28** Charge division across a switch.

When we look at the network's behavior over several cycles, we see that much worse things can happen. As shown in Figure 4-28, when a switch connects two capacitors not driven by the power supply, current flows to place the same voltage across the two capacitors. The final amounts of charge depend on the ratio of the capacitances. **Charge division** can produce arbitrary voltages on intermediate nodes. These bad logic values can be propagated to the output of the switch network and wreak havoc on the logic connected there. Consider the value of each input and

of the parasitic capacitance between each pair of switches/terminals over time:

time	i	$C_{ia}$	a	$C_{ab}$	b	$C_{bc}$	c	$C_{co}$
0	1	1	1	1	1	1	1	1
1	0	0	1	0	0	1	0	1
2	0	0	0	1/2	1	1/2	0	1
3	0	0	0	1/2	0	3/4	1	3/4
4	0	0	1	0	0	3/4	0	3/4
5	0	0	0	3/8	1	3/8	0	3/4

The switches can shuttle charge back and forth through the network, creating arbitrary voltages, before presenting the corrupted value to the network's output. Charge sharing can be easily avoided—design the switch network so that its output is always driven by a power supply. There must be a path from  $V_{DD}$  or  $V_{SS}$  through some set of switches to the output for every possible combination of inputs. Since charge can be divided only between undriven capacitors, always driving the output capacitance ensures that it receives a valid logic value.

The severity of charge sharing suggests that strong measures be used to ensure the correct behavior of switch logic networks. One way to improve the reliability of transmission gates is to insert buffers before and after them.

## 4.7 Combinational Logic Testing

---

Once we have designed our logic, we must develop tests to allow manufacturing to separate faulty chips from good ones. A **fault** is a manifestation of a manufacturing defect; faults may be caused by mechanisms ranging from crystalline dislocations to lithography errors to bad etching of vias. In this section, we will introduce some techniques for testing logic networks and discuss how they relate to the actual yield of working chips.

---



---

### 4.7.1 Gate Testing

*fault models*

Testing a logic gate requires a **fault model**. The simplest fault model considers the entire logic gate as one unit; more sophisticated models consider the effects of faults in individual transistors in the gate.

*stuck-at-0/1 model*

The most common fault model is the **stuck-at-0/1** model. Under this model, the output of a faulty logic gate is 0 (or 1), independent of the value of its inputs. The fault does not depend on the logic function the gate computes, so any type of gate can exhibit a stuck-at-0 (S-A-0) or stuck-at-1 (S-A-1) fault. Detecting a S-A-0 fault simply requires applying a set of inputs that sets a fault-free gate’s output to 1, then examining the output to see if it has the true or faulty value.

a	b	fault-free	S-A-0	S-A-1
0	0	1	0	1
0	1	1	0	1
1	0	1	0	1
1	1	0	0	1

**NAND**

a	b	fault-free	S-A-0	S-A-1
0	0	1	0	1
0	1	0	0	1
1	0	0	0	1
1	1	0	0	1

**NOR**


**Figure 4-29** True and faulty behavior for stuck-at-0/1 faults.

*testing difficulty*

Figure 4-29 compares the proper behavior of two-input NAND and NOR gates with their stuck-at-0 and stuck-at-1 behavior. While the output value of a gate stuck at 0 isn’t hard to figure out, it is instructive to compare the difficulty of testing for S-A-0 and S-A-1 faults for each type of gate. A NAND gate has three input combinations which set a fault-free gate’s output to 1; that gives three ways to test for a stuck-at-0 fault. There is only one way to test for stuck-at-1—set both inputs to 0. Similarly, there are three tests for stuck-at-1 for a NOR gate, but only one stuck-at-0 test.

The number of input combinations that can test for a fault becomes important when gates are connected together. Consider testing the logic network of Figure 4-30 for stuck-at-0 and stuck-at-1 faults in the two NAND gates, assuming, for the moment, that the inverter is not faulty. We can test both NAND gates for stuck-at-0 faults simultaneously, using, for example, **abc = 011**. (A set of values simultaneously applied

**Figure 4-30** A simple logic network that requires two tests.

 

to the inputs of a logic network is called a **vector**.) However, there is no way to test both NAND gates simultaneously for stuck-at-1 faults: the test requires that both NAND gate inputs are 1, and the inverter assures that only one of the NAND gates can receive a 1 from the  $b$  input at a time. Testing both gates requires two vectors:  $abc = 00-$  (where  $-$  means the input's value is a don't-care, so that doesn't matter) and  $abc = -10$ .

#### *limitations of fault models*

The stuck-at-0/1 model for faults doesn't correspond well to real physical problems in CMOS fabrication. While a gate's output may be stuck at 0 by a short between the gate's output and  $V_{SS}$ , for example, that manufacturing error is unlikely to occur. The stuck-at-0/1 model is still used for CMOS because many faults from a variety of causes are exposed by testing vectors designed to catch stuck-at faults. The stuck-at model, however, does not predict all faults in a circuit; it is comforting to have a fault model that corresponds more closely to real processing errors.


#### *stuck-open model*

One such model is the **stuck-open** model [Gal80], which models faults in individual transistors rather than entire logic gates. A stuck-open fault at a transistor means that the transistor never conducts—it is an open circuit. As Figure 4-31 shows, a stuck-open transistor in a logic gate prevents the gate from pulling its output in one direction or the other, at least for some of its possible input values. If  $t_1$  is stuck open, the gate cannot pull its output to  $V_{DD}$  for any input combination that should force the gate's output to 1. In contrast, if  $t_2$  is stuck open, the gate can pull its output to  $V_{SS}$  when  $a = 1$  but not when  $b = 1$ .

This example also shows why reliably catching a stuck-open fault requires a *two cycle* test. If the gate's output is not driven to  $V_{DD}$  or  $V_{SS}$  due to a stuck-open fault, the gate's output value depends on the charge stored on the parasitic capacitance at its output. If we try setting  $b = 1$  to test for a stuck-open fault at  $t_2$ , for example, if the last set of inputs



**Figure 4-31** A circuit model for stuck-open faults.

 

applied to the gate was  $ab = 01$ , the gate charged its output to logic 0; when  $b$  is set to 0 to test  $t_2$ , the output will remain at 0, and we can't tell if the gate's output is due to a fault or not. Testing the stuck-open fault at  $t_2$  requires setting the logic gate's output to one value with one vector, then testing with another vector whether the gate's output changes. In this case, we must first apply  $ab = 00$  to set the gate's output to 1; then, when we apply  $ab = 01$ , the gate's output will be pulled down to 0 if  $t_2$  is not faulty but will remain at 1 if  $t_2$  is stuck open.

#### *delay fault model*

Both stuck-at and stuck-open faults check for function. We can also treat delay problems as faults: a **delay fault** [Lin87] occurs when the delay along a path falls outside specified limits. (Depending on the circuit, too-short paths may cause failures as well as too-long paths.) Delay faults can be modeled in either of two ways: a **gate delay fault** assumes that all the delay errors are lumped at one gate along the path; a **path delay fault** is the result of accumulation of delay errors along the entire path. Detecting either type of fault usually requires a large number of tests due to the many paths through the logic. However, since delay faults reduce yield, good testing of delay faults is important. If delay faults are not adequately caught in the factory, the bad chips end up in customers' hands, who discover the problems when they plug the chips into their systems.


### 4.7.2 Combinational Network Testing

*controllability and observability*

Just as network delay is harder to compute than the delay through an individual gate, testing a logic gate in a network is harder than testing it in isolation. Testing a gate inside a combinational network requires exercising the gate in place, without direct access to its inputs and outputs. The problem can be split into two parts:

- **Controlling** the gate's inputs by applying values to the network's primary inputs.
- **Observing** the gate's output by inferring its value from the values at the network's primary outputs.

**Figure 4-32**  
Testing for combinational faults.

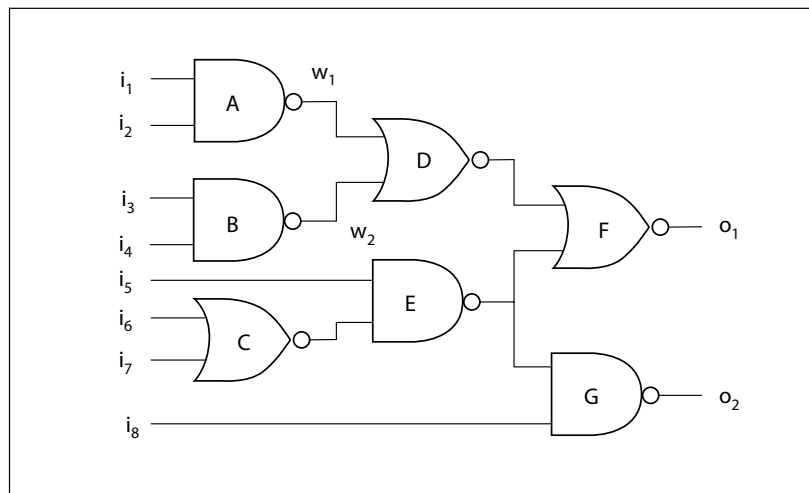

*justifying values*

Consider testing gate D in Figure 4-32 for a stuck-at-0 fault. The first job is to control D's inputs to set both to 0, also called **justifying** 0 values on the inputs. We can justify the required values by working backward from the pins to the primary inputs. To set wire w1 to 0, we need to make gate A's output 0, which we can do by setting both its inputs to 1. Since those wires are connected to primary inputs, we have succeeded in justifying w1's value. The other required 0 can be similarly controlled through B.

*observing values*


The second job is to set up conditions that let us observe the fault at the primary outputs—one or more of the primary outputs should have different values if D is stuck-at 0. Observing the fault requires both working forward and backward through the network. D's faulty behavior can be observed only through F—we need to find some combination of input values to F that gives one output value when D is 1 or 0. Setting

F's other input to 0 has the desired result: if D's output is good, the input combination 10 results in a 0 at F's output; if D is faulty, the 00 inputs give a 1 at the output. Since F is connected to a primary output, we don't have to propagate any farther, but we do have to find primary input values that make F's other input 0. Justification tells us that  $i_5 = 1, i_6 = 0, i_7 = 0$  provides the required value;  $i_8$ 's value doesn't matter for this test. Many tests may have more than one possible sequence. Testing D for stuck-at-1 is relatively easy, since three input combinations form a test. Some tests may also be combined into a single vector, such as tests for F and G.

*test generation is hard*

Finding a test for a combinational fault is NP-complete [Gar79]—finding the test will, in the worst case, require checking every possible input combination. However, much random logic is relatively easy to test, and many harder-to-test structures have well-known tests. In practice, programs do a relatively good job of generating combinational test patterns.

**Figure 4-33** Combinational fault masking.

 

Not all faults in a combinational network can be tested. In Figure 4-33, testing the NOR gate for stuck-at-0 requires setting both its inputs to 0, but the NAND gate ensures that one of the NOR's inputs will always be 1. Observing the NAND gate's stuck-at-0 fault requires setting the other input of the NOR gate to 0, but that doesn't allow the NAND gate's fault to be exercised. In both cases, the logic is untestable because it is redundant. Simplifying the logic gives:

$$\begin{aligned}
 f &= [\overline{ab + \bar{b}}] \\
 &= [\bar{a} + \bar{b} + b] \\
 &= 0
 \end{aligned}$$

The entire network could be replaced by a connection to  $V_{SS}$ . Any irredundant logic network can be completely tested. While it may seem dumb to introduce redundancies in a network—they make the logic larger and slower as well as less testable—it often isn't easy to recognize redundancies.

### 4.7.3 Testing and Yield

#### *testing goals*

It is worth considering our goals for testing. Can we ensure that the chips coming off the manufacturing line are totally defect-free? No—it is impossible to predict all the ways a chip can fail, let alone test for them all. A somewhat more realistic goal is to choose one or several fault models, such as the stuck-at-0/1 model, and test for all possible modeled faults. Even this goal is hard to achieve because it considers multiple faults. An even more modest goal is to test for all *single faults*—assume that only one gate is faulty at any time. Single-fault coverage for stuck-at-0/1 faults is the most common test; many multiple faults are discovered by single-fault testing, since many of the fault combinations are independent.

#### *testing and yield*

The simulation vectors used for design verification typically cover about 80% of the single-stuck-at-0/1 faults in a system. While it may be tempting to leave it at that, 80% fault coverage lets an unacceptable number of bad parts slip into customers' hands. Williams and Brown [Wil81] analyzed the field reject rate as a function of the yield of the manufacturing process (called  $Y$ ) and the coverage of manufacturing defects (called  $T$ ). They found, using simple assumptions about the distribution of manufacturing errors, that the percentage of defective parts allowed to slip into the customers' hands was

$$D = 1 - Y^{(1-T)} \quad (\text{EQ 4-25})$$

What does this equation mean in practice? Let's be generous for a moment and assume that testing for single stuck-at-0/1 covers all manufacturing defects. If we use our simulation vectors for testing, and our process has a yield of 50%, then the defect rate is 13%—that is, 13% of the chips that pass our tests are found by our customers to be bad. If we increase our fault coverage to 95%, the defect rate drops to 3.4%—better, but still unacceptably large. (How would you react if 3.4% of all the quarts of milk you bought in the grocery store were spoiled?) If we increase the fault coverage to 99.9%, the defect rate drops to 0.07%, which is closer to the range we associate with high quality.

But, in fact, single stuck-at-0/1 testing is not sufficient to catch all faults. Even if we test for all the single stuck-at faults, we will still let defective chips slip through. So how much test coverage is sufficient? Testing folklore holds that covering 99-100% of the single stuck-at-0/1 faults results in low customer return rates, and that letting fault coverage slip significantly below 100% results in excessive defect rates.

## 4.8 References

---

Dogleg channel routing was introduced by Deutsch [Deu76]. Devadas *et al.* [Dev91] describe algorithms for eliminating false paths during combinational logic delay analysis. Lawrence Pillage and Lawrence Pileggi are two well-known researchers in interconnect analysis who are in fact the same person; Prof. Pileggi reverted to his family's traditional name. Algorithms for technology-independent performance optimization of combinational logic have been developed by Singh *et al.* [Sin88]. Jha and Kundu [Jha90] discuss CMOS testing methods in detail.


## 4.9 Problems

---


Use the parameters for the 180 nm process of Chapter 2 whenever process parameters are required, unless otherwise noted.


Q4-1. Compute the density of these channels. Vertically aligned pins are shown with dotted lines:

a)

 

b)

 

 

Q4-2. Design a hierarchical stick diagram in the style of Example 4-1 for each of these logic networks. Use the gate types as shown. Choose a placement in the layout and show all necessary wires.


- a)  $\text{NAND2}(a, \text{NOR3}(b, c, d))$ .
- b)  $\text{XOR}(\text{NAND2}(a, b), \text{NAND2}(\text{NOT}(c), d))$ .
- c)  $\text{AOI221}(a, \text{NAND2}(b, c), \text{NOR2}(d, e), f, g)$ .

Q4-3. For each of these logic networks, draw the logic diagram and find the critical path, assuming that the delay through all two-input gates is 2 and the delay through an inverter is 1.


- a)  $\text{NAND2}(\text{NAND2}(a, b), \text{NOT}(c))$ .
- b)  $\text{NAND2}(\text{NAND2}(a, \text{NOT}(b)), \text{NAND2}(c, d))$ .
- c)  $\text{NAND2}(\text{NAND2}(a, b), \text{NAND2}(c, d))$ .

Q4-4. Use logical effort to compute the delay through each logic network of Question Q4-3. Assume all transistors are of minimum size and each output drives a minimum-size inverter and  $P=1$ .

 
Q4-5. For each of these pin configurations, draw a spanning tree and a Steiner tree that connects the points.



b)

 


c)

 

Q4-6. For each of these channels, swap pins (interchange the positions of pairs but don't change the overall locations of pins) to reduce crosstalk.


a)

 


4.9 Problems

265

b)

 

c)

 


Q4-7. Design a switch logic network for the function  $f = a'b + c$  using two different styles:

- a) Constant inputs.
- b) Non-constant inputs.


Q4-8. How many tests are required to fully test for S-A-0 faults for a network with 8 primary inputs?

Q4-9. Give the values for the primary inputs that allow each of the identified faults in these networks to be tested one at a time:

a)

 



 

Q4-10. Draw a simple logic network with an untestable fault.

---



---

# 5

# Sequential Machines


## Highlights:

Latches and flip-flops.

Clocking structures and timing disciplines.

Sequential system design.

Verification and testing of FSMs.

 

Model system for clock skew in flip-flop based machines (Figure 5-34).

---

## 5.1 Introduction

---

A **sequential machine** is a machine for which the output values depend not only on the present input values but also the history of previous inputs. The sequential machine's memory lets us build much more sophisticated functions; it also complicates design, validation, and testing.

In this chapter we will learn the design methods common to all sequential systems. Section 5.2 introduces the memory elements that we add to combinational logic to build sequential machines. Section 5.3 describes our basic model of synchronous sequential machines. Section 5.4 discusses how to determine the speed at which a sequential machine will run. Section 5.5 discusses how to generate a clock that drives a sequential machine. Section 5.6 surveys methods for optimizing and implementing sequential machines. Section 5.10 talks about how to optimize a sequential machine's power consumption. Section 5.8 introduces methods for verifying a sequential machine's design. Section 5.9 describes the challenges of testing sequential machines.

---

## 5.2 Latches and Flip-Flops

---

Latches and flip-flops are the circuits that we use to add memory to a sequential machine. In this section, we will determine the characteristics we desire in a latch or flip-flop and introduce some circuits for these functions. We will start with a brief introduction to timing diagrams, which we use to describe the operation of latches and flip-flops.

### 5.2.1 Timing Diagrams


*timing diagrams*

Logic behavior is sometimes specified as **timing diagrams**. An example timing diagram is shown in Figure 5-1. The system described by this diagram shows communication from *d* to *c* to signal followed by a response from *c* back to *d*. The *d* line is specified as either **unknown**, **changing**, or **stable**: the unknown value is the horizontal line through the signal value; the changing value are the diamond-shaped points and the stable value is shown as a pair of low and high horizontal lines. The data line can take on different values; unlike the control signal, we do not want to tie the timing specification to a given data value. An

---

---

**Figure 5-1** A simple timing diagram.

 

unknown value indicates that the data value on the wire is not useful, perhaps because no component on the wire is driving the data lines. A changing value indicates a transition between unknown and stable states.

Figure 5-1 also shows timing constraints between the  $d$  and  $c$  signals. The head and tail of the arrow tell us what is constrained while the label tells us the value of the timing constraint. The arrow represents an inequality relating the times of events on the  $d$  and  $c$  signals. If we denote the time of  $d$  becoming stable as  $t_d$  and the time of  $c$  rising to 1 as  $t_c$ , then the arrow tells us that

$$t_c \geq t_d + t_1. \quad (\text{EQ 5-1})$$

## 5.2.2 Categories of Memory Elements

### *memory elements*

Building a sequential machine requires **memory elements** that read a value, save it for some time, and then can write that stored value somewhere else, even if the element's input value has subsequently changed. A Boolean logic gate can compute values, but its output value will change shortly after its input changes. Each alternative circuit used as a memory element has its own advantages and disadvantages.

A generic memory element has an internal memory and some circuitry to control access to the internal memory. In CMOS circuits, the memory is formed by some kind of capacitance or by positive feedback of energy from the power supply. Access to the internal memory is controlled by

## 5.2 Latches and Flip-Flops

271

*memory element characteristics*

the *clock* input—the memory element reads its **data** input value when instructed by the clock and stores that value in its memory. The output reflects the stored value, probably after some delay.

Different types of memory elements differ in many key respects:

- exactly what form of clock signal causes the input data value to be read;
- how the behavior of *data* around the read signal from *clock* affects the stored value;
- when the stored value is presented to the output;
- whether there is ever a combinational path from the input to the output.

Introducing a terminology for memory elements requires caution—many terms are used in slightly or grossly different ways by different people. We choose to follow Dietmeyer’s convention [Die78] by dividing memory elements into two major types:


- **Latches** are transparent while the internal memory is being set from the data input—the (possibly changing) input value is transmitted to the output.
- **Flip-flops** are not transparent—reading the input value and changing the flip-flop’s output are two separate events.

Within these types, many subclasses exist. But the latch vs. flip-flop dichotomy is most important because, as we will see in Section 5.3, the decision to use latches or flip-flops dictates substantial differences in the structure of the sequential machine.

Memory elements can also be categorized along another dimension, namely the types of data inputs they present.

- The most common data input type in VLSI design is the **D-type** memory element. Think of “D” as standing for data—the Q output of the memory element is determined by the D input value at the clocking event.
  - The **T-type** memory element toggles its state when the T input is set at the clocking event.
  - The **SR-type** memory element is either set by the S input or reset by the R input (the S and R inputs are not allowed to be 1 simultaneously).
  - The **JK-type** is similar but its J and K inputs can both be 1. The other memory element types can be built using the JK-type as a component.
- 
-

**Figure 5-2** Setup and hold times.

 


*timing parameters*

The two most commonly quoted parameters of a memory element are its **setup time** and **hold time**, which define the relationship between the clock and input data signals. The data value to be latched must remain stable around the time the clock signal changes value to ensure that the memory element retains the proper value. In Figure 5-2, the memory element stores the input value around the clock's falling edge. The setup time is the minimum time the data input must be stable before the clock signal changes, while the hold time is the minimum time the data must remain stable after the clock changes. The setup and hold times, along with the delay times through the combinational logic, determine how fast the system can run. The **duty cycle** of a clock signal is the fraction of the clock period for which the clock is active.

### 5.2.3 Latches

**Figure 5-3** A dynamic latch circuit.

 

*dynamic latch*

The simplest memory element in MOS technology is the **dynamic latch** shown in Figure 5-3. It is called dynamic because the memory value is not refreshed by the power supply and a latch because its output follows its input under some conditions. The latch is a D-type, so its input is D and its output is Q'. The inverter connected to the output should be familiar. The **storage capacitance** has been shown in dotted lines since

it is a parasitic component; this capacitance has been named  $C_g$  since most of the capacitance comes from the gates of the transistors in the inverter.

The latch capacitance is guarded by a fully complementary transmission gate. Dynamic latches generally use p-n pair switches because they transmit logic 0 and 1 equally well and provide better storage on the capacitor. (The inverter requires both p- and n-type transistors, so the area savings from an n-type transmission gate would be small.) The transmission gate is controlled by two clock signals,  $\phi$  and  $\phi'$ —a complementary switch requires both true and false forms of the control signal.


#### *latch operation*

The latch's operation is straightforward. When the transmission gate is closed, whatever logic gate is connected to the D input is allowed to charge or discharge  $C_g$ . As the voltage on  $C_g$  changes,  $Q'$  follows in complement—as  $C_g$  goes to low voltages,  $Q'$  follows to high voltages, and *vice versa*. When the transmission gate opens,  $C_g$  is disconnected from any logic gate that could change its value. Therefore, the value of the latch's output  $Q'$  depends on the voltage of the storage capacitor: if the capacitor has been discharged, the latch's output will be a logic 1; if the storage capacitor has been charged, the latch's output will be a 0. Note that the value of  $Q'$  is the logical complement of the value presented to the latch at D; we must take this inversion into account when using the latch. To change the value stored in the latch, we can close the transmission gate by setting  $\phi = 1$  and  $\phi' = 0$  and change the voltage on  $C_g$ .

When operating the latch, we must be sure that the final voltage stored on  $C_g$  is high enough or low enough to produce a valid logic 1 or 0 voltage at the latch's output. The storage capacitance adds delay, just as does any other parasitic capacitance; we must be sure that the logic gate connected to the latch's input has time to drive  $C_g$  to its final value before  $\phi$  is set to 0 and the latch is closed. This latch does not keep its value forever. Parasitic resistances on the chip conspire to leak away the charge stored in the capacitor. A latch's value can usually be maintained for about a millisecond ( $10^{-3}$  s). Since gate delays range in the picoseconds ( $10^{-12}$  s), however, memory degradation doesn't present a significant problem, so long as the clock ticks regularly. The memory's value is restored when a new value is written to the latch, and we generally want to write a new value to the latch as quickly as possible to make maximum use of the chip's logic.



**Figure 5-4** A stick diagram of a dynamic latch.

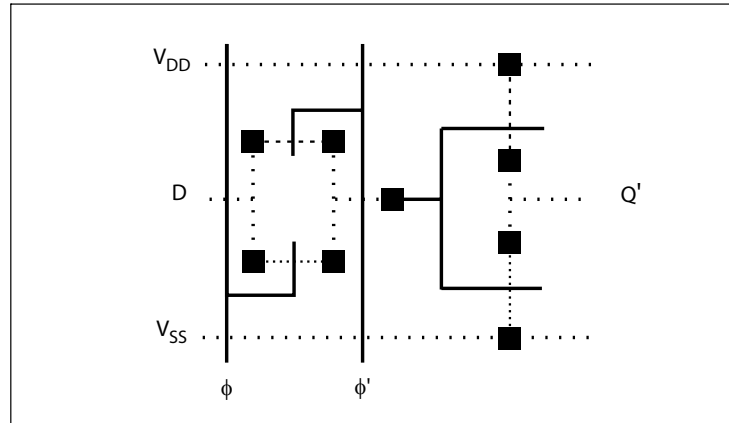

#### *dynamic latch layout*


Figure 5-4 shows one possible stick diagram for a dynamic latch. The familiar inverter is on the right-hand side of the cell and the transmission gate is on the left. Figure 5-5 shows a layout of the latch. This latch's setup time is determined by the time required to charge the storage capacitance. The hold time is dominated by the time required to turn off the transistors in the transmission gate.

#### *multiplexed latch*

We should consider one simple but useful extension of the basic dynamic latch, the **multiplexed latch** shown in Figure 5-6. This latch has two data inputs,  $D1$  and  $D2$ ; the control signals  $A$  and  $B$  (and their complements) control which value is loaded into the latch;  $A$  and  $B$  should be the AND of the clock and some control signal. To ensure that a valid datum is written into the latch,  $A$  and  $B$  must never simultaneously be 1. This latch, which can be extended to more inputs, is useful because either of two different pieces of data may be loaded into a latch, depending on the value of an independently computed condition.

#### *quasi-static latch*

The dynamic latch has a small layout, but the value stored on the capacitor leaks away over time. The **recirculating latch** eliminates this problem by supplying current to constantly refresh the stored value. A recirculating latch design is shown in Figure 5-7. This latch is called **quasi-static** because the latched data will vanish if the clocks are stopped, but as long as the clocks are running, the data will be recirculated and refreshed. The latch is also said to be **static on one phase** because the stored data will be saved so long as the clock controlling the feedback connection remains high. During  $\phi_1$ , if the latch is to be loaded with a new value,  $LD$  is set to 1, turning on the transmission gate and changing the value stored on the first inverter's gate capacitance. During

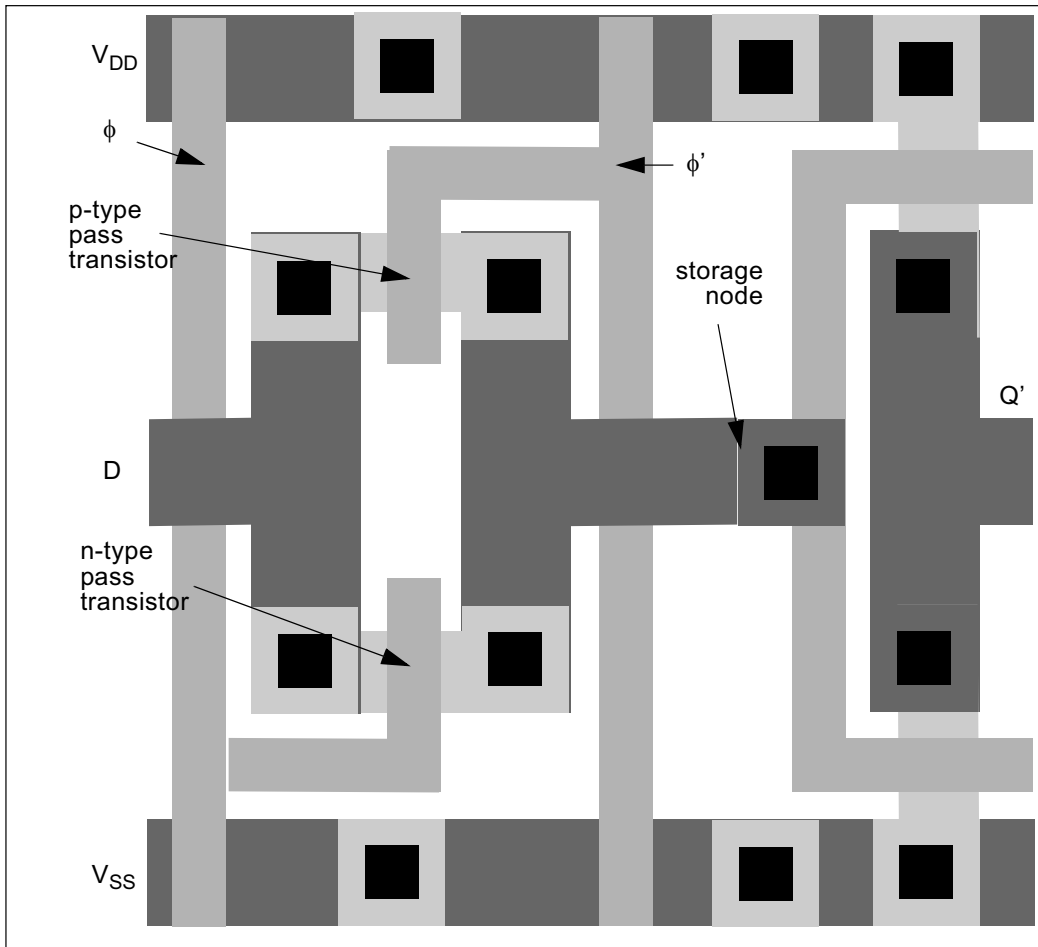


**Figure 5-5** A layout of a dynamic latch.

$\phi_2$ , the two inverters are connected in a cycle; since there is an even number of inverters in the cycle, their values reinforce each other. So long as the  $\phi_2$  clock ticks, the latch will be repeatedly refreshed.


*latches and charge sharing*

This latch can suffer from charge sharing when placed in a larger layout. The latch's value is stored on node A. When  $\phi_2$  is high, the storage node is connected to the latch's output; if the output node has a

**Figure 5-6** A multiplexed dynamic latch.

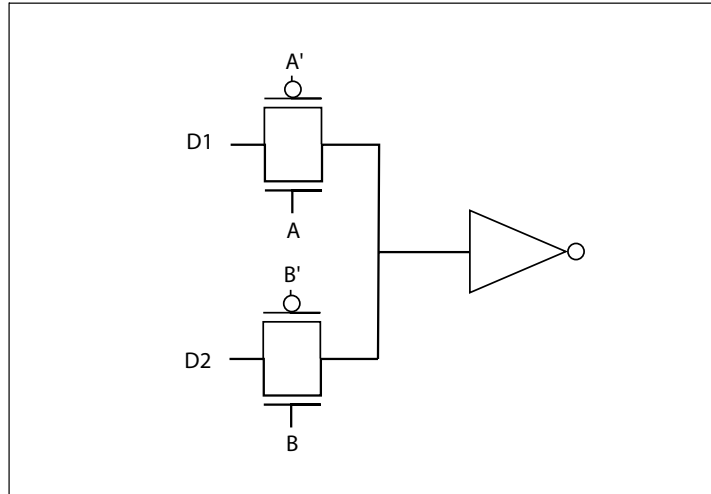

**Figure 5-7** A recirculating quasi-static latch.

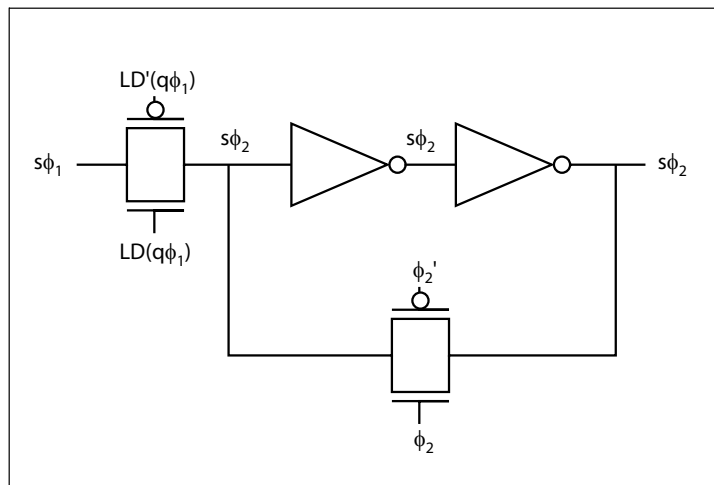


large capacitance, the charge stored there will redistribute itself to the storage node, destroying its value. Another way to look at this problem is that the output inverter won't be able to drive the large capacitance to its final value in the clock period, and the storage node's value will be destroyed as a side effect since it is connected to the output capacitance by the transmission gate. If you need to drive a large capacitance with this latch (for example, when the latch drives a long wire), you can add a

buffer to the output to present an insignificant capacitance to the latch's feedback loop.


*clocked inverter*

The **clocked inverter**, shown in Figure 5-8, lets us build more sophisticated latch circuits. As implied by its schematic symbol, the clocked inverter is controlled by its clock input  $\phi$ . When  $\phi = 1$ , both  $n1$  and  $p1$  are turned on and the circuit acts as a normal inverter. When  $\phi = 0$ , both transistors are turned off and the output is disconnected from the rest of the inverter circuit. The control transistors  $p1$  and  $n1$  are closest to the output to ensure that the output is disconnected as quickly as possible when  $\phi$  goes low. The clocked inverter is a clever way of combining transmission gate and logic gate functions into a single, compact circuit.

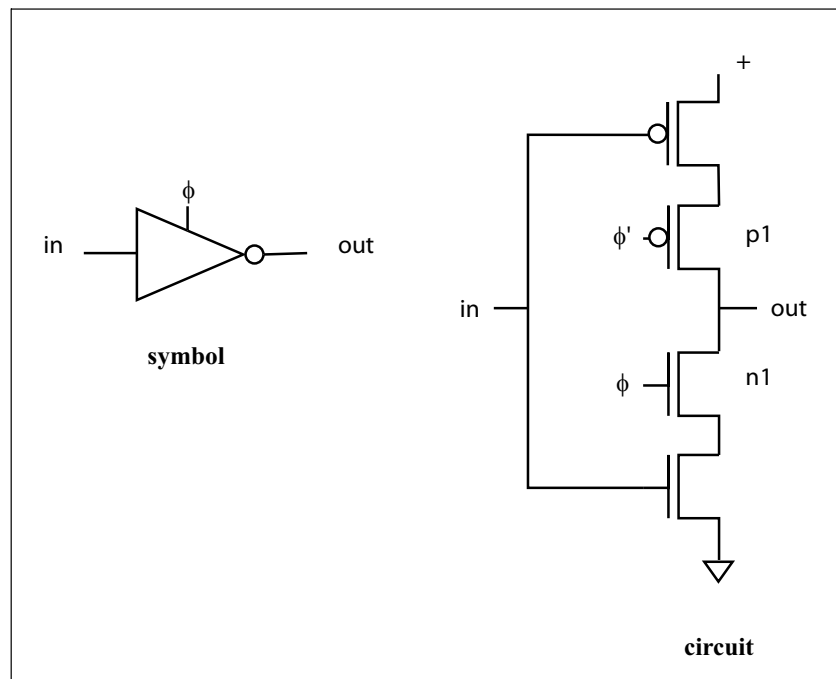

**Figure 5-8** A clocked inverter.


A latch circuit built from clocked inverters is shown in Figure 5-9. This latch takes a clock and its complement and has a non-inverting output. When  $\phi = 0$ ,  $\phi' = 1$  and the inverters  $i2$  and  $i3$  form a positive feedback loop that retains the latch's value. When  $\phi = 1$ ,  $i2$  is turned off, breaking the feedback loop, and  $i1$  is turned on to inject a new value into the loop.

 

**Figure 5-9** A D latch built from clocked inverters.

The hold time depends on the time required to turn off the clocked inverter. An alternative design uses a weak inverter rather than a clocked inverter for i2; if i1 is much stronger than i2, i1 can flip the state of the inverter pair when it is enabled.

**Figure 5-10** A regenerative latch.

 

*advanced latches*

Figure 5-10 shows a latch with feedback that was used in the DEC Alpha 21064 [Dob92]. Both stages of the latch use the clocked inverter structure in their pulldown networks. The two p-type transistors in the

latch's second stage form the feedback loop for the latch. When the latch value is set to 1 by a 0 value from the first stage while the clock is high, the output also turns off the upper p-type transistor, reinforcing the output value. If the first stage output goes to 1 and then subsequently to 0 without a clock event, the clocked inverter structure prevents the p-type feedback pair from flipping state.

Cells that require both true and complement forms of the clock usually generate  $CLK'$  internally. Such circuits often require close synchronization between the true and complement clocks, which is very difficult to achieve when the two are distributed from a distant driver. In many standard cells, the cell's clock input is connected to two inverters; this is largely a bookkeeping measure to ensure that the load presented to the clock signal by the cell is independent of the cell's internals. One inverter delivers  $CLK'$  while the other feeds another inverter to regenerate  $CLK$ . These two chains obviously don't have the same delay. One way to equalize their delays is to insert a transmission gate before the single-inverter to slow down that path. However, if the clock duty cycle and circuit are such that overlapping phases are a serious concern, circuit simulation with accurate parasitics may be warranted.

#### 5.2.4 Flip-Flops



*types of flip-flops*

There are two major types of flip-flops: **master-slave** and **edge-triggered**. The structure of a master-slave flip-flop is shown in Figure 5-11. It is built from two back-to-back latches called, naturally enough, the master and the slave. The master latch reads the data input when the clock is high. Meanwhile, the internal inverter assures that the slave latch's clock input is low, insulating the slave latch from changes in the master's output and leaving the flip-flop's output value stable. After the clock has gone low, the slave's clock input is high, making it transparent, but a stable value is presented to the slave by the master. When the clock moves back from 0 to 1, the slave will save its value before the master's output has a chance to change. An edge-triggered flip-flop uses additional circuitry to change the flip-flop's state only at a clock edge; a master-slave flip-flop, in contrast, is sensitive to the input as long as the clock remains active.

*D-type flip-flop*

Figure 5-12 shows a D-type master-slave flip-flop built from the D-type quasi-static latch. This circuit follows the basic structure shown in Figure 5-11, using the quasi-static latch structure for each of the component latches.

 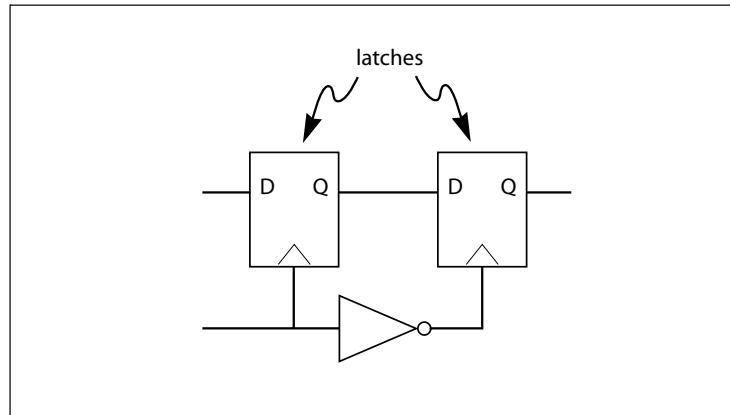**Figure 5-11** A master-slave flip-flop built from latches.

 


**Figure 5-12** A quasi-static D-type flip-flop.

### *SR flip-flop*

Figure 5-13 shows the circuit diagram for an SR-type clocked flip-flop [Rab96]. (The traditional SR-type flip-flop, built from cross-coupled NOR gates, does not have a clock input.) This circuit uses a pair of cross-coupled inverters to implement the storage nodes. The additional transistors flip the state according to the SR protocol. This flip-flop is fully static and consumes no quiescent power. It can be used as a building block for more complex flip-flops.

**Figure 5-13** An SR-type flip-flop.



### 5.3 Sequential Systems and Clocking Disciplines


It is now time to study large sequential systems built from combinational networks and memory elements. We need to understand how to build a sequential system that performs a desired function, paying special attention to the clocks that run the memory elements to ensure that improper values are never stored; we also need to understand how to build a testable sequential machine.

#### *FSM structure*

The structure of a generic sequential system—also known as a finite-state machine or FSM—is shown in Figure 5-14. Memory elements hold the machine's state; the machine's inputs and outputs are also called **primary inputs** and **primary outputs**. If the primary outputs are a function of both the primary inputs and state, the machine is known as a **Mealy machine**; if the primary outputs depend only on the state, the machine is called a **Moore machine**. A properly interconnected set of sequential systems is also a sequential system. It is often convenient to break a large system into a network of communicating machines: if decomposed properly, the system can be much easier to understand; it may also have a smaller layout and run faster.



**Figure 5-14** Structure of a generic sequential system.

 

### 5.3.1 Clocking Disciplines

#### *rules for FSM construction*

We need reliable rules that tell us when a circuit acts as a sequential machine—we can't afford to simulate the circuit thoroughly enough to catch the many subtle problems that can occur. A **clocking discipline** is a set of rules that tell us:

- how to construct a sequential system from gates and memory elements;
- how to constrain the behavior of the system inputs over time.

Adherence to the clocking discipline ensures that the system will work at *some* clock frequency. Making the system work at the required clock frequency requires additional analysis and optimization.

#### *signal types*

The constraints on system inputs are defined as **signal types**, which define both how signals behave over time and what signals can be combined in logic gates or memory elements. By following these rules, we can ensure that the system will operate properly at some rate; we can then worry about optimizing the system to run as fast as possible while still functioning correctly.

*clocking rules*

Different memory element types require different rules, so we will end up with a family of clocking disciplines. All disciplines have two common rules, however. The first is simple:

**Clocking rule 1:** *Combinational logic gates cannot be connected in a cycle.*

Gates connected in a cycle form a primitive memory element and cease to be combinational—the gates' outputs depend not only on the inputs to the cycle but the values running around the cycle. In fact, this rule is stronger than is absolutely necessary. It is possible to build a network of logic gates which has cycles but is still combinational—the values of its outputs depend only on the present input values, not past input values. However, careful analysis is required to ensure that a cyclic network is combinational, whereas cycles can be detected easily. For most practical circuits, the acyclic rule is not overly restrictive.

The second common rule is somewhat technical:

**Clocking rule 2:** *All components must have bounded delay.*

This rule is easily satisfied by standard components, but does rule out synchronizers for asynchronous signals.

### 5.3.2 One-Phase Systems for Flip-Flops

The clocking discipline for systems built from flip-flops is simplest, so let's consider that first. A flip-flop system looks very much like that of the generic sequential system, with a single rank of memory elements.


*conservative properties for signals*

We can define conditions that the clock and data signals must satisfy that are conservative but safe. A flip-flop system has one type of clock signal,  $\phi$ , and one type of data signal,  $S$ , as shown in Figure 5-15. The figure assumes that the flip-flops read their inputs on the positive (0→1) clock edge. The data inputs must have reached stable values at the flip-flop inputs on the rising clock edge, which gives this requirement on the primary inputs:

**Flip-flop clocking rule 1:** *All primary inputs can change only in an interval just after the clock edge. All primary inputs must become stable before the next clock edge.*

The length of the clock period is adjusted to allow all signals to propagate from the primary inputs to the flip-flops. If all the primary inputs

**Figure 5-15** Signal types in a flip-flop system.

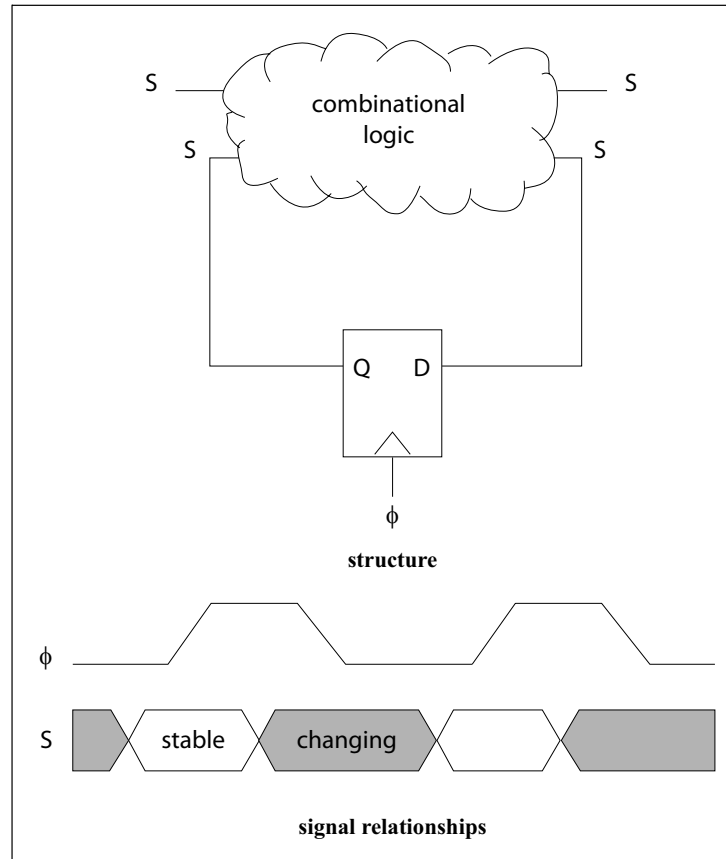

satisfy these conditions, the flip-flops will latch the proper next state values. The signals generated by the flip-flops satisfy the clocking discipline requirements.

### 5.3.3 Two-Phase Systems for Latches

*multiple ranks of latches*

A single rank of flip-flops cutting the system's combinational logic is sufficient to ensure that the proper values will be latched—a flip-flop can simultaneously send one value to its output and read a different value at its input. Sequential systems built from latches, however, are normally built from two ranks of latches. To understand why, consider the relationships of the delays through the system to the clock signal that controls the latches, as illustrated in Figure 5-16. The delay from the


present state input to the next state output is very short. As long as the latch's clock is high, the latch will be transparent. If the clock signal is held high long enough, the signal can make more than one loop around the system: the next state value can go through the latch, change the value on the present state input, and then cause the next state output to change.

*two-sided clocking constraints*

In such a system, the clock must be high long enough to securely latch the new value, but not so long that erroneous values can be stored. That restriction can be expressed as a **two-sided** constraint on the relative lengths of the combinational logic delays and the clock period:

- the latch must be open less than the shortest combinational delay;
- the period between latching operations must be longer than the longest combinational delay.

**Figure 5-16** Single latches may let data shoot through.

 

It is possible to meet two-sided constraint, but it is very difficult to make such a circuit work properly.

*strict two-phase system*


A safer architecture—the **strict two-phase** clocking discipline system—is shown in Figure 5-17. Each loop through the system is broken by two ranks of latches:

**Two-phase clocking rule 1:** *Every cycle through the logic must be broken by  $n \phi_1$  latches and  $n \phi_2$  latches.*

*non-overlapping clocks*

The latches are controlled by the **non-overlapping** clock phases shown in Figure 5-18. A  $\phi_1$ -high,  $\phi_2$ -high sequence forms a complete clock cycle. The non-overlapping clocks ensure that no signal can propagate

**Figure 5-17** The strict two-phase system.

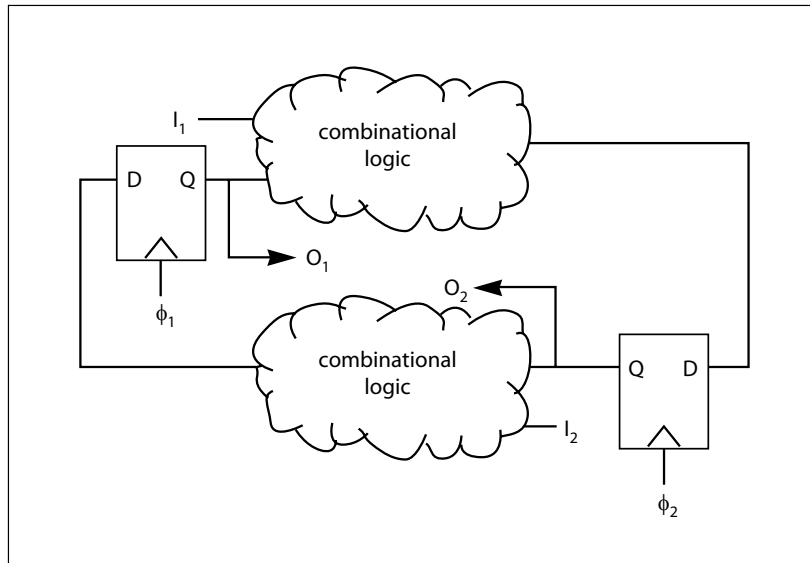


all the way from a latch's output back to its input. When  $\phi_1$  is high, the  $\phi_2$ -controlled latches are disabled; when  $\phi_2$  is high, the  $\phi_1$  latches are off.


*one-sided clocking constraints*

As a result, the delays through combinational logic and clocks in the strict two-phase system need satisfy only a **one-sided** timing constraint: each phase must be longer than the longest combinational delay through that phase's logic. A one-sided constraint is simple to satisfy—if the clocks are run slow enough, the phases will be longer than the maximum combinational delay and the system will work properly. (A chip built from dynamic latches that is run so slowly that the stored charge leaks away won't work, of course. But a chip with combinational logic delays over a millisecond wouldn't be very useful anyway.)

**Figure 5-18** A two-phase, non-overlapping clock.

 

It is easy to see that we can stretch the clock phases and inter-phase gaps to ensure that the strict two-phase system works. The inputs to the combinational logic block at the  $\phi_1$  latch outputs are guaranteed to have settled by the time  $\phi_1$  goes low; the outputs of that block must have settled by the time  $\phi_2$  goes low for the proper values to be stored in the  $\phi_2$  latches. Because the block is combinational there is an upper bound on the delay from settled inputs to settled outputs. If the time between the falling edges of  $\phi_1$  and  $\phi_2$  is made longer than that maximum delay, the correct state will always be read in time to be latched. A similar argument can be made for the  $\phi_1$  latches and logic attached to their outputs. Therefore, if the clock cycle is properly designed, the system will function properly.

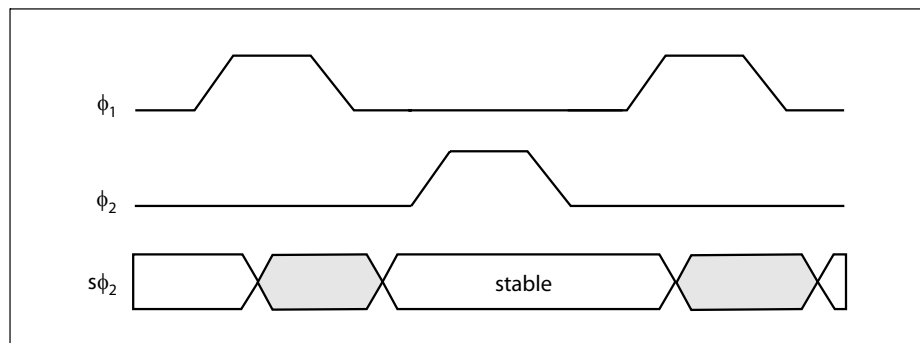

**Figure 5-19** A stable  $\phi_2$  signal.


#### *clock types*

The strict two-phase system has two clock types,  $\phi_1$  and  $\phi_2$ . Each clock type has its own data type [Noi82], the **stable** signal, which is equivalent to a **valid** signal on the opposite clock phase. Figure 5-19 shows the two clock phases and the output of a  $\phi_1$ -clocked latch. The latch output changes only during a portion of the  $\phi_1$  phase. It therefore meets the setup and hold requirements of the succeeding  $\phi_2$  latch once the clock phase durations are properly chosen. Because the signal's value is settled during the entire  $\phi_2$  portion of the clock cycle, it is called **stable**  $\phi_2$ , abbreviated as  $s\phi_2$ . The output of a  $\phi_2$ -clocked latch is stable  $\phi_1$ . A  $s\phi_2$  signal is also called **valid**  $\phi_1$ , abbreviated as  $v\phi_1$ , since it becomes valid around the time the  $\phi_1$  latch closes. Similarly, a signal that is stable during the entire  $\phi_1$  portion of the clock is known as **stable**  $\phi_1$  or  $s\phi_1$ .


*combinations of clocking types*

Figure 5-20 summarizes how clocking types combine. Combinational logic preserves signal type: if all the inputs to a gate are  $s\phi_1$  then its output is  $s\phi_1$ . Clocking types cannot be mixed in combinational logic: a gate cannot have both  $s\phi_1$  and  $s\phi_2$  inputs. The input to a  $\phi_1$ -controlled latch is  $s\phi_1$  and its output is  $s\phi_2$ .

**Figure 5-20**  
How strict two-phase clocking types combine.

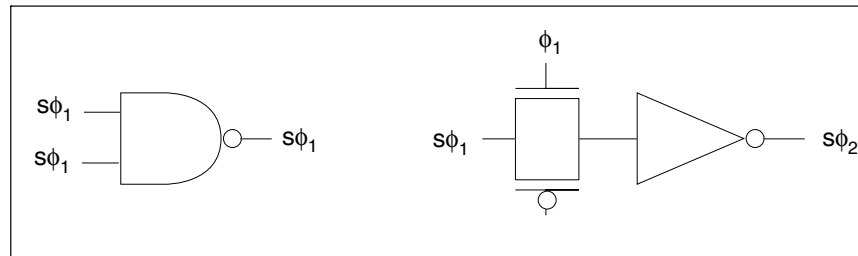

**Figure 5-21**  
Clocking types in the strict two-phase system.

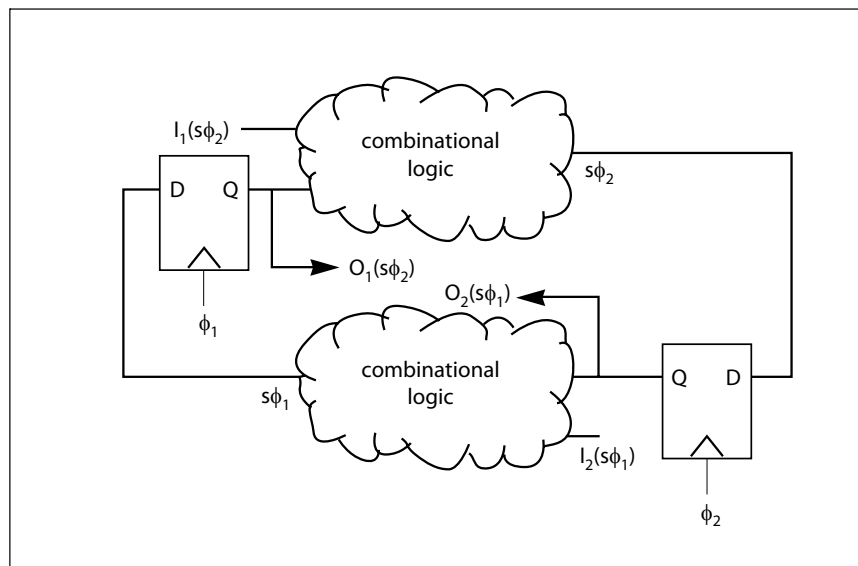

*signal types in an FSM*

Figure 5-21 shows how signal types are used in the strict two-phase system. The system can have inputs on either phase, but all inputs must be stable at the defined times. The system can also have outputs on either phase. When two strict two-phase systems are connected, the connected inputs and outputs must have identical clocking types. Assigning clocking types to signals in a system ensures that signals are properly com-

bined, but it will not guarantee that all loops are broken by both  $\phi_1$  and  $\phi_2$  latches.

*two-coloring*

This check can be performed by **two-coloring** the block diagram. To two-color a schematic, color  $\phi_1$  and all signals derived from it red, and all  $\phi_2$ -related signals green. For the system to satisfy the two-phase clocking discipline, the two-colored diagram must satisfy these rules:

- No latch may have an input and output signal of the same color.
- The latch input signal and clock signal must be of the same color.
- All signals to a combinational logic element must be of the same color.


The two-coloring check is a simple way to ensure that the rules of the clocking discipline are satisfied.

The next example builds a shift register from latches operated by a two-phase clock.
 
### Example 5-1 Shift register design

The simplest machine we can build with the dynamic latch is a **shift register**. An  $n$ -bit shift register has a one-bit input and a one-bit output; the value at the input on a clock cycle appears at the output  $n$  clock cycles later. We can save design time by building a single cell and replicating it to create the complete shift register. We will design a component that stores a value for one clock cycle, then connect together  $n$  copies of the component so the value is shifted from one to the next for  $n$  clock cycles.


The basic bit storage component is built from a pair of latches. The schematic for a two-bit shift register looks like this:



The stick diagram for a single shift register cell is identical to the dynamic latch cell, though we want to be sure that the input and output




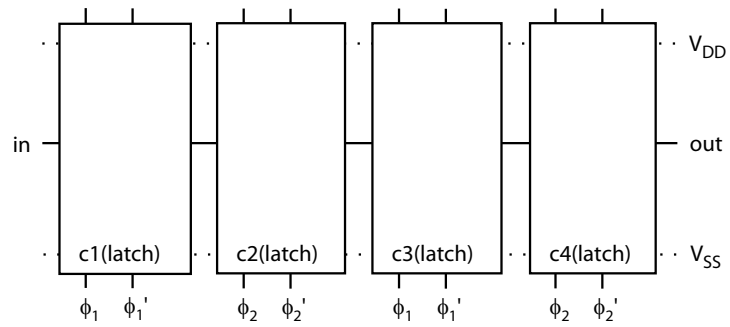
are both in poly so they can be directly connected. To build a shift register, we simply **tile** or **abut** the cells to make a linear array:



This arrangement gives us a large number of clock phase lines through the cell. Eventually, the  $\phi_1$ s will be connected together, etc. Exactly how we do that depends on the design of the other components around this shift register.

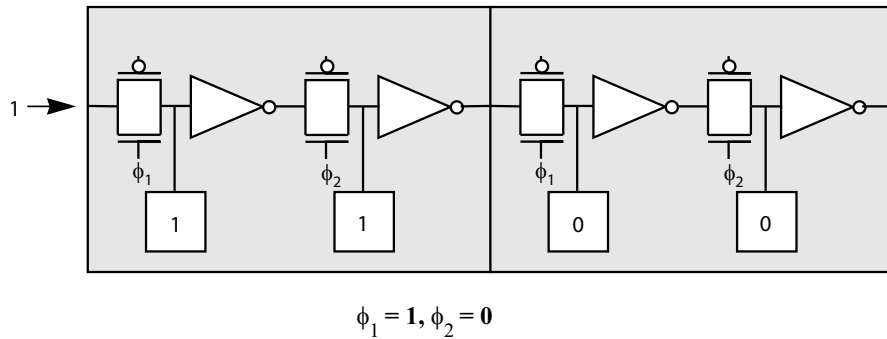The shift register's operation over one cycle looks like this:



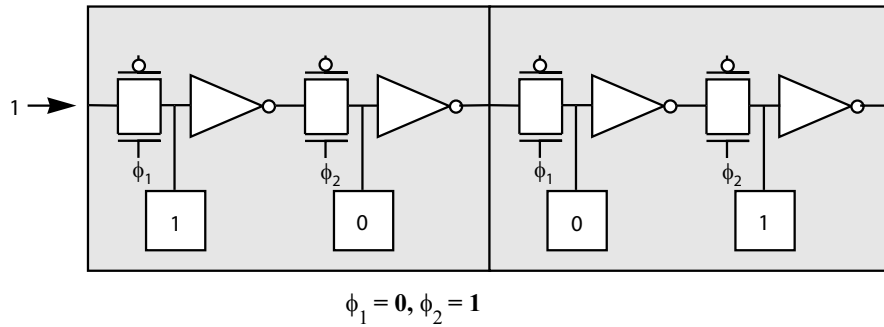

In the first phase, when  $\phi_1 = 1$ , the first latch in each bit is loaded with the value input to that bit. In the second phase, when  $\phi_2 = 1$ , that value is transferred to the second bit in the latch. So after one cycle of operation, the bit that appeared at the output of the first bit has been transferred to the output of the second and last bit of the shift register.


*qualified clock*

The multiplexed latch of Figure 5-6 needs a new type of control signal, the **qualified clock**. In the strict two-phase system there are two qualified clock types, qualified  $\phi_1$  ( $q\phi_1$ ) and qualified  $\phi_2$  ( $q\phi_2$ ). Qualified clocks may be substituted for clocks at latches. Since a static latch controlled by a qualified clock is no longer refreshed on every clock cycle, the designer is responsible for ensuring that the latch is reloaded often enough to refresh the storage node and to ensure that at most one transmission gate is on at a time. Qualified clocks are generated from the logical AND of a stable signal and a clock signal. For instance, a  $q\phi_1$  signal is generated from a  $s\phi_1$  signal and the  $\phi_1$  clock phase. When the clock is run slowly enough, the resulting signal will be a stable 0 or 1 through the entire  $\phi_1$  period.

*clocking types and quasi-static latches*


The quasi-static latch of Figure 5-7 does not satisfy the strict clocking discipline. First, it requires qualified clocks to operate; second, its feedback loop makes the type of its output problematic. If the clocking types shown in Figure 5-22 are used, the latch will operate properly in a strict two-phase system. The latch itself works even though it does not internally obey the clocking discipline—synchronous machine design hides many circuit difficulties in the memory elements.

**Figure 5-22**  
Clocking types  
in the  
recirculating  
latch.

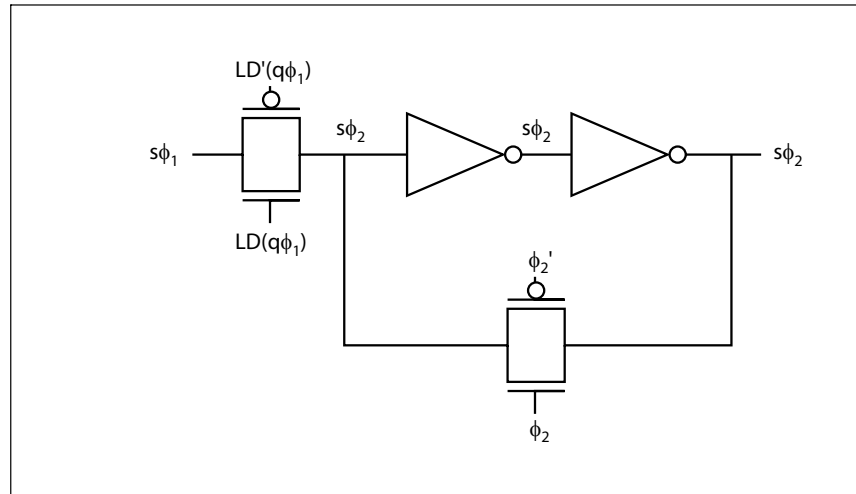

### 5.4 Performance Analysis

Clocking disciplines help us construct systems that will operate at some speed. However, we usually want the system to run at some minimum clock rate. We saw in Section 4.3 how to determine the delays through combinational logic. We need additional analysis to ensure that the machine will run at the clock rate we want.

 

**Figure 5-23** A sequential system with unbalanced delays.

*logic delays*

The desired clock period determines the maximum allowable delays through the combinational logic. Because most machines are built from several blocks of combinational logic and the clock period is determined by the *longest* combinational delay, the worst-case delay through the system may not be obvious when you look at the component blocks of


	<p>combinational logic in isolation. Consider the system of Figure 5-23: one path from flip-flop to flip-flop has one adder while the other has two. The system's clock period will be limited by the two-adder path. In some cases, the result of a long path is not used every cycle—for example, the flip-flop may be conditionally loaded. The system's clock period is still limited by the delay through this occasionally used path, since we can't predict the cycles on which that path will be used.</p>
<i>register characteristics</i>	<p>Our analysis must also take into account the timing characteristics of the registers used in the design. We have already seen that latch-based systems have more complicated timing relationships even when we consider only correctness; determining the clock rate of a latch-based system is also somewhat harder.</p>
<i>skew</i>	<p>Finally, we must consider the effects of <b>clock skew</b>. One of the basic assumptions of sequential machine design is that the clock is ideal—the clock arrives instantaneously at all points in the design. That assumption doesn't hold for systems of any reasonable size. Clock skew is the relative delay between the arrival of the clock signal at different physical points in the system. We can factor skew into our performance analysis and understand how it limits clock rate; this analysis helps us determine what parts of our system are most sensitive to clock skew.</p>
<i>retiming</i>	<p>In many cases, we have freedom in where we place memory elements. We will look at retiming, an algorithm for optimally placing memory elements, in Section 5.4.4.</p>
<i>reliability</i>	<p>Reliability is partially determined by performance concerns in sequential systems. A variety of physical causes can result in transient errors, many of which are due to timing problems. We will briefly look at some techniques for detecting and correcting errors in Section 5.4.5.</p>

### 5.4.1 Performance of Flip-Flop-Based Systems

To start our analysis of machines with flip-flops, let us make some semi-ideal assumptions:

- The clock signal is perfect, with no rise or fall times and no skew. The clock period is  $P$ .
  - We will assume for simplicity that the flip-flops store new values on the rising clock edge.
  - The flip-flops have setup time  $s$  and propagation time  $p$ .
  - The worst-case delay through the combinational logic is  $C$ .
- 
-

**Figure 5-24** Model system for performance analysis of flip-flop-based machines.

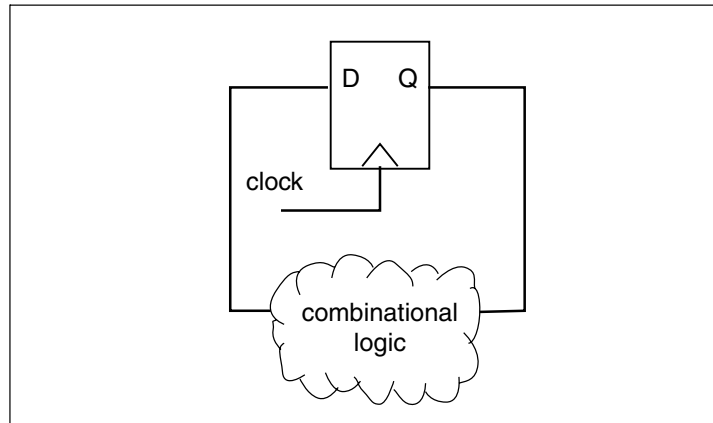

The structure of our sequential machine is shown in Figure 5-24. This is a very generic structure that describes machines with multiple flip-flops and as many combinational logic blocks as necessary.

**Figure 5-25** Timing of the semi-ideal flip-flop-based system.

 


Figure 5-25 shows how the various delays through the system fall into the clock period. The physical parameters of the combinational logic and flip-flops contribute to overall delay:

- The flip-flop's propagation time ( $p$ ) determines how long it takes for the new value to move from the flip-flop's input to its output.

- Once the new value reaches the flip-flop's data output, the new values start to propagate through the combinational logic. They require  $C$  time to compute the results.
- The results must arrive at the flip-flop one setup time ( $s$ ) before the next rising clock edge.


*clock period*

We can therefore write our constraint on the clock period as

$$P \geq C + s + p. \quad (\text{EQ 5-2})$$

Longer clock periods (lower clock frequencies) will also work. Notice that this discussion does not rely on the **duty cycle** of the clock (the duty cycle is the percentage of the clock period for which the clock is high). The duty cycle does not matter here because the flip-flop is edge-triggered.

**Figure 5-26**  
Constraints with  
rise and fall times.

 


*rise and fall times*

If we relax one of our assumptions about the clock, we end up with a clock signal with non-zero rise and fall times, as shown in Figure 5-26. In practice, the clock's rise and fall times are noticeable when compared to the other system delays because clock nets are large and hard to drive at high speeds. The rise ( $t_r$ ) and fall time ( $t_f$ ) add to the overall clock period:

$$P \geq C + s + p + t_r. \quad (\text{EQ 5-3})$$

*min/max delays*

One additional non-ideality that you may occasionally see mentioned is **minimum** and **maximum delays**. We have assumed so far that delays

 **Figure 5-27** Min/max delays.

are known—we can provide a single number that accurately reflects the delay through the component. However, delay may vary for several reasons:

- Manufacturing variations may cause different parts to exhibit different delays.
- As we saw in Section 3.3.4, delay may vary with temperature.

Min/max delays provide bounds on the delay—if the delay is given as  $[t_1, t_2]$  then the delay is at least  $t_1$  and at most  $t_2$  but can vary anywhere in between. Figure 5-27 shows a timing diagram with min-max delays on a clock signal that goes between 0 and 1, but they can also be applied to logic stable/changing values in general logic signals.

In the worst case, min/max delays can cause substantial problems. If each component exhibits min/max delays and we do not know anything about the relationships between the components' delays, we must assume that delay bounds add—after going through two components, the delay bounds would be  $[2t_1, 2t_2]$  and so on. Since we must assume that the signal is not valid during any part of the min/max delay window, we must run the system more slowly unless we can more accurately determine the actual delays through the logic.


However, on a single chip the delays through the components are in fact correlated. The physical parameters that determine delay through the logic and wires vary only slowly over the chip. This means that it is unlikely that one gate on the chip would have the best-case delay while the other would have the worst-case delay. The best-case/worst-case range characterizes variations over all the chips. Therefore, within a chip, min/max bounds tend to be considerably smaller than the min/max

bounds across chips. When designing multi-chip systems, we need to make much more pessimistic assumptions.

### 5.4.2 Performance of Latch-Based Systems

The analysis of latch-based systems follows the same general principles. But the paths through the combinational logic are more complex because latches are transparent.

**Figure 5-28**  
Model system for performance analysis of latch-based machines.

 

*latch-based model system*


Figure 5-28 shows the model system we will use to analyze a two-phase latch-based machine. The delays through the two blocks of combinational logic are  $C_1$  and  $C_2$ ; we will assume that all the latches have the same setup and propagation times of  $s$  and  $p$ . We will also assume for convenience that all latches close at the downward edge of their clock.

*two-phased timing analysis*

Figure 5-29 shows the timing chart for the two-phased system. First consider the upper block of logic  $C_1$ , which is fed by the  $\phi_1$ -controlled latch. The inputs to that block are not stable until  $h$  time units after the downward transition of  $\phi_1$ . They then propagate through the block with  $C_1$  delay and must arrive  $s$  time units before the downward transition of  $\phi_2$ . A similar analysis can be made for propagation through the  $C_2$  block. This gives a constraint on the clock period of
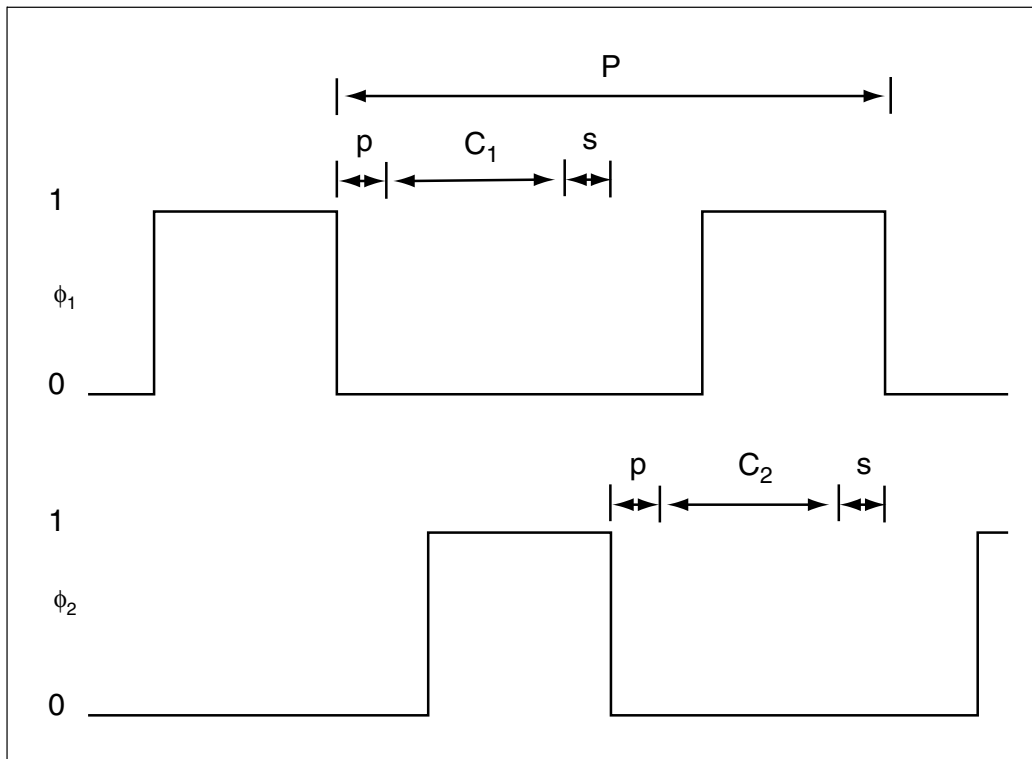
$$P \geq C_1 + C_2 + 2s + 2p. \tag{EQ 5-4}$$

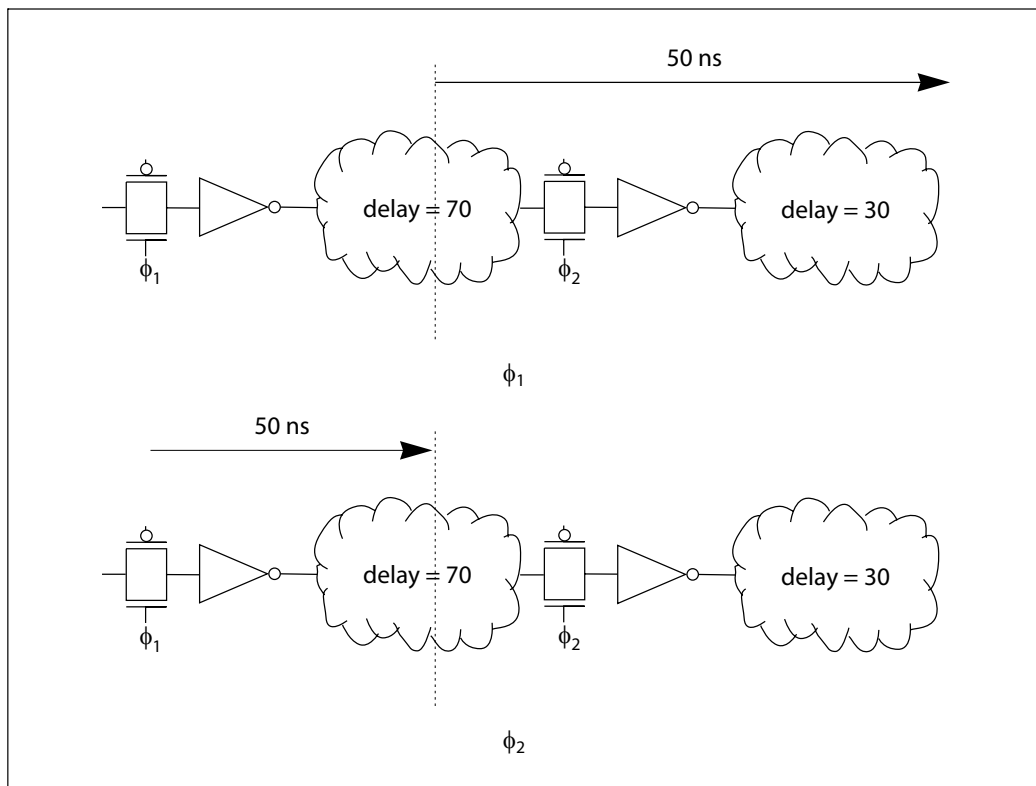




**Figure 5-29** Timing chart for a two-phased system.

#### *hacking FSM timing*

However, we can improve these results (though implementing this scheme is tricky and not recommended). If the signal from  $C_1$  arrives early, it can shoot through the  $\phi_2$  latch and start to propagate through the  $C_2$  block. This head start can reduce the total period if a short path in  $C_1$  feeds a long path in  $C_2$ . In a latch-based system we can equalize the length of each phase to 50 ns, as shown in Figure 5-29, by taking advantage of the transparency of latches. Ignore for a moment the setup and hold times of the latches to simplify the explanation. Signals that become valid at the end of  $\phi_2$  propagate through the short-delay combinational logic. If the clock phases are arranged so that  $\phi_1 = 1$  when they arrive, those signals can shoot through the  $\phi_1$  latch and start the computation in the long-delay combinational block. When the  $\phi_1$  latch closes, the signals are kept stable by the  $\phi_1$  latch, leaving the  $\phi_2$  latch free to open and receive the signals at the end of the next 50 ns interval. How-




**Figure 5-30** Spreading a computation across two phases in a latch-based system.

ever, this scheme violates the strict two-phase clocking discipline. Making sure that you have properly measured the delays and have not violated a timing constraint can be tricky.

### 5.4.3 Clock Skew

#### *skew problems*

**Skew** describes a relative delay or offset in time between any two signals. Skew causes problems when we think we are combining two sets of values but are in fact combining a different set of values. We may see skew between two data signals, a data signal and a clock, or between clock signals in a multi-clock system. In Figure 5-31, the registers that provide inputs  $a$  and  $b$  produce valid signals over the range  $[0, 5 \text{ ns}]$ . At those  $a$  and  $b$  inputs, the two signals are aligned in time to be simultane-

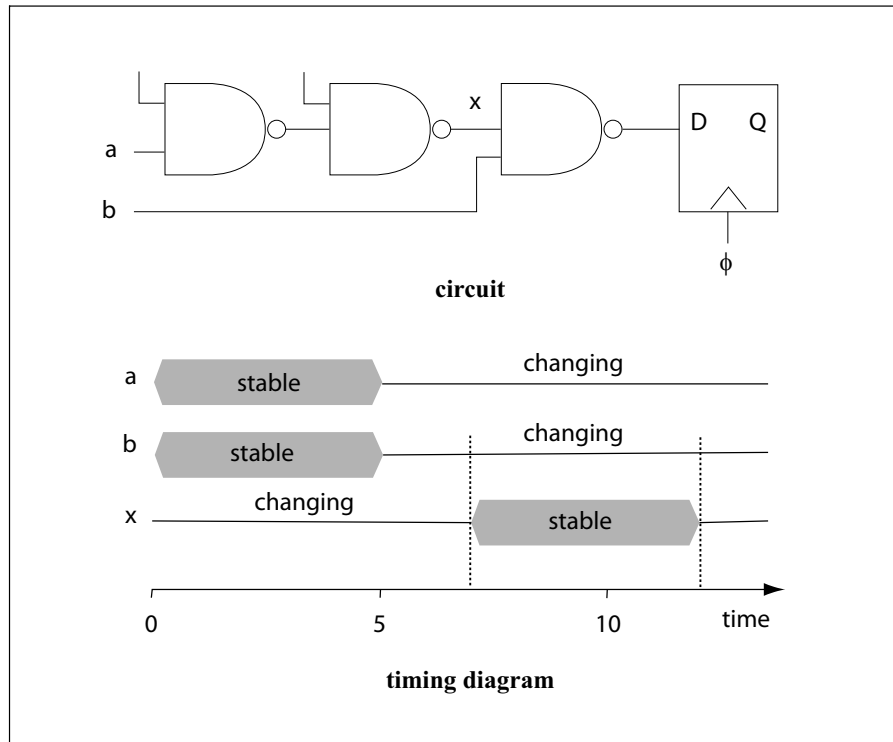


**Figure 5-31** A circuit that introduces signal skew relative to a clock.

ously valid. By the time  $a$ 's signal has propagated to point  $x$ , however, the combinational logic has delayed that signal so that it does not become valid until after  $b$  has ceased to be valid. As a result, the gate that combines  $b$  and  $x$  produces garbage during the time window marked by the dotted lines. However, this sort of problem shouldn't occur in a system that satisfies a clocking discipline, since  $a$  and  $b$  should remain stable until the end of the clock period.


*clock skew*

But in synchronous design, skew of one of the clocks can be fatal. Figure 5-32 illustrates clock skew. The clock is delayed relative to its source. If, for example, the signal provided to the latch is valid from 0 to 5 ns but the clock edge does not arrive at the latch until 6 ns, then the latch will store a garbage value. The difficulty of solving this problem depends on the source of the delay on the clock line.

**Figure 5-32** Clock skew.

 

**Figure 5-33** Clock skew and qualified clocks.

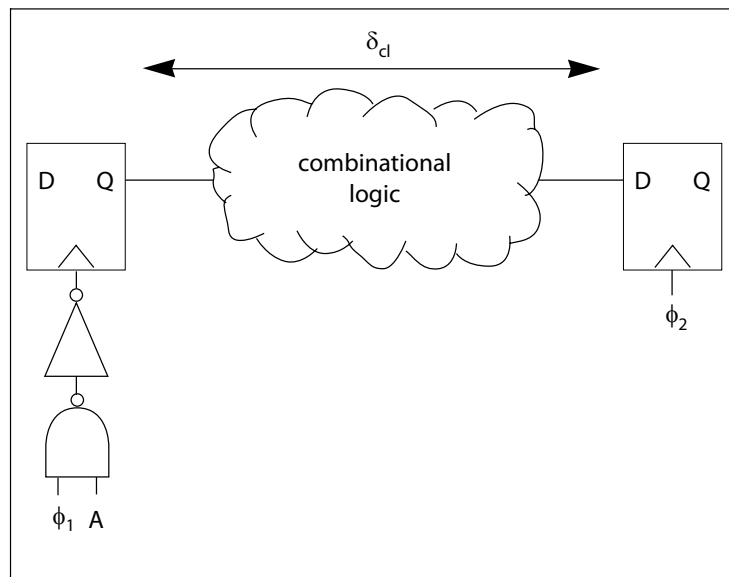


*sources of clock skew*

Clocks can be skewed for several reasons:

- If they are from external sources, they may arrive skewed.
- The delays through the clock network may vary with position on the chip.
- Qualified clocks may add delay to some clock destinations and not others.
- Skew can vary with temperature due to temperature dependencies on gate/buffer delay and wire delay. In a 130 nm process, clock skew can increase by 10% when the junctions at different points on the chip differ in temperature by 40°C [Sat05, Ped06].

*skew and qualified clocks*

Qualified clocks are a common source of clock skew. Consider the circuit of Figure 5-33: the  $\phi_1$  latch is run by a qualified clock while the  $\phi_2$  latch is not. When the  $\phi_1$  signal falls at the system input, the clock input to the latch falls  $\delta_{clk}$  time later. In the worst case, if  $\delta_{clk}$  is large enough, the  $\phi_1$  and  $\phi_2$  phases may both be 1 simultaneously. If that occurs, signals can propagate completely through latches and improper values may be stored.

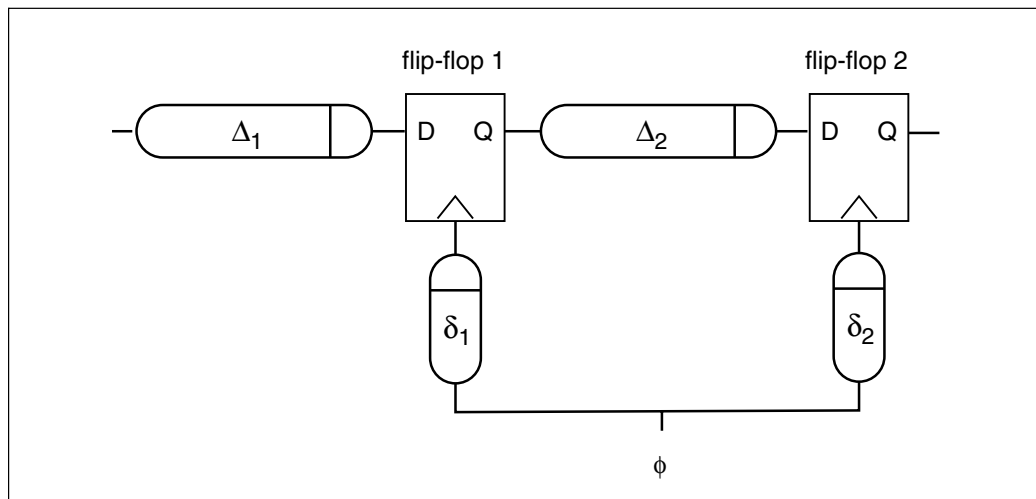

**Figure 5-34** Model system for clock skew analysis in flip-flop-based machines.

*skew in flip-flop systems*

We can build a simple model to understand how clock skew causes problems in flip-flop systems. The model is shown in Figure 5-34. The clock  $\phi$  is distributed to two flip-flops; each connection has its own

skew. The combinational logic blocks feeding each flip-flop each have their own delays  $\delta_1$  and  $\delta_2$ . Clock skew is measured from one point to another: the skew from the clock input of flip-flop 1 to the clock input of flip-flop 2 is  $s_{12} = \delta_1 - \delta_2$  and the skew from flip-flop 2's clock input to flip-flop 1's clock input is  $s_{21} = \delta_2 - \delta_1$ . The clock controls when the D input to each flip-flop is read and when the Q output changes. Clock skew gives the signal at the D input more time to arrive but it simultaneously gives the signal produced at the Q output less time to reach the next flip-flop. If we assume that each flip-flop instantaneously reads its D input and changes its Q output, then we can write this constraint on the minimum clock period  $T$ :

$$T \geq \Delta_2 + \delta_1 - \delta_2 = \Delta_2 + s_{12}. \tag{EQ 5-5}$$

This formula tells us that the clock period must be adjusted to take into account the late arrival of the clock at flip-flop 1. This formula also makes it clear that if the clock arrives later at flip-flop 2 than at flip-flop 1, we actually have more time for the signal to propagate.

**Figure 5-35** Timing in the skew model.

 


Figure 5-35 shows that as the clock skew  $\delta_1 - \delta_2$  increases, there is less time for the signal to propagate through the combinational logic. As the clock edge  $\phi_1$  moves forward in time, the output of flip-flop 1  $Q_1$  is delayed. This in turn delays the input to flip-flop 2  $D_2$ , pushing it closer to missing the clock edge  $\phi_2$ .


Equation 5-5 is easy to use in the case when we can choose the clock period after we know the combinational logic delay and the skew. However, the more common situation is that we are given a target clock period, then design the logic. It is often useful to know how much skew we can tolerate at a given flip-flop. For this case, we can rewrite the relation as

$$s_{12} \geq T + \Delta_2. \quad (\text{EQ 5-6})$$

*taming clock skew*

What can we do about clock skew? Ideally, we can distribute the clock signal without skew. In custom chips, a great deal of effort goes into designing a low-skew clock distribution network. We will discuss clock distribution in more detail in Section 7.3.3.


**Figure 5-36** Skew in a clock distribution tree.

 

In practice, we cannot always eliminate skew. In these cases, we can exploit physical design to minimize the effects of skew. Consider the clock distribution tree of Figure 5-36. Each output of the tree has its own delay so there are many possible skew values between pairs of taps on the clock tree. The skew between taps that are physically close is often less than the skew between taps that are further apart. By proper placement of the combinational logic we can minimize the skew between adjacent ranks of flip-flops. The next example looks at how to deal with clock skew.

 
**Example 5-2**  
**Dealing with**  
**clock skew**

The delays in our clock distribution network are distributed like this:



The placement of logic around the clock tree will affect both the combinational logic delays and the clock skew. Let's consider several examples.


Here is a very bad case:

 

This design has both large clock skew and long wires that lead to large combinational delays.




This case is better:

 

We have no clock skew here but we still have long wires.

This case is even better:

 

This design reduces the combinational delay and keeps the flip-flops within one island of clock skew.

*skew in latch-based systems*

Sakallah, Mudge, and Olukotun [Sak92] developed a set of constraints which must be obeyed by a latch-controlled synchronous system. Their formulation allows an arbitrary number of phases and takes into account propagation of signals through the latches. While the constraints must

be solved by an algorithm for problems of reasonable size, studying the form of the constraints helps us understand the constraints which must be obeyed by a latch-controlled system.

The system clock period is  $T_c$ . The clock is divided into  $k$  phases  $\phi_1, \dots, \phi_k$ , each of which is specified by two values: the start time  $s_i$ , relative to the beginning of the system clock period, of the  $i^{\text{th}}$  phase; and  $T_i$ , the duration of the active interval of the  $i^{\text{th}}$  phase. Connectivity is defined by two  $k \times k$  matrices.  $C_{ij} = 1$  if  $i \geq j$  and 0 otherwise; it defines whether a system clock cycle boundary must be crossed when going from phase  $i$  to phase  $j$ .  $K_{ij} = 1$  if any latch in the system takes as its input a signal from phase  $\phi_i$  and emits as its output a signal of phase  $\phi_j$  and is 0 otherwise. We can easily write basic constraints on the composition of the clock phases:

- periodicity requires that  $T_i \leq T_c, i = 1, \dots, k$  and  $s_i \leq T_c, i = 1, \dots, k$ ;
- phase ordering requires that  $s_i \leq s_{i+1}, i = 1, \dots, k-1$ ;
- the requirement that phases not overlap produces the constraints  $s_i \geq s_j + T_j - C_{ji}T_c, \forall (i,j) \ni K_{ij} = 1$ ;
- clock non-negativity requires that  $T_c \geq 0, T_i \geq 0, i = 1, \dots, k$ , and  $s_i \geq 0, i = 1, \dots, k$ .

We now need constraints imposed by the behavior of the latches. The latches are numbered from 1 to  $l$  for purposes of subscripting variables that refer to the latches. The constraints require these new constraints and parameters:

- $p_i$  is the clock phase used to control latch  $i$ ; we need this mapping from latches to phases since we will in general have several latches assigned to a single phase.
- $A_i$  is the **arrival time**, relative to the beginning of phase  $p_i$ , of a valid signal at the input of latch  $i$ .
- $D_i$  is the **departure time** of a signal at latch  $i$ , which is the time, relative to the beginning of phase  $p_i$ , when the signal at the latch's data input starts to propagate through the latch.
- $Q_i$  is the earliest time, relative to the beginning of phase  $p_i$ , when latch  $i$ 's data output starts to propagate through the combinational logic at  $i$ 's output.
- $\Delta_{DCi}$  is the setup time for latch  $i$ .
- $\Delta_{DQi}$  is the propagation delay of latch  $i$  from the data input to the data output of the latch while the latch's clock is active.

- $\Delta_{ij}$  is the propagation delay from an input latch  $i$  through combinational logic to an output latch  $j$ . If there is no direct, latch-free combinational path from  $i$  to  $j$ , then  $\Delta_{ij} = -\infty$ . The  $\Delta$  array gives all the combinational logic delays in the system.


The latches impose setup and propagation constraints:

- Setup requires that  $D_i + \Delta_{DCi} \leq T_{pP}$ ,  $i = 1, \dots, l$ . These constraints ensure that a valid datum is set up at the latch long enough to let the latch store it.
- Propagation constraints ensure that the phases are long enough to allow signals to propagate through the necessary combinational logic. We can use a time-zone-shift equation to move a latch variable from one clock phase to another:  $S_{ij} \equiv s_i - (s_j + C_{ij}T_c)$ . A signal moving from latch  $j$  to latch  $i$  propagates in time  $Q_j + \Delta_{ij}$ , relative to the beginning of phase  $p_j$ . We can use the time-zone-shift formula to compute the arrival time of the signal at latch  $i$  measured in the time zone  $p_i$ , which is  $Q_j + \Delta_{ij} + S_{p_i p_j}$ . The signal at the input of latch  $i$  is not valid until the latest signal has arrived at that latch: the time  $A_i = \max_j(Q_j + \Delta_{ij} + S_{p_i p_j})$ . To make sure that propagation delays are non-negative, we can write the constraints as  $D_i = \max(0, A_i)$ ,  $i = 1, \dots, l$ .
- Solving the constraints also requires that we constrain all the  $D_i$ 's to be non-negative.

Optimizing the system cycle time requires minimizing  $T_c$  subject to these constraints.

#### 5.4.4 Retiming

In many cases, we can move registers to balance combinational delays. A simple example of **retiming** [Lei83] is shown in Figure 5-37. Moving the register from the output of the NAND to its inputs doesn't change the combinational function computed, only the time at which the result is available. We can often move registers within the system to balance delays without changing the times of the signals at the primary inputs and outputs. In the example of Figure 5-23, we could move the middle flip-flop to split the middle addition in two. CAD tools can retime logic by using an optimization algorithm.

 

**Figure 5-37** Retiming preserves combinational function.

### 5.4.5 Transient Errors and Reliability

#### *detecting and correcting errors*


A variety of causes—temperature gradients, alpha particles, marginal component parameters, etc.—can cause transient errors. Transient errors can be detected and corrected in some cases. There are two major techniques for correcting errors: **on-the-fly** correction substitutes a correct value for an incorrect one using combinational logic, so that the rest of the system does not see any delay; **rollback** causes the system to return to an earlier state where the value can be recomputed.

#### *redundancy and diversity*

Redundant computational units are one important technique for detecting and correcting errors. For example, **triple modular redundancy** uses three identical units that are fed the same inputs. A voter compares the results and chooses the value selected by the majority of the units (assuming that they do not all disagree). Another common technique is **design diversity**, in which redundant units are implemented using different components (and often different design teams). Design diversity aims to reduce common factors across the design that may disable a large part of the system. Siewiorek and Swarz [Sie98] discuss reliable system design in detail.

#### *razor latches*

One technique for identifying errors is the **razor latch** [Ern03]. As shown in Figure 5-38, the razor latch includes two latches that are clocked at slightly different times: one is clocked by the system clock,

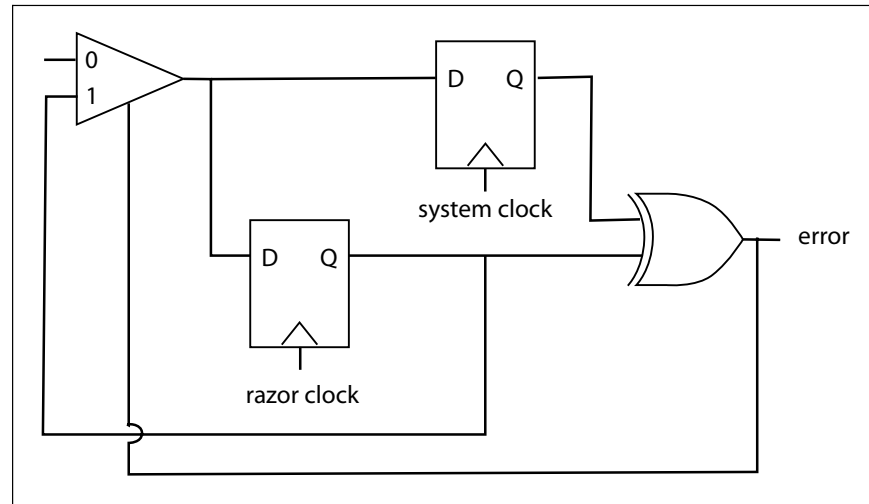

**Figure 5-38** A razor latch.


the other by a razor clock that is slightly later than the system clock. If the value was not stable at the end of the system clock, the values in the two latches will be different. In this case, the XOR gate identifies the error and the value from the razor latch is used as the output value.

## 5.5 Clock Generation

Generating a high-speed clock is a non-trivial problem in itself. Many chips require clock signals of frequencies much too high to be driven onto the chip from the pads. As a result, the high-frequency clock must be generated on-chip from a lower-frequency input. Furthermore, the on-chip clock must be aligned in phase with the external reference—multiple chips are usually driven from the same external reference clock, and they will not communicate properly if their internal clocks are not phase-locked.

### *phase-locked loops*


The **phase-locked loop (PLL)** shown in Figure 5-39 is commonly used to generate the on-chip clock signal. The higher-frequency output clock is generated by a voltage-controlled oscillator (VCO). The VCO's frequency is controlled by the feedback loop of the PLL. The signal generated by the PLL is divided down to the frequency of the input reference

 

**Figure 5-39** Block diagram of a phase-locked loop for clock generation.

clock; the phase detector compares the difference in phases between the input and output clocks; a filter is imposed between the phase detector and VCO to ensure that the PLL is stable. The PLL is designed to quickly lock onto the input clock signal and to follow the input clock with low jitter. The phase-locked loop compares the input clock to the internal clock to keep the internal clock in the proper phase relationship. The circuit design of PLLs is beyond the scope of this book, but several articles [You92, Bow95, Man96] and a book [Raz98] describe PLL circuits used in high-speed chips.

**Figure 5-40** A delay-locked loop.

 

#### *delay-locked loops*

Many chips use circuits that minimize the delay from the off-chip clock input to the internal clock signals; this can be particularly important for asynchronous designs. The **delay-locked loop** shown in Figure 5-40 is one circuit commonly used for this purpose. It compares the input clock to the internal clock using a filter. The output of the filter controls the delay in a variable delay line so as to align the clock edges on the input and internal clock lines.

## 5.6 Sequential System Design

---

To design a sequential machine, we need to first specify it, and then implement it. This section covers several methods for specifying FSMs and techniques for choosing a good implementation for the FSM.

### 5.6.1 Structural Specification of Sequential Machines

*counters as sequential machines*

Now that we know how to construct reliable sequential machines, we can experiment with building real sequential machines, starting with a specification of function and finishing with a layout. We have already designed the simplest sequential machine—the shift register with no combinational logic. The shift register is relatively boring, not only because it has no combinational logic, but for another reason as well: there is no feedback, or closed path, between the latches. A binary counter is a simple system that exhibits both properties. We will define the counter as a *structure*: an  $n$ -bit counter will be defined in terms of interconnected one-bit counters.

The next example describes the design of a counter.

---


#### **Example 5-3** **A counter**

A one-bit counter consists of two components: a specialized form of adder, stripped of unnecessary logic so that it can only add 1; and a memory element to hold the value. We want to build an  $n$ -bit binary counter from one-bit counters.

What logical function must the one-bit counter execute? The truth table for the one-bit counter in terms of the present count stored in the latch and the carry-in is shown below. The table reveals that the next value of the count is the exclusive-or (XOR) of the current count and  $C_{in}$ , while the carry-out is the AND of those two values.


count	$C_{in}$	next count	$C_{out}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

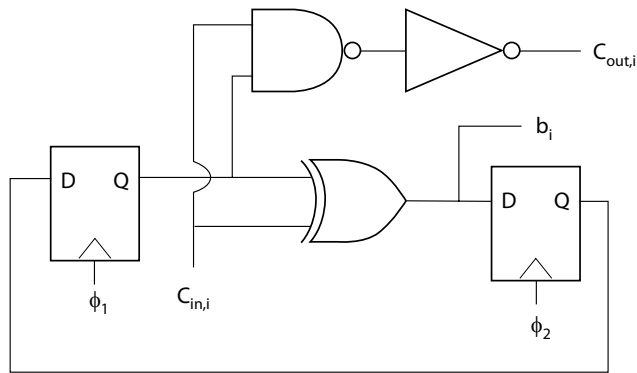Here is a logic schematic for the one-bit counter:



The AND function is built from a NAND gate and an inverter. The latches in this counter have the same basic connections as the latches in the shift register, except that logic is added between the  $\phi_1$  and  $\phi_2$  latches to compute the count. The next count is loaded into one latch while  $\phi_2$  is high, then transferred to the other latch during  $\phi_1$ , allowing the next count cycle to be computed.

 The  $n$ -bit counter's structure looks like this:




Each bit has one input and two outputs: the input  $C_{in,i}$  is the carry into the  $i^{th}$  bit; the output  $b_i$  is the current value of the count for that bit; and



$C_{out,i}$  is the carry out of the bit. The carry-in value for the  $0^{th}$  bit is 1; on each clock cycle this carry value causes the counter to increment itself. (The counter, to be useful, should also have a reset input that forces all bits in the counter to 0; we have omitted it here for simplicity.)

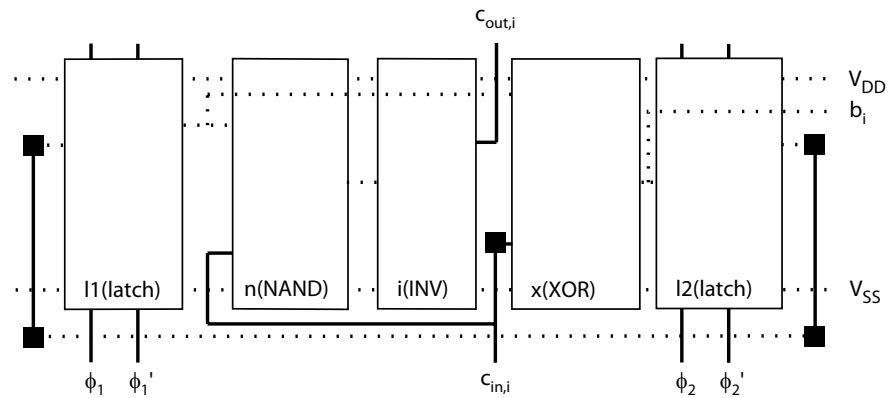Here is a hierarchical stick diagram for the one-bit counter:



It has been designed to tile vertically to form an  $n$ -bit counter. All the one-bit counter's components are arranged in one long row. The  $\phi_1$  and  $\phi_2$  latches are on opposite ends of the cell, so a long metal wire must be used to connect them. The connections between the logic gates are relatively simple, though care must be taken to route the wires over cells so they do not create inadvertent shorts.

### 5.6.2 State Transition Graphs and Tables

*functional specification of FSMs*

To build complex sequential systems, we need powerful specification techniques. We described the counter of Example 5-3 as a structure. A more abstract and powerful specification is **functional**—describing the next-state and output functions directly, independent of the structure used to compute them. We can then use programs to generate the Mealy or Moore structure of Figure 5-14 to generate an initial structure, which can be optimized by CAD tools. Some behaviors are cumbersome to specify as state transition tables or graphs and are best described as structures—a register file is a good example of a sequential machine

*state transition tables  
and graphs*

best described structurally—but functional descriptions of FSMs occur in nearly every chip design.

An FSM can be specified in one of two equivalent ways: as a **state transition table** or a **state transition graph**. Either is a compact description of a sequential machine's behavior. The next example shows how to design a simple machine from a state transition table.

### Example 5-4 A 01-string recognizer

Consider as an example a very simple FSM with one input and one output. If the machine's inputs are thought of as a string of 0's and 1's, the machine's job is to recognize the string "01"—the FSM's output is set to 1 for one cycle as soon as it sees "01." This table shows the behavior of the recognizer machine over time for a sample input:


time	0	1	2	3	4	5
input	0	0	1	1	0	1
present state	bit1	bit2	bit2	bit1	bit1	bit2
next state	bit2	bit2	bit1	bit1	bit2	bit1
output	0	0	1	0	0	1

We can describe the machine's behavior as either a state transition graph or a state transition table. The machine has one input, the data string, and one output, which signals recognition. It also has two states: **bit1** is looking for "0", the first bit in the string; **bit2** is looking for the trailing "1". Both representations specify, for each possible combination of input and present state, the output generated by the FSM and the next state it will assume.

Here is the state transition table:

input	present state	next state	output
0	bit1	bit2	0
1	bit1	bit1	0
0	bit2	bit2	0
1	bit2	bit1	1

 And here is the equivalent state transition graph:



Assume that the machine starts in state `bit1` at time  $t=0$ . The machine moves from `bit1` to `bit2` when it has received a 0 and is waiting for a 1 to appear on the next cycle. If the machine receives a 0 in state `bit2`, the “01” string can still be found if the next bit is a 1, so the machine stays in `bit2`. The machine recognizes its first “01” string at  $t=2$ ; it then goes back to state `bit1` to wait for a 0. The machine recognizes another “01” string at  $t=5$ .

Translating the state transition graph/table into a chip layout requires several steps, most of which are familiar from the counter design. The first step is to **encode** the machine’s states into binary values, a step also known as **state assignment**. We didn’t discuss the encoding of the counter machine because we already knew a good encoding, namely, two’s-complement binary numbers. All the counter’s signals were specified as binary values, which mapped directly into the 0s and 1s produced by logic gates.


The present and next state values of a machine specified as a state transition graph, however, are **symbolic**—they may range over more than two values, and so do not map directly into Boolean 0s and 1s. This string-recognizer machine has only two states, but even in this simple case we don’t know which state to code as 0 and which as 1. The encoding problem is difficult and important because the choice of which Boolean value is associated with each symbolic state can change the amount of logic required to implement the machine.

Encoding assigns a binary number, which is equivalent to a string of Boolean values, to each symbolic state. By substituting the state codes into the state transition table, we obtain a **truth table** which specifies the combinational logic required to compute the machine’s output and

next state. If we choose the encoding bit1 = 0, bit2 = 1 for the 01-string recognizer, we obtain this truth table:


input	present state	next state	output
0	0	1	0
1	0	0	0
0	1	1	0
1	1	0	1

 From the encoded state transition table we can design the logic for to compute the next state and the output, either manually or by using logic optimization. Here is one logic network for the 01-string recognizer:



Inspection shows that the gates in fact implement the functions described in the truth table. Creating a logic network for this machine is easy but the task is more difficult for machines with larger state transition tables. Luckily, programs can design small, fast logic networks for us from encoded state transition tables. For example, we can use a set of synthesis tools that will take a truth table, optimize the logic, then create a standard-cell layout. The resulting layout looks somewhat different than our hand-designed examples because the standard cells's transistors are designed to drive larger loads and so are much wider than the

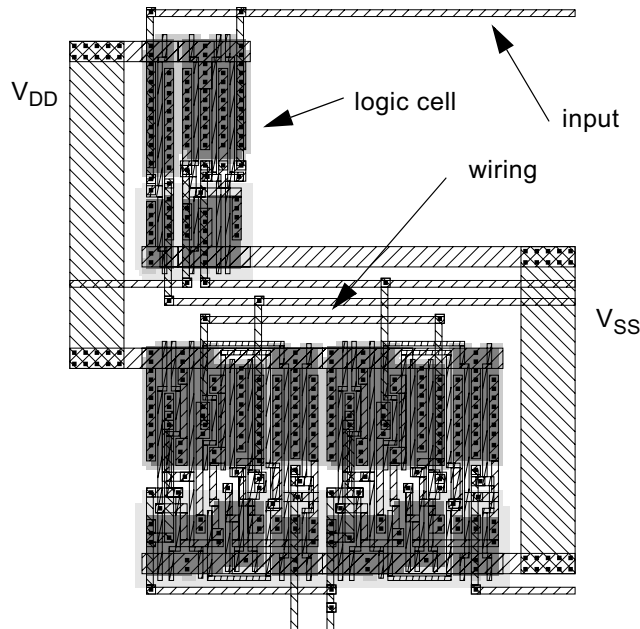ones we have been drawing by hand, but the layout is still two rows of CMOS gates with wiring in between:



If necessary, we can use a layout editor to examine the layout and determine exactly how the logic functions were designed and where the transistors for each gate were placed. However, one of the nicest things about synthesis tools (well-debugged tools, at least) is that we don't have to worry about how they did their job. All we need to know is the position of each input and output around the edge of the layout cell.

---


A slightly more complex example of finite-state machine designs is a controller for a traffic light at the intersection of two roads. This example is especially interesting in that it is constructed from several communicating finite-state machines; just as decomposing stick diagrams into cells helped organize layout design, decomposing sequential machines into communicating FSMs helps organize machine design.

---

---
 
### Example 5-5 A traffic light controller

We want to control a road using a traffic light:




There are many possible schemes to control when the light changes. We could alternate between giving the two roads green lights at regular intervals; that scheme, however, wouldn't give us an interesting sequential machine to study. A slightly more complex and interesting system can be built by taking traffic loads into account. The highway will generally have more traffic, and we want to give it priority; however, we do not want to completely block traffic on the farm road from crossing the highway. To balance these competing concerns, we install traffic sensors on the farm road at the intersection. If there is no traffic waiting on the farm road, the highway always has a green light. When traffic stops at the farm road side of the intersection, the traffic lights are changed to give the farm road a green light as long as there is traffic. But since this simple rule allows the highway light to be green for an interval too short to be safe (consider a second farm road car pulling up just as the highway light has returned to green), we ensure that the highway light (and, for similar reasons, the farm light) will be green for some minimum time.

We must turn this vague, general description of how the light should work into an exact description of the light's behavior. This precise description takes the form of a state transition graph. How do we know

that we have correctly captured the English description of the light's behavior as a state transition table? It is very difficult to be absolutely sure, since the English description is necessarily ambiguous, while the state transition table is not. However, we can check the state transition table by mentally executing the machine for several cycles and checking the result given by the state transition table against what we intuitively expect the machine to do. We can also assert several universal claims about the light's behavior: at least one light must be red at any time; lights must always follow a *green* → *yellow* → *red* sequence; and a light must remain green for the chosen minimum amount of time.

 
We will use a pair of communicating sequential machines to control the traffic light:



The system consists of a counter and a sequencer. Both are finite-state machines, but each serves a different purpose in the system. The counter counts clock cycles, starting when its `reset` input is set to 1, and signals two different intervals—the `short` signal controls the length of the yellow light, while the `long` signal determines the minimum time a light can be green.

The sequencer controls the behavior of the lights. It takes as inputs the car sensor value and the timer signals; its outputs are the light values,

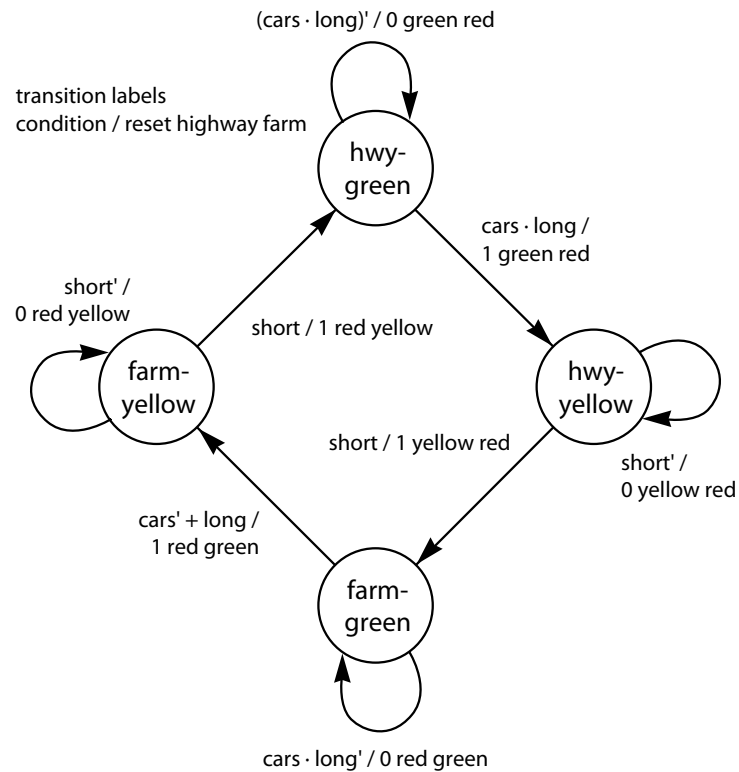along with the timer reset signals. The sequencer's state transition graph looks like this:



The states are named to describe the value of one of the lights; the complete set of light values, however, is presented at the machine's outputs on every cycle. Tracing through the state transition graph shows that this sequencer satisfies our English specification: the highway light remains green until cars arrive at the farm road (as indicated by the sensor) and the minimum green period (specified by the long timeout) is met. The machine then sets the highway light to yellow for the proper amount of time, then sets the highway light to red and the farm light to green. The farm light remains green so long as cars pull up to the intersection, but no longer than the long timeout period. Inspection also shows that the state transition graph satisfies all our assertions: one light is always red, each light always changes colors in the *green*  $\rightarrow$  *yellow*  $\rightarrow$  *red*



sequence; and each light, when it turns green, remains green for at least the period specified by the long timer.

We can also write the state transition graph as a table. Some of the transitions in the graph are labeled with OR conditions, such as `cars + long`. Since each line in a state transition table can only refer to the AND of input conditions, we must write the OR conditions in multiple lines. For example, one line can specify a transition out of the `farm-green` state when `cars = 1`, while another can specify the same next state and outputs when `long = 0`.

The sequencer and counter work in tandem to control the traffic light's operation. The counter can be viewed as a subroutine of the sequencer—the sequencer calls the counter when it needs to count out an interval of time, after which the counter returns a single value. The traffic light controller could be designed as a single machine, in which the sequencer counts down the long and short time intervals itself, but separating the counter has two advantages. First, we may be able to borrow a suitable counter from a library of pre-designed components, saving us the work of even writing the counter's state transition table. Second, even if we design our own counter, separating the machine states that count time intervals (counter states) from the machine states that make decisions about the light values (sequencer states), clarifies the sequencer design and makes it easier to verify.

We can implement each machine in the traffic light controller just as any other FSM, moving from the state transition table through logic to a final layout. We can either design custom layouts or synthesize standard-cell layouts from optimized logic. However, we have the additional problem of how to connect the two machines. We have three choices. The least palatable is to write a combined state transition table for the sequencer and counter, then synthesize it as a single FSM. Since the states in the combined machine are the Cartesian product of the states in the two component machines, that machine is unacceptably large. The simplest solution is to design each machine separately, then wire them together by hand. This option requires us to intervene after the FSM synthesis task is done, which we may not want to do. The third alternative is to interrupt the FSM synthesis process after logic design, splice together the net lists for the two machines, and give the combined net list to standard cell placement and routing.

---

### 5.6.3 State Assignment

State assignment is the design step most closely associated with FSMs. (Input and output signals may also be specified as symbolic values and encoded, but the state variable typically has the most coding freedom because it is not used outside the FSM.) State assignment can have a profound effect on the size of the next state logic, as shown in the next example.

#### Example 5-6 Encoding a shift register

Here is the state transition table for a two-bit shift register, which echoes its input bit two cycles later:

input	present state	next state	output
0	s00	s00	0
1	s00	s10	0
0	s01	s00	1
1	s01	s10	1
0	s10	s01	0
1	s10	s11	0
0	s11	s01	1
1	s11	s11	1

The state names are, of course, a hint at the optimal encoding. But let's first try another code:  $s00 = 00$ ,  $s01 = 01$ ,  $s10 = 11$ ,  $s11 = 10$ . We'll name the present state bits  $S_1S_0$ , the next state bits  $N_1N_0$ , and the input  $i$ . The next state and output equations for this encoding are:

$$output = S_1\bar{S}_0 + \bar{S}_1S_0$$

$$N_1 = i$$

$$N_0 = i\bar{S}_1 + iS_1$$

Both the output and next state functions require logic. Now consider the shift register's natural encoding—the history of the last two input bits. The encoding is  $s00 = 00$ ,  $s10 = 10$ ,  $s01 = 01$ ,  $s11 = 11$ . Plugging these code values into the symbolic state transition table shows that this encoding requires no next state or output logic:

$$\begin{aligned} \text{output} &= S_0 \\ N_1 &= i \\ N_0 &= S_1 \end{aligned}$$

*common factors from states*

This example may seem contrived because the shift register function is regular. But changes to the state codes can significantly change both the area and delay of sequencers with more complex state transition graphs. State codes can be chosen to produce logic that can be swept into a common factor during logic optimization—the common factors are found during logic optimization, but exist only because the proper logic was created during state assignment.

State assignment creates two types of common factors: factors in logic that compute functions of the present state; and factors in the next state logic. Input encoding can best be seen as the search for common factors in the symbolic state transition table. Consider this state machine fragment:

input	present state	next state	output
0	s1	s3	1
0	s2	s3	1

If we allow combinations of the present state variable, we can simplify the state transition table as:


input	present state	next state	output
0	$s1 \vee s2$	s3	1

How can we take advantage of the OR by encoding? We want to find the smallest logic that tests for  $s1 \vee s2$ . For example, if we assume that the state code for the complete machine requires two bits and we encode the state variables as  $s1 = 00$ ,  $s2 = 11$ , the present state logic is  $\overline{S_1}\overline{S_0} + S_1S_0$ . The smallest logic is produced by putting the state codes as close together as possible—that is, minimizing the number of bits in which

the two codes differ. If we choose  $s1 = 00$ ,  $s2 = 01$ , the present state logic reduces to  $\bar{s}_1$ .

As shown in Figure 5-41, we can interpret the search for symbolic present state factors in the state transition table as a forward search for common next states in the state transition graph [Dev88]. If two states go to the same next state on the same input, the source states should be coded as close together as possible. If the transitions have similar but not identical input conditions, it may still be worthwhile to encode the source states together.

**Figure 5-41** Common next states.

 


*relationships  
between codes*

Figure 5-42 illustrates the relationship between bit differences and distance between codes. We can embed a three-bit code in a three-dimensional space: one axis per code bit, where each axis includes the values 0 and 1. Changing one code bit between 0 and 1 moves one unit through the space. The distance between 000 and 111 is three because we have to change three bits to move between the two codes. Putting two codes close together puts them in the same subspace: we can put two codes in the 00- subspace and four in the 1- subspace. We can generate many coding constraints by searching the complete state transition graph; the encoding problem is to determine which constraints are most important.

We can also search backward from several states to find common present states. As shown in Figure 5-44, one state may go to two different states on two different input values. In this case, we can minimize the amount of logic required to compute the next state by making the sink

**Figure 5-42** State codes embedded in a three-dimensional space.

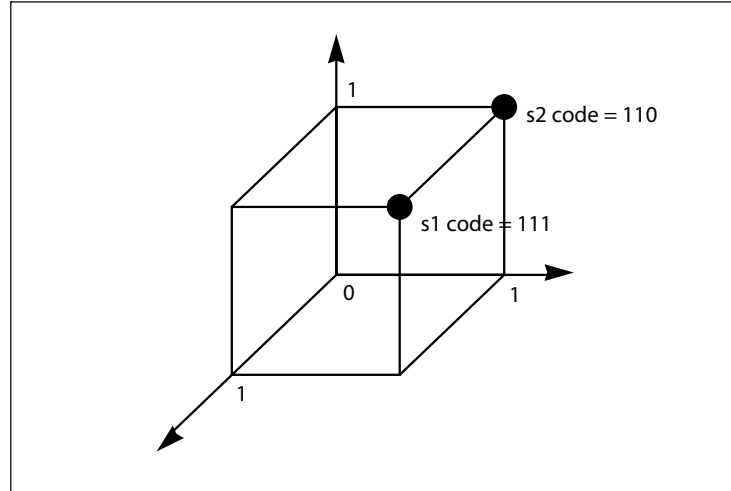

states' codes as close as possible to the source state's code. Consider this example:


input	present state	next state	output
0	s0	s1	1
1	s0	s2	1

We can make use of the input bit to compute the next state with the minimum amount of logic: if  $s0 = 00$ , we can use the input bit as one bit of the codes for  $s1$  and  $s2$ :  $s1 = 10$ ,  $s2 = 11$ . One bit of the next state can be computed independently of the input condition. Once again, we have encoded  $s1$  and  $s2$  close together so that we need the smallest amount of logic to compute which next state is our destination.


*state assignment and delay*

So far, we have looked at codes that minimize the area of the next state logic and the number of registers. State assignment can also influence the delay through the next state logic; reducing delay often requires adding state bits. Figure 5-43 shows the structure of a typical operation performed in either the next-state or the output logic. Some function  $f()$  of the inputs is computed. This value will usually control a conditional operation: either a conditional output or a conditional change in state. Some test of the present state is made to see if it is one of several states. Then those two results are combined to determine the proper output or

**Figure 5-43** An FSM computes new values from the primary inputs and state.

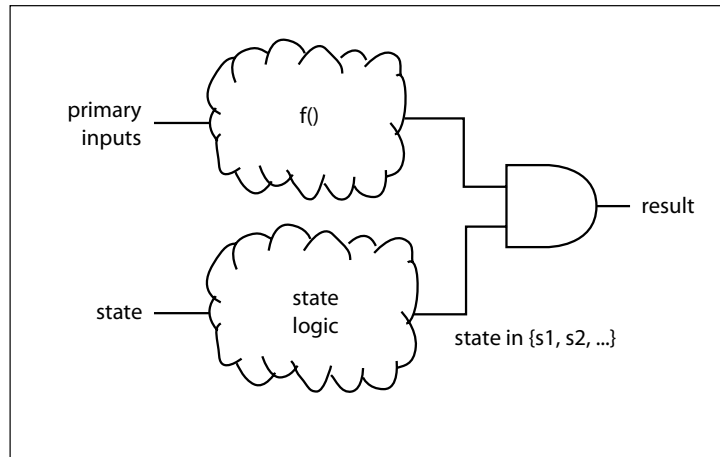


**Figure 5-44** Common present states.

 

next state. We can't do much about the delay through  $f()$ , but we can choose the state codes so that the important steps on the state are easy to compute. Furthermore, the FSM probably computes several  $f()$ s for different operations, which in general don't have the same delay. If we can't make all computations on the state equally fast, we can choose the codes so that the fastest state computations are performed on the FSM's critical path.

As shown in Figure 5-45, state codes can add delay both on the output and next state sides. On the output logic side, the machine may need to compute whether the present state is a member of the set that enables a certain output—in the example, the output is enabled on an input condition and when the present state is either s2 or s4. The delay through the

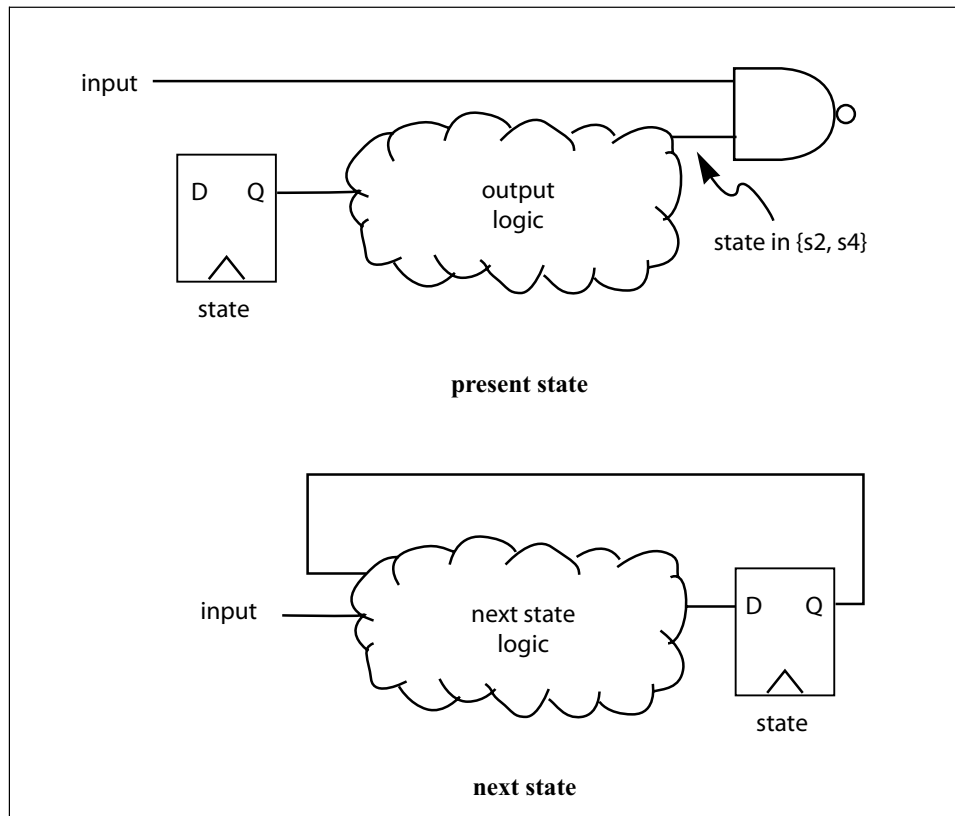

**Figure 5-45** How state codes affect delay.

logic that computes the state subset depends on whether the state codes were chosen to make that test obvious.

#### *one-hot codes*

A **one-hot code** uses  $n$  bits to encode  $n$  states; the  $i^{\text{th}}$  bit is 1 when the machine is in the  $i^{\text{th}}$  state. We can use such a code to easily compute state subset membership, by simply computing the OR of the state bits in the subset. But this solution has two problems. First, it requires a lot of memory elements for the present state: a machine with 64 states requires at least six memory elements for arbitrary codes, but 64 states for a one-hot encoding. Second, one-hot encoding doesn't help if an output depends on more than one state. It's best to examine the machine for time-critical outputs that depend on the present state and to construct codes that efficiently represent the time-critical state combinations, then use area-minimizing coding for the rest of the states.


On the next state side, the machine needs to compute the next state from the inputs and the present state. The delay to compute the next state depends on the complexity of the next-state function. The fastest next-state logic uses the result of the test of the primary inputs to independently change bits in the state code. For example, setting bit 0 of the next state to 1 and bit 2 to 0 is relatively fast. Computing a new value for bit 0, then setting bit 2 to the complement of bit 1 is slower.

## 5.7 Power Optimization

### *glitches and power*

As was described in Section 4.3, eliminating glitching is one of the most important techniques for power reduction in CMOS logic. Glitch reduction can often be applied more effectively in sequential systems than is possible in combinational logic. Sequential machines can use registers to stop the propagation of glitches, independent of the logic function being implemented.

**Figure 5-46** Flip-flops stop glitch propagation.

 

### *retiming and glitches*

Many sequential timing optimizations can be thought of as retiming [Mon93]. Figure 5-46 illustrates how flip-flops can be used to reduce power consumption by blocking glitches from propagating to high capacitance nodes. (The flip-flop and its clock connection do, of course, consume some power of their own.) A well-placed flip-flop will be positioned after the logic with high signal transition probabilities and before high capacitance nodes on the same path.

### *blocking glitch propagation*

Beyond retiming, we can also add extra levels of registers to keep glitches from propagating. Adding registers can be useful when there are more glitch-producing segments of logic than there are ranks of flip-



flops to catch the glitches. Such changes, however, will change the number of cycles required to compute the machine's outputs and must be compatible with the rest of the system.

Proper state assignment may help reduce power consumption. For example, a one-hot encoding requires only two signal transitions per cycle—on the old state and new state signals. However, one-hot encoding requires a large number of memory elements. The power consumption of the logic that computes the required current-state and next-state functions must also be taken into account.

---

## 5.8 Design Validation

---

### *design verification problems*

A sequential machine is a chunk of logic large enough to demand its own validation strategy. You can verify functionality both from the top down—checking that your logic matches the machine's description—and from the bottom up—extracting the circuit from the layout and comparing the results of its simulation with the simulation results from the logic network you specified. You must also make sure that the system runs at the required rate; one of the advantages of building sequential systems according to a clocking methodology is that we can verify performance without simulation.

### *verification tools*

You may have access to true verification tools, which can automatically compare a combinational logic or sequential machine description against the implementation, using tautology or FSM equivalence algorithms. You are more likely to use simulation to validate your design. You can simulate a single description of your machine, such as the register-transfer description, to be sure you designed what you wanted; you can also compare the results of two different simulations, such as the logic and register-transfer designs, to ensure that the two are equivalent. You may need to use several simulators to verify the design, depending on your available tools:

- A register-transfer simulator exhibits the correct cycle-by-cycle behavior at its inputs and outputs, but the internal implementation of the simulator may have nothing to do with the logic implementation. Several specialized languages for hardware description and simulation have been developed. Hardware simulation languages, such as VHDL and Verilog, provide primitives that model the parallelism of logic gate evaluation, delays, *etc.*, so that a structural description such as a net list automatically provides accurate simulation. In a
- 
-

pinch, a C program makes a passable register-transfer simulator: the component is modeled as a procedure, which takes inputs for one cycle and generates the outputs for that cycle. However, hardware modeling in C or other general-purpose programming languages requires more attention to the mechanics of simulation.

- A logic simulator accepts a net list whose components are logic gates. The simulator evaluates the output of each logic gate based on the values presented at the gate's inputs. You can trace through the network to find logic bugs, comparing the actual value of a wire to what you think the value should be. Verilog and VHDL can be used for logic simulation: a library provides simulation models for the logic gates; a net list tells the simulation system how the components are wired together.
- A switch simulator models the entire system—both combinational logic gates and memory elements—as a network of switches. Like a logic simulator, the simulator evaluates individual nets, but the simulation is performed at a lower level of abstraction. A switch simulator can find some types of charge sharing bugs, as well. You must use a switch simulator if your circuit contains mixed switch and gate logic; a switch simulator is most convenient for a circuit extracted from a complete layout, since the circuit extractor generates a net list of transistors.

You should simulate your sequential machine specification—register-transfer description, state transition graph, etc.—before designing the logic to implement the machine. If you specify the wrong function and don't discover the error before implementation, you will waste a lot of logic and layout design before you discover your mistake. This step ensures that your formal description of behavior matches your informal requirements.

*comparing different levels of abstraction*

To verify your implementation, you should check your logic design against the register-transfer/sequential machine description. Once again, catching any errors before layout saves time and effort. That is definitely true if you design the logic yourself; if the logic was designed by a CAD tool, the results are probably correct, though the more paranoid designers among you may want to perform some simulation to make sure the logic optimizer didn't make a mistake.

You should also extract the circuit from your completed layout, simulate it using the same inputs you used to simulate your logic, and compare the results. Switch or circuit simulation not only check the correctness of the layout, they also identify charge-sharing bugs that can be found only in a switch-level design. Simulation tests that are comprehensive

enough to ensure that your original logic design was correct should also spot differences between the logic and the layout. If you do not have a logic simulator available, but you do have layout synthesis, one way to simulate the logic is to generate a layout, then extract a switch-level circuit and simulate it.

If you specify a schematic or net list of the logic before layout, a net list comparison program can check the layout against that schematic. The net list extracted from the layout will use n-type and p-type transistors as its components. If the schematic was designed in terms of logic gates, it can be expanded to a transistor-level schematic. A net list comparison program tries to match up the components and nets in the two schematics to produce a one-to-one correspondence between the two net lists. Such programs usually require that only a few major signals— $V_{DD}$ ,  $V_{SS}$ , clocks, and the primary inputs and outputs—be identified. If the program can't match up the two net lists, it will try to identify a small part of each circuit that contains the error.

#### *performance verification*

Performance verification—making sure the system runs fast enough—can be separated from functionality if the system is properly designed. If we have obeyed a clocking methodology, we know that the system will work if values arrive at the memory elements within prescribed times. Timing analysis algorithms such as those described in Section 4.3 are the best way to ensure that the chip runs at the required rate. Circuit or timing simulation should be used to optimize paths that are expected to be critical. However, unexpected critical paths may have crept into the design. Timing analysis is the guardian that ensures that the paths you optimized are in fact the critical paths.

---

## 5.9 Sequential Testing

---

We studied in the last chapter manufacturing faults in combinational networks and how to test them. Now we are prepared to study the testing of sequential systems, which is made much harder by the inaccessibility of the memory elements to the tester.

#### *ATPG*


A suite of test vectors for a chip is generated using a combination of CAD techniques called **automatic test pattern generation** (ATPG) and expert human help. Test generation for combinational networks can be done entirely automatically. Automated methods for sequential circuits are improving, but manual intervention is still required in many cases to

---

---


provide full test coverage. The designer or test expert may be able to find a test for a fault that a program cannot. Often, however, it is better to redesign a hard-to-test chip to make it easier to find test vectors. Not only does **design for testability** let automatic test generation programs do more of the work, it reduces the risk that the chip will be abandoned in frustration with low test coverage.

**Figure 5-47** Testing a sequential machine.

 

*sequential  
testing challenges*

Testing a sequential system is much harder than testing a combinational network because you don't have access to all of the inputs and outputs of the machine's combinational logic. Figure 5-47 shows a sequential machine. We want to test the NAND gate for a stuck-at-1 fault at its output, which requires applying 1 to both its inputs. Setting one input to 1 is easy, since the gate's input is tied to one of the machine's primary inputs. (If there were combinational logic between  $i_1$  and the NAND gate's input, finding the proper stimulus would be hard, but we could still apply the value directly, assuming the logic is not redundant.) The other input is more difficult, because it is fed only by logic tied to the machine's state registers. Setting the NAND gate's lower input to 1 requires driving the NOR gate's output to 0; this can be done only when the machine is in a state that has a 1 for either  $ps_0$  or  $ps_1$ . Although there

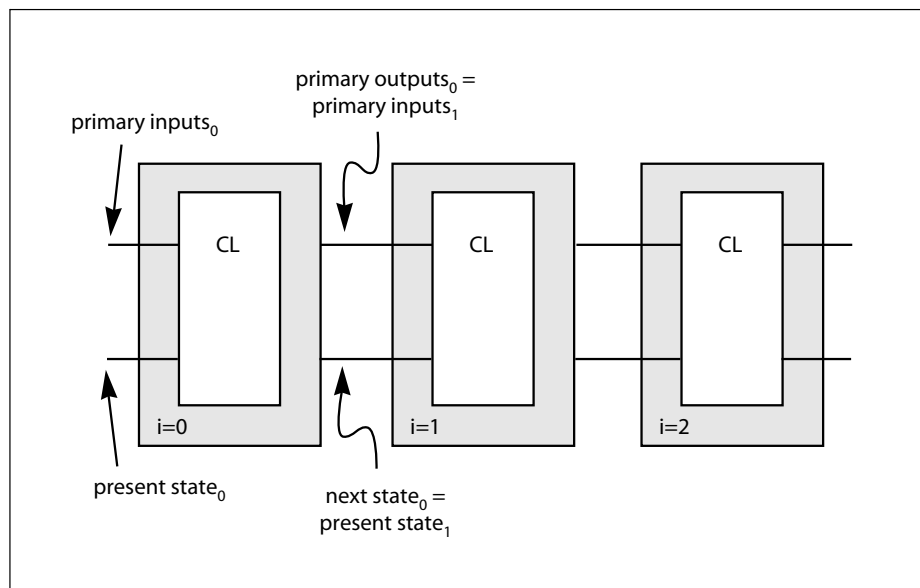


**Figure 5-48** Time-frame expansion of a sequential test.

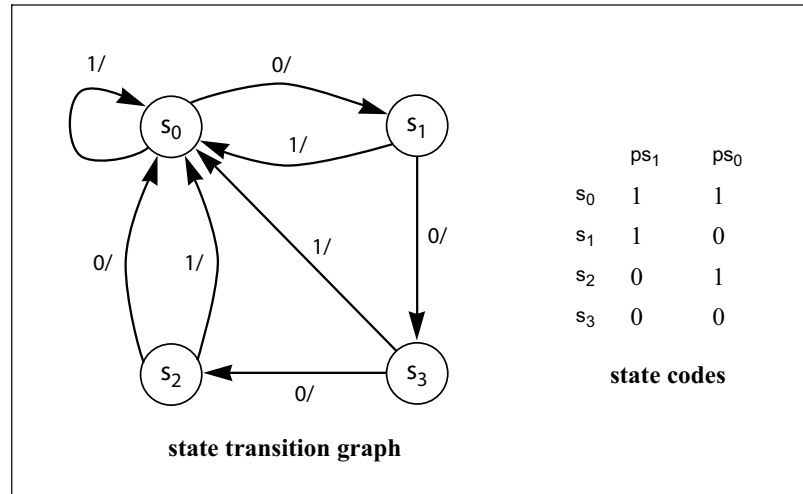may be several states that meet this criterion, getting the machine to a proper state may take several cycles. Testing a single fault in the combinational logic may take many, many cycles, meaning that testing all the faults becomes much more expensive than for purely combinational logic.

The state transition graph and state encoding for the machine of Figure 5-47 are given in Figure 5-49. Examining the state transition graph helps us understand how hard it can be to test for a fault in a sequential system. When we start the test sequence, we may not know the machine's present state. (Even if the machine is reset at power-up time, the previous test may have left it in one of several different states.) In that case, we have to find a sequence of inputs to the FSM that drive it to the desired state independent of its starting state. Since this machine has a reset input that lets us get to  $s_0$  from any state in one cycle, we can get to  $s_3$  in three cycles by the sequence  $* \rightarrow s_0 \rightarrow s_1 \rightarrow s_3$ , where  $*$  stands for any state.

**Figure 5-49** A state transition graph to test.




At this point, we can apply  $i_1 = 0$ , run the machine for one more cycle, and perform the test. Of course, some of the combinational logic's primary outputs may be connected only to the next state lines in a way that the result of the test is not visible at the primary outputs. In this case, we must run the machine for several cycles until we observe the test's outcome at the machine's primary outputs.

*states and justification*

State assignment may make it impossible to justify the required values in the machine's combinational logic. The next example illustrates the problem.

 **Example 5-7**  
**Unreachable**  
**states**

We are given this state transition graph to implement:




This machine has three states. Let's choose the state assignment  $s_0 = 00$ ,  $s_1 = 01$ ,  $s_2 = 10$ . Since this state code has two bits, our implementation will actually have *four* states. However, let's ignore this complication for the moment and design the machine's combinational logic taking into account only the states specified in the state transition graph. The truth table for the encoded machine is:

i	$S_1 S_0$	$N_1 N_0$
0	00	01
1	00	00
0	01	10
1	01	00
0	10	00
1	10	00

The equations for the next-state logic are  $N_1 = i'S_1'S_0$ ,  $N_0 = i'S_1'S_0'$ . This next-state logic creates transitions for the remaining state code, 11.

 When we use this combinational logic, the state transition graph of the machine we actually implement is this:



If the machine happens to start in state 11 at power-up, we can apply an input to get it to one of the specified states, but there is no way to get the machine from any of our specified states to the 11 state. If any part of the machine, such as the output logic, requires the present state to be 11 to test for a fault, we can't test for that fault. A **strongly connected** state transition graph has a path from any state to any other state. A reset signal goes a long way to making a state transition graph strongly connected and more easily testable.

#### *multiple-fault behavior*


To make sequential testing even more difficult, a single fault in the logic can mimic a multiple fault. **Time-frame expansion**, illustrated in Figure 5-48, helps us understand this phenomenon. A sequential test can be analyzed by unrolling the hardware over time: one copy of the hardware is made for each cycle; the copies are connected so that the next state outputs at time  $t$  are fed to the present state inputs of the time  $t+1$  frame. Time-frame expansion helps us visualize the justification and propagation of the fault over several cycles.

Copying the combinational logic clearly illustrates how a single fault mimics multiple-fault behavior in a sequential test. Each time-frame will have its own copy of the fault. Over several cycles, the faulty gate can block its own detection or observation. Any test sequence must work around the fault under test on every cycle. Test generation programs can help create test vector suites for a machine. But, given the inherent difficulty of testing, we cannot expect miracles. Proper design is the only way to ensure that tests can be found. The chip must be



designed so that all logic is made accessible enough that faults can be exercised and the results of a combinational test can be propagated to the pins. Many design-for-testability techniques take advantage of particularities of the component or system being designed; others impose a structure on the system.

**Figure 5-50** A level-sensitive scan design (LSSD) system.

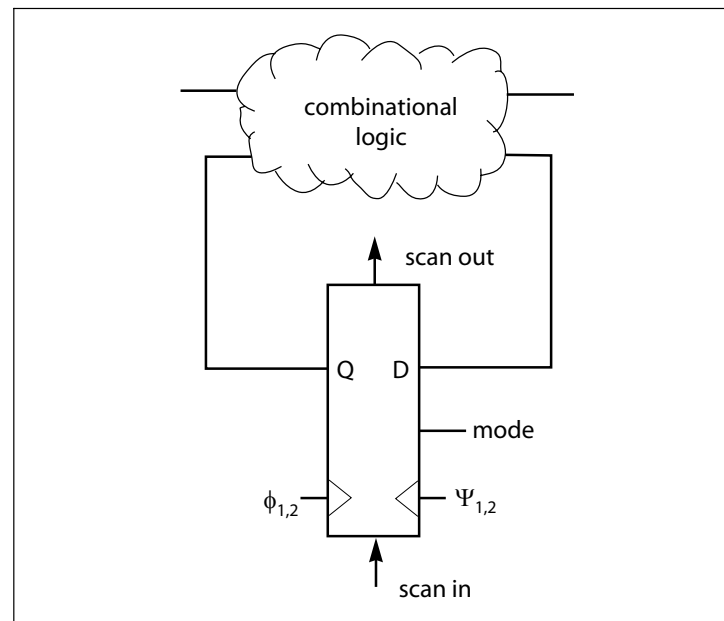


*scan design*

**Scan design** turns a sequential testing problem into combinational testing by making the present state inputs and next state outputs directly accessible. **LSSD** (level-sensitive scan design) was invented at IBM; another scan-path methodology was developed independently at NEC. An LSSD system uses special latches for memory elements, and so runs in two phases. As shown in Figure 5-50, the system has non-scan and scan modes. In non-scan mode, the latches are clocked by  $\phi_1$  and  $\phi_2$  and the system operates as any other two-phase system. In scan mode, the latches are clocked by the  $\psi_1$  and  $\psi_2$  clocks, and the latches work as a shift register. The latches are connected in a chain so that all the present state can be shifted out of the chip and the new state can be shifted in.

Figure 5-51 illustrates the logic design of an LSSD latch [Wil83]. Each LSSD latch can function as a regular latch in non-scan mode and includes latches for both scan-mode clock phases. The memory elements used as components in the scan latch are normal, non-LSSD

5.9 Sequential Testing

**Figure 5-51** The structure of an LSSD latch.

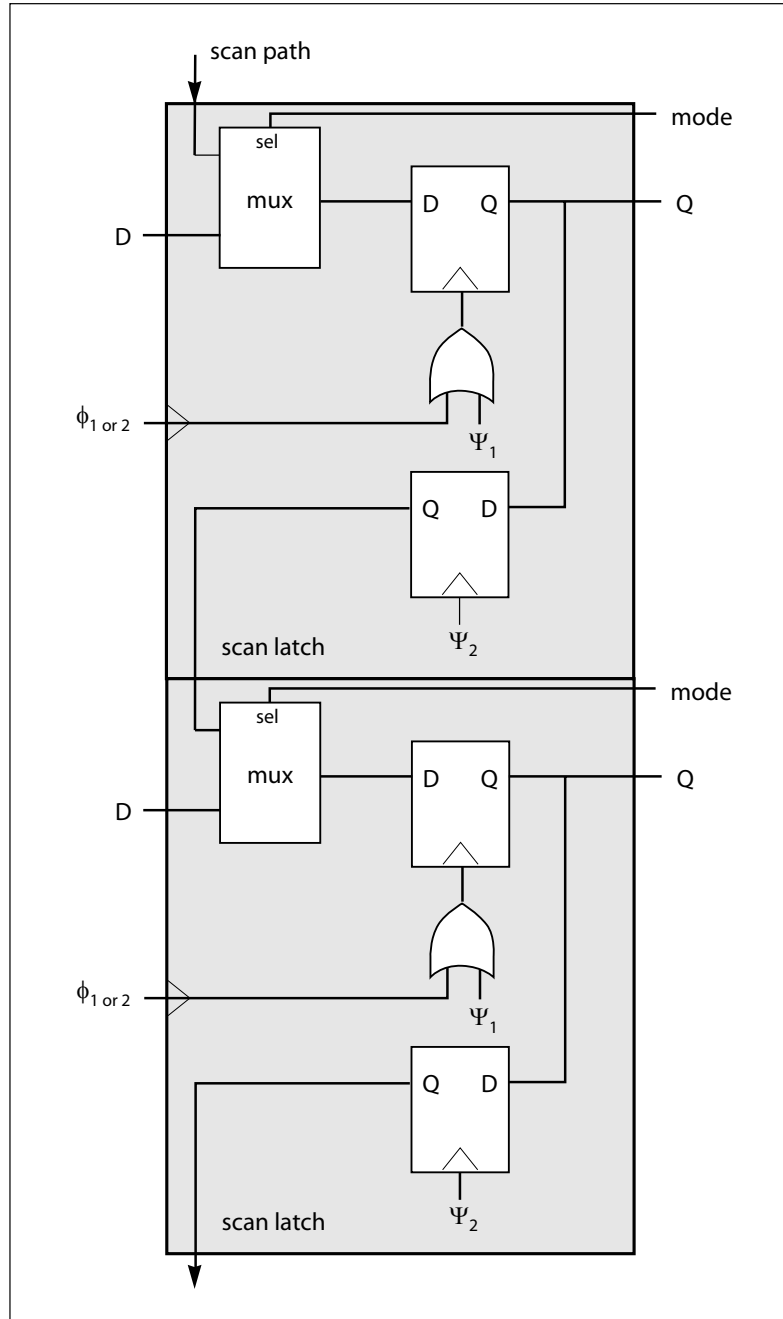

latches. The latch closest to the D input is shared by the normal and scan paths; the multiplexer at its input determines whether the value clocked into the latch is from the data input or the scan path. The second latch is used only for scan mode. The two latches together form a strict two-phase system in scan mode. This LSSD latch operates as a normal latch in non-scan mode and as a pair of latches in scan mode. The delay through this latch is slightly longer thanks to the multiplexer at the input.

---

## 5.10 References

Dietmeyer [Die78] gives the most comprehensive and well-structured survey of memory elements. The Mississippi State University (MSU) Cell Library [MSU89] contains combinational logic, latch, and flip-flop designs. The traffic light controller machine was originally presented in books by Unger [Ung69] and Mead and Conway [Mea80]. The “01”-string recognizer machine was developed at Stanford by Prof. Robert Mathews. The two-phase clocking discipline for latches was introduced in David Noice *et al.* [Noi82].


---

## 5.11 Problems


- Q5-1. Draw a stick diagram for a two-input dynamic mux latch.
- Q5-2. Draw a stick diagram for a D-latch built from clocked inverters.
- 
-

Q5-3. Which of these state machines is a Mealy machine? Explain.

a)

 

b)

 


Q5-4. Show the clocking types for all signals in a four-bit shift register, assuming that the data input to the shift register is  $s\phi_1$ .

Q5-5. If you want to connect a state machine built with flip-flops to a latch-based state machine using the clocking discipline, how much you change the flip-flop machine?

Q5-6. Modify Equation 5-2 to give the clock period constraint for a system with two combinational logic blocks separated by flip-flops.

Q5-7. Is a single-phase or a two-phase system more sensitive to clock skew? Justify your answer.

 Q5-8. You are given a clock tree of the following form:



We can connect logic to the points a, b, c, d, and e. We want to use the clock tree to drive a five-state pipeline of machines M1-M2-M3-M4-M5, with M1 as the input and M5 as the output. Given that each leg of the clock tree has a skew of 1 ps, place the machines M1-M5 at points a, b, c, d, and e to equalize clock skews.

Q5-9. Draw a block diagram for an eight-bit shift register built from two four-bit shift registers, which is in turn built from one-bit shift registers.

Q5-10. Draw a state transition graph for a simple combination lock. The lock machine has ten inputs 0-9 plus a reset input. The combination is entered as a sequence of three values to the ten numeric inputs; the reset input can be used to start over. When the correct combination (use 345 as the combination for this example) is found, the open output is asserted.

Q5-11. Draw state transition graphs that repeatedly executes these function, assuming that each statement requires one clock cycle to execute:

```

a)
  if (c)
    a <= c and d;
  else
    d <= e or f;
  end;
  
```

## 5.11 Problems

343

```
b)
w <= a or b;
if (c)
    x <= a and c;
else
    x <= b or c;
end;
```

```
c)
w <= a or b;
if (c)
    x <= a and c;
    y <= b or d;
else
    x <= b or c;
end;
```

Q5-12. How many different state assignments are possible for a machine with 4 states? With 16 states?

Q5-13. How many inputs are required to exhaustively simulate a state machine with two primary inputs and four states?

Q5-14. Draw a block diagram for a four-bit counter with an LSSD scan chain.

---

---



# 6

## Subsystem Design

### Highlights:

Pipelines and data paths.

Adders.

Multipliers.

Memory.

PLAs.

FPGAs.

Image sensors.


Buses and networks-on-chips.

Standards for IP.

---

---



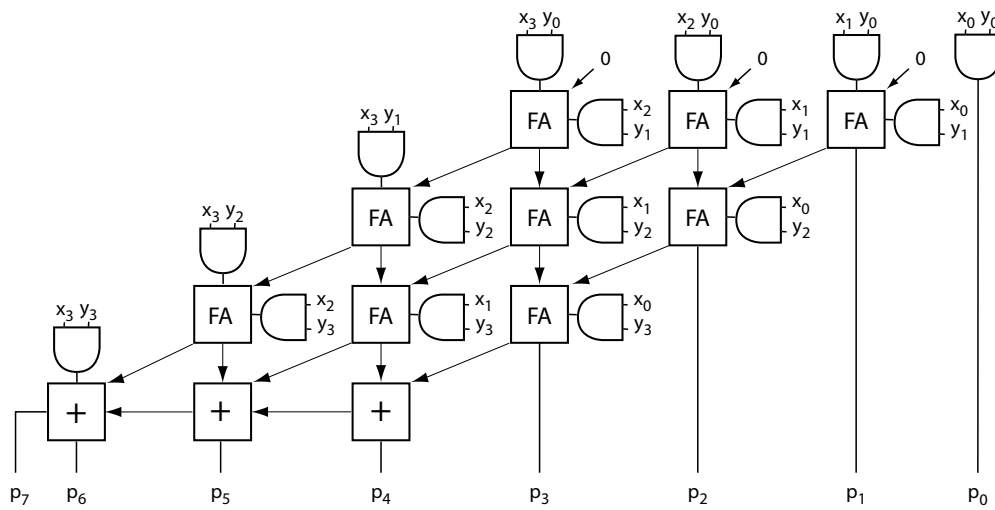

Structure of an array multiplier (Figure 6-12).

---

## 6.1 Introduction

---

### *chips and their subsystems*

Most chips are built from a collection of subsystems: adders, register files, state machines, etc. Of course, to do a good job of designing a chip, we must be able to properly design each of the major components. Studying individual subsystems is also a useful prelude to the study of complete chips because a single component is a focused design problem. When designing a complete chip, such as the HP 7200 CPU shown in Figure 6-1, we often have to perform several different types of computation, each with different cost constraints. A single component, on the other hand, performs a single task; as a result, the design choices are much more clear.

### *subsystem optimization*


As always, the cost of a design is measured in area, delay, and power. For most components, we have a family of designs that all perform the same basic function, but with different area/delay trade-offs. Having access to a variety of ways to implement a function gives us architectural freedom during chip design. Area and delay costs can be reduced by optimization at each level of abstraction:

- **Layout.** We can make microscopic changes to the layout to reduce parasitics: moving wires to pack the layout or to reduce source/drain capacitance, adding vias to reduce resistance, etc. We can also make macroscopic changes by changing the placement of gates, which may reduce wire parasitics, reduce routing congestion, or both.
- **Circuit.** Transistor sizing is the first line of defense against circuits that inherently require long wires. Advanced logic circuits, such as precharged gates, may help reduce the delay within logic gates.
- **Logic.** As we saw in Chapter 3, redesigning the logic to reduce the gate depth from input to output can greatly reduce delay, though usually at the cost of area.
- **Register-transfer and above.** Proper placement of memory elements makes maximum use of the available clock period. Proper encoding of signals allows clever logic designs that minimize logic delay. Pipelining provides trade-offs between clock period and latency.

While it may be tempting to optimize a design by hacking on the layout, that is actually the least effective way to achieve your desired area/delay design point. If you choose to make a circuit faster by tweaking the layout and you fail, all that layout work must be thrown out when you try a new circuit or logic design. On the other hand, changing the register-

---

---

 

**Figure 6-1** The HP 7200 CPU. (© Copyright 1996 Hewlett-Packard Company. Reproduced with permission.)

transfer design does not preclude further work to fine-tune area or performance. The gains you can achieve by modifications within a level of abstraction grow as you move up the abstraction hierarchy: layout modifications typically give 10%–20% performance improvement; logic redesign can cut delay by more than 20%; we will see how the register-transfer modifications that transform a standard multiplier into a Booth multiplier can cut the multiplier’s delay in half. Furthermore, layout improvements take the most work—speeding up a circuit usually requires modifying many rectangles, while the architecture can be easily changed by redrawing the block diagram. You are best off pursuing the largest gains first, at the highest levels of abstraction, and doing fine-tuning at lower levels of abstraction only when necessary.

Logic and circuit design are at the core of subsystem design. Many important components, foremost being the adder, have been so extensively studied that specific optimizations and trade-offs are well understood. However, there are some general principles that can be applied to subsystems. We will first survey some important design concepts, then delve into the details of several common types of subsystem-level components.

We will start with a description of several logical and arithmetic operators: shifters in Section 6.2, adders in Section 6.3, ALUs in Section 6.4, and multipliers in Section 6.5. We will then move onto memories in Section 6.6 and image sensors in Section 6.7, which bear a striking resemblance to memory arrays. We will then discuss two types of structured logic: field-programmable gate arrays in Section 6.8 and programmable logic arrays in Section 6.9. We will then consider buses and networks-on-chips in detail in Section 6.10. We will close with a discussion of data path design in Section 6.11. Section 6.12 describes some standards for IP specification and implementation that are useful when building subsystem-level IP.

---

## 6.2 Combinational Shifters

---

### *shifters*


A **shifter** is most useful for arithmetic operations since shifting is equivalent to multiplication by powers of two. Shifting is necessary, for example, during floating-point arithmetic. The simplest shifter is the shift register, which can shift by one position per clock cycle. However, that machine isn’t very useful for most arithmetic operations—we gen-

---

---

erally need to shift several bits in one cycle and to vary the length of the shifts.

**Figure 6-2** How a barrel shifter performs shifts and rotates.

 

*barrel shifter*

A **barrel shifter** [Mea80] can perform  $n$ -bit shifts in a single combinational function, and it has a very efficient layout. It can rotate and extend signs as well. Its architecture is shown in Figure 6-2. The barrel shifter accepts  $2n$  data bits and  $n$  control signals and produces  $n$  output bits. It shifts by transmitting an  $n$ -bit slice of the  $2n$  data bits to the outputs. The position of the transmitted slice is determined by the control bits; the exact operation is determined by the values placed at the data inputs. Consider two examples:


- Send a data word  $d$  into the top input and a word of all zeroes into the bottom input. The output is a right shift (imagine standing at the output looking into the barrel shifter) with zero fill. Setting the control bits to select the top-most  $n$  bits is a shift of zero, while selecting the bottom-most  $n$  bits is an  $n$ -bit shift that pushes the entire word out of the shifter. We can shift with a ones fill by sending an all-ones word to the bottom input.
- Send the same data word into both the top and bottom inputs. The result is a rotate operation—shifting out the top bits of a word causes those bits to reappear at the bottom of the output.

How can we build a circuit that can select an arbitrary  $n$  bits and how do we do it in a reasonably sized layout? A barrel shifter with  $n$  output bits is built from a  $2n$  vertical by  $n$  horizontal array of cells, each of which has a single transistor and a few wires. The schematic for a small group of contiguous cells is shown in Figure 6-3. The core of the cell is a transmission gate built from a single n-type transistor; a complementary transmission gate would require too much area for the tubs. The control lines run vertically; the input data run diagonally upward through the system; the output data run horizontally. The control line values are set so that exactly one is 1, which turns on all the transmission gates in a single column. The transmission gates connect the diagonal input wires to the horizontal output wires; when a column is turned on, all the inputs

6.2 Combinational Shifters

351

**Figure 6-3** A section of the barrel shifter.

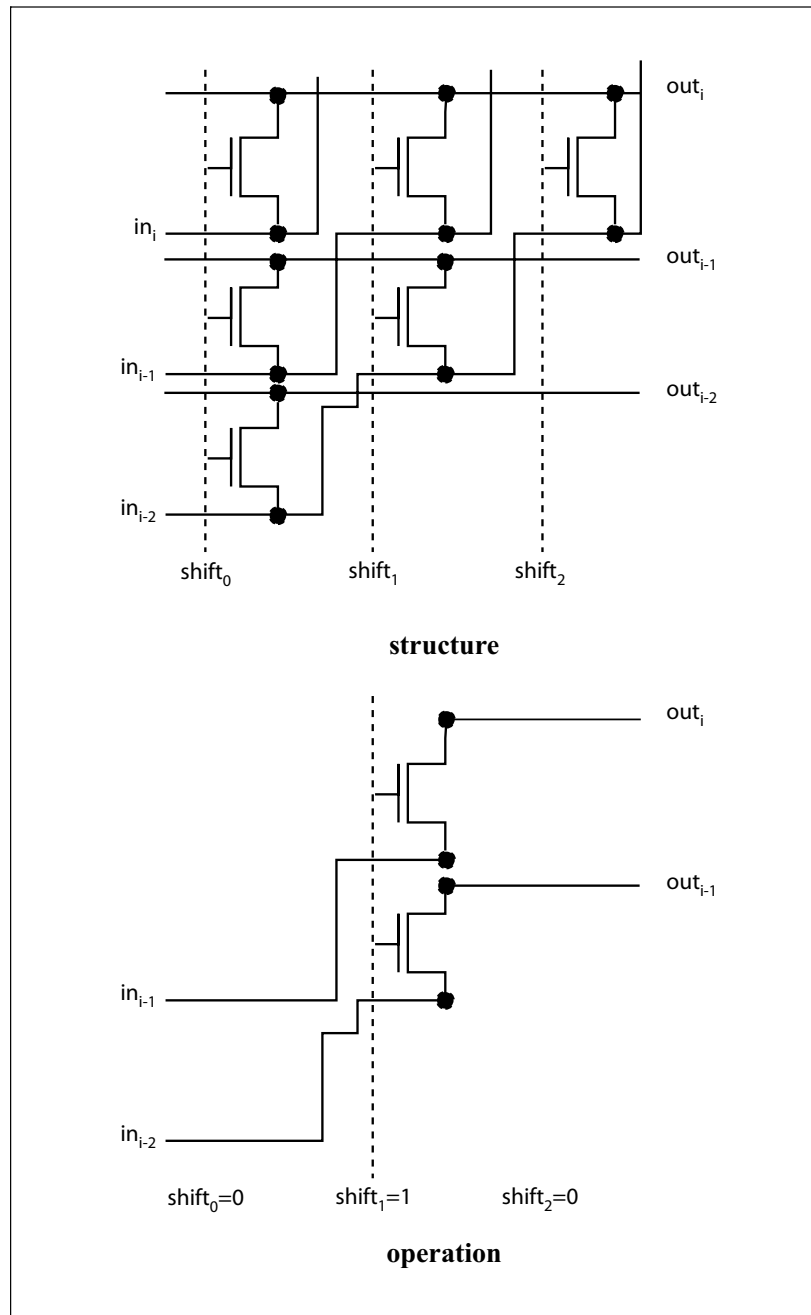

are shunted to the outputs. The length of the shift is determined by the position of the selected column—the farther to the right it is, the greater the distance the input bits have travelled upward before being shunted to the output.

Note that, while this circuit has many transmission gates, each signal must traverse only one transmission gate. The delay cost of the barrel shifter is largely determined by the parasitic capacitances on the wires, which is the reason for squeezing the size of the basic cell as much as possible. In this case, area and delay savings go hand-in-hand.

### 6.3 Adders

---

The adder is probably the most studied digital circuit. There are a great many ways to perform binary addition, each with its own area/delay trade-offs. A great many tricks have been used to speed up addition: encoding, replication of common factors, and precharging are just some of them. The origins of some of these methods are lost in the mists of antiquity. Since advanced circuits are used in conjunction with advanced logic, we need to study some higher-level addition methods before covering circuits for addition.

*full adder*

The basic adder is known as a **full adder**. It computes a one-bit sum and carry from two addends and a carry-in. The equations for the full adder's functions are simple:

$$\begin{aligned} s_i &= a_i \oplus b_i \oplus c_i \\ c_{i+1} &= a_i b_i + a_i c_i + b_i c_i \end{aligned} \quad \text{(EQ 6-1)}$$

In these formulas,  $s_i$  is the sum at the  $i^{\text{th}}$  stage and  $c_{i+1}$  is the carry out of the  $i^{\text{th}}$  stage.

*ripple-carry adder*

The  $n$ -bit adder built from  $n$  one-bit full adders is known as a **ripple-carry adder** because of the way the carry is computed. The addition is not complete until the  $n-1^{\text{th}}$  adder has computed its  $s_{n-1}$  output; that result depends on  $c_i$  input, and so on down the line, so the critical delay path goes from the 0-bit inputs up through the  $c_i$ 's to the  $n-1$  bit. (We can find the critical path through the  $n$ -bit adder without knowing the exact logic in the full adder because the delay through the  $n$ -bit carry chain is so much longer than the delay from  $a$  and  $b$  to  $s$ .) The ripple-carry adder is area efficient and easy to design but is slow when  $n$  is large.

---

*carry-lookahead adder*

Speeding up the adder requires speeding up the carry chain. The **carry-lookahead adder** is one way to speed up the carry computation. Carry-lookahead adders are not often used in VLSI but they illustrate some important principles that are used in many other adders. The carry-lookahead adder breaks the carry computation into two steps, starting with the computation of two intermediate values. The adder inputs are once again the  $a_i$ 's and  $b_i$ 's; from these inputs,  $P$  (propagate) and  $G$  (generate) are computed:

$$\begin{aligned} P_i &= a_i + b_i \\ G_i &= a_i \cdot b_i \end{aligned} \quad \text{(EQ 6-2)}$$

If  $G_i = 1$ , there is definitely a carry out of the  $i^{\text{th}}$  bit of the sum—a carry is generated. If  $P_i = 1$ , then the carry from the  $(i-1)^{\text{th}}$  bit is propagated to the next bit. The sum and carry equation for the full adder can be rewritten in terms of  $P$  and  $G$ :

$$\begin{aligned} s_i &= c_i \oplus P_i \oplus G_i \\ c_{i+1} &= G_i + P_i c_i \end{aligned} \quad \text{(EQ 6-3)}$$

The carry formula is smaller when written in terms of  $P$  and  $G$ , and therefore easier to recursively expand:


$$\begin{aligned} c_{i+1} &= G_i + P_i \cdot (G_{i-1} + P_{i-1} \cdot c_{i-1}) \\ &= G_i + P_i G_{i-1} + P_i P_{i-1} \cdot (G_{i-2} + P_{i-2} \cdot c_{i-2}) \\ &= G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + P_i P_{i-1} P_{i-2} c_{i-2} \end{aligned} \quad \text{(EQ 6-4)}$$

The  $c_{i+1}$  formula of Equation 6-4 depends on  $c_{i-2}$ , but not  $c_i$  or  $c_{i-1}$ . After rewriting the formula to eliminate  $c_i$  and  $c_{i-1}$ , we used the speedup trick of Section 4.3—we eliminated parentheses, which substitutes larger gates for long chains of gates. There is a limit beyond which the larger gates are slower than chains of smaller gates; typically, four levels of carry can be usefully expanded.


A depth-4 carry-lookahead unit is shown in Figure 6-4. The unit takes the  $P$  and  $G$  values from its four associated adders and computes four carry values. Each carry output is computed by its own logic. The logic for  $c_{i+3}$  is slower than that for  $c_i$ , but the flattened  $c_{i+3}$  logic is faster than the equivalent ripple-carry logic.



There are two ways to hook together depth- $b$  carry-lookahead units to build an  $n$ -bit adder. The carry-lookahead units can be recursively connected to form a tree: each unit generates its own  $P$  and  $G$  values, which are used to feed the carry-lookahead unit at the next level of the tree. A simpler scheme is to connect the carry-ins and carry-outs of the units in a ripple chain. This approach is most common in chip design because the wiring for the carry-lookahead tree is hard to design and area-consuming.

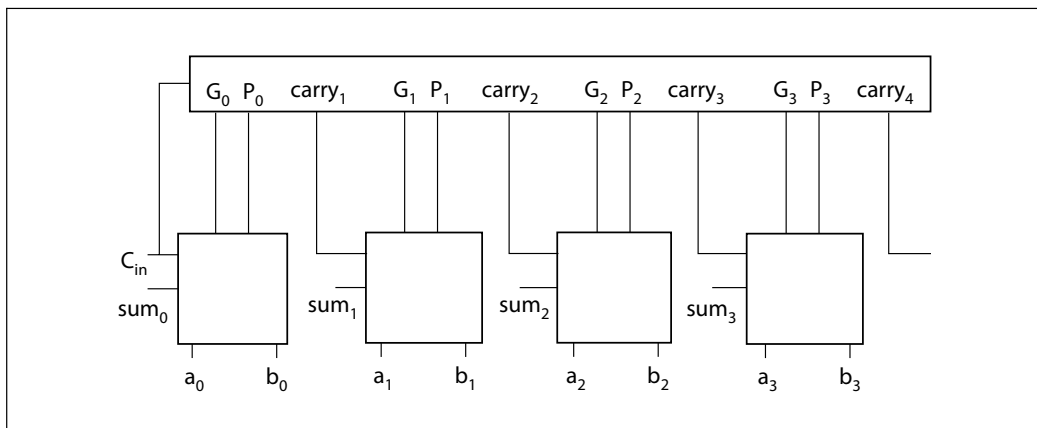

**Figure 6-4** Structure of a carry lookahead adder.

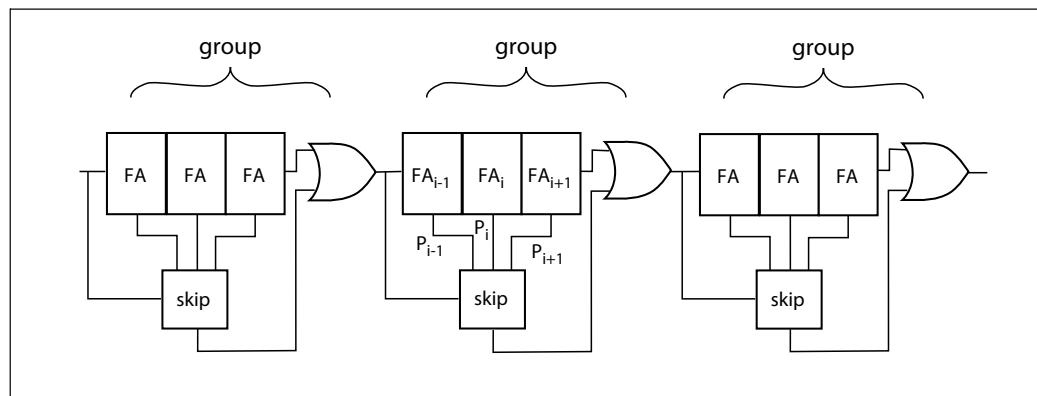

**Figure 6-5** The carry chain in a carry-skip adder.

*carry-skip adder*

The **carry-skip adder** [Leh61] looks for cases in which the carry out of a set of bits is the same as the carry in to those bits. This adder makes a different use of the carry-propagate relationship. As illustrated in Figure 6-5, a carry-skip adder is typically organized into  $m$ -bit *groups*; if the carry is propagated for every bit in the stage, then a bypass gate sends the stage's carry input directly to the carry output. The structure of the carry chain for a carry-skip adder divided into groups of bits is shown in Figure 6-7. A true carry into the group and true propagate condition  $P$  at every bit in the group is needed to cause the carry to skip.

It is possible to determine the optimum number of bits in a group [Kor93]. The worst case for the carry signal occurs when there is a carry propagated through every bit, but in this case  $P_i$  will be true at every bit. Therefore, the longest path for the carry begins when the carry is generated at the bottom bit of the bottom group (rippling through the remainder of the group), is skipped past the intermediate groups, and ripples through the last group; the carry must necessarily ripple through the first and last groups to compute the sum. Using some simple assumptions about the relative delays for a ripple through a group and skip, Koren estimates the optimum group size for an  $n$ -bit word as


$$k_{\text{opt}} = \sqrt{n/2}. \quad (\text{EQ 6-5})$$

Since the carry must ripple through the first and last stages, the adder can be further speeded up by making the first and last groups shorter than this length and by lengthening the middle groups.

*carry-select adder*

The **carry-select adder**, shown in Figure 6-7, computes two versions of the addition with different carry-ins, then selects the right one. As with the carry-skip adder, the carry-select adder is typically divided into  $m$ -bit stages. The second stage computes two values: one assuming that the carry-in is 0 and another assuming that it is 1. Each of these candidate results can be computed by your favorite adder structure. The carry-out of the previous stage is used to select which version is correct: multiplexers controlled by the previous stage's carry-out choose the correct sum and carry-out. This scheme speeds up the addition because the  $i^{\text{th}}$  stage can be computing the two versions of the sum in parallel with the  $(i-1)^{\text{th}}$ 's computation of its carry. Once the carry-out is available, the  $i^{\text{th}}$  stage's delay is limited to that of a two-input multiplexer.

No matter what style of circuit is used for the carry chain, we can size transistors to reduce the carry chain delay to some extent by increasing transistor sizes. In a carry-lookahead adder, the carry-in signal is of medium complexity; depending on the exact logic implementation,

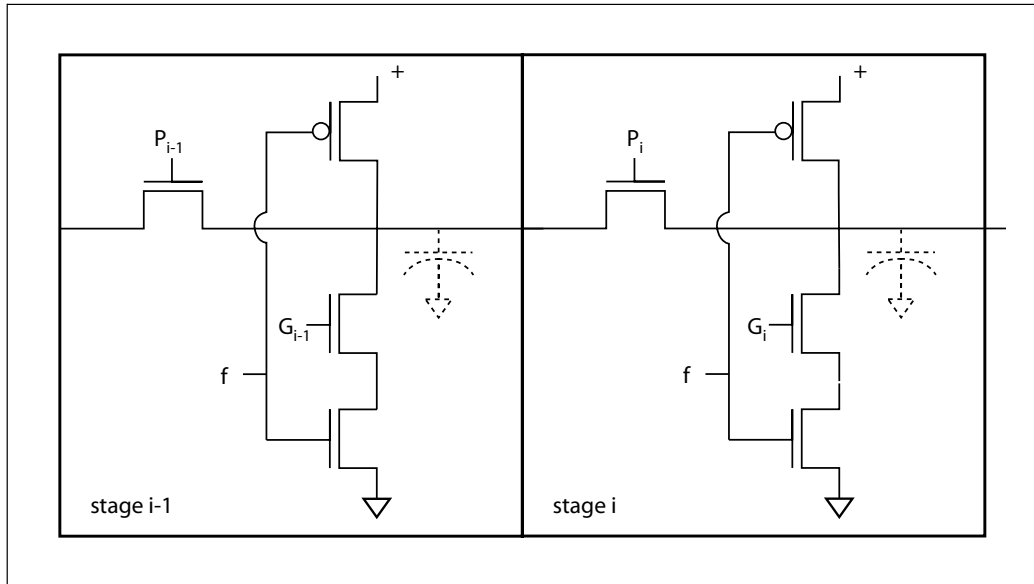


**Figure 6-6** A Manchester carry chain.

either  $P$  or  $G$  will be most critical, with the other signal being less critical than carry-in. At the adder's high-order bits, the non-carry outputs of the carry chain also become critical, requiring larger transistors; otherwise, the stages of an optimally-sized adder are identical.

*Manchester carry chain*

Precharged circuits are an obvious way to speed up the carry chain. One of the most interesting precharged adders is the **Manchester carry chain** [Mea80], which computes the sum from  $P$  and  $G$ . Two bits of a Manchester carry chain are shown in Figure 6-6. The storage node, which holds the complement of the carry ( $c_i'$ ), is charged to 1 during the precharge phase. If  $G_i = 1$  during the evaluate phase, the storage node is discharged, producing a carry into the next stage. If  $P_i = 1$ , then the  $i^{th}$  storage node is connected to the  $(i-1)^{th}$  storage node; in this case, the  $i^{th}$  storage node can be discharged by the  $P_{i-1}$  pulldown or, if the  $C_{i-1}$  trans-

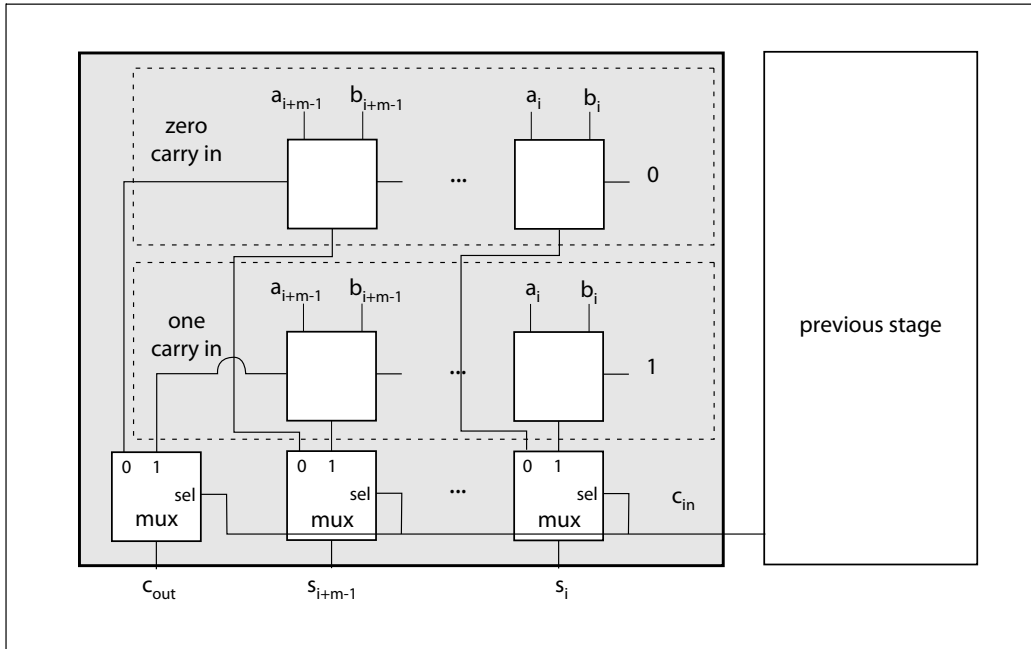


**Figure 6-7** The carry-select adder.

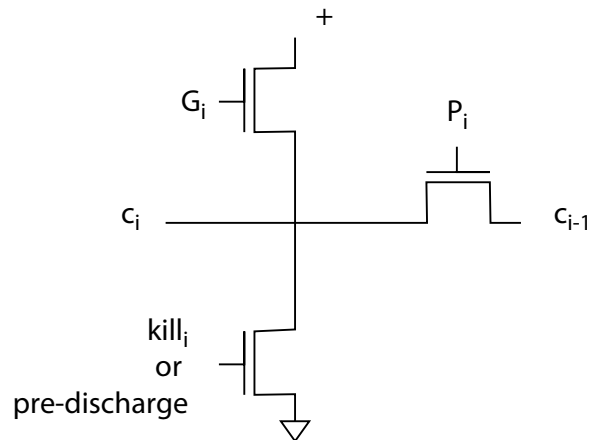mission gate is on, by a preceding  $P$  pulldown. In the worst case, the  $n$ - $1$ <sup>th</sup> storage node will be discharged through the 0<sup>th</sup> pulldown and through  $n$  transmission gates, but in the typical case, the pulldown path for a storage node is much shorter. The widest transistors should be at the least-significant bit stage since they see the largest load. The next example describes the use of a Manchester carry chain in a high-performance microprocessor.

### Example 6-1 Carry chain of the DEC Alpha 21064 microprocessor

The first DEC Alpha microprocessor, the 21064, used a Manchester carry chain [Dob92]. That processor had a 64-bit word with the carry chain organized into groups of 8 bits to enable byte-wise operation. The carry circuit at each stage was made entirely of n-type devices:



The carry chain uses carry propagate, generate, and kill signals. The chain is pre-discharged and then selectively charged using the n-type pullups. Pre-discharging was used to avoid the threshold drop on the carry signal introduced by precharging through an n-type device; precharging to  $V_{DD} - V_t$  was deemed to provide unacceptable noise margins. The pass transistors for the carry were sized with the largest transistors at the least-significant bit.


Each group of eight bits was organized into a 32-bit carry-select, and a logarithmic carry-select technique was used to generate the 64-bit sum. As a result, there were two carry chains in each 8-bit group: one for the zero-carry-in case and another for the one-carry-in case.

#### *serial adder*

**Serial adders** present an entirely different approach to high-speed arithmetic—they require many clock cycles to add two  $n$ -bit numbers, but with a very short cycle time. Serial adders can work on nybbles (4-bit words) or bytes, but the bit-serial adder [Den85], shown in Figure 6-8 is

the most extreme form. The data stream consists of three signals: the two numbers to be added and an LSB signal that is high when the current data bits are the least significant bits of the addends. The addends appear LSB first and can be of arbitrary length—the end of a pair of numbers is signaled by the LSB bit for the next pair. The adder itself is simply a full adder with a memory element for the carry. The LSB signal clears the carry register. Subsequently, the two input bits are added with the carry-out of the last bit. The serial adder is small and has a cycle time equal to that of a single full adder.

**Figure 6-8** A bit-serial adder.

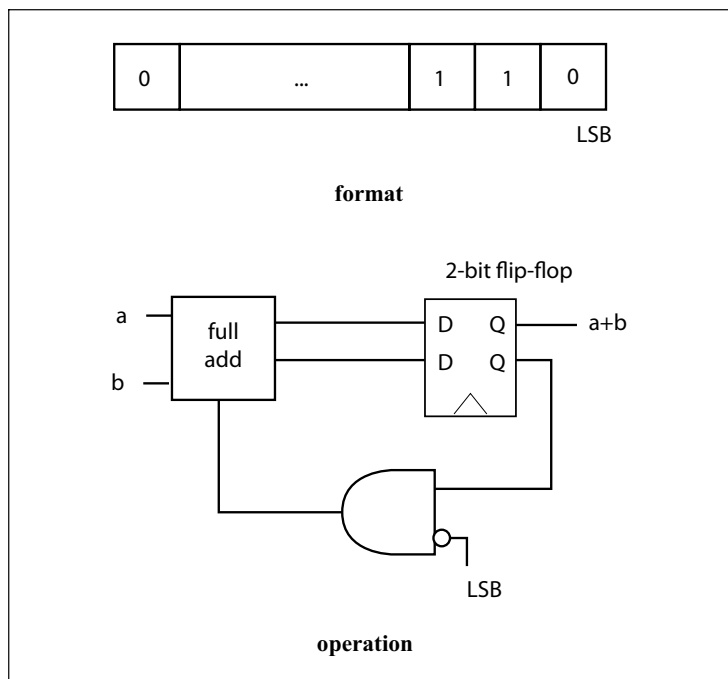

*adder power consumption*

Callaway and Schwartzlander [Cal96] evaluated the power consumption of several types of parallel adders. They found that, in general, slower adders consume less power. The exception is the carry-skip adder, which uses less current than the ripple-carry adder because, although it consumes a higher peak current, the current falls to zero very quickly.

## 6.4 ALUs


### *ALUs as modified adders*

The **arithmetic logic unit**, or **ALU**, is a modified adder. While an ALU can perform both arithmetic and bit-wise logical operations, the arithmetic operations' requirements dominate the design.

### *ALU opcodes*

A basic ALU takes two data inputs and a set of control signals, also called an **opcode**. The opcode, together with the ALU's carry-in, determine the ALU's function. For example, if the ALU is set to add, then  $c_0 = 0$  produces  $a+b$  while  $c_0 = 1$  produces  $a+b+1$ .

**Figure 6-9** A mux-based ALU.

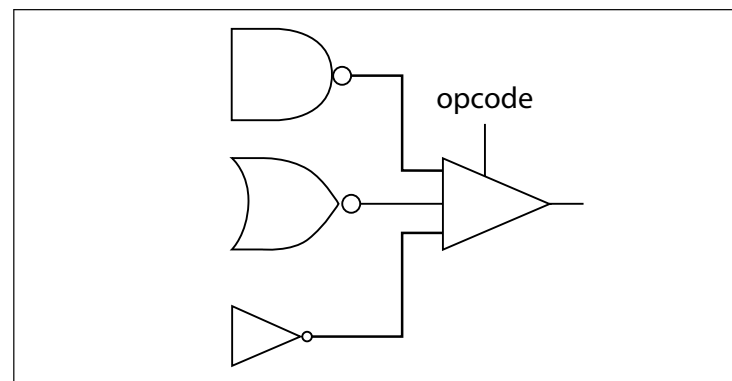

### *mux-based ALUs*


A basic ALU can be built using a multiplexer—a set of gates implements each possible function in the ALU and the multiplexer selects the one that is needed. Figure 6-9 shows an ALU that performs AND, OR, and NOT functions. The select input to the multiplexer serves as the opcode input for the ALU.

## 6.5 Multipliers

### *digit-by-digit multiplication*

Multiplier design starts with the elementary school algorithm for multiplication. Consider the simple example of Figure 6-10. At each step, we multiply one digit of the multiplier by the full multiplicand; we add the result, shifted by the proper number of bits, to the partial product. When we run out of multiplier digits, we are done. Single-digit multiplication is easy for binary numbers—binary multiplication of two bits is performed by the AND function. The computation of partial products and

**Figure 6-10** Multiplication using the elementary school algorithm.

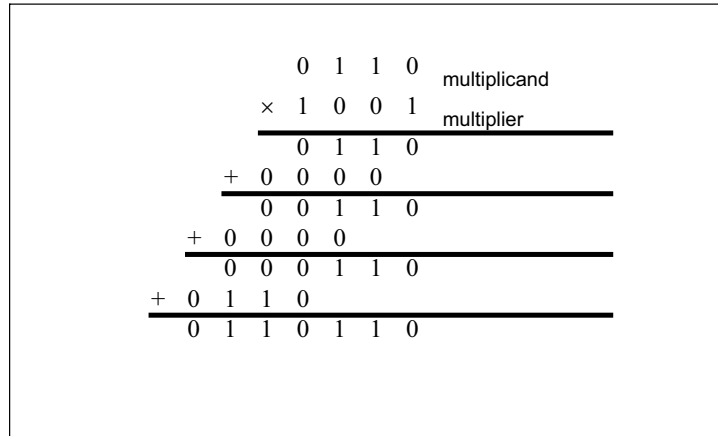

their accumulation into the complete product can be optimized in many ways, but an understanding of the basic steps in multiplication is important to a full appreciation of those improvements.

*serial-parallel multiplier*


One simple, small way to implement the basic multiplication algorithm is the **serial-parallel** multiplier of Figure 6-11, so called because the  $n$ -bit multiplier is fed in serially while the  $m$ -bit multiplicand is held in parallel during the course of the multiplication. The multiplier is fed in least-significant bit first and is followed by at least  $m$  zeroes. The result appears serially at the end of the multiplier chain. A one-bit multiplier is simply an AND gate. The sum units in the multiplier include a combinational full adder and a register to hold the carry. The chain of summation units and registers performs the shift-and-add operation—the partial product is held in the shift register chain, while the multiplicand is successively added into the partial product.

*signed multiplication*

One important complication in the development of efficient multiplier implementations is the multiplication of two's-complement signed numbers. The **Baugh-Wooley multiplier** [Bau73] is the best-known algorithm for signed multiplication because it maximizes the regularity of the multiplier logic and allows all the partial products to have positive sign bits. The multiplier  $X$  can be written in binary as

$$X = x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i2^i, \tag{EQ 6-6}$$



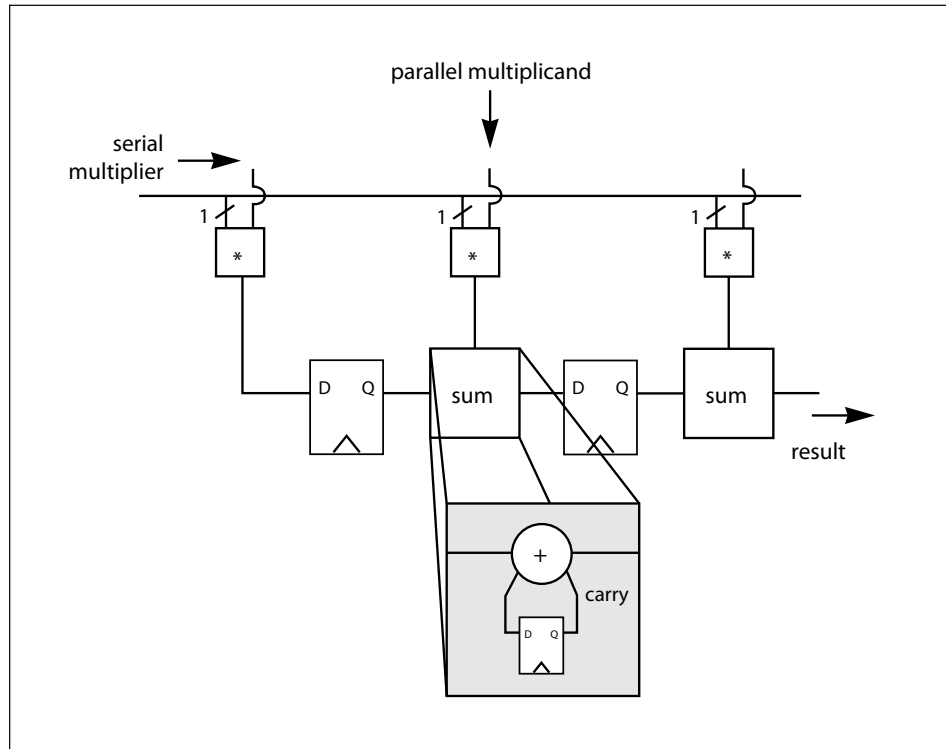

**Figure 6-11** Basic structure of a serial-parallel multiplier.

where  $n$  is the number of bits in the representation. The multiplicand  $Y$  can be written similarly. The product  $P$  can be written as

$$P = p_{2n-1}2^{2n-2} + \sum_{i=0}^{2n-2} p_i 2^i \tag{EQ 6-7}$$

When this formula is expanded to show the partial products, it can be seen that some of the partial products have negative signs:

$$P = \tag{EQ 6-8}$$

$$\left[ x_{n-1}y_{n-1}2^{2n-2} + \sum_{i=0}^{n-2} \sum_{j=0}^{n-2} x_i y_j 2^{i+j} \right] - \left[ \sum_{i=0}^{n-2} (x_{n-1}y_i + y_{n-1}x_i) 2^{n-1+i} \right]$$

The formula can be further rewritten, however, to move the negative-signed partial products to the last steps and to add the negation of the partial product rather than subtract. Further rewriting gives this final form:

$$P = 2^{n-1} \left( -2^n + 2^{n-1} + \bar{x}_{n-1} 2^{n-1} + x_{n-1} + \sum_{i=0}^{n-2} x_{n-1} \bar{y}_i 2^i \right). \quad (\text{EQ 6-9})$$

Each partial product is formed with AND functions and the partial products are all added together. The result is to push the irregularities to the end of the multiplication process and allow the early steps in the multiplication to be performed by identical stages of logic.

#### *array multiplier*


The elementary school multiplication algorithm (and the Baugh-Wooley variations for signed multiplication) suggest a logic and layout structure for a multiplier that is surprisingly well-suited to VLSI implementation—the **array multiplier**. The structure of an array multiplier for unsigned numbers is shown in Figure 6-12. The logic structure is shown in parallelogram form both to simplify the drawing of wires between stages and also to emphasize the relationship between the array and the basic multiplication steps shown in Figure 6-10. As when multiplying by hand, partial products are formed in rows and accumulated in columns, with partial products shifted by the appropriate amount. In layout, however, the  $y$  bits generally would be distributed with horizontal wires since each row uses exactly one  $y$  bit.

Notice that only the last adder in the array multiplier has a carry chain. The earlier additions are performed by full adders which are used to reduce three one-bit inputs to two one-bit outputs. Only in the last stage are all the values accumulated with carries. As a result, relatively simple adders can be used for the early stages, with a faster (and presumably larger and more power-hungry) adder reserved for the last stage. As a result, the critical delay path for the array multiplier follows the trajectory shown in Figure 6-13.

#### *Booth encoding*


One way to speed up multiplication is **Booth encoding** [Boo51], which performs several steps of the multiplication at once. Booth's algorithm takes advantage of the fact that an adder-subtractor is nearly as fast and small as a simple adder. In the elementary school algorithm, we shift the multiplicand  $x$ , then use one bit of the multiplier  $y$  if that shifted value is to be added into the partial product. The most common form of Booth's algorithm looks at three bits of the multiplier at a time to perform two stages of the multiplication.

Figure 6-12  
Structure of an  
unsigned array  
multiplier.

 

## 6.5 Multipliers

365

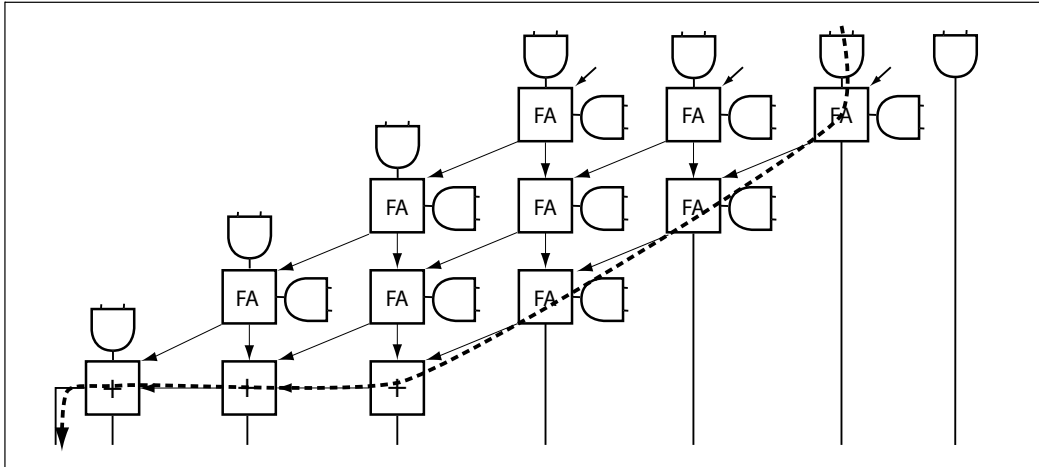

**Figure 6-13** The critical delay path in the array multiplier.

Consider once again the two's-complement representation of the multiplier  $y$ :

$$y = (-2)^n y_n + 2^{n-1} y_{n-1} + 2^{n-2} y_{n-2} + \dots \quad (\text{EQ 6-10})$$

We can take advantage of the fact that  $2^a = 2^{a+1} - 2^a$  to rewrite this as

$$y = 2^n (y_{n-1} - y_n) + 2^{n-1} (y_{n-2} - y_{n-1}) + 2^{n-2} (y_{n-3} - y_{n-2}) + \dots \quad (\text{EQ 6-11})$$

Now, extract the first two terms:

$$2^n (y_{n-1} - y_n) + 2^{n-1} (y_{n-2} - y_{n-1}) \quad (\text{EQ 6-12})$$

Each term contributes to one step of the elementary-school algorithm: the right-hand term can be used to add  $x$  to the partial product, while the left-hand term can add  $2x$ . (In fact, since  $y_{n-2}$  also appears in another term, no pair of terms exactly corresponds to a step in the elementary school algorithm. But, if we assume that the  $y$  bits to the right of the decimal point are 0, all the required terms are included in the multiplication.) If, for example,  $y_{n-1} = y_n$ , the left-hand term does not contribute to the partial product. By picking three bits of  $y$  at a time, we can determine whether to add or subtract  $x$  or  $2x$  (shifted by the proper amount, two bits per step) to the partial product. Each three-bit value overlaps

with its neighbors by one bit. Table 6-1 shows the contributing term for each three-bit code from  $y$ .

**Table 6-1** Actions during Booth multiplication.

$y_i y_{i-1} y_{i-2}$	increment
0 0 0	0
0 0 1	x
0 1 0	x
0 1 1	2x
1 0 0	-2x
1 0 1	-x
1 1 0	-x
1 1 1	0

Let's try an example to see how this works:  $x = 011001$  ( $25_{10}$ ),  $y = 101110$  ( $-18_{10}$ ). Call the  $i^{th}$  partial product  $P_i$ . At the start,  $P_0 = 00000000000$  (two six-bit numbers give an 11-bit result):

1.  $y_1y_0y_{-1} = 100$ , so  $P_1 = P_0 - (10 \cdot 011001) = 11111001110$  .
2.  $y_3y_2y_1 = 111$ , so  $P_2 = P_1 + 0 = 11111001110$  .
3.  $y_5y_4y_3 = 101$ , so  $P_3 = P_2 - 0110010000 = 11000111110$  .


In decimal,  $y_1y_0y_{-1}$  contribute  $-2x \cdot 1$ ,  $y_3y_2y_1$  contribute  $0 \cdot 4$ , and  $y_5y_4y_3$  contribute  $-x \cdot 16$ , giving a total of  $-18x$ . Since the multiplier is  $-18$ , the result is correct.

Figure 6-14 shows the detailed structure of a Booth multiplier. The multiplier bits control a multiplexer that determines what is added to or subtracted from the partial product. Booth's algorithm can be implemented in an array multiplier since the accumulation of partial products still forms the basic trapezoidal structure. In this case, a column of control bit generators on one side of the array analyzes the triplets of  $y$  bits to determine the operation in that row.

*Wallace tree*

Another way to speed up multiplication is to use more adders to speed the accumulation of partial products. The best-known method for speeding up the accumulation is the **Wallace tree** [Wal64], which is an adder tree built from **carry-save adders**, which is simply an array of full adders whose carry signals are not connected, as in the early stages of


**Figure 6-14** Structure of a Booth multiplier.

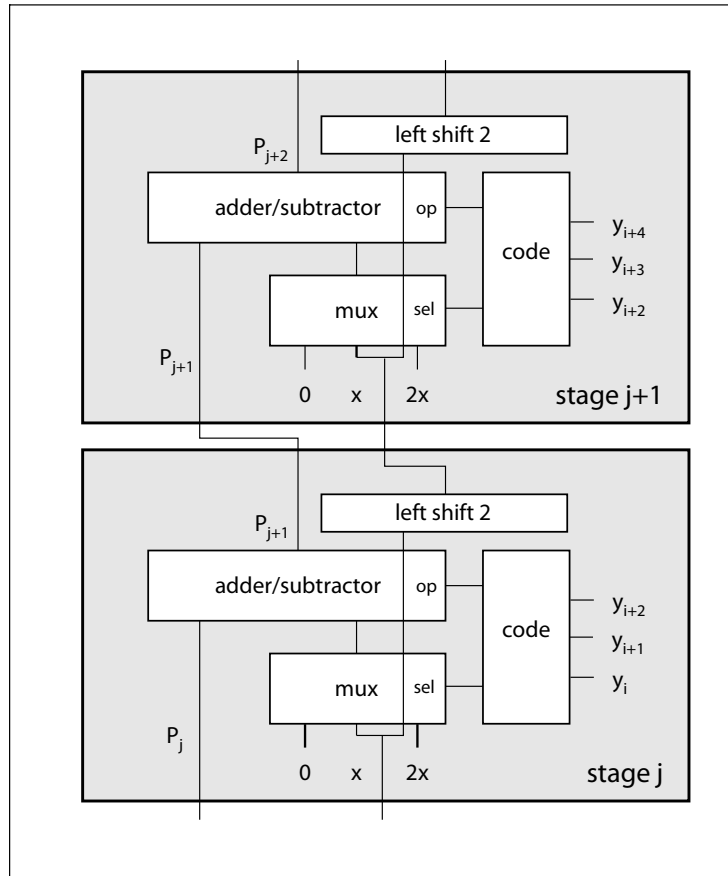

the array multiplier. A carry save adder, given three  $n$ -bit numbers  $a$ ,  $b$ ,  $c$ , computes two new numbers  $y$ ,  $z$  such that  $y + z = a + b + c$ . The Wallace tree performs the three-to-two reductions; at each level of the tree,  $i$  numbers are combined to form  $\lceil 2i/3 \rceil$  sums. When only two values are left, they are added with a high-speed adder. Figure 6-15 shows the structure of a Wallace tree. The partial products are introduced at the bottom of the tree. Each of the  $z$  outputs is shifted left by one bit since it represents the carry out.

A Wallace tree multiplier is considerably faster than a simple array multiplier because its height is logarithmic in the word size, not linear. However, in addition to the larger number of adders required, the Wallace tree's wiring is much less regular and more complicated. As a

**Figure 6-15**  
Structure of a  
Wallace tree.

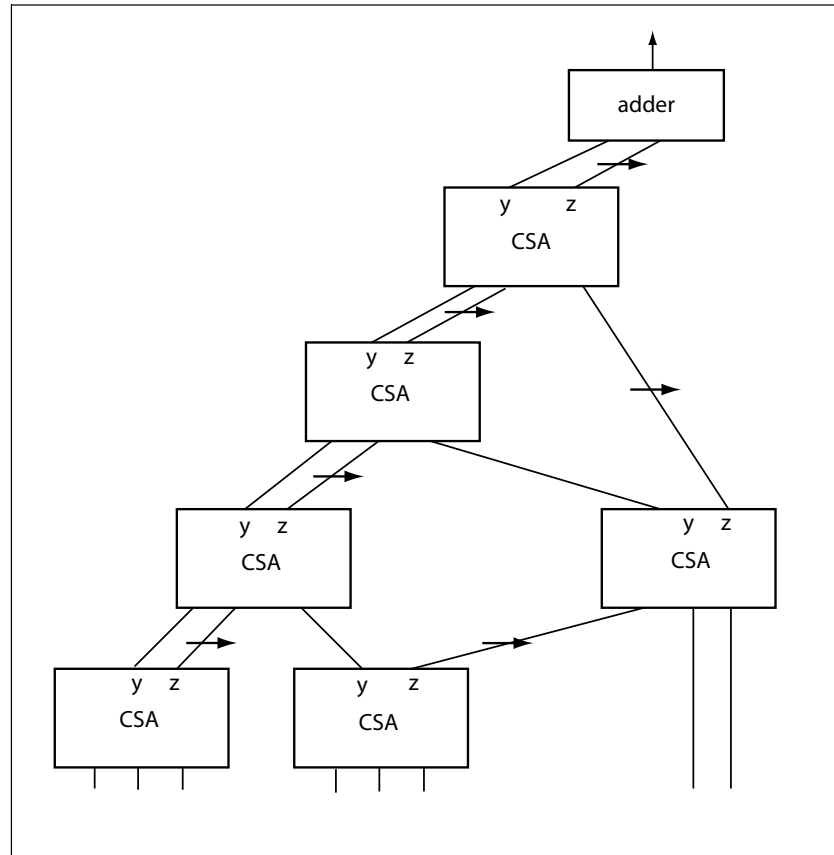

result, Wallace trees are often avoided by designers who do not have extreme demands for multiplication speed and for whom design complexity is a consideration.

Callaway and Schwartzlander [Cal96] also evaluated the power consumption of multipliers. They compared an array multiplier and a Wallace tree multiplier (both without Booth encoding) and found that the Wallace tree multiplier used significantly less power for bit widths between 8 and 32, with the advantage of the Wallace tree growing as word length increased.

---

## 6.6 High-Density Memory

---

So far, we have built memory elements out of circuits that exhibit mostly digital behavior. By taking advantage of analog design methods, we can build memories that are both smaller and faster. Memory design is usually best left to expert circuit designers; however, understanding how these memories work will help you learn how to use them in system design. On-chip memory is becoming increasingly important as levels of integration increase to allow both processors and useful amounts of memory to be integrated on a single chip [Kog95].

### *types of memory*

**Read-only memory** (ROM), as the name implies, can be read but not written. It is used to store data or program values that will not change, because it is the densest form of memory available. An increasing number of digital logic processes support **flash memory**, which is the dominant form of electrically erasable PROM memory. There are two types of read-write **random access memories**: **static** (SRAM) and **dynamic** (DRAM). SRAM and DRAM use different circuits, each of which has its own advantages: SRAM is faster but uses more power and is larger; DRAM has a smaller layout and uses less power. DRAM cells are also somewhat slower and require the dynamically stored values to be periodically refreshed, just as in a dynamic latch. Flash memory is electrically-erasable ROM with erase circuitry that is shared over large blocks.

Some types of memory are available for integration on a chip, while others that require special processes are generally used as separate chips. Commodity DRAMs are based on a one-transistor memory cell. That cell requires specialized structures, such as poly-poly capacitors, which are built using special processing steps not usually included in ASIC processes. A design that requires high-density ROM or RAM is usually partitioned into several chips, using commodity memory parts. Medium density memory, on the order of one kilobyte, can often be put on the same chip with the logic that uses it, giving faster access times, as well as greater integration. Flash is available in many logic processes at some additional cost.


A RAM or ROM is used by presenting it with an address and receiving the value stored at that address some time later. Details differ, of course: large memories often divide the address into row and column sections, which must be sent to the memory separately, for example. The simplest and safest way to use memory in a system is to treat it as a strict sequen-

---

---



**Figure 6-16** Architecture of a high-density memory system.

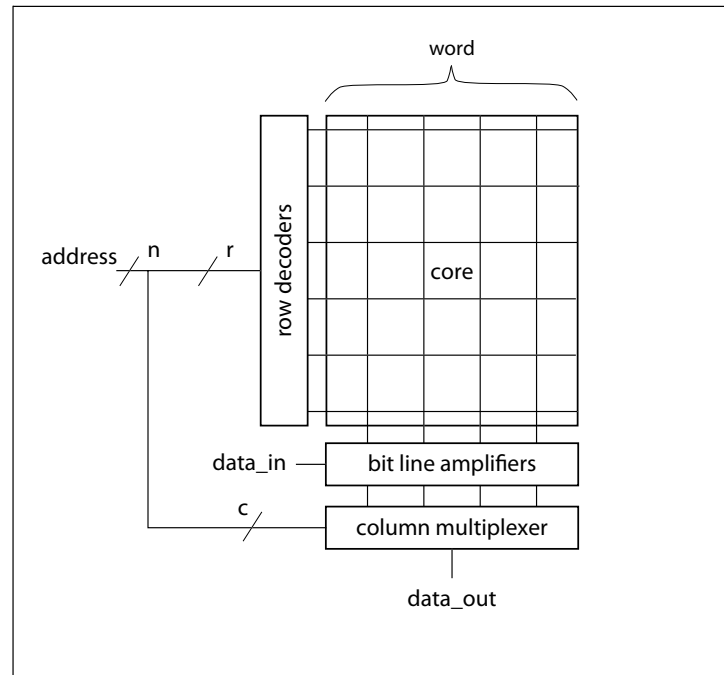

tial component: send the address to the memory on one cycle and read the value on the next cycle.



*generic memory architecture*

The architecture of a generic RAM/ROM system is shown in Figure 6-16. Think of the data stored in the memory core as being organized into  $n$  bit-wide words. The address decoders (also known as row decoders) translate the binary address into a unary address—exactly one word in the core is selected. A read is performed by having each cell in the selected word set the bit and bit' lines to the proper values: bit = 1, bit' = 0 if a 1 is stored in the array, for example. The bit lines are typically precharged, so the cell discharges one of the lines. The bit lines are read by circuits that sense the value on the line, amplify it to speed it up, and restore the signal to the proper voltage levels. A write is performed by setting the bit lines to the desired values and driving that value from the bit lines into the cell. If the core word width is narrower than the final word width (for example, a one-bit wide RAM typically has a core much wider than one bit to make a more compact layout), a multiplexer uses the bottom few bits of the address to select the desired bits out of the word.

*row decoders*

The row decoders are not very complex: they typically use NOR gates to decode the address, followed by a chain of buffers to allow the circuit to drive the large capacitance of the word line. There are two major choices for circuits to implement the NOR function: pseudo-nMOS and precharged. Pseudo-nMOS circuits are adequate for small memories, but precharged circuits offer better performance (at the expense of control circuitry) for larger memory arrays. Figure 6-17 shows a precharged row decoder; the true and complement forms of the address lines can be distributed vertically through the decoders and connected to the NOR pulldowns as appropriate for the address to be decoded at that row.

**Figure 6-17** A precharged row decoder.

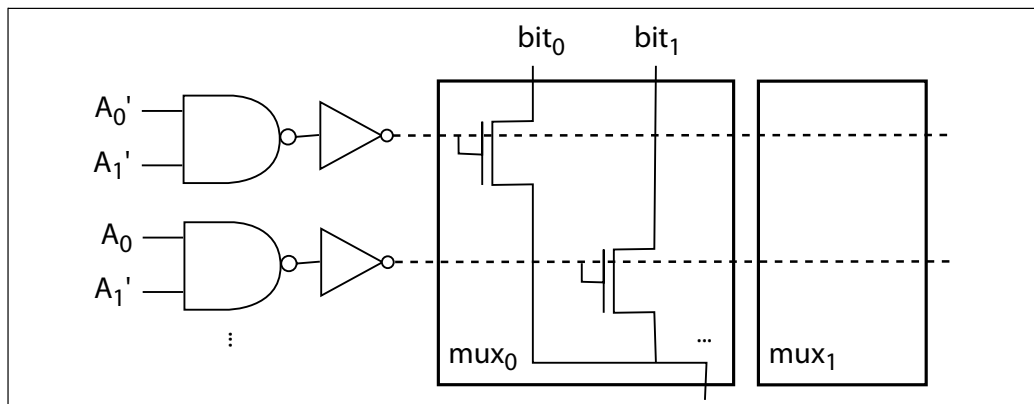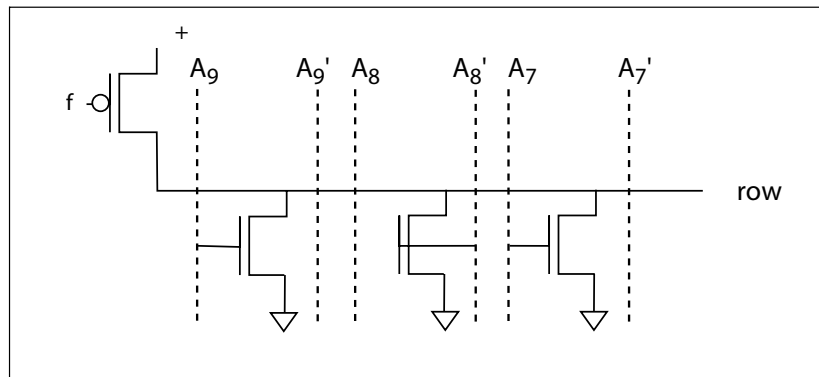


**Figure 6-18** A column decoding scheme.

*column decoders*

The column decoders are typically implemented as pass transistors on the bit lines. As shown in Figure 6-18, each output bit will be selected from several columns. The multiplexer control signals can be generated at one end of the string of multiplexers and distributed to all the mux cells.

### 6.6.1 ROM

**Figure 6-19** Design of a ROM core.

 


*ROM core cell circuit*

A read-only memory is programmed with transistors to supply the desired values. A common circuit is the NOR array shown in Figure 6-19. It uses a pseudo-nMOS NOR gate: a transistor is placed at the word-bit line intersection for which  $\text{bit}' = 0$ .

### 6.6.2 Static RAM

Basic static RAM circuits can be viewed as variations on the designs used for latches and flip-flops; more aggressive static RAMs make use of design tricks originally developed for dynamic RAMs to speed up the system.

**Figure 6-20**  
Design of an  
SRAM core cell.

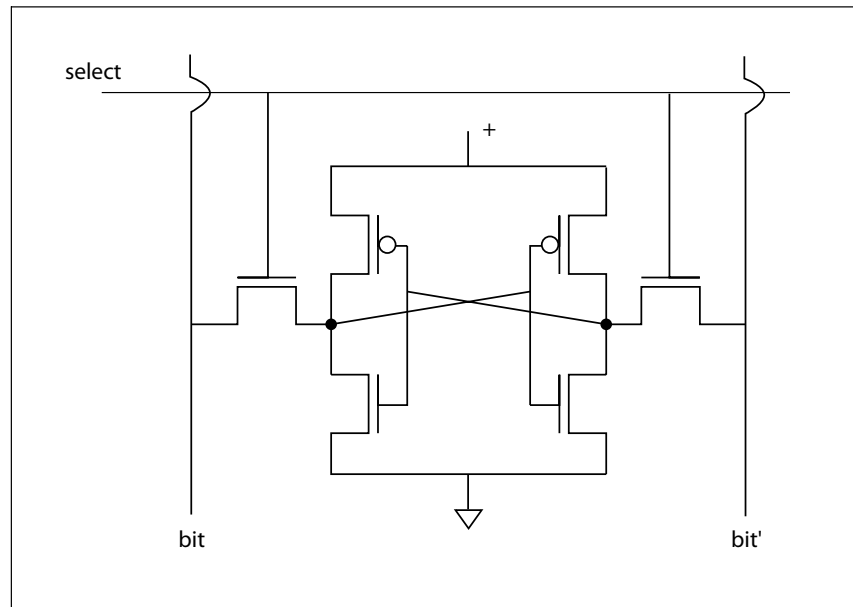


*SRAM core cell circuit*

The SRAM core circuit is shown in Figure 6-20. The value is stored in the middle four transistors, which form a pair of inverters connected in a loop (try drawing a gate-level version of this schematic). The other two transistors control access to the memory cell by the bit lines. When  $\text{select} = 0$ , the inverters reinforce each other to store the value. A read or write is performed when the cell is selected:


- To read,  $\text{bit}$  and  $\text{bit}'$  are precharged to  $V_{DD}$  before the  $\text{select}$  line is allowed to go high. One of the cell's inverters will have its output at 1, and the other at 0; which inverter is 1 depends on the value stored. If, for example, the right-hand inverter's output is 0, the  $\text{bit}'$  line will be drained to  $V_{SS}$  through that inverter's pulldown and the  $\text{bit}$  line will remain high. If the opposite value is stored in the cell, the  $\text{bit}$  line will be pulled low while  $\text{bit}'$  remains high.
- To write, the  $\text{bit}$  and  $\text{bit}'$  lines are set to the desired values, then  $\text{select}$  is set to 1. Charge sharing forces the inverters to switch values, if necessary, to store the desired value. The bit lines have much higher capacitance than the inverters, so the charge on the bit lines is enough to overwhelm the inverter pair and cause it to flip state.

The layout of a pair of SRAM cells in the SCMOS rules is shown in Figure 6-23.

**Figure 6-21** A differential pair sense amplifier for an SRAM.

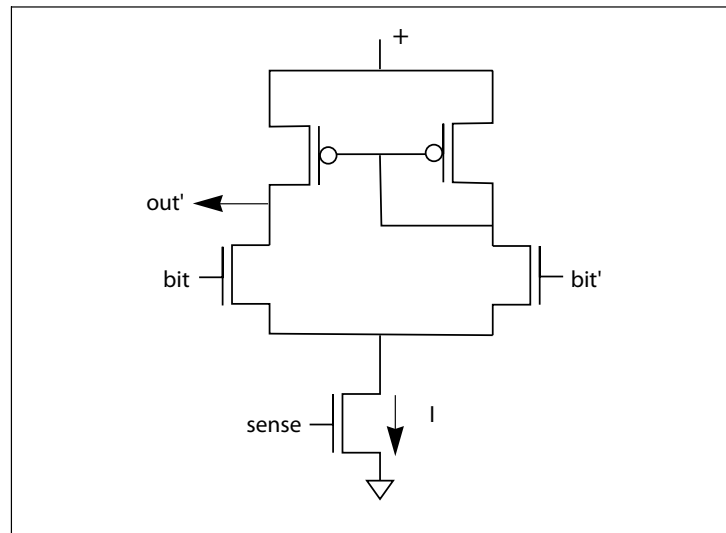

**Figure 6-22** An SRAM precharge circuit.

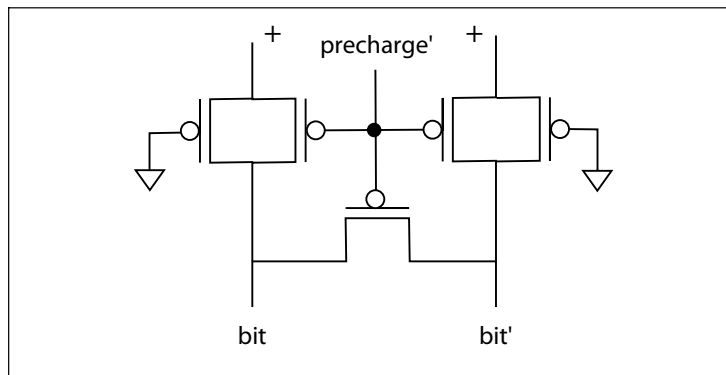


### *sense amplifier*

A **sense amplifier**, shown in Figure 6-21, makes a reasonable bit line receiver for modest-size SRAMs. The n-type transistor at the bottom acts as a switchable current source—when turned on by the *sense* input, the transistor pulls a fixed current  $I$  through the sense amp's two arms. Kirchoff's current law tells us that the currents through the two branches must sum to  $I$ . When one of the bit lines goes low, the current through that leg of the amplifier goes low, increasing the current in the other leg. P-type transistors are used as loads. For an output of the opposite polarity, both the output and the pullup bias connection must be switched to the opposite sides of the circuit. More complex circuits can determine the bit line value more quickly [Gla85].


*bit line precharging*

A precharging circuit for the bit lines is shown in Figure 6-22. Precharging is controlled by a single line. The major novelty of this circuit is the transistor between the bit and bit' lines, which is used to equalize the charge on the two lines.

**Figure 6-23**  
Layout of a pair  
of SRAM core  
cells.

 *multi-port RAMs*

Many designs require multi-ported RAMs. For example, a register file is often implemented as a multi-port SRAM. Each port consists of address input, data outputs, and select and read/write lines. When select is

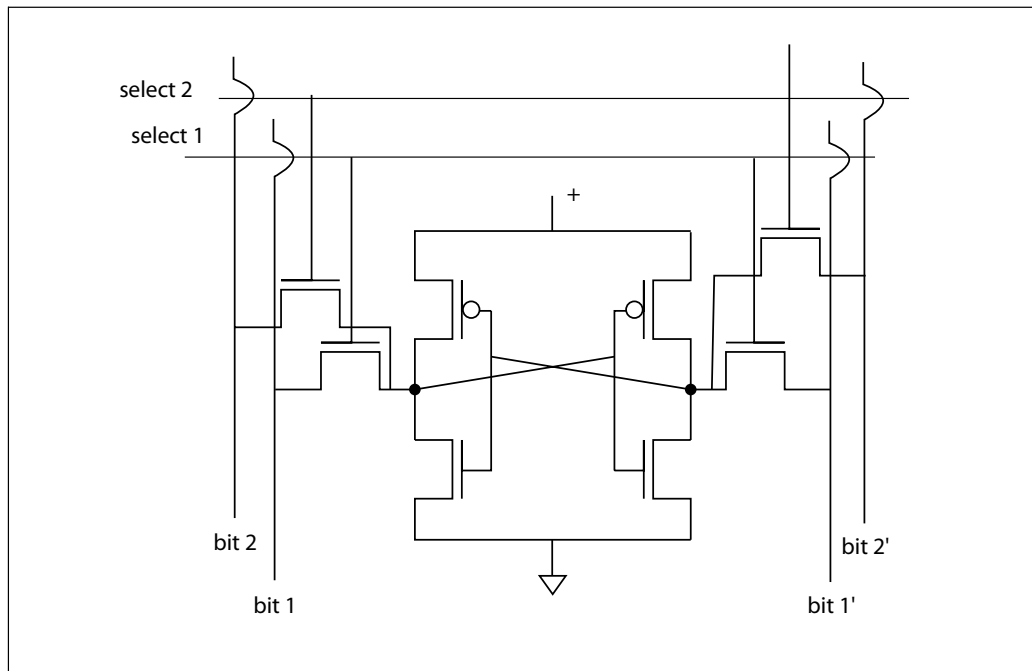

**Figure 6-24** A dual-ported SRAM core cell.


asserted on the  $i^{\text{th}}$  port, the  $i^{\text{th}}$  address is used to read or write the addressed cells using the  $i^{\text{th}}$  set of data lines. Reads and writes on separate ports are independent, although the effect of simultaneous writes to a port are undefined. The circuit schematic for a two-port SRAM core cell is shown in Figure 6-24. Each port has its own pair of access transistors. The transistors in the cross-coupled inverters must be resized moderately to ensure that multiple port activations do not affect the stored value, but the circuit and layout designs do not differ radically from the single-ported cell.

### 6.6.3 The Three-Transistor Dynamic RAM

#### *3T RAM*

The simplest dynamic RAM cell uses a three-transistor circuit [Reg70]. This circuit is fairly large and slow. It is sometimes used in ASICs because it is denser than SRAM and, unlike one-transistor DRAM, does not require special processing steps.

**Figure 6-25** Design of a three-transistor DRAM core cell.

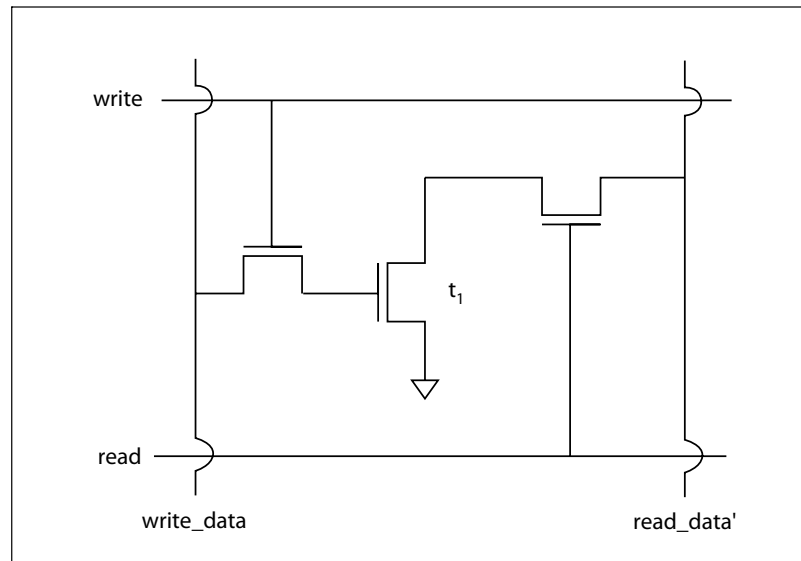

### 3T RAM core cell

The three-transistor DRAM circuit is shown in Figure 6-25. The value is stored on the gate capacitance of  $t_1$ ; the other two transistors are used to control access to that value:

- To read, `read_data'` is precharged to  $V_{DD}$ . We then set `read` to 1 and `write` to 0. If  $t_1$ 's gate has a stored charge, then  $t_1$  will pull down the `read_data'` signal, else `read_data'` will remain charged. `read_data'`, therefore, carries the complement of the value stored on  $t_1$ .
- To write, the value to be written is set on `write_data`, `write` is set to 1, and `read` to 0. Charge sharing between `write_data` and  $t_1$ 's gate capacitance forces  $t_1$  to the desired value.

### RAM refresh

Substrate leakage will cause the value in this cell to decay. The value must be **refreshed** periodically—a refresh interval of 1 ms is consistent with the approximate leakage rate of typical processes. The value is refreshed by rewriting it into the cell, being careful of course to rewrite the original value.




### 6.6.4 The One-Transistor Dynamic RAM

#### *1T DRAM*

The one-transistor DRAM circuit quickly supplanted the three-transistor circuit because it could be packed more densely, particularly when advanced processing techniques are used. The term one-transistor is somewhat of a misnomer—a more accurate description would be one-transistor/one-capacitor DRAM, since the charge is stored on a pure capacitor rather than on the gate capacitance of a transistor. The design of one-transistor DRAMs is an art beyond the scope of this book. But since embedded DRAM is becoming more popular, it is increasingly likely that designers will build chips with one-transistor DRAM subsystems, so it is useful to understand the basics of this memory circuit.


**Figure 6-26** Circuit diagram for a one-transistor DRAM core cell.

 


#### *1T RAM core cell*

Figure 6-26 shows the circuit diagram of a one-transistor DRAM core cell. The cell has two external connections: a bit line and a word line. The value is stored on a capacitor guarded by a single transistor. Setting the word line high connects the capacitor to the bit line. To write a new value, the bit line is set accordingly and the capacitor is forced to the proper value. When reading the value, the bit line is first precharged before the word line is activated. If the storage capacitor is discharged, then charge will flow from the bit line to the capacitor, lowering the voltage on the bit line. A sense amp can be used to detect the dip in voltage; since the bit line provides only a single-ended input to the bit line, a reference voltage may be used as the sense amp's other input. One common way to generate the reference voltage is to introduce dummy cells that are precharged but not read or written. This read is destructive—the zero on the capacitor has been replaced by a one during reading. As a result, additional circuitry must be placed on the bit lines to pull the bit line and storage capacitor to zero when a low voltage is detected on the bit line. This cell's value must also be refreshed periodically, but it can be refreshed by reading the cell.

**Figure 6-27** Cross-section of a pair of stacked-capacitor DRAM cells.

 

**Figure 6-28** Cross-section of a one-transistor DRAM cell built with a trench capacitor.

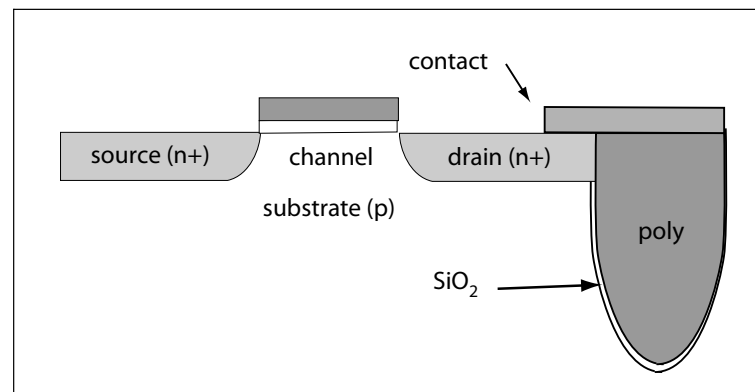

### DRAM structures


Modern DRAMs are designed with three-dimensional structures to minimize the size of the storage cell. The two major techniques for DRAM fabrication are the **stacked capacitor** and the **trench capacitor**. The cross-section of a pair of stacked capacitor cells is shown in Figure 6-27 [Tak85]. The cell uses three layers of polysilicon and one level of metal: the word line is fabricated in poly 1, the bottom of the capacitor in poly 2, and the top plate of the capacitor in poly 3. The bit line is run in metal above the capacitor structures. The capacitor actually wraps around the access transistor, packing a larger parallel plate area in a smaller surface area. The bottom edge of the bottom plate makes the contact with the access transistor, saving additional area. The trench capacitor cell cross-section is shown in Figure 6-28 [Sun84]. A trench is etched into the chip, oxide is formed, and the trench is filled with polysilicon. This structure automatically connects the bottom plate to the grounded substrate; a contact is used to directly connect the polysilicon plate to the access transistor.

One should not expect one-transistor DRAMs that can be fabricated on a logic process to be equivalent to commodity DRAMs. The processing steps required to create a dense array of capacitors are not ideal for effi-

cient logic transistors, so high-density DRAMs generally have lower-quality transistors. Since transistors make up a relatively small fraction of the circuitry in a commodity DRAM, those chips are optimized for the capacitors. However, in a process designed to implement large amounts of logic with some embedded DRAM, processing optimizations will generally be made in favor of logic, resulting in less-dense DRAM circuitry. In addition, the sorts of manufacturing optimizations possible in commodity parts are also not generally possible in logic-and-DRAM processes, since more distinct parts will be manufactured, making it more difficult to measure the process. As a result, embedded DRAM will generally be larger and slower than what one would expect from evaluating commodity DRAM in a same-generation process.

### 6.6.5 Flash Memory

**Figure 6-29** A floating gate device.

 

#### *floating-gate transistors*

Flash memory is a form of electrically erasable ROM. The device used to build flash memories is the **floating gate transistor** [Sze81], shown in Figure 6-29. This device has two gates, one of which (the lower gate) is disconnected. A charge can be placed on the floating gate by applying large voltages across the upper gate and the drain; Fowler-Nordheim tunneling is the physical effect that allows current to flow across the oxide. When the floating gate is charged, it turns on the transistor; when the floating gate is discharged, it turns off the transistor. The floating gate charge will remain for years.


#### *flash architectures*

Two major architectures for flash memory are in use: NOR flash and NAND flash. Not only do these architectures use different circuits, but they present different logical interfaces to the system.

#### *NOR flash*


A NOR flash cell and its associated pullup are shown in Figure 6-30. NOR flash is identical in structure to ROM, except that every word/bit

**Figure 6-30** A NOR flash cell.

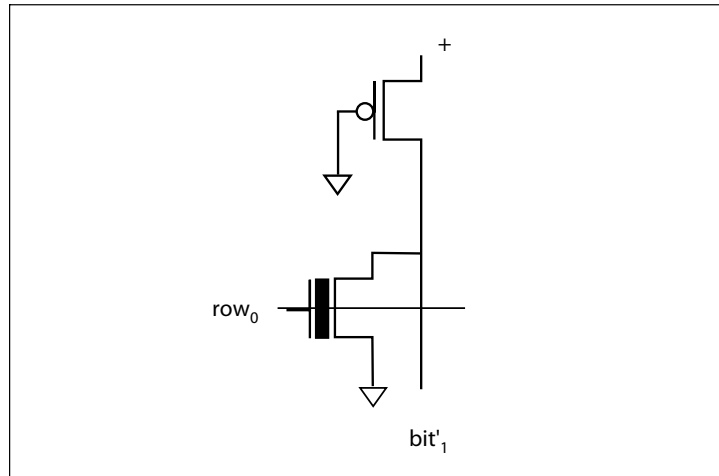

line intersection is populated with a floating gate transistor. NOR flash can be used as a random-access memory, just like any other ROM.

**Figure 6-31** A two-bit NAND flash cell.

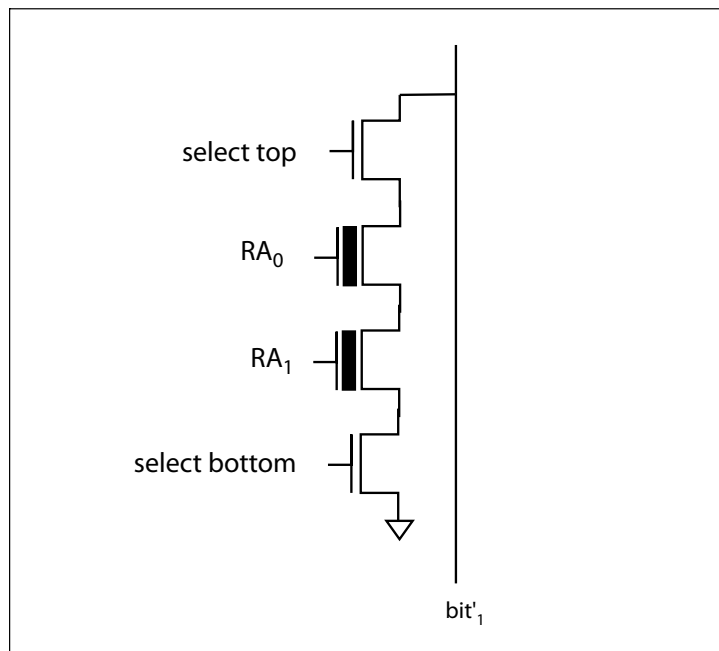

*NAND flash*

NAND flash, in contrast, is designed to provide a banked memory structure. Memory banks can be addressed independently, allowing higher data rate transfers. NAND flash was originally designed to support multimedia applications that require high bandwidths, but it is fast becoming the dominant flash architecture.

Figure 6-31 shows a two-bit NAND flash cell. The two storage bits are accessed using the RA signals. The NAND series connection is guarded by standard n-type transistors. To program a cell, we would set SELECT TOP to a high voltage, SELECT BOTTOM to ground, and the RA that controls the desired transistor to a high voltage. To prevent adjacent columns from being programmed, we set the other RAs to an intermediate voltage. Those transistors then conduct but are not programmed. The value to be programmed is put on the bit line.

---

## 6.7 Image Sensors

---

*photodiodes and image sensors*

Electronic image sensors can be fabricated using the same basic silicon technology used for VLSI systems. As shown in Figure 6-32, a silicon diode acts as detector of photons; the most common form of detector is the **photodiode** [Sze81]. When the photodiode absorbs a photon, it generates one electron that becomes part of the **photocurrent**. The absorption band of silicon happens to be in the visible band of light. The absorption coefficient  $\alpha$  of silicon is such that most visible light is absorbed within the first 20  $\mu\text{m}$  of silicon, which means that the photodiodes are sufficiently close to the surface that they can be manufactured with standard techniques.


The photocurrent density as a function of the photon flux that reaches a unit area of the photodiode is given by

$$j_{ph} = \frac{qF_0}{\alpha} \cdot \frac{(1 - e^{-\alpha x_1})}{x_1} \cdot \frac{(e^{-\alpha x_2} - e^{-\alpha x_3})}{(x_3 - x_2)} A/cm^2, \quad (\text{EQ 6-13})$$

where  $F_0$  is the photon flux in photons per square centimeter,  $x_1$  and  $x_2$  are the boundaries of the depletion region, and  $x_3$  is the bottom of the photodiode's p-type region. Typical photocurrents run in the tens to hundreds of nanoamperes per  $\text{cm}^2$ .

---

**Figure 6-32**  
A photodiode.

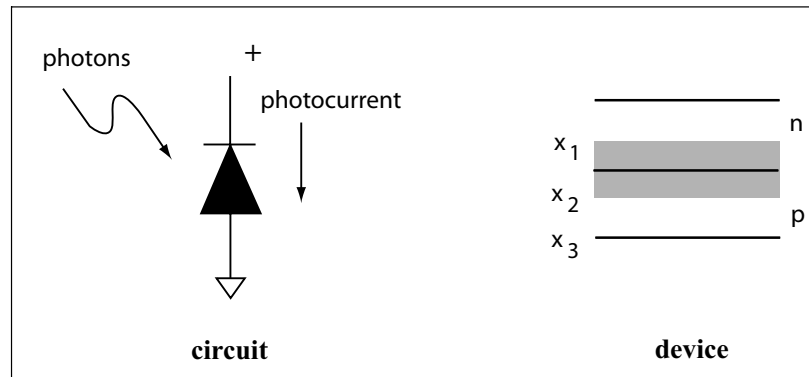

A photodiode can be used to build a **pixel** that measures the light intensity at one point in the image. An image sensor includes a 2-D array of pixels and circuitry that allows the system to access those pixels.

#### *image sensor architectures*

Two very different architectures can be used to organize an image sensor. Both use photodiodes as their photosensors, but they vary significantly in how they move pixel values off-chip. The first widely-used silicon image sensors was the **charge-coupled devices (CCDs)** [Boy70] to move pixel values. A detailed discussion of CCDs is beyond the scope of this book, but they manipulate potentials along the chip to move charge from pixels as in a bucket brigade. CCDs remain to this day the most sensitive silicon image sensors due to the very high efficiency with which CCDs move charge from a pixel to the pads. But CCDs require specialized fabrication steps that are not compatible with bulk CMOS technology.


#### *CMOS image sensor*

The CMOS image sensor [Fos95] can be fabricated on standard CMOS processes. A CMOS image sensor uses circuits very similar to those used in memories to access the pixels: a row line selects a row of pixels to be read while bit lines run vertically to take the pixel values to amplifiers and outputs.

The dominant form of pixel circuit in use today is the **active pixel sensor (APS)**, shown in Figure 6-33. This circuit uses an amplifier in each pixel to drive the bit line quickly. A reset transistor is used to reset the pixel to zero before an exposure. The word line turns on the amplifier, which drives the bit line. Unlike a digital memory, the output value on the bit line is analog.

The amplifier takes up additional space in the pixel beyond that required by the access transistor; this is area that cannot be used for the photo-

**Figure 6-33** Design of an active pixel sensor.

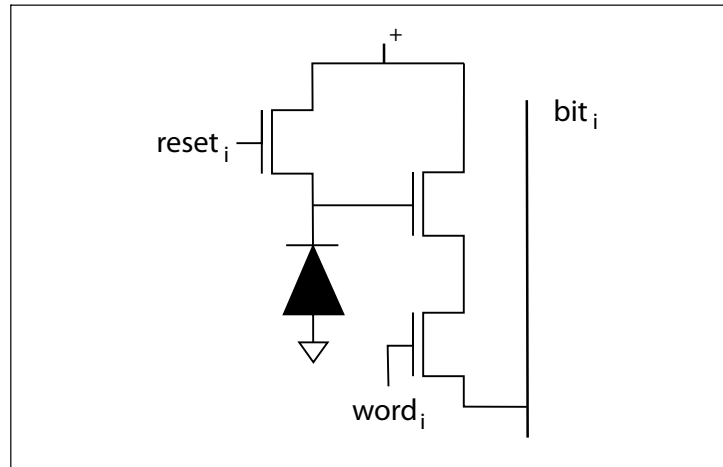

diode. The ratio of photodiode area to total pixel area is known as the **fill factor**. Below  $0.5\ \mu\text{m}$ , transistors are small enough that the fill factor is acceptably high to build useful image sensors.

**Figure 6-34** Organization of a column of pixels.

 


Figure 6-34 shows the readout circuitry for a row of pixels. A bias transistor sets the proper voltage on the bit line. The pixel selected by the


word line charges the column capacitance. Once all the pixels in a word have been read, they can be transferred to an output amplifier one at a time by turning on the column amplifier for each column.

## 6.8 Field-Programmable Gate Arrays

A **field-programmable gate array** (FPGA) is a block of programmable logic that can implement multi-level logic functions. FPGAs are most commonly used as separate commodity chips that can be programmed to implement large functions. However, small blocks of FPGA logic can be useful components on-chip to allow the user of the chip to customize part of the chip's logical function.

An FPGA block must implement both combinational logic functions and interconnect to be able to construct multi-level logic functions. There are several different technologies for programming FPGAs, but most logic processes are unlikely to implement anti-fuses or similar hard programming technologies, so we will concentrate on SRAM-programmed FPGAs.

**Figure 6-35** A lookup table.

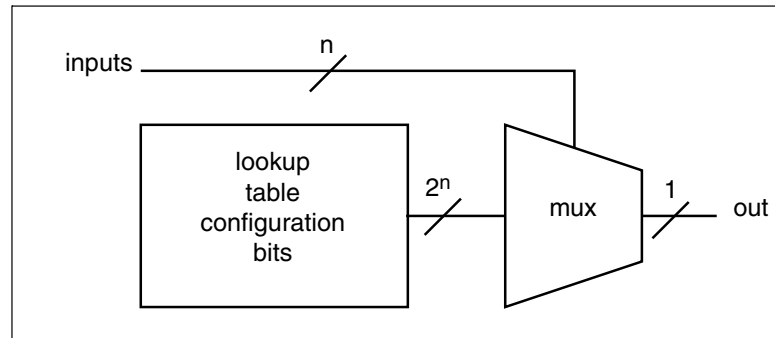

*lookup tables*

The basic method used to build a **combinational logic block (CLB)**—also called a **logic element**—in an SRAM-based FPGA is the **lookup table (LUT)**. As shown in Figure 6-35, the lookup table is an SRAM that is used to implement a truth table. Each address in the SRAM represents a combination of inputs to the logic element. The value stored at that address represents the value of the function for that input combination. An  $n$ -input function requires an SRAM with  $2^n$  locations. Because a basic SRAM is not clocked, the lookup table logic




*programming  
a lookup table*

element operates much as any other logic gate—as its inputs change, its output changes after some delay.

Unlike a typical logic gate, the function represented by the logic element can be changed by changing the values of the bits stored in the SRAM. As a result, the  $n$ -input logic element can represent  $2^{2^n}$  functions (though some of these functions are permutations of each other). A typical logic element has four inputs. The delay through the lookup table is independent of the bits stored in the SRAM, so the delay through the logic element is the same for all functions. This means that, for example, a lookup table-based logic element will exhibit the same delay for a 4-input XOR and a 4-input NAND. In contrast, a 4-input XOR built with static CMOS logic is considerably slower than a 4-input NAND. Of course, the static logic gate is generally faster than the logic element.

**Figure 6-36** A flip-flop in a logic element.

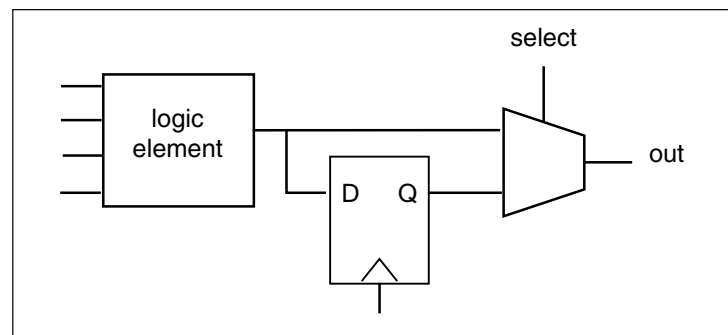

Logic elements generally contain registers—flip-flops and latches—as well as combinational logic. A flip-flop or latch is small compared to the combinational logic element (in sharp contrast to the situation in custom VLSI), so it makes sense to add it to the combinational logic element. Using a separate cell for the memory element would simply take up routing resources. As shown in Figure 6-36, the memory element is connected to the output; whether it stores a given value is controlled by its clock and enable inputs.


*complex logic elements*

Many FPGAs also incorporate specialized adder logic in the logic element. The critical component of an adder is the carry chain, which can be implemented much more efficiently in specialized logic than it can using standard lookup table techniques.

The wiring channels that connect to the logic elements' inputs and outputs also need to be programmable. A wiring channel has a number of

programmable connections such that each input or output generally can be connected to any one of several different wires in the channel.

**Figure 6-37** An interconnect point controlled by an SRAM cell.

 

*programmable  
interconnection points*

Figure 6-37 shows a simple version of an **interconnection point**, often known as a **connection box**. A programmable connection between two wires is made by a CMOS transistor (a pass transistor). The pass transistor's gate is controlled by a static memory program bit (shown here as a D register). When the pass transistor's gate is high, the transistor conducts and connects the two wires; when the gate is low, the transistor is off and the two wires are not connected. A CMOS transistor has a good off-state (though off-states are becoming worse as chip geometries shrink). In this simple circuit, the transistor also conducts bidirectionally—it doesn't matter which wire has the signal driver. However, the pass transistor is relatively slow, particularly on a signal path that includes several interconnection points in a row.


## 6.9 Programmable Logic Arrays

*PLAs for two-level logic*

The **programmable logic array (PLA)** is a specialized circuit and layout design for two-level logic. While the PLA is not as commonly used in CMOS technology as in nMOS, due to the different gate circuits used in the two technologies, CMOS PLAs can efficiently implement certain types of logic functions.

*PLA architecture*

The architecture of a PLA, as shown in Figure 6-38, is very simple: it uses two levels of logic, one implementing the ANDs (called **product terms**) and another implementing the ORs. One of the best features of the PLA is that it can compute several functions at once, which can share product terms. Two-level functions are built from both the true and complement forms of the variables, so the inputs supply both forms, usually with a pair of inverters on the true form as buffers. Some sort of buffer is usually placed at the output. The architecture also suggests the

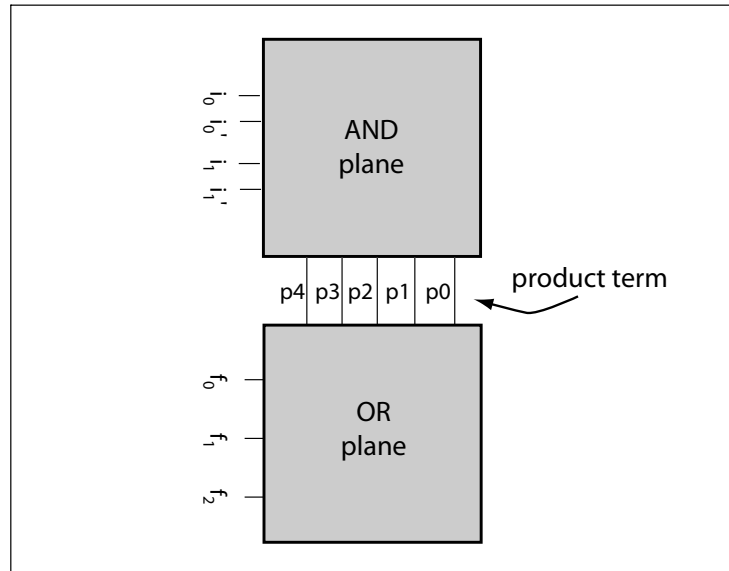**Figure 6-38** Organization of a PLA.


attractiveness of the layout: the inputs to the AND plane flow vertically, while the outputs flow horizontally and emerge at the right side. The OR plane is simply a 90° rotation of the AND plane. Such a layout can be very compact, but we need to find a gate structure compatible with this layout organization.

#### *PLA circuits*

We clearly cannot use fully complementary gates for this layout style—wiring both the pullups and pulldowns would be too complex. The most common form of the CMOS PLA uses precharged gates for both AND and OR planes [Sho88]. Using a non-complementary gate lets us use very regular layouts for the wires: input signals are evenly spaced in one direction and output signals are also evenly spaced in the perpendicular direction. Figure 6-39 shows a logic diagram for a doubly-precharged PLA circuit. Setting the precharge lines low enables the p-type pullup to precharge the planes; bringing the precharge lines low enables the n-type evaluation transistor. The circuits in the AND and OR planes are identical, except for programming transistors, which determine the PLA's **personality**.


#### *PLA layout*

In the AND plane, each precharged gate's output node runs vertically through the cell. Pulldowns run between the output node and  $V_{SS}$  lines that run parallel to the output lines; inputs run horizontally to be attached to the pulldowns' gates. The AND and OR planes are very sim-

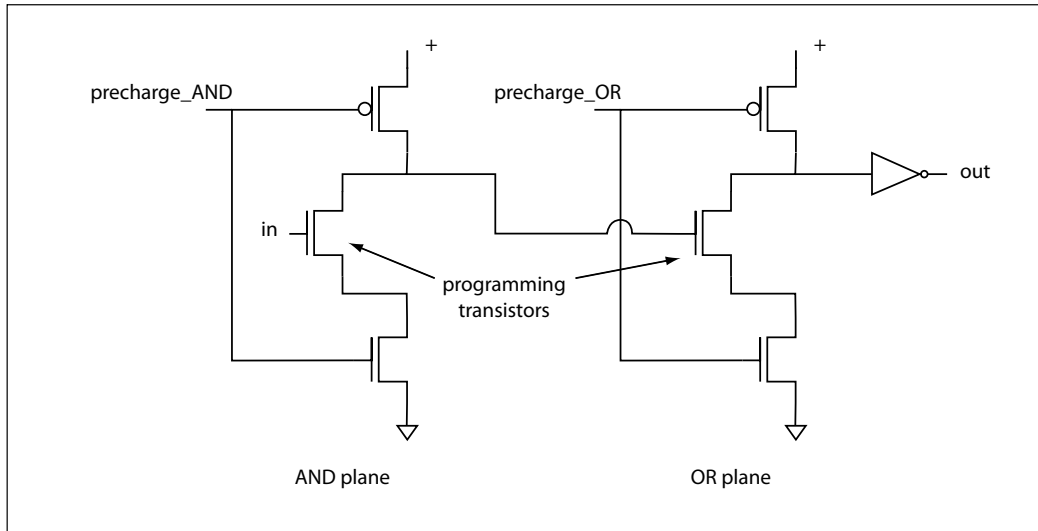

**Figure 6-39** Precharged gates for the AND and OR planes of a PLA.

**Figure 6-40** A section of a PLA AND/OR plane.

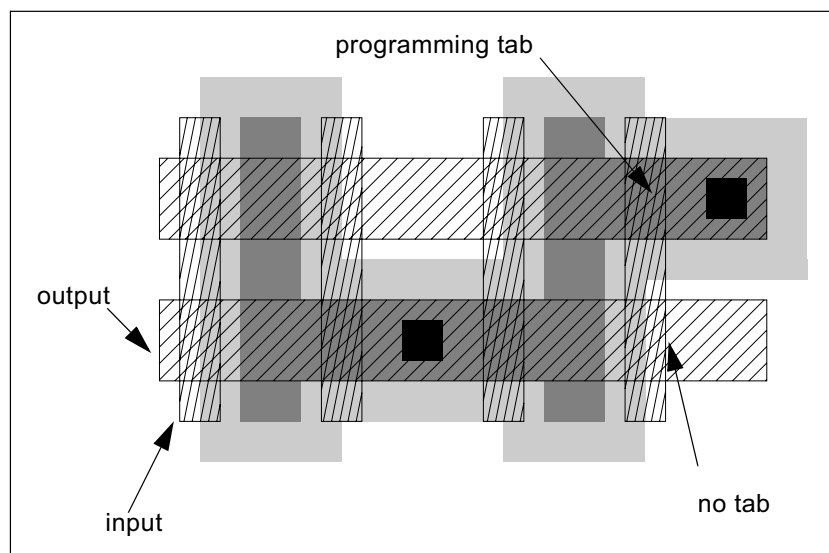

ple to generate. We first lay down a grid of wires for input signals,  $V_{SS}$ , and output signals. We can create a pulldown transistor at the intersection of input and output signals by adding small amounts of diffusion

and poly along with a via. The pulldown can be added to the wiring by superimposing one cell on another; the pulldown cell is called a **programming tab** thanks to the shape of the transistor and via. The same cell can be used for both planes since the OR plane is simply a 90° rotation of the AND plane. Figure 6-40 shows a section of an AND/OR plane with four inputs running vertically in poly and two outputs running horizontally in metal 1. Each pair of input lines shares a ground line running in n-diffusion; pairs also share open space for a programming tab's via, so that one via can be used for two pulldown transistors on opposite sides of the via.

*PLA delay*

The delay through the PLA is determined largely by the load introduced by the vertical and horizontal wires. The neat layout of the PLA keeps us from using large transistors in the pulldowns to speed up the gates—a large pulldown would not only add blank space down the entire row but would also lengthen the perpendicular wires. This doubly-precharged structure also complicates clocking.

*PLA applications*

Which functions are best implemented as PLAs? Those functions that are true for about half their input vectors are well-suited. If the PLA has very few programming tabs, we are wasting most of its area and are probably better off using fully complementary gates. If the PLA is nearly full, we can complement the functions to produce a nearly empty PLA. PLAs are also good for implementing several functions that share many common product terms, since the AND-OR structure makes it easy to send one product term to many different ORs. CPU microcode often has these characteristics.

*PLA optimizations*

Standard two-level minimization algorithms can be used to optimize the PLA personality. An optimization unique to PLAs is **folding**. If one region of the PLA is empty of programming tabs, it may be possible to remove that section and fold another section of the PLA into the newly freed space. Folding can leave the PLA with inputs and outputs on all four sides. While folding can dramatically reduce the size of the PLA, it also makes the PLA's layout very sensitive to changes. A small change in the logic may require a use of a single programming tab in the region removed for folding, enough to undo the entire folding operation. Folded PLAs may, with a small logic change, unfold themselves like origami pieces in the middle of a chip design, destroying floorplans that relied on the small size of the folded PLA. As a result, PLA folding is less popular today than it was when PLAs first came into common use.

## 6.10 Buses and Networks-on-Chips


In this section, we will examine the design of interconnect subsystems: buses and networks-on-chips. Buses are widely used to connect to microprocessors and as a common interconnect. Buses also allow us to explore a new style of logic design, asynchronous logic. Networks-on-chips are more sophisticated forms of interconnect that are increasingly necessary on large chips. Our discussion of protocols for buses is also one of the foundations of network-on-chip design. We will cover several topics in bus design, ranging from circuits to protocols, and close with a discussion of network-on-chip design.

### 6.10.1 Bus Circuits

A bus is a common connection. At the core of this common connection is a large wire that serves as the communication channel. Buses are bi-directional, so we cannot use buffers to refresh the signal as it travels along the bus. This puts a large burden on the circuits driving the bus.

The circuits used for a bus must provide this common connection across a long region. Although the logical function of a bus may be seen as multiplexing, it is generally not feasible to distribute the control signals required for muxes over the distances encountered in a bus.


**Figure 6-41** A pseudo-nMOS bus circuit.

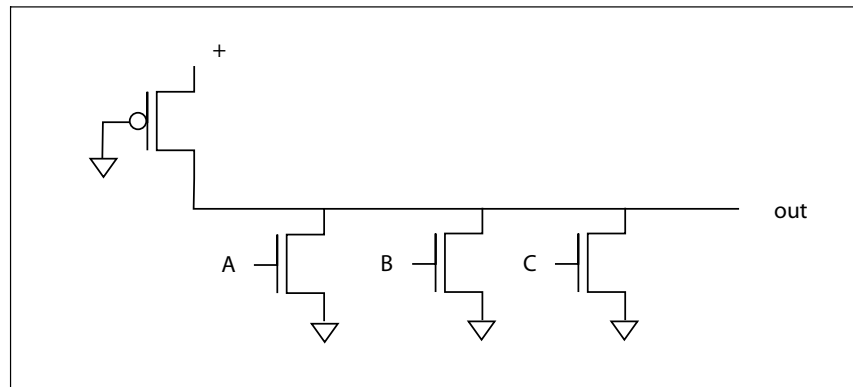

*distributed NOR bus*

One style of bus circuit is the distributed NOR gate: the common wire forms the NOR gate's output, while pull-downs at the sources select the source and set the NOR gate's output. (All devices connected to the bus can read it in this scheme.) The circuit choices for buses are much like

**Figure 6-42** A precharged bus circuit.

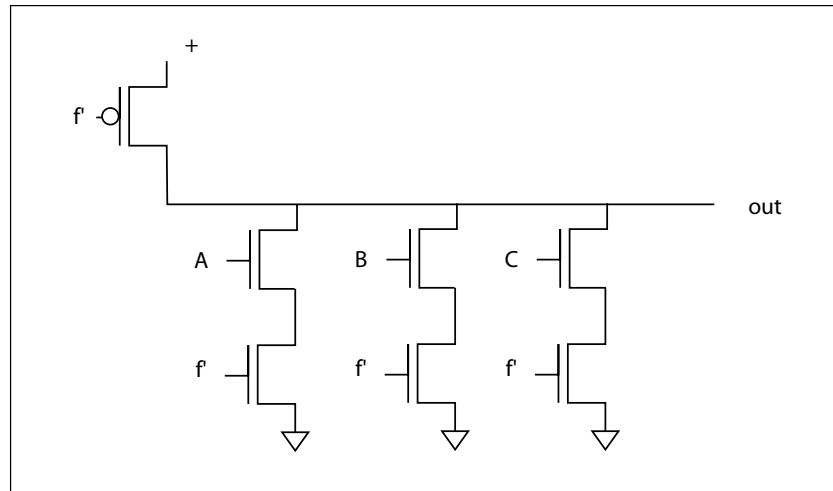

those for the advanced gate circuits of Section 3.5: pseudo-nMOS, shown in Figure 6-41, and precharged, shown in Figure 6-42. The trade-offs are also similar: the pseudo-nMOS bus is slow but does not require a separate precharge phase.

#### *three-state bus*

An alternative is the three-state bus, as shown in Figure 6-43. Each input has its own three-state driver. The bus presents a large capacitance, including both the bus wire itself and the capacitance of all the bus outputs. As a result, these drivers would typically use an exponentially-tapered driver chain using the techniques of Section 3.3.8. A local control signal determines when the device can write onto the bus. The control signals must be timed such that two drivers are not on simultaneously.



### 6.10.2 Buses as Protocols

#### *buses implement protocols*

A **bus** is, most fundamentally, a common connection. It is often used to refer to a physical connection that carries a **protocol** for communication between processing elements. The physical and electrical characteristics of the bus are closely matched to the protocol in order to maximize the cost-effectiveness of the bus system.

A simple bus-based system is shown in Figure 6-44. The bus allows us to construct a system out of communicating components. The components in the system communicate via a series of wires. Some of these

**Figure 6-43**  
A bus with three-state drivers.

 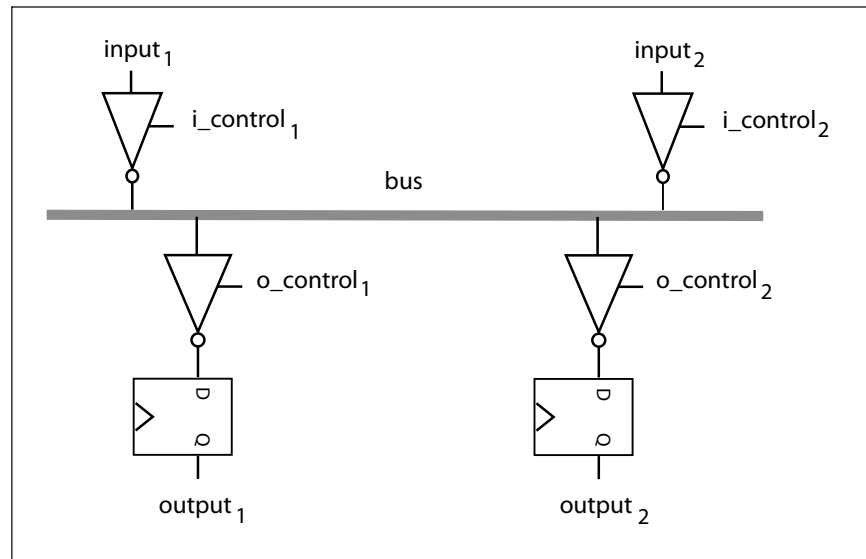

**Figure 6-44** A bus-based system.

wires carry data while others carry the control information for the protocol. The bus specification includes electrical characteristics of these components: voltages, currents, maximum capacitive loads, etc. The bus specification also includes the protocol for how to use the control and data signals to communicate between the components connected to the bus.



### 6.10.3 Protocols and Specifications

A protocol is an agreed-upon means for communication. While the protocol ultimately describes the complete system, the best way to understand a protocol is often by looking at the behavior of the components that are communicating. Once we understand what each component expects from the other component and what it does in return, then it is easier to understand the flow of communication embodied in the protocol.

#### *events on signals*

We often talk about events on signals as **assertions** or **deassertions** rather than as 1 or 0. An assertion event may be logically true but at a zero voltage because that can be more reliably signaled over the particular physical medium in use. Assert/deassert terminology gives us some independence from the physical representation of signals that is often useful.

#### *protocols and state transition graphs*

Protocols for digital systems are often described as state transition graphs. Each component in the system has a state; inputs from other components cause it to move to different states and to emit outputs. Those new states may be good if the component gets the protocol signal that it expects; the states may also represent bad conditions if the component doesn't see the behavior it expects from other components.

The state machines used to describe protocols are not the synchronous state machines that we have used for logic design. We use **event-driven** state machines to describe protocols. These state machines are similar in behavior to event-driven simulators—the machine changes state only when it observes an input event. An event is, in general, a change in a signal. One might implement a protocol using a synchronous state machine that polls the input signal, but at the interface the user can only tell that the machine responds to these events.


#### *timing diagrams and protocols*

One way to specify a part of the protocol used by the bus is with a timing diagram. It describes one scenario of the bus operation; several such scenarios are generally needed to fully specify the protocol.

#### *four-cycle handshake*

Let us use a simple example to show how protocols can be described. Figure 6-45 shows the activity during a **four-cycle handshake**, a protocol that is the basic building block for many more complex protocols. A four-cycle handshake is used to reliably communicate between two systems. At the end of the protocol, not only is some information transferred (either implicitly by performing the handshake or by passing data in the middle of the handshake) but both sides know that the communication was properly completed.

**Figure 6-45** Events in a four-cycle handshake.

 

The four-cycle handshake uses two signals, **enq** (*enquiry*) and **ack** (*acknowledge*). Each signal is output by one component and received by the other. The handshake allows the two components to reliably exchange information.

**Figure 6-46** Components in a four-cycle handshake.

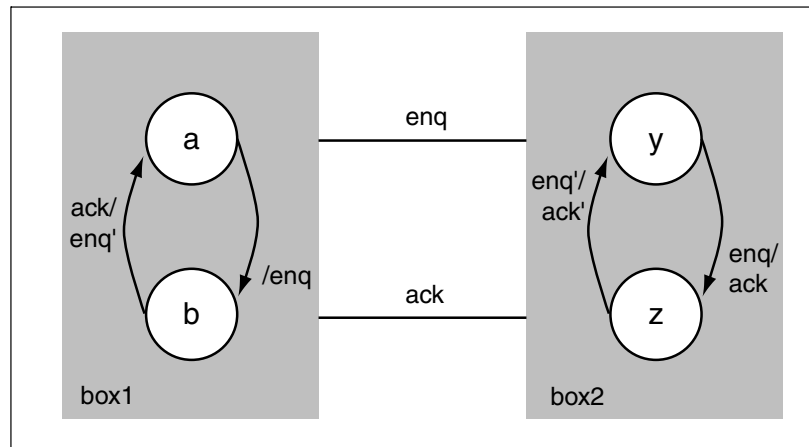


Figure 6-46 shows the two components in more detail. The *enq* and *ack* signals move between the components. The figure shows the state machine describing the protocol in each component machine. The protocol allows *box1* to signal *box2*; that signal could be a simple completion signal or it could be used to tell *box2* that *box1* has some data ready.

Let us first consider *box1*:

1. *Box1* raises *enq* to tell *box2* that it is ready. (This action is instigated by some other activity within *box1*.)
2. When *box1* sees an *ack*, it lowers *enq* to tell *box2* that it saw the acknowledgement.


Once *box1* has responded to the *ack* signal from *box2*, it returns to its original state and is ready for another round.

Let us consider the same transaction from the side of *box2*:

1. When *box2* sees *enq* go high, it goes into a new state and sends an *ack* to *box1*.
2. When *box2* sees *enq* go low, it sets *ack* low and returns to its original state.

Just as *box1* returns to its original state once the handshake is complete, *box2* also returns to its original state and is ready to perform the handshake protocol once again. If we want to use the handshake simply to allow *box1* to tell *box2* that it is ready, then the handshake itself is enough. If we want to pass some additional data, we would pass it after *box2* has raised *ack* and before *box1* lowers *enq*.

**Figure 6-47** The combined state transition graph for the four-cycle handshake.

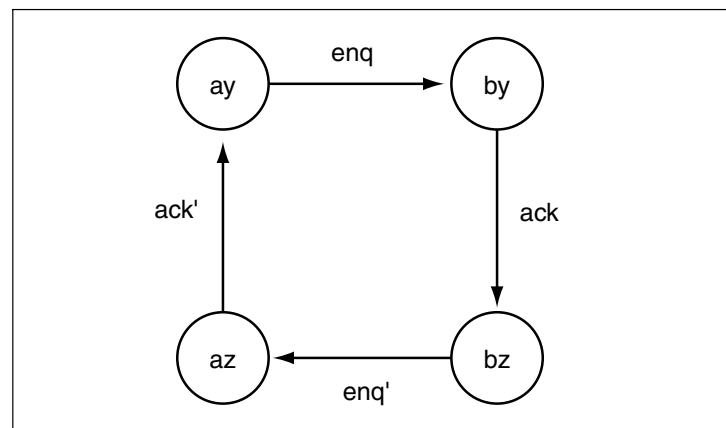


If we want to see the overall action of the protocol, we can form the Cartesian product of the two state machines that describes the two components. The product machine for the four-cycle handshake is shown in Figure 6-47. Forming the Cartesian product actually causes the *enq* and *ack* signals to disappear but we have shown them as events on the transition between states. The names of each Cartesian product state is the

combination of the names of the two component states that combined to make it. We can now see that the combination of *box1* and *box2* go through four states during the four-cycle handshake:

1. *ay* is the initial state in the protocol. The system leaves that state when *enq* is asserted.
2. *by* is the state in which *enq* is active but has not yet been acknowledged.
3. *bz* has both *enq* and *ack* asserted. Data can be passed between *box1* and *box2* in this state.
4. *az* has *enq* deasserted by *ack* still asserted. The system leaves this state for *ay* when *ack* is deasserted.

**Figure 6-48** Events in a two-cycle handshake.

 

*two-cycle handshake*

An even simpler protocol is the two-cycle handshake. This protocol is less reliable but is sometimes good enough for basic signaling. As shown in Figure 6-48, the two-cycle handshake uses *enq* but not *ack*. The enquiry is simply asserted and then deasserted.

**Figure 6-49** Components in a two-cycle handshake.

 


Figure 6-49 shows the component state machines for the two-cycle handshake. Because *box1* does not receive an *ack*, it must guess as to when to deassert *enq*. This makes the protocol less reliable but it does provide some basic signaling. We generally use some sort of timer to determine how long to wait before deasserting *enq*. Either a counter or a logic path with a known delay can provide us with the necessary delay.


### 6.10.4 Logic Design for Buses

*asynchronous logic in buses*

Why use timing diagrams to describe protocols? Why not use state transition graphs? Why design systems that depend on particular delay values? Because buses often connect components that do not (and cannot) share a common, synchronized clock. As a result, the bus must use asynchronous logic for communication. Because the types of asynchronous logic used in buses often depends upon timing values, we use timing diagrams to show the necessary timing constraints. In this section we will study the design of buses using asynchronous logic.

Asynchronous buses represent a compromise between performance and cost. Buses are generally used to connect physically distributed components that are far enough apart that significant propagation delays are incurred when sending signals from one component to another. If all communications were run to a common clock, that clock would run very slowly. It certainly doesn't make sense to force the components to run their internal clocks at the same rate as the external bus. So the bus must be designed to hide timing problems from the components. Many modern buses do in fact use clock signals distributed on the bus with all bus signals synchronized to that clock. However, the bus clock runs much more slowly than and independent of the components' internal clocks.

**Figure 6-50** An asynchronous element.

 


*control signals as clocks*

Consider the simple circuit of Figure 6-50. A flip-flop is used to capture a data value from the outside world. The data comes into the flip-flop on the *d* signal; *d* is guaranteed to be stable for a certain minimum period.

But when does it arrive? The flip-flop requires a clock signal that obeys the setup and hold times of the flip-flop. We use the  $c$  signal to tell the flip-flop when the data on  $d$  is ready. This costs an extra signal but it provides a good deal of timing flexibility. Even if we cannot guarantee absolute delays between the components on the bus, we can design the bus so that the relative delays between signals on the bus are closely matched. (This requires carefully controlling crosstalk, capacitive load, *etc.*, but it can be done.) Because the relative delays of  $d$  and  $c$  are known, generating them with the proper timing at the source ensures that they will arrive at the destination with the same timing relationship. Thus, we can generate the timing information required by the flip-flop and send it along with the data itself.

**Figure 6-51** Timing constraints on a flip-flop.

 

#### *capturing events*

We will use flip-flops (or latches) to capture signals sent over the bus. We must be more careful about timing constraints when we design logic for a bus. In a fully synchronous system, we tend to separate combinational logic delays and clock skew, controlling the clock skew so that we only have to check a straightforward delay requirement for all the logic. Every signal on a bus, in contrast, may have its own timing. The fundamental requirements for a flip-flop are its setup and hold times. These constraints then become constraints on the incoming data and control signals. In Figure 6-51, the  $t_1$  constraint comes from the flip-flop's setup time while the  $t_2$  constraint comes from its hold time. We can draw a similar timing diagram for a latch-based bus receiver.

*timing constraints*

These two constraints are defined in terms of the events on the *c* and *d* lines. We can name the events as follows:

- $t_{d1}$  = time at which *d* becomes stable;
- $t_{d2}$  = time at which *d* stops being stable;
- $t_{c1}$  = time at which *c* rises.

If the setup time of a flip-flop is  $t_s$  and its hold time is  $t_h$ , then we can write  $t_1$  and  $t_2$  as

$$t_1 = t_{c1} - t_{d1} \geq t_s, \tag{EQ 6-14}$$

$$t_2 = t_{d2} - t_{c1} \geq t_h. \tag{EQ 6-15}$$

The equations for  $t_1$  and  $t_2$  define them in terms of events on the bus while the inequalities constrain the minimum time between the events. We don't in general know the exact times at which  $t_{d1}$  and  $t_{d2}$  happen. But the constraint is written in terms of the difference of the two times, which we can directly relate to the flip-flop setup and hold times. Given a particular technology, we determine its setup and hold times and substitute those values into the inequalities.

*communication and timing*

All the timing constraints on the bus ultimately come from the components used to build the bus. How we view them depends on our point of view in the bus. Our own component imposes **timing constraints** that must be satisfied from the inside. The component with which we want to communicate imposes **timing requirements** from the outside.

**Figure 6-52** Two components communicating over a bus.


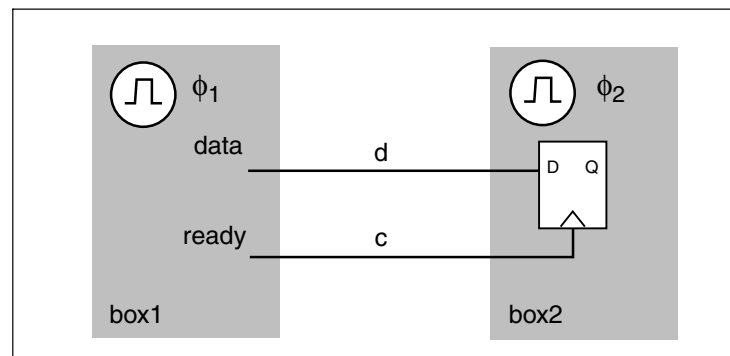


Figure 6-52 shows the flip-flop-based bus receiver in the context of the bus. *Box1* wants to send a value to *box2*. Each component has its own clock:  $\phi_1$  for *box1* and  $\phi_2$  for *box2*. For the moment, let us assume that

*box1* somehow generates the data signal and a ready signal that has the proper timing relationship to the data. Those two signals are sent along the bus's *d* and *c* wires. The *c* control signal causes the flip-flop to remember the data on *d* as it arrives.


**Figure 6-53** A metastable state in a register.

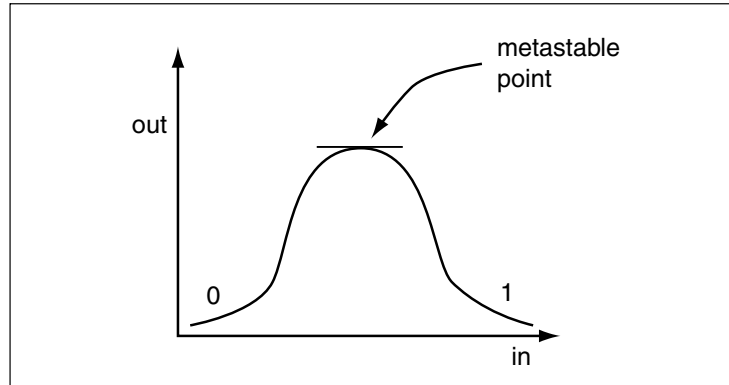

*metastability*


One problem we must consider when transmitting signals asynchronously is **metastability** [Cha72]. A flip-flop or latch typically remembers a 1 or 0 reliably. As shown in Figure 6-53, the register has two stable states representing 0 and 1. However, if the data does not satisfy the setup and hold times and is changing around the critical interval for the clock, then a bad value may be stored. If the captured value is near the stable 0 or 1 state, then the memory element will quickly roll down the hill to the stable value. However, if the value is in the metastable region, then the memory element captures a value that is finely balanced between the stable 0 and 1 states. This metastable point is not totally stable because the value will eventually move toward either 0 or 1. However, the amount of time it takes the memory element to move to a 0 or 1 is unbounded. Either the receiver must be able to detect a metastable state and wait for it to resolve or the receiver will get a corrupt value.

**Figure 6-54** A multi-stage synchronizer that minimizes metastability problems.

 



We can minimize the chance of metastability with the **multi-stage synchronizer** shown in Figure 6-54. It has two flip-flops, both under control of the clock that controls the receiving logic. The key part of the design is that the data is captured twice: the signal is sampled by the first flip-flop and that result is resampled by the second flip-flop. Because the synchronizer is basically a shift register, it takes two clock cycles to see the received value. But even if the first register goes metastable, it is less likely that the second register will also go metastable. Metastability cannot be eliminated, however, and there is always a small chance that the output of the multistage synchronizer will be metastable. It is possible to build a multistage synchronizer with more stages, but the additional stages will only slightly improve the probability of eliminating metastability and will definitely add latency.

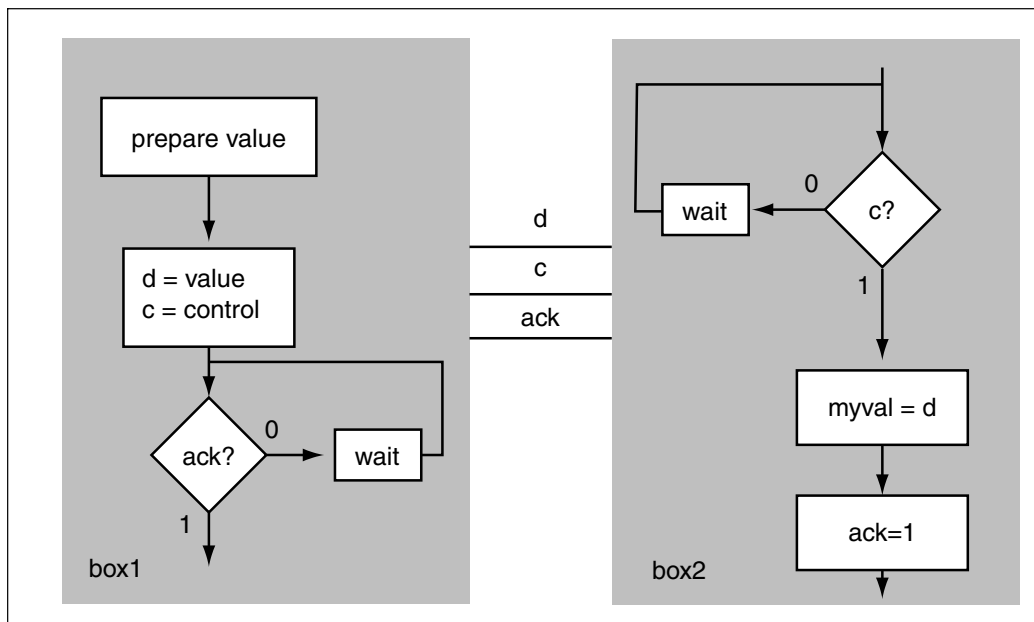


**Figure 6-55** A flowchart of communication on a bus.

#### *bus protocols and events*

Now that we understand how to receive asynchronous signals, we can start to consider the complete bus system. Before delving back into the components and their timing requirements, let us step back to remember the functionality of a bus transaction. Figure 6-55 shows a flowchart that functionally approximates the behavior of the components on the bus. We say *approximates* because flowcharts are not designed for asyn-

chronous behavior, but this chart gives you a basic idea of the flow of control between the two components. This chart shows a handshake so that we can consider how to generate an acknowledgment from the receiver. Once *box1* has prepared the value it wants to send, it then transmits both the data and an associated control signal. Meanwhile, *box2* is waiting for that control signal. When it sees the control, it saves the value and sends an acknowledgment. Once *box1* sees the *ack* event, it goes on to further processing. We have already seen the circuitry used for *box2* to receive the event; we also need circuitry for *box1* to generate the event and for *box2* to generate an acknowledgment.

**Figure 6-56** Bus logic for *box1*.

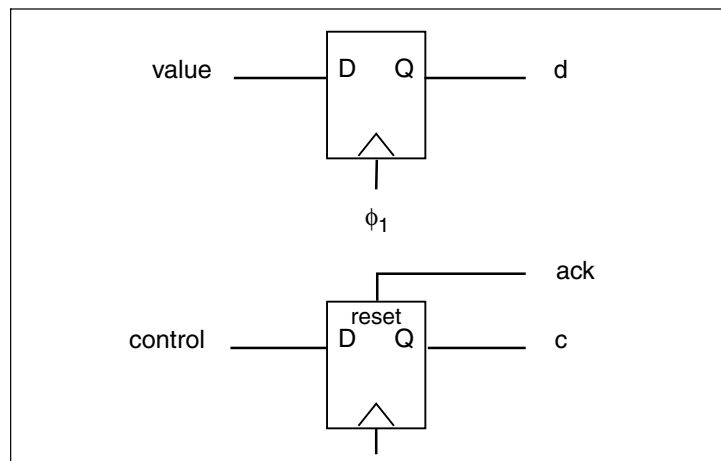


#### *logic implementations*


Figure 6-56 shows the bus logic in *box1*. The data value is stored in a flip-flop to be held on the bus. The control signal for the bus is generated by another flip-flop. The *ack* signal causes the flip-flop that holds the control value to reset itself. Because both flip-flops are clocked by the internal clock  $\phi_1$ , we know that they will acquire their values at the same time. If we need to change the delay of *c* relative to *d* in order to meet setup and hold constraints on the other side, we can add delay to one of the signals using a delay element.

Figure 6-57 shows the logic on the *box2* side of the bus. The first flip-flop captures the data signal using *c* as a clock for activation. The next flip-flop samples *c* to tell when the data has arrived. After one tick of the internal clock  $\phi_2$  that flip-flop sends out an acknowledge signal. When *c* goes low, it resets the second flip-flop to drop the *ack* signal.

**Figure 6-57** Bus logic for *box2*.

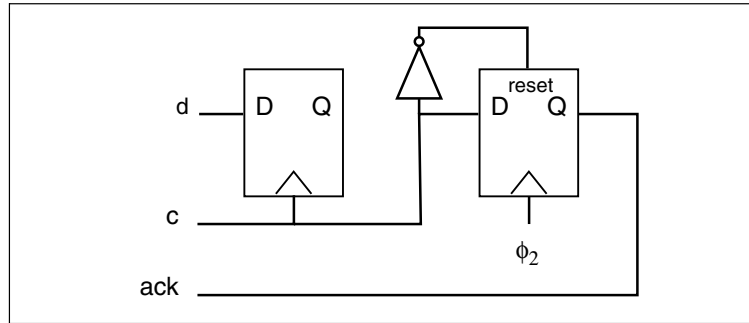

**Figure 6-58** A timing diagram for the bus.

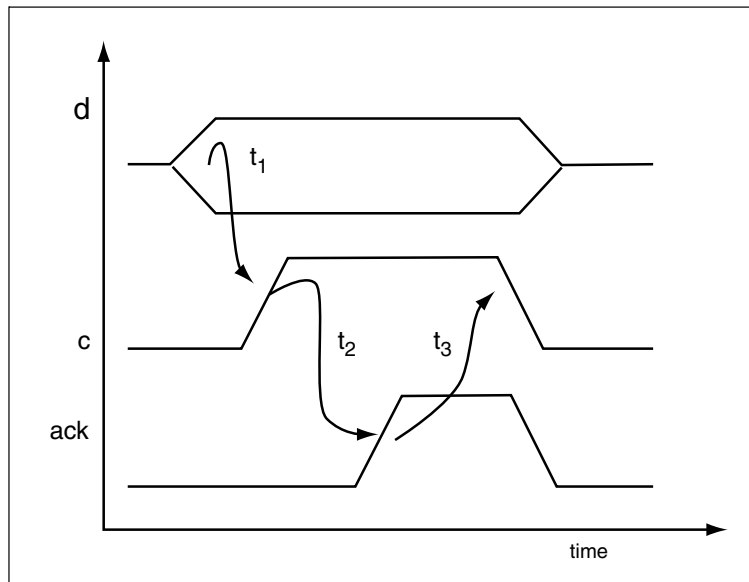

*bus timing*

Figure 6-58 shows a timing diagram for the bus. We can write some timing relations for this bus, using these names for the events:

- $t_{d1}$  = time at which  $d$  becomes stable;
- $t_{d2}$  = time at which  $d$  stops being stable;
- $t_{c1}$  = time at which  $c$  rises;
- $t_{c2}$  = time at which  $c$  falls;
- $t_{ack1}$  = time at which  $ack$  rises.

If the setup and hold times of all the flip-flops are  $t_s$  and  $t_h$  respectively then we can write the constraints as

$$t_1 = t_{c1} - t_{d1} \geq t_s, \quad (\text{EQ 6-16})$$

$$t_2 = t_{ack1} - t_{c1} \geq t_h. \quad (\text{EQ 6-17})$$

$$t_3 = t_{c2} - t_{ack1} \geq t_h. \quad (\text{EQ 6-18})$$

We could also constrain the fall time of the  $ack$  against the next bus cycle to be sure that enough time is left to properly capture the value.

### 6.10.5 Microprocessor and System Buses

*types of buses*


Buses are often used to connect microprocessors to memories and peripherals. Microprocessor buses have come to influence the design of other buses as well. As shown in Figure 6-59, a **local bus** is used to connect the microprocessor to high-speed memory while a **system bus** is used to connect the local bus to peripherals. The component that connects two buses is called a **bridge**. A local bus must provide very high performance to avoid slowing down the microprocessor during the fetch-execute cycle; system buses come in a wide variety of cost/performance points. However, these two different types of buses share some common characteristics due to their common heritage.

Buses usually talk to devices using addresses. Each device on the bus is assigned an address or a range of addresses. The device responds when it sees its address on the address lines. Separate lines are used to send and receive data. Further lines are used to provide the control signals required to show when data and addresses are valid, etc.


*master-slave operation*

Buses are generally **master-slave** systems: one component controls the operation of the bus and the other devices follow along. A slave device may send data on the bus but only when the master tells it to. The mas-

**Figure 6-59** Buses connected by a bridge.

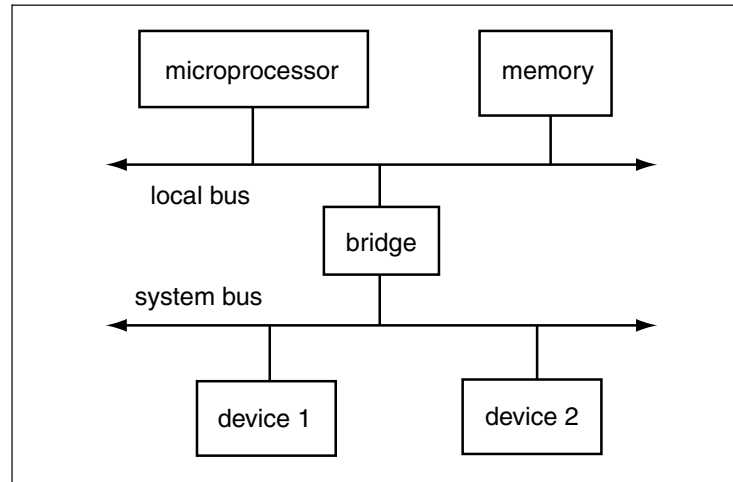

ter, in contrast, initiates all the various types of operations on the bus. In a microprocessor system the microprocessor typically acts as the bus master. The other components in the system are assigned addresses to identify them.

 

**Figure 6-60** Basic signals in a bus.

*signals on buses*

Figure 6-60 shows some of the basic signals in the bus. The *ctrl*, *adrs*, and *data* lines are used for basic bus transactions, such as reads and writes. When another device wants to become the bus master for some time, it uses the *bus request* and *bus grant* signals. This protocol is typically a four-cycle handshake, with the handshake completed only when

*bus characteristics and standards*

the new bus master has finished and returns control to the default bus master. The process of choosing a master for the bus is known as **bus arbitration**. Bus arbitration logic must be carefully designed: not only must it be fast, it also cannot afford to grant two devices mastership of the bus under any circumstance.

Buses differ greatly in their details:

- **physical** The bus standard often specifies size of the connector and cards.
- **electrical** Different voltages and currents may be used for signaling. The bus may also define the maximum capacitive load allowed.
- **protocols** Buses may use different protocols that trade off speed and flexibility.

The Peripheral Component Interconnect (PCI) bus [Min95] is a widely used standard originally developed for PCs. The PCI standard is very complex. The next example touches upon some aspects of PCI to illustrate some bus concepts.

---

**Example 6-2**  
**The PCI bus**

PCI was developed as a high-speed system bus to replace ISA and Micro Channel in PCs. The standard has been extended several times and PCI variants are now used in a wide variety of digital systems.

The standard describes both 33 MHz and 66 MHz implementations. PCI uses a non-terminated bus and its electrical design takes advantage of reflections to reduce the switching time on the bus. The bus includes a clock signal, CLK, that has a 30 ns period at 33 MHz and a 15 ns period at 66 MHz.

The bus has several types of signals (the PCI spec uses # to mean negation):

- System signals:
  - **CLK** The system clock is an input to all PCI devices.
  - **RST#** The reset signal initializes all PCI configuration registers, state machines, and drivers.

- Address/data bus:
  - **AD[31:0]** The combined address and data bus, normally 32 bits but can be extended to 64 bits.
  - **C/BE#[3:0]** Command or byte enable defines the type of transaction.
  - **PAR** Set by the sender to ensure even parity on the address lines and C/BE#.
- Transaction control signals:
  - **FRAME#** Indicates the start and duration of the transaction.
  - **TRDY#** Target ready is driven by the currently-addressed target and is asserted when the target is ready to complete the current data transfer.
  - **IRDY#** Initiator ready is driven by the bus master and indicates that the initiator is driving valid data onto the bus.
  - **STOP#** Allows the target to tell the initiator to stop the transaction.
  - **IDSEL** Initiation device select is used as a chip select while accessing device configuration registers.
  - **LOCK#** Locks the currently-addressed memory target.
  - **DEVSEL#** Device select is asserted by the target when it has decoded its address.
- Arbitration signals:
  - **REQ#, GNT#** Request and grant lines from each device are connected to the bus arbiter. The arbiter determines which device will be the next master.
- Interrupt request signals:
  - **INTA#, INTB#, INTC#, INTD#** Allow devices to request interrupts.
- Error reporting signals:
  - **PERR#, SERR#** Used to report parity and system errors, respectively.


PCI handshakes to transfer data. The source of the data must assert its ready signal when it drives data onto the bus. The receiver does not have to respond immediately and only raises its ready line when it is ready to receive. If the receiver takes more than one clock cycle to respond, the

---

---

intervening clock periods are known as **wait states**. Once a sender or receiver indicates that it is ready to complete a data phase, it cannot change its control lines until that phase is done.

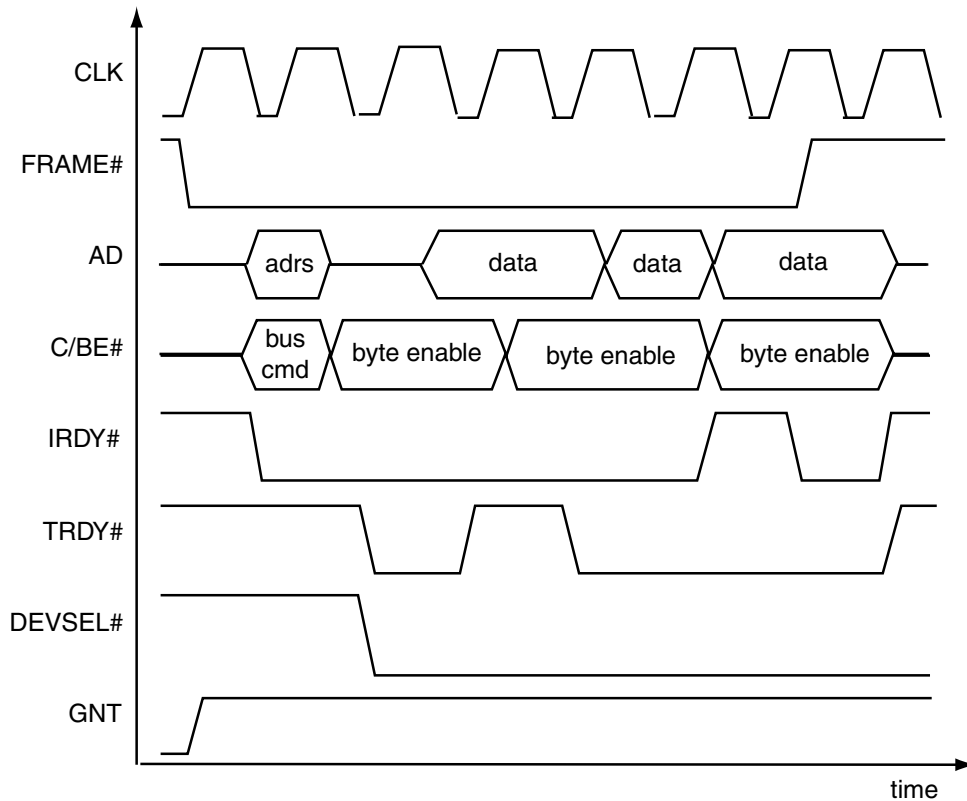Here is a timing diagram for a sample read transaction, in which an initiator reads several locations from a device:



The read transaction starts with the initiator asserting a valid start address and command on the bus and raising FRAME#. The address is written onto AD and the command asserted onto C/BE.

On the next cycle, the initiator stops driving AD. This cycle is used to turn around the AD lines, ensuring that two devices don't try to drive them at the same time. The initiator uses the C/BE lines on this cycle to signal which byte lanes will be used. It also asserts IRDY# to show that it is ready to receive the first datum from the device.



On the third cycle, the target device asserts DEVSEL# to show that it has recognized its address. It also starts to drive the data onto the AD bus and asserts TRDY# to show that the data is on AD. Since the second cycle was used to turn around AD, the target device can now safely drive the data onto AD without electrical conflicts.

PCI supports multi-word transfers. When the initiator continues to assert IRDY# but does not deassert FRAME#, the transaction continues to the next data item. The address is sent at the start of the transaction but not with every datum. The target must remember the starting address and increment it as necessary to keep track with the current address.

If the target needs a wait state, it can deassert TRDY# to tell the initiator that it needs more time. A total of three data elements are transferred on this bus transaction. Two of them require wait states—each datum can take a different number of wait states.

At the end of the transfer, the initiator deasserts IRDY# and the target deasserts TRDY# and DEVSEL#. The PCI bus is now ready for the next transaction.

The PCI bus is arbitrated by a central arbiter. Each potential master is connected to the arbiter by its own REQ# and GNT# signals. A device can remain master as long as it wants after it gains bus mastership. The arbiter's main task is to choose the next bus master when several devices simultaneously request the bus. The PCI standard does not define the arbitration algorithm but it does require that a fairness algorithm be used to avoid deadlocks on the bus. *Round-robin* is a common example of a fair arbitration scheme.

PCI allows the bus arbitration process to occur while a transfer is taking place. The new master gains control of the bus at the end of the current transfer. *Hidden arbitration* improves bus performance by overlapping arbitration time with other activities.

---

### 6.10.6 Networks-on-Chips

#### *NoCs as subsystems*

Large chips are sufficiently complex that we need to use packet-based networks, not just wires, to transport data. The processing elements (PEs) may be CPUs or hardwired units. The network must connect memories and I/O ports as well as processing elements. A **network-on-chip (NoC)** provides facilities for data transfer between a large number of units. The network-on-chip serves as an excellent subsystem for com-

---

---

munication: it encapsulates physical and circuit design and provides an abstract interface for processors and memories.


*NoC terminology*

A network-on-chip is built of **nodes** and **links**. A node may be a processing element or memory; it may also be an intermediate point in the network. The two major types of network nodes are **switches**, which do not process information, and **routers**, which perform more complex tasks. A link transmits bits between nodes in the network. A **packet** holds a destination address and its associated data. Packets in NoCs are usually relatively small (compared to Internet Protocol packets) and of uniform size, and are therefore often referred to as **flits**.

*NoC modeling*


Serpanos and Wolf [Ser07] analyzed the asymptotic characteristics of networks-on-chips and provided basic models for performance. They assumed that the NoC connected  $N$  cores (processing elements, memories, or I/O ports); they normalized distances to the size of a core in one dimension, so a string of  $N$  cores side-by-side has length  $N$ .

**Figure 6-61**  
Electrical model  
for a bus.

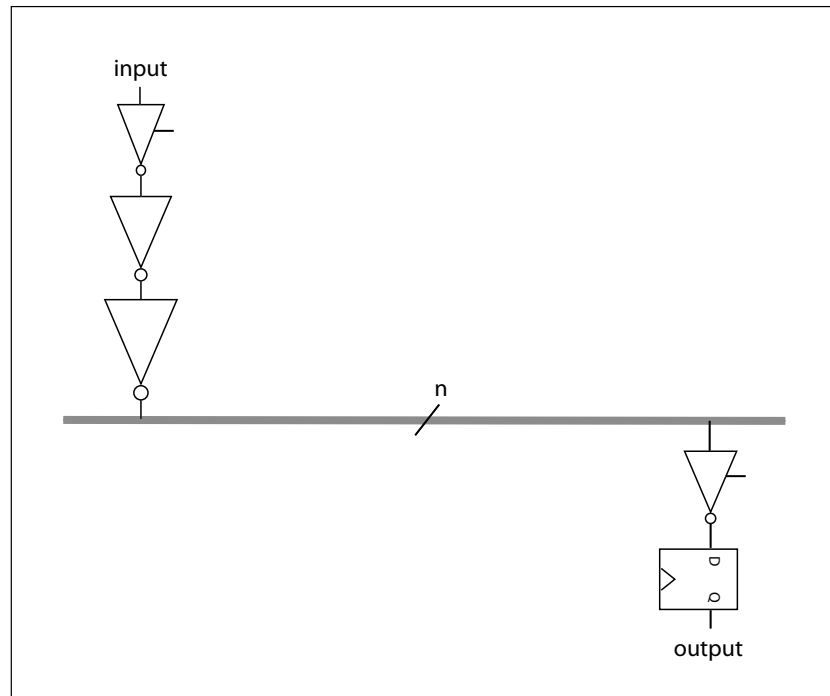

The simplest type of network is a bus, which we will use as a reference against which to compare our more sophisticated networks. Figure 6-61 shows an electrical model for a bus [Ser07]. Each bus input is connected to a chain of cascaded drivers whose delay is described by Equation 3-17. The bus trunk is a set of long wires. Because the bus is bi-directional, we model it as an unbuffered long wire whose delay is given by Equation 6-25. Each output has a three-state driver and a register. The

**Figure 6-62** A crossbar.

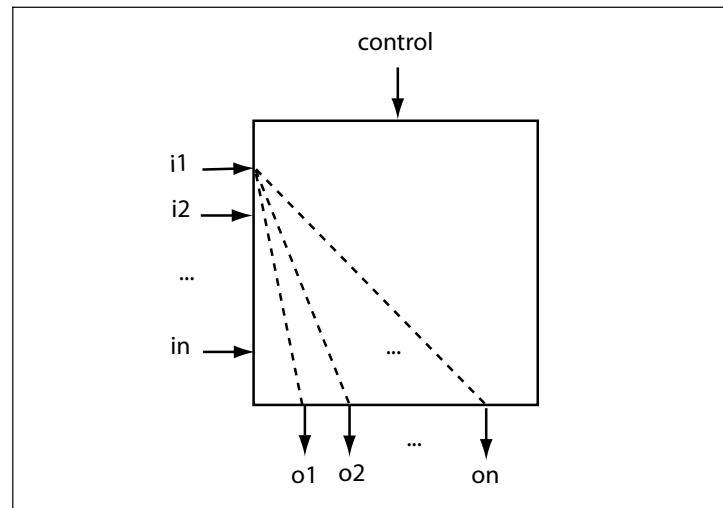

largest components of the delay are the cascaded drivers at the input and the bus trunk. They found the bus delay to be:


$$\delta_b = k_1 C_L^{1/k} N^{1/k} + k_2 N + k_3 N^2. \tag{EQ 6-19}$$

*crossbar*

An important category of switch is the **crossbar**. As shown in Figure 6-62, a standard crossbar has  $N$  inputs and  $N$  outputs as well as a control input. Any input may be connected to any output or to any combination of outputs as determined by the control. For example, input 2 may be connected simultaneously to outputs 0 and 5.

One way to make a crossbar is using switches as shown in Figure 6-63. A wire from each input connects to  $N$  switches; each switch is connected to one of the  $N$  output wires. (Alternative circuits can also be used at the crosspoints: a transmission gate or a three-state buffer. Both provide improved performance at the expense of a larger crosspoint cell.) Separate control lines determine what switches are on: each output

**Figure 6-63** Model for a switch-based crossbar.

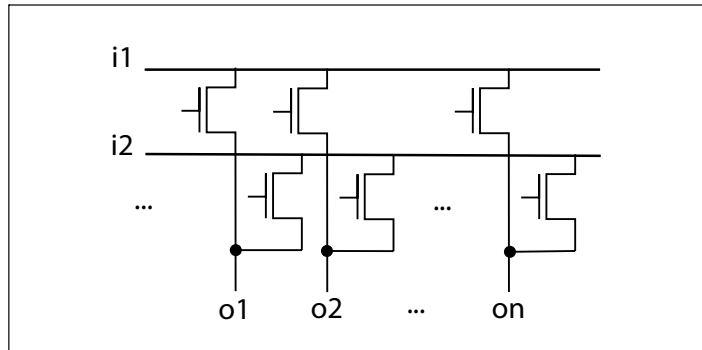

is controlled by  $n$  control signals, one for each switch, giving  $n^2$  control signals for the entire mux. A multicast connection can be made simply by turning on more than one switch. Serpanos and Wolf showed that the delay of this style of crossbar is dominated by the buffered transmission delay formula of Equation 3-40 and can be approximated by

$$\delta_c = 2.5\sqrt{N}\sqrt{R_0C_0R_{int}C_L}. \tag{EQ 6-20}$$

An alternative design uses multiplexers [Cho92]. As shown in Figure 6-64, a tree of 2-to-2 multiplexers is used to select the desired input for each output. Several possible circuits can be used for the multiplexer cell; Dutta *et al.* [Dut98] used a transmission-gate multiplexer. Serpanos and Wolf showed that the delay through this type of crossbar can be approximated by

$$\delta_{cm} = 2\delta_{mux}\log(N-1). \tag{EQ 6-21}$$

*crossbar control*

The crossbar requires logic to generate its control signals. A very simple control scheme is a counter that always sends packets in a given interval to a predetermined location. A more sophisticated controller generates the crossbar control based upon the flit address.


*asymptotic delay comparison*

The asymptotic delay of these different networks are summarized in Figure 6-65 [Ser07]. These results show that the delay of crossbars grows much more slowly than that of the bus. As a result, the relative clock speed of crossbars increases over that of buses as the number of cores on the network increases.

*multi-stage networks*

Multi-stage networks are composed of switches and links. A variety of network topologies can be built [Dua02]. One important design consid-

**Figure 6-64** Architecture of a multiplexer-based crossbar.

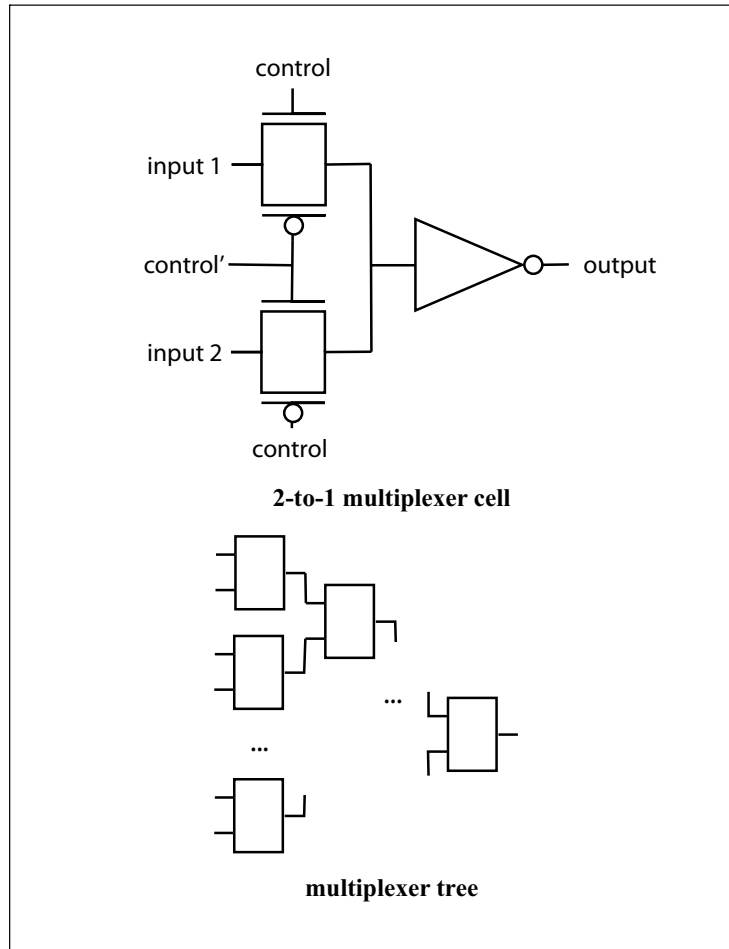

eration in the network is the depth and location of registers. NoCs are usually introduced because data cannot cross the chip in one clock cycle, so registers are necessary at some point. Registers can be placed at the switch inputs or outputs or within the links themselves.

*link design*

Although wide-area networks are often designed with serial links, networks-on-chips may take advantage of the relatively cheap wires available in VLSI. The width of the link, whether an explicit clock is used, and other design choices must be made. The techniques of Section 3.7 and Section 3.8 can be used to design the design the drivers for the links.

**Figure 6-65** Asymptotic comparison of networks [Ser07].


type	delay
bus	$O(N^2)$
switch-based crossbar	$O(\sqrt{N})$
mux-based crossbar	$O(\log N)$

## 6.11 Data Paths

*logical and physical structures*

A **data path** is both a logical and a physical structure: it is built from components that perform typical data operations, such as addition and it has a layout structure that takes advantage of the regular logical design of the data operators. Data paths typically include several types of components: registers (memory elements) store data; adders and ALUs perform arithmetic; shifters perform bit operations; counters may be used for program counters. Buses connected these operators together.

**Figure 6-66** Structure of a typical bit-slice data path.

 


*bit slices*

Most data operations are regular—adders, ALUs, shifters, and other operators can be constructed from arrays of smaller components. The cleanest way to take advantage of this regularity in most cases is to design the layout as a **bit-slice**, as shown in Figure 6-66. A bit-slice, as the name implies, is a one-bit version of the complete data path, and the


$n$ -bit data path is constructed by replicating the bit-slice. Typically, data flows horizontally through the bit-slice along point-to-point connections or buses, while control signals (which provide read and write signals to registers, opcodes for ALUs, etc.) flow vertically.

**Figure 6-67** Abutting cells may require moving pins or stretching.

 

Bit-slice layout design requires careful, simultaneous design of the cells that comprise the data path. Since the bit-slice must be stacked vertically, any signals that pass through the cells must be tilable—the signals must be aligned at top and bottom. Horizontal constraints are often harder to satisfy. The  $V_{DD}$  and  $V_{SS}$  lines must run horizontally through the cells, as must buses. Signals between adjacent cells must also be aligned. While the vertical wires usually distribute signals, the horizontal wires are often interrupted by logic gates. The transistors in the cells impose constraints on the layout that may make it hard to place horizontal connections at the required positions. As shown in Figure 6-67, cells often need to be stretched beyond their natural heights to make connections with other cells.

**Figure 6-68** A simple wiring plan.

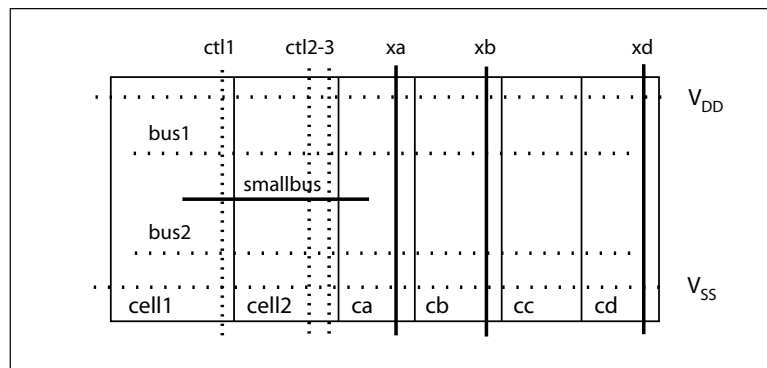

*layer assignments*

The data path's layout design also requires careful consideration of layer assignments. With a process that provides two levels of metal, metal 1 is typically used for horizontal wires and metal 2 for vertical wires. A **wiring plan** helps organize your thoughts on the wires required, their posi-

tions, and the best layers to use for each wire. A black-and-white wiring plan is shown in Figure 6-68; you should draw your wiring plans in color to emphasize layer choices.

*registers*

Two circuit design problems unique to data path design are registers and buses. The circuit chosen for the register depends on the number of registers required. If only a few registers are needed, a standard latch or flip-flop from Section 5.2 is a perfectly reasonable choice. If many registers are required, area can be saved by using an  $n$ -port static RAM, which includes one row enable and one pair of bit lines for each port. Although an individual bit/word can allow only one read or write operation at a time, the RAM array can support the simultaneous, independent reading or writing of two words simply by setting the select lines of the two words high at the same time. One SRAM port is required for each bus in the data path.

---

## 6.12 Subsystems as IP

---

*standards for IP*

When we design a standard cell library, the logical functions are easy to identify and specify, since they generally map onto common register-transfer components. However, as we move to higher levels of abstraction, we need to be more careful about how we describe our modules. As a result, an important part of IP-based design is standards. IP is most useful when transferred between organizations—it can be bought or sold between companies; transfers within a large company are often almost as complex as sales between companies. Standards for the IP itself and the documentation that accompanies the IP are critical for the successful use of the IP. Even within an organization, standards help to increase the lifetime of IP. IP that is designed to a certain style can be transformed and updated more reliably; documentation also helps future designers use and update the IP.

*OCP*

The OCP Partnership (<http://www.ocpip.org>) administers the Open Core Protocol. OCP is designed to help IP components for systems-on-chips to plug-and-play together. OCP defines a socket that separates a core's computational activity from its communication interface.

*SPIRIT*

The SPIRIT Consortium (<http://www.spiritconsortium.org>) administers the SPIRIT standard for the documentation of IP. SPIRIT captures metadata about an IP component in the XML language; information in this form is designed to be shared among tools from multiple vendors. This

---

---



information can be used to guide design creation, configuration, and verification.

The next example describes an open-source bus standard.

---

### **Example 6-3**

## **The Wishbone Interconnection Architecture Standard**

Wishbone [Ope02]<sup>1</sup> is a standard for interconnect of system-on-chip components. Wishbone supports a wide range of implementations based on a standard for signals and protocols.

The basic unit of Wishbone is the master-slave interface. This interface defines a handshaking protocol for the transfer of data between the master and slave, as controlled by the master. A master may be connected to one or more slaves.

Wishbone signals use naming conventions as documentation. Input signals end with `_I` and output signals end with `_O`.

The master-slave interface includes several basic signals:

- The `RST_I` (reset) and `CLK_I` (clock) signals are supplied by the interconnect system to both the master and slave.
- The `ADRS` signal goes from the master to the slave. It appears as `ADRS_O` on the master and `ADRS_I` on the slave. Addresses may be up to 64 bits.
- The data signals are unidirectional. The master output `DATA_O` is connected to the slave input `DATA_I`; the slave output `DATA_O` is connected to the master input `DATA_I`. These signals may be 8, 16, 32, or 64 bits wide. `SEL` signals (`SEL_O` on the master, `SEL_I` on the slave) are used to select subsets of these data signals.
- A write enable signal `WE` goes from the master (`WE_O`) to the slave (`WE_I`).
- The strobe signal (`STB_O` on the master, `STB_I` on the slave) indicates when the data is valid.
- The acknowledge signal (`ACK_I` on the master, `ACK_O` on the slave) is used by the slave to indicate successful transfer of data.
- The cycle signal (`CYC_O` on the master, `CYC_I` on the slave) is used to indicate when a valid bus transfer is in progress.

Wishbone defines three types of bus transfers: the single read/write, the block read/write, and the read/modify/write (RMW).

---

1. <http://www.opencores.org/projects.cgi/web/wishbone/wishbone>


---

Let's consider a single read transfer. At the start of the transfer, the master asserts address, write enable, select, strobe, and cycle. The slave that is addressed puts the data on its data output lines and asserts acknowledge. The master then stores the data presented by the slave and negates its strobe signal.

Wishbone does not mandate the type of interconnect used to implement master-slave connections. A Wishbone-compliant interconnect system may use point-to-point wiring, a bus, a crossbar, or any other interconnect topology.

Wishbone mandates a minimum set of documentation for any IP core that complies with the standard. The documentation must include elements such as signal names and widths, endianness, and constraints on the clock signal.

**Figure 6-69** Functional verification of soft IP.

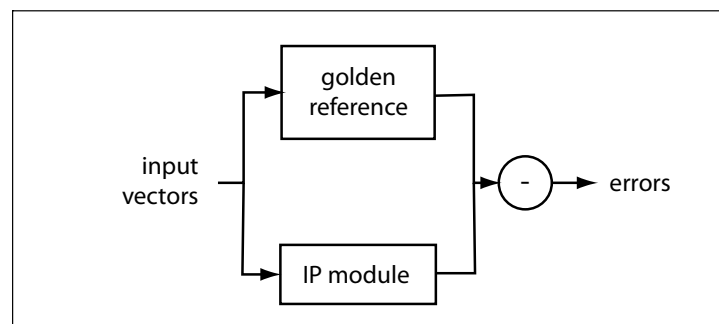

*functional verification  
of soft IP*

Because soft IP is not bound to a particular technology, design verification concentrates on functionality. As shown in Figure 6-69, a golden reference is prepared that calculates the proper output given an input. This golden reference should either be included in the module's specification or easily derivable from the specification. By simulating the IP module and generating the expected outputs, we can determine whether they agree. If they do not agree, the error may be in either the IP module or the golden reference, but hopefully the golden reference is accurate and error-free. The IP module and/or the golden reference can be implemented on an FPGA to speed up the comparison process. The input vectors should be chosen to thoroughly exercise the module; given that this process is performed only once, before the IP module is released, we can afford to generate a large input vector set.

*quality assurance*

The most widely used quality assurance process for IP modules is the **Quality Intellectual Property (QIP) Metric** from the VSI Alliance

(<http://www.vsi.org>). The metric is embodied in a Microsoft Excel spreadsheet, available from the VSIA Web site, that allows IP providers to assess many different aspects of their models. The result is a set of scores that can be quickly scanned by IP users to help them understand whether your IP module meets their needs. The next example looks at the QIP process in more detail.

---

### **Example 6-4** **The QIP Metric**

The QIP Metric spreadsheet is divided into several pages, each of which can be accessed in Microsoft Excel by a tab.

The summary page has entries for some basic information about the vendor. It also provides the scores that are generated as information throughout the spreadsheet is filled in. Several of these questions are multiple choice. Under type of IP, you can select hard IP, digital soft IP, verification IP, software IP, or mixed-mode IP; your selection will determine the questions in the rest of the spreadsheet. If you select hard IP, additional rows will appear that ask you to specify the type of hard IP: digital, analog or analog mixed signal (AMS), I/O and electrostatic discharge (ESD), memory, or microelectrical mechanical system (MEMS). Another line allows you to specify the names of several process technologies supported by this hard IP. Under type of assessment you can select vendor, vendor and integration, or vendor integration and development. You can also select whether to see summaries or by-category display of information. Questions throughout the remainder of the spreadsheet are categorized as to their importance: imperative, rule, guideline, or optional.

The vendor assessment page asks a number of questions about the IP vendor. These questions are not specific to a particular module. The questions cover many important topics: processes, verification, quality assurance, revision control, distribution, consistency, liabilities, support, documentation, deliverables, and vendor confidence.

The hard IP integration page for digital modules asked about IP maturity assessment, documentation quality, and ease of integration. Documentation quality questions cover the IP integration manual, characterization report, test plan, test chip report, silicon interoperability, and release notes document. Ease-of-integration questions include configurability and parameterization, build environment, extensibility, system level modeling, hardware interfaces, block-level verification environment, electrostatic discharge protection, ease of integration rules, and system-on-chip integration.

---

---

Hard IP development for digital modules covers IP ease of reuse and design and verification quality. Ease of integration questions include configurability and parameterization, build environment, portability, extensibility, system-level modeling, block-level verification environment, electrostatic discharge protection, and ease of integration rules. Design quality questions cover internal design documentation and design detail (systems engineering, analog design, schematics, physical design, design style, scripts, and design for test and manufacturing). Verification quality questions include basic verification techniques, coverage, configuration, simulation and regression scripts, and silicon validation.

The soft IP integration page relates to IP ease-of-reuse and design and verification quality. Questions on ease of reuse relate to an assessment of the maturity of the IP module, documentation, and ease of integration. The documentation questions ask for several different types of documentation: product brief, IP integration manual, detailed data sheet, programmers' reference manual, and release notes. Questions on ease of integration cover configurability/parameterization, build environment, portability, extensibility, system level modeling, application programming interfaces (APIs), hardware interfaces, ease of synthesis, block-level self-test, and SoC verification assistance. Questions on design relate to embedded memories, reset guidelines, coding styles (including clocking and synthesis) design-for-test and manufacturing and scripts. Questions on verification quality include configuration, regression and simulation, verification components, protocol checking, and process checklist.

The soft IP development page is also divided into IP ease of reuse and design and verification quality sections. Ease of reuse questions consider configurability and parameterization, portability, extensibility, hardware interfaces, ease of synthesis, and block-level self test. Design and verification quality questions consider internal IP design documentation, design detail, and verification quality.

The quality levels page describes in detail the scores associated with different levels of achievement. The definitions page gives definitions of many terms used in the metrics.

---

---

## 6.13 References

---

*Introduction to Algorithms* by Cormen, Leiserson, and Rivest [Cor90] includes a detailed comparison of the computational complexities of various addition and multiplication schemes. As they point out, asymptotically efficient algorithms aren't always the best choice for small  $n$ . I am indebted to Jack Fishburn for an explanation of transistor sizing in carry chains. Books by Shoji [Sho88] and Glasser and Dobberpuhl [Gla85] describe circuit designs for interesting components; *The MIPS-X RISC Microprocessor* [Cho89] provides a good survey of the components used for a CMOS microprocessor. Hodges and Jackson [Hod83] give a good introduction to RAM and ROM design; more detailed discussions can be found in Glasser and Dobberpuhl and Shoji. The static RAM layout of Figure 6-23 was designed by Kirk Nolan of Princeton University. Keitel-Schulz and Wehn [Kei01] discuss embedded DRAM technologies. This description of image sensors is based upon the class notes of Prof. Abbas El Gamal of Stanford; Nakamura's book [Nak06] describes the state-of-the-art in image sensors in detail. Books by Jantsch and Tenhunen [Jan03] and De Micheli and Benini [DeM06] describe network-on-chip design in detail.

---

## 6.14 Problems


---

Q6-1. Design a barrel shifter built from static gates and clocked inverters. Draw a schematic for a cell and for a tiling of cells similar to the drawings for the pass-transistor version of Figure 6-3.

Q6-2. Design a ripple-carry adder using NAND gates and inverters:

- a) Draw a schematic for a full adder cell.
  - b) Size the transistors in a four-bit full adder using logical effort.
- 
-

 Q6-3. Here is a one-bit carry unit using P and G:



Size the transistors in the gates using logical effort, ignoring any connections to the adders.

Q6-4. Draw a logic diagram for the carry-skip logic for  $m=3$ .

Q6-5. Draw a transistor-level schematic for a four-bit Manchester carry chain. Use it to show the critical delay path for these values of  $a$  and  $b$  addends (assume that the carry in is 0):

- $a = 1010, b = 1011$ .
- $a = 0110, b = 1011$ .
- $a = 1111, b = 0001$ .

Q6-6. Draw a logic diagram for an ALU that performs these functions:  $a$  AND  $b$ ,  $a$  OR  $b$ ,  $a$  XOR  $b$ , NOT  $a$ ,  $a + b$ ,  $a - b$ .

Q6-7. Draw a logic diagram for the adder/subtractor of a Booth multiplier.

Q6-8. Draw a transistor-level circuit diagram for a pseudo-nMOS row decoder.

Q6-9. Draw a transistor-level circuit diagram for a three-input SRAM core cell.

Q6-10. Estimate the size of a lookup table in the style of Figure 6-35 when  $n=2$  (4 configuration bits). To make your estimate, assume that the average transistor and associated wiring and other layout elements is  $1 \mu\text{m}^2$ ; make your estimate by counting the number of transistors in the lookup table component. Ignore the circuitry necessary to load the configuration bits.

Q6-11. Draw a transistor-level circuit diagram for a simple FPGA interconnection network. The network has four inputs: north, south, east, and west. Each of these signals can be connected to the others in any combination using configuration bits. Ignore the circuitry necessary to load the configuration bits.

Q6-12. Write inequalities for the timing constraints of Figure 6-51 that show how  $t_1$  and  $t_2$  are determined from  $t_s$ , the flip-flop setup time, and  $t_h$ , the flip-flop hold time.

Q6-13. Draw a timing diagram similar to the diagram of Figure 6-51 that shows the timing requirements on a latch-based bus receiver. Explain the origin of each of the timing requirements.

Q6-14. Show the timing constraints that might be required between the end of one four-cycle handshake to the beginning of the next.

Q6-15. Draw a state transition graph for a simple bus that performs read operations but does not allow wait states—all transfers take one cycle. The bus uses a clock signal. Define all other signals required on the bus.

Q6-16. Draw a state transition graph for the PCI read operation shown in Example 6-2.

Q6-17. Derive the bus delay model of Equation 6-19.

Q6-18. Draw a transistor-level circuit diagram for a 2-input x 2-output crossbar made from switches.

Q6-19. Draw a transistor-level circuit diagram for a 2-input x 2-output crossbar made from tri-state buffers.

---

---

# 7

# Floorplanning

## Highlights:

Floorplanning styles and methodology.


Global routing.

Clock distribution.

Power distribution.

Packaging and pads.



 

A slicable floorplan (Figure 7-8).

---

## 7.1 Introduction

---

In the last chapter we built architectures from fairly abstract components. This chapter looks at the chip in more detail. We will assume that the block diagram is fixed; now we will study chip-level layout and circuit design. The size of the design problem requires us to develop different methods than we used to design the layout for a single NAND gate. But the basic objectives—area, delay, power—are still the same.

The next section describes methodologies for designing floorplans. Section 7.3 concentrates on global signals, including power and clock. Section 7.4 touches upon methodologies for floorplanning. Section 7.5 describes the characteristics of packaging and off-chip connections, including pads.

---

## 7.2 Floorplanning Methods

---

This section concentrates on placement and routing at the chip level. We start with a discussion of the basic problems in floorplanning, then move onto routing and its effects on placement.

### 7.2.1 Chip-Level Physical Design

*chip-level layout*

**Floorplanning** is chip-level layout design. When designing a leaf cell, we used transistors and vias as our basic components; floorplanning uses the adders, registers, and FSMs as the building blocks. The fundamental difference between floorplanning and leaf-cell design is that floorplanning works with components that are much larger than the wires connecting them. This great size mismatch forces us to analyze the layout differently and to make different trade-offs during design.


*floorplan styles*

Many chips are composed from cells of a variety of shapes and sizes, as shown in Figure 7-1. We call the layout cells **blocks** during floorplanning because we use them like building blocks to construct the floorplan. In **bricks-and-mortar** style layout, the cells may have radically different sizes and shapes. The layout program must place the components on the chip by position and orientation, leaving sufficient space between the components for the necessary wires. Blocks may be redesigned to change their aspect ratio in order to improve the floorplan. As

---

---

**Figure 7-1** A typical layout, built from a variety of styles.

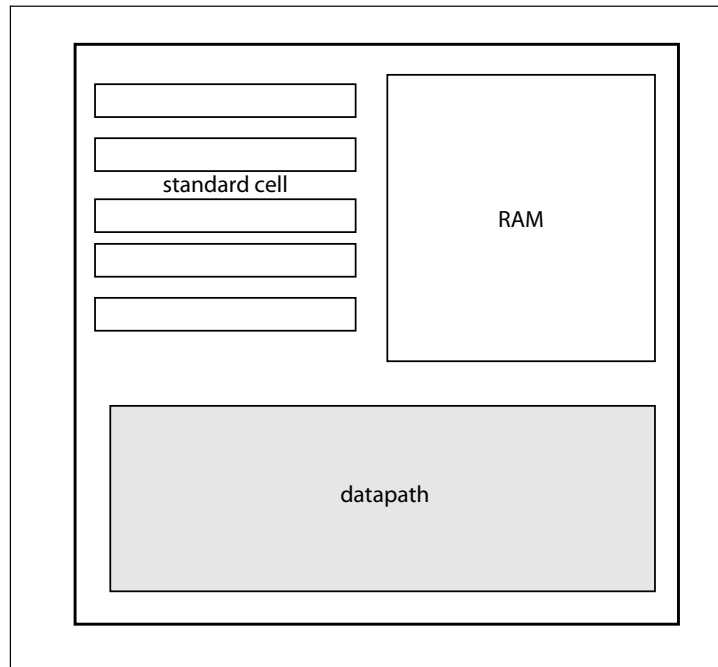

we will see, the more complex traffic pattern of wiring areas makes routing wires in a bricks-and-mortar layout much harder than in a standard cell layout. (Some people use the term *standard cell* for any layout, including bricks-and-mortar, that is built from pre-designed components. Since *standard cell* is a much abused term, be sure you understand its meaning in the context in which it is used.)

The next example shows the floorplan for a large chip.

---

### **Example 7-1** **Floorplan of the** **IBM Power 2** **Super Chip**

The IBM Power 2 Super Chip (P2SC) is a microprocessor with over 15 million transistors (5.7 million logic, 9.3 million cache) on an  $18.2 \times 18.4 \text{mm}^2$  die. The chip is fabricated in a  $0.27\mu\text{m}$ , 5-level-metal process. The chip comes in 120 and 135 MHz versions.

---

The chip photomicrograph has been overlaid below with the floorplan showing the major functional units:

 


Photo courtesy of IBM.

This chip is large enough that each of the units in the chip-level floorplan has its own internal floorplan. The DCU units contain memory arrays as well as driver and control logic. The ICU unit contains several data paths along with the necessary control logic.

---

---

*phases of floorplanning*

Floorplanning is divided into three phases: block placement, global routing, and detailed routing. These three phases successively refine the design until the layout is complete. Block placement, as the name implies, places the blocks on the chip.

Floorplanning occurs throughout the design process:

- Early in the design process, a floorplan is designed using estimates of the sizes of the blocks and of the number of wires between those blocks. The area required for wiring is estimated during floorplanning. This initial floorplan serves as a budget for the design—if the sizes of components or of wires actually implemented are significantly different from those in the initial floorplan, the floorplan needs to be rethought. Having a budget for blocks and wires encourages the designers of those sections to live within their allocated areas.
- The design of the initial floorplan defines the interface requirements for the blocks. Once those blocks are designed, the chip layout can be assembled from the blocks. Blocks may need to be modified due to errors in estimating the properties of the blocks during floorplanning.

*global and detailed routing*

Even with layout design divided into placement and routing, the design of the complete chip layout is a daunting task. Chip-level wiring design is usually divided into two phases: **global routing** assigns wires to routing channels between the blocks; **detailed routing** designs the layouts for the wiring. Placement and global routing divide the routing region into smaller sections that can be designed independently, greatly simplifying the detailed routing of those sections.

*floorplanning tools*

Interactive floorplan editors and global placement-and-routing tools are a big help in floorplan design. The size of the floorplan and the disparity in scales between large blocks and individual wires make it difficult to manage a manually-designed floorplan. Floorplanning tools may allow you to enter blocks with pinouts, plot rat's nests to evaluate routability, define routing channels, and perform global routing. Global layout tools perform detailed block placement, global routing, and detailed routing, making sure that the results of the various switchbox and channel routing tools are assembled into a complete layout.

The routing methodologies used for digital signals are inadequate for the strict electrical requirements of power/ground and clock nets.  $V_{DD}$  and  $V_{SS}$  must be supplied to the logic gates with minimal voltage drop and must be adequately wide to carry the required current. Clocks must


be distributed throughout the chip to minimize skew. We will discuss the design of these special wires in more detail in Section 7.3.

### 7.2.2 Block Placement and Channel Definition

#### *block placement*


A first cut at floorplanning is to arrange the blocks to minimize wasted space. As illustrated in Figure 7-2, a good way to manually experiment with floorplans is to draw the blocks on graph paper, cut them out, and arrange them on another block of graph paper. A block is characterized by its area and its **aspect ratio** (the ratio of its width to its height). The wiring between the blocks (such as a rat's nest plot) can be used to adjust the positions of the blocks.

**Figure 7-2** A floorplan sketch.

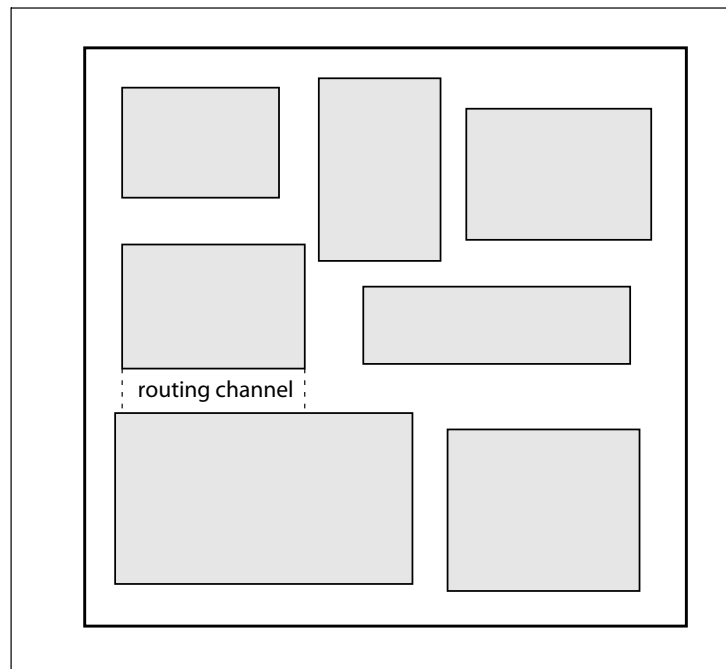

Don't forget to try different rotations and reflections of the blocks. The more similar the blocks, the easier they are to interchange. Interchangeability makes wiring optimization easier. You will probably not be able to avoid a design with a few large blocks and a few small ones, but it may be worthwhile to combine or split some of the blocks, especially blocks built from standard cells, to equalize block sizes as much as possible.

Experimentation with floorplans may suggest that a change to the shape or size of a block would make the floorplanner's job much easier. Changing the shape of a block or splitting a block in two may make use of white space that cannot be removed any other way. If area is important, floorplanning before block design starts can help guide the design of blocks. However, blocks are not infinitely malleable. The internal reorganization of wires and components necessary to change a block's aspect ratio may make it larger, particularly if the block is a tightly designed array of tiled cells; the larger cell may not fit in the desired hole, even with its new shape. Redesigning a block may also unacceptably increase internal delays by making critical wires too long. Floorplanning and block design should go hand-in-hand for best results, but neither can dominate the other.

 

**Figure 7-3** Alternative channel definitions.


#### *routing*

Too much floorplanning without consideration of routing is dangerous. In fact, it is hard to talk about placement without global routing, because most placement decisions are determined by the space needed for wires, not block shape. We have already seen routing channels, which have pins defined on two opposite sides and so can be stretched in one dimension to accommodate more wires. A **switchbox** is a routing area with connections anywhere along its four sides, which means that it cannot grow in either direction. Switchboxes are useful in connecting abutting channels. To take wiring into account during placement, we must define routing channels and switchboxes, then assign nets to paths through those channels/switchboxes. (The job of designing each routing channel/switchbox is left until later.)

#### *channel definition*

The first job is to define the routing channels and switchboxes. We want to break up the space between the blocks into rectangular regions for simplicity during detailed routing; this step is known as **channel defini-**

**tion**, though it defines both two-sided channels and four-sided switchboxes. A natural idea is to use the blocks' edges to define the routing channels; while that idea is useful, it doesn't uniquely define a set of channels for a floorplan. Figure 7-3 shows several examples of channel definition. In each case, we use the blocks to define the ends of rectangular routing regions—think of each block casting a shadow over the space left for routing, with each shadow defining its own routing region.

 

**Figure 7-4** Channel definition changes with block spacing.

Channel definition has no single solution for two different reasons. First, by moving the lighting to change the shadows cast, we can change the channel definition. There is no way to choose the optimum division of the chip into routing regions, though it is probably best to use fewer, larger channels than to break the chip into many small regions. Second, we can change the way shadows are cast by changing the distance between the blocks, as shown in Figure 7-4.

#### *channel height*


We don't know the space required between two blocks—the **channel height**—until we know the number of wires routed through the channel; the best solution is to base the spacing on a rough guess of the required wiring capacity. In both cases, small changes to the problem can give us very different configurations of routing channels and switchboxes with which to work. However, it is very difficult to tell until detailed routing is complete which is best. Often, any of several choices will give roughly equivalent results.

#### *channel graph*

The full geometric description of the channels and switchboxes is cumbersome for global routing—all we really need is the topology of the paths between blocks. The **channel graph** reduces the floorplan to a description of the routes between blocks. As shown in Figure 7-5, each channel is represented by a node. An edge is added between two nodes if those channels abut each other. The paths through the graph correspond to global routes—paths from channel to channel. For example,



**Figure 7-5** The channel graph.

 

two distinct paths from channel A to channel B are (AC, CB) and (AC, CD, DE, EB). Which path is better depends on the locations of the pins to be connected and the congestion of the channels. At this point, the exact layout of the wire within each channel doesn't matter; that is to be determined by detailed routing.


#### *T connections*

If two channels intersect at a T, we can directly connect them. However, the channels in the channel graph cannot be routed in arbitrary order, and that fact influences our choice of floorplan designs. Figure 7-6 illustrates the problem. The connections to a channel are made at its top and bottom; we have complete control over the placement of pins along those edges, but the track to which a wire is assigned is determined by the routing algorithm or human designer. When two channels meet, the top and bottom pins of one are determined, in part, by the tracks of another. We don't know where a wire through the two channels will enter the vertical channel until it is assigned a track in the horizontal channel. Therefore, we must route the horizontal channel first. Any nets in the horizontal channel that connect to the vertical channel must be extended to the far end of the channel. The extended net defines an **end pin** of the first channel on the second channel.


#### *windmills are hard to route*

Channel ordering is a problem for placement and global routing because some channel graphs don't have any feasible routing order. Figure 7-7 shows a **windmill** [Pre79]. Careful examination shows that each channel depends on the one to its left: B depends on A, C on B, D on C, and D on A. As a result, there is no channel we can route first and guarantee that the complete structure can be successfully routed.

**Figure 7-6** Channels must be routed in order.

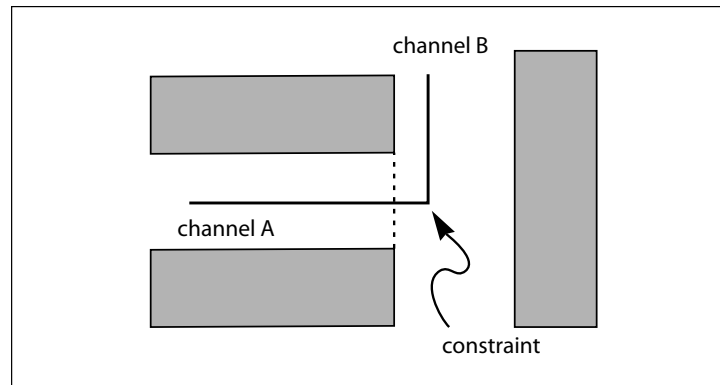


**Figure 7-7** Windmill structures introduce irresolvable constraints on routing order.

 

*slicing structure ensures routability*

The best solution to windmills is to avoid them completely. If the floorplan is a **slicing structure** [Ott80], as shown in Figure 7-8, it has no windmills. A slicing structure can be recursively sliced down to its blocks—a slice is a straight cut through the routing region that separates the chip into two sections. Each section forms a smaller floorplan that can be cut again. Note that there need be only one slice through the whole chip—successive slices can cut the pieces cut by the original slice. (A standard cell layout has several parallel slices through the complete floorplan.) Since a windmill cannot be sliced, any floorplan that is slicable is guaranteed to have no windmills. As a result, its channels can be routed in order such that all the pins on every channel are well-defined at the time it is routed.

**Figure 7-8** A slicable floorplan.

 


### 7.2.3 Global Routing

#### *routing algorithms*

A good algorithm for hand routing is the **line-probe** method introduced by Mikami and Tabuchi [Mik68] and by Hightower [Hig69]. Line-probe routing can work on arbitrary-shaped routing regions; for the moment, we will restrict ourselves to the rectangular switchbox area, with each wire segment already routed as an additional obstruction in the switchbox. As shown in Figure 7-9, the line-probe algorithm starts at one pin on the net and constructs a series of lines along which the other pin may lie. The first probe line is perpendicular to the face which holds the pin and extends to the first obstacle encountered. If the other pin can be reached from this probe line, we are done. If not, we move to the far end of the probe line and construct a new, perpendicular line. A probe line stops when it hits the switchbox edge or an existing wire segment. The search stops when a probe line runs past the other pin or when there is nowhere left to probe. The route between the pins follows the probe lines. This algorithm may not find the shortest route for the wire—it is not even guaranteed to find an existing path. But it often works in practice and is very fast.

#### *utilization as a metric*

We want to choose a global routing that gives the best detailed routing for all the channels and switchboxes. However, it is difficult to estimate the exact results of detailed routing at this stage. At this level of abstraction, a good goal is to equalize **channel utilization**—the number of wires that start, end, or flow through a channel. Density gives a good estimate of utilization without routing the channels. Your goal is to assign wires to paths such that all channels are about equally full. A few rules help:

 **Figure 7-9** Line-probe routing.

- The first nets to route are those whose delays are critical. These wires need to be as short as possible, so they should get priority for the channels that give the shortest paths.
- Some wires may stay entirely within one channel or require a short trip between a few channels with one obvious choice. Route these wires early to get them out of the way.
- Don't be afraid to rip up and reroute wires. You must route the wires in some order. If you find that an earlier decision was bad, remove the wires that are in the way, route the new wires, then reroute the ripped-up wires.


It may be necessary to go through the placement-global routing cycle several times. Some wiring problems may not be fixable by ripping up other wires. If necessary, change the floorplan to get around serious problems. Remember, however, that floorplans are complex—a change that improves one wire's route may make another important wire's route much worse. Repeatedly designing floorplans and global routes is also tedious; you are much more likely to try several floorplans and converge on a good one if you have a CAD tool that can do the detail work for you.

#### 7.2.4 Switchbox Routing

*switchboxes vs. channels*


Switchbox routing is harder than channel routing because we can't expand the switchbox to make room for more wires. As shown in Figure

**Figure 7-10** A switchbox formed at the intersection of two channels.

 

7-10, a switchbox may be used to route wires between intersecting channels. The track assignments at the ends of the channels define the pins for the switchbox. It is often possible to define channels without requiring switchboxes, but switchboxes may sometimes be necessary in floorplanning.

**Figure 7-11** Net ordering can be critical when routing switchboxes.

 

Since a switchbox has fixed pins on all four sides, there are no obvious preferred directions to suggest layer assignments. It is tempting to use the same layer to route both horizontal and vertical segments of a wire, but that can create problems, as shown in Figure 7-11. If the A and B pins are on the same layer, routing B as shown completely blocks A—there is no room to insert a via for the A net.

A common strategy for switchbox routing is to arbitrarily pick layers for vertical and horizontal problems, then to treat the switchbox as a routing

problem with fixed pins at the ends of the channel. While a channel routing algorithm may sometimes fail due to the added constraints, channel routing algorithms can often give reasonably good results in such circumstances.


## 7.3 Global Interconnect

---

In this section, we concentrate on global interconnect. We first look in more detail at the properties of the many layers of wiring available on modern chips. We then consider power distribution and clock distribution in more detail.

### 7.3.1 Interconnect Properties and Wiring Plans

Not all wires are the same. We need to plan our use of wiring layers to make the best use of our available resources.

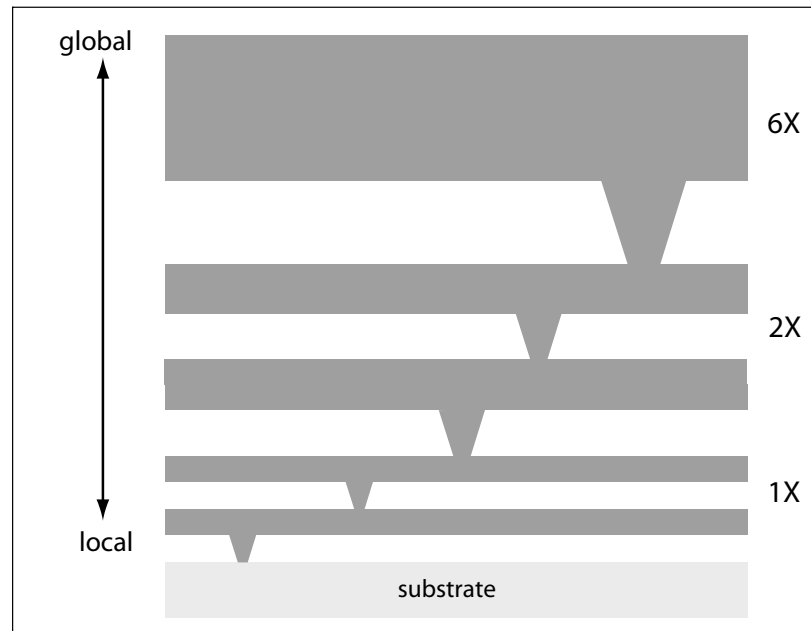

**Figure 7-12** Wiring layers provide several domains of interconnect.

---

---

*resistance vs. size*

Echoing the wiring configuration that we saw in the photomicrograph of Figure 2-15, Figure 7-12 illustrates the wide range in wire dimensions that are available on modern chips. We saw in Section 2.5.2 that wire resistance per unit length grows quadratically if we scale down wire width and height. To combat this problem, manufacturing processes make larger wires on the upper layers. A 2X layer is twice the size of the lowest, most scaled interconnect layer.

There is good news and bad news about these non-scaled interconnects. The good news is that the higher layers provide lower resistance and delay. The bad news is that, since the wires are larger, we can fit fewer wires on a layer, meaning that the interconnect on these layers isn't as rich as that on the lower layers.

*global and local interconnect*

To make best use of these layers, we must use different layers for different lengths of wiring. Each layer is most appropriate for a certain domain of connections: the lowest layers are used for local interconnect, intermediate layers are used for mid-range interconnect, and the top layers are used for global interconnect. One implication of this wire planning strategy is that we need to use a lot of vias. As we go from layer to layer, we must allocate space for the vias required. And because vias only go to nearby layers, we must go from layer to layer to make a connection from the top layer to the bottom layer.

*cost of repeater*

Another implication of the properties of interconnection layers is that repeaters for the wires on higher-level layers are even more expensive than they appear to be. The repeater is located on the substrate, so vias must go from the layer that is being buffered all the way down to the substrate, as well as back up the layers to return the output signal. A driver costs not just the silicon area on the substrate but also all the intermediate vias and wires. As we go to higher levels of interconnect, the cost of these repeaters increases.

*thermal effects*

As we saw in Section 3.7.1, temperature variations cause wire delay to change. Thermal gradients on the chip cause the resistance of wires that cross the gradient to change. This change in delay can substantially affect a system's timing properties, depending on the signal that is affected. These thermal effects need to be taken into account during all phases of wiring design.

### 7.3.2 Power Distribution


*power distribution problems*

Power distribution presents several significant problems. First, we must design a global power distribution network that runs both  $V_{DD}$  and  $V_{SS}$  entirely in metal. Second, we must size wires properly so that they can

handle the required currents. Third, we must ensure that the transient behavior of the power distribution network does not cause problems for the logic to which it supplies current. While keeping all these problems in mind, we must tackle two types of power supply loss:

- IR drops from steady state currents;
- $L \frac{di}{dt}$  drops from transient current.

**Figure 7-13** A floorplan that isolates a ground pin.

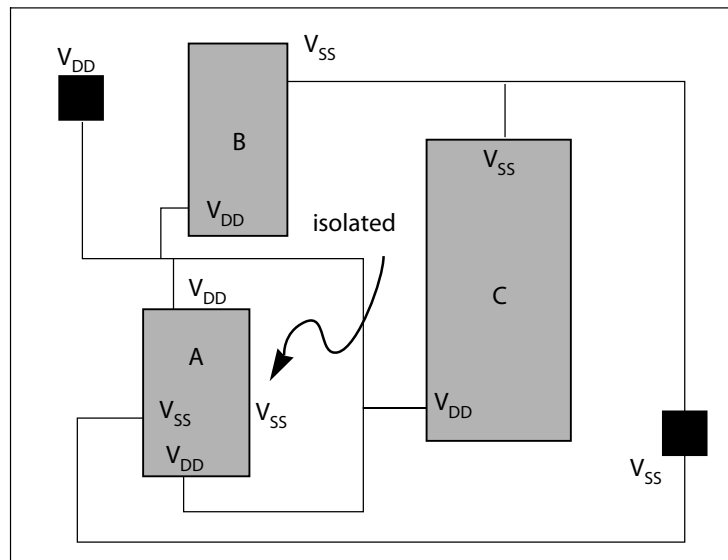

#### *power network planarity*


Design of a planar power network requires attention to cell design even before routing begins. If we orient all the cells so that their  $V_{DD}$  pins are all on the same side of a dividing line through the cell, we are guaranteed that a planar routing exists [Sye82]. Conversely, if we don't satisfy the pin placement condition, we are guaranteed that a planar routing does not exist. We can ensure consistent power/ground pin placement either by reordering power/ground pins or by internally routing  $V_{DD}$  and  $V_{SS}$  connections—if each cell has only one  $V_{DD}$  and one  $V_{SS}$  pin, the condition is guaranteed to be satisfied. An example of an ill-conceived floorplan is shown in Figure 7-13: one of A's  $V_{SS}$  pins becomes surrounded by the  $V_{DD}$  net.

#### *metal migration and wire sizing*

We encountered the metal migration limit in Section 2.4—if too much current is carried through a wire, the wire quickly disintegrates. Power lines are usually routed as trees, with the power supply at the root and the logic gates connected to the twigs. As seen in Figure 7-14, each



**Figure 7-14**  
Interdigitated power and  
ground trees.

 

branch must be wide enough to carry the currents in all of its branches. If your logic gates use only a few standard transistor sizes, computing power line width is easy: compute the power consumed by the gates on each twig, then move up the tree, adding together the power requirements of branches at one level to get the required sizes for the branches at the next level.

When designing large chips, using simple rules to choose power supply widths may not be sufficient. Metal migration is not the only problem in power supply distribution. Large currents that do not cause metal migration may still cause **power supply noise** due to impedance-induced drops in the power supply network. Circuit simulations of the power supply network, using high-level models for major components that model their current requirements over time, can be used to analyze the power network.

#### *power supply transients*


The logic across the chip draws varying amounts of current over the power supply wiring. These currents vary over both short time scales (charging and discharging loads) and longer time intervals (power management shutdowns). If the electrical characteristics of the power supply network are not carefully designed, then transients in the power can cause errors in the operation of the logic.

The next example illustrates potential problems in the design of large power supply networks.

---

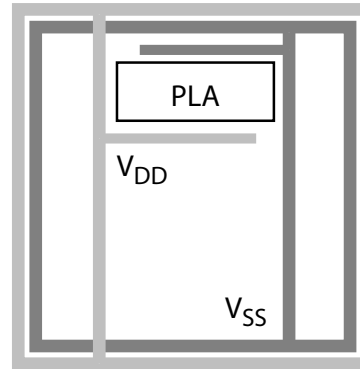**Example 7-2**  
**Power**  
**distribution in the**  
**BELLMAC-32A**

The BELLMAC-32A [Sho82] was an early 32-bit single-chip microprocessor. Here is the basic layout of the power bus:



The layout was designed with power pads at both ends, which reduced power bus noise by a factor of four, since both impedance and switching current were cut in half.

The designers conducted circuit simulations to determine the impedance-induced noise on the power bus. An early design resulted in a 2 V swing on the power lines. The large voltage spike was due to the precharging of PLAs, which occurred on the same clock phase as the precharging of a large decoder. Adding pads was insufficient to reduce the power bus noise to an acceptable level. The problem was solved by changing the timing of the PLA precharge phase—precharging was moved to a phase different than that used to precharge the decoder.

---


This example shows how major events with many correlated transistor actions, such as precharging, can be responsible for power noise. Initialization also causes problems in modern microprocessors. Most large microprocessors no longer use single-cycle resets. They instead reset the machine over several cycles to avoid large amounts of activity that can cause current spikes. This naturally complicates the sequential design of the machine.

---

*power distribution grids*

In a large chip, power is distributed using several metal layers. The upper layers are larger in both width and height. The layers closer to the silicon are smaller in both dimensions. Global power distribution happens on the upper layers; connections on the lower layers move power down to the circuits. In a typical power distribution grid, each layer is interdigitated, with alternating  $V_{DD}$  and  $V_{SS}$  lines. Power lines on alternate layers are orthogonal to each other to minimize coupling between the layers.

**Figure 7-15** Decoupling capacitor behavior.

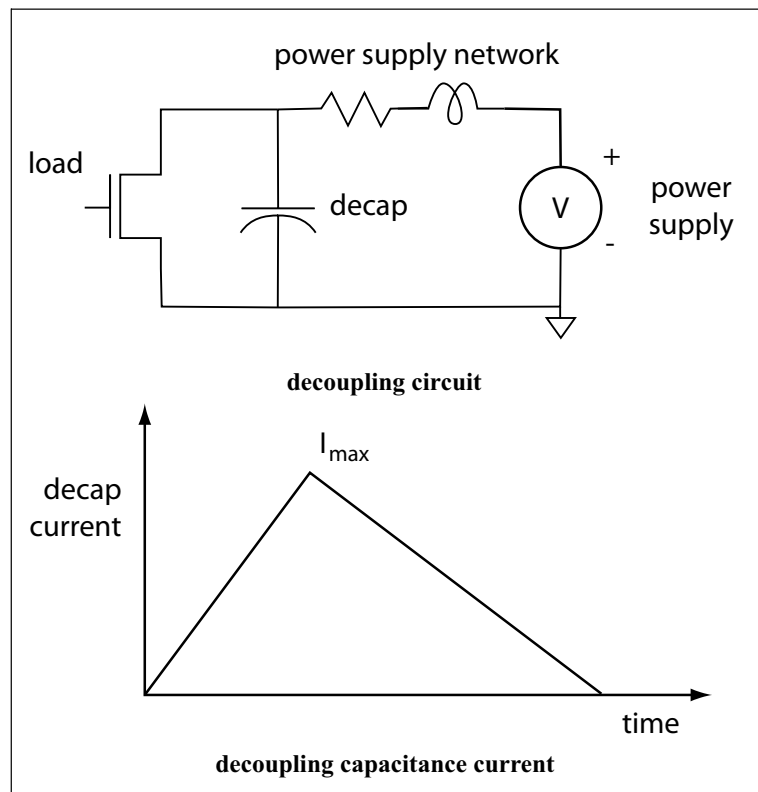*decoupling capacitors*

**Decoupling capacitors (decaps)**—capacitors across the power supply pins—are traditionally used in printed-circuit board design to reduce power supply noise. In large chips, particularly those with inductive wiring, decoupling capacitors may be used on-chip as well. Figure 7-15 shows a simple model for a decoupling capacitor. The decoupling capacitor sits between the load circuit that requires current and the power supply. The power supply network includes its own parasitic

capacitance and inductance—if the power supply wiring were ideal, we would not need decaps. When the logic is changing state, it draws increased current that draws down the decoupling capacitor. The decap is then recharged through the power supply network. The decap and power supply network must be designed so that the voltage droop across the decap—which is the effective power supply for the logic connected to it—is within some specified tolerance.

One DEC Alpha microprocessor [Gie97] uses 250 nF of on-chip capacitance to decouple the power supply. This microprocessor also illustrates a more radical approach to power supply decoupling: a separate chip is bonded directly on top of the microprocessor to add 1  $\mu\text{f}$  of decoupling capacitance. The chip capacitor uses a 2  $\text{cm}^2$  pMOS device to implement the large capacitance. The decoupling capacitor is connected to the microprocessor with approximately 160 wirebond pairs. An alternative solution to power supply noise is to modify the sequential design of the machine.

Popovich *et al.* [Pop06] determined the effective radius of a decoupling capacitor, which is determined by the load produced by the logic circuits and the rate at which the decoupling capacitor can be recharged. They showed that the effective radius of a decoupling capacitor in a modern fabrication process is several hundreds of microns.

### 7.3.3 Clock Distribution


*clock distribution  
challenges*

The problems caused by clock skew were discussed in Section 5.6. The main job of clock routing design is to control clock skew from the clock pad to all the memory elements. The major obstacle to clock distribution is capacitance, with resistance playing a secondary but important role.

Gate capacitance cannot be avoided on a clock line even on modest-size chips. The clock signal is by far the largest capacitive load on a large chip. Clock distribution is made more challenging by the fact that the large capacitive load must be driven to produce a very sharp transition. The slope of the gate signal affects switching speed. A slow-rising clock edge will cause serious performance problems.

Clocking is a floorplanning problem because clock delay varies with position on the chip. As a result, clock delay must be taken into account both in the placement of logic blocks and in the design of the clocking network. Figure 7-16 shows a typical map of clock delay vs. position, where height on the surface above the chip gives the clock delay at that point. Memory elements that are logically related should be connected to the clock tapped at roughly the same position, implying that

**Figure 7-16** Clock delay vs. position.

 

those memory elements and the combinational logic between them should all be placed close together in the layout. The designers of the Alpha processor built such a delay map of the clock signal to determine when the clock arrived at latches throughout the chip [Dob92].

#### *controlling clock skew*

There are two complementary ways to improve clock distribution:

- **Physical design.** The layout can be designed to make clock delays more even, or at least more predictable.
- **Circuit design.** The circuits driving the clock distribution network can be designed to minimize delays using several stages of drivers.


In general, both techniques must be used to distribute a clock signal with adequate characteristics.

#### *H trees*

Let us first consider the physical design of clock distribution networks. The two most common styles of physical clocking networks are the **H tree** and the **balanced tree**. The H tree is a very regular structure which allows predictable delay. The balanced tree takes the opposite approach of synthesizing a layout based on the characteristics of the circuit to be clocked.

An H tree is shown in Figure 7-17. It is a recursive construction of Hs—given one level of H structure, four smaller H structures can be added at the four endpoints of the H bars. The H tree structure can be recursively refined to any level of required detail. The widths of the

**Figure 7-17**  
An H tree.

 

wires in the H tree can be adjusted to account for variations in load capacitance to equalize skew throughout the H tree. Buffers can also be added into the H tree network to increase drive capability. An H tree network can be thought of as a top-down clock distribution methodology since the floorplan of the H tree determines the floorplan of the logic to which it is connected. Since skew increases with physical distance in the H tree, memory elements must be grouped together to make use of the same or nearby distribution points in the H tree network.



*balanced tree networks*

A balanced tree clock network, illustrated in Figure 7-18, is generated by placement and routing. Memory elements are clustered into groups. The clustering is used to guide placement and a clocking tree is then synthesized based on the skew information generated during clustering. The tree is irregular in shape but has been balanced during design to minimize skew. Once again, wire widths can be varied in the tree and buffers can be added. Several tools exist for generating balanced clock trees.

*driver circuits*

Two strategies can be used to distribute the clock: using a driver chain, as shown in Section 3.3.8, to drive the entire load from a single point; or

**Figure 7-18** A balanced clock tree.

  

**Figure 7-19** A clock distribution tree.


distributing drivers through the clock wiring, forming a hierarchical clock distribution system [Fri86]. If a hierarchical system like the one in Figure 7-19 is used, the resistance and capacitance of the clock wiring needs to be analyzed to determine the points at which buffers should be

inserted. Of course, since the drivers will probably be inverting, care must be taken to use an even number of driver stages to avoid delivering an inverted clock signal to the memory elements.

The next example describes the design of a clocking network which uses a regular physical design with a sophisticated clock driving network.

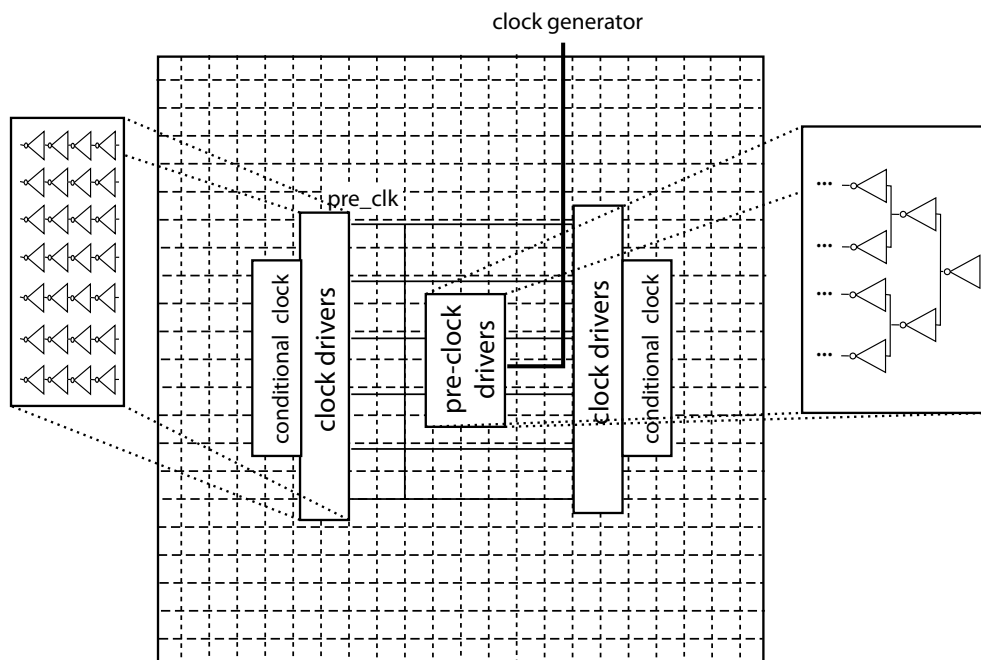**Example 7-3**  
**Clock distribution in the DEC Alpha 21164**

The DEC Alpha 21164 [Bow95] contains 16.5 million transistors on a 16.5mm × 18.1mm die. Here is the basic floorplan of the clock distribution system:



The clock generator drives the first stage of clock driver, located on the center of the chip and known as the pre-clock driver. This network consists of a six-level inverter tree and generates 24 outputs on the PRE\_CLK signal shown in the figure. That signal is fed to two final



clock driver systems, one on each side of the chip. Each final clock driver contains 44 drivers with four levels of inverters on each output. The last clock driver inverter level has a total gate width of 58 cm. The system also includes a set of 12 conditional clock drivers on each side. The final clock drivers are connected to a regular clock grid, shown in the figure as dotted lines. The clock grid is laid out in metal 3 and metal 4.

The clock interconnect and gate load present a total capacitive load of 3.75  $pF$ . The clocking network provides the clock to instruction and execution units within 65  $ps$  of skew.

---

## 7.4 Floorplan Design

---

In this section, we will discuss some general concepts in floorplanning.

### 7.4.1 Floorplanning Tips

Floorplanning a moderate-size chip is necessary but not overwhelming. A few simple rules of thumb help you get to an easy-to-implement, easy-to-change design more quickly.

- **Develop a wiring plan.** You should think about how to use layers to make connections as part of planning your wiring. The horizontal metal 1/vertical metal 2 scheme used by channel routers is an example of a wiring plan. Sketch the plan to help you think about rational, regular schemes for assigning layers to wires. Using different layers for different directions or for different types of nets helps reduce alternatives to a manageable number and make choices clearer. Hand-crafted blocks, such as data paths, may have their own wiring plans.
  - **Sweep small components into larger ones.** Block diagrams often have isolated gates or slightly larger components. While these small components help describe system operation, they create lots of problems during floorplanning: they require extra effort for power/ground routing and they disrupt the flow of wires across the chip. Put these small components into an existing larger block or create a glue logic block to contain all the miscellaneous elements.
- 
-

- **Design wiring that looks simple.** If your sketch of the block diagram or floorplan looks like a plate of spaghetti, it will be hard to route. More importantly, it will be harder to change the design when you need to make logic changes or redesign to reduce delays. Move blocks, then move pin locations to simplify routing topology.
- **Design planar wiring.** A set of nets is planar if all the nets can all be routed in the plane without crossing. While most interesting chips don't have planar wiring, a subset of the wires may be planar. It may help organize your thinking to first design a floorplan on which the most important signals have a planar routing, then add the less-critical signals later.
- **Draw separate wiring plans for power and clock signals.** You may want to include these signals in your floorplan sketch, but they may be hard to distinguish from the maze of signals on the chip. A separate chart of power and clock routing will help you convince yourself that your design is good for signals, power, and clock.
- **Vias as thermal pipes.** A simple step that can be taken to improve the temperature characteristics of the chip is to add dummy vias in higher-level metal layers. These vias help conduct heat away from the lower layers.
- **Floorplan for thermal balance.** A more sophisticated measure is to modify the floorplan to reduce hot spots. If some parts of the circuit consume more current than others, then those modules will create hot spots. Moving hot spots farther away from each other will help to improve heat dissipation and reduce the risk of thermal runaway.

### 7.4.2 Design Validation

*validation during  
chip assembly*

Chip assembly is when your earlier efforts at design verification are judged—if you did a good job of checking the pieces, the chip should work relatively quickly. As with subsystems, design validation breaks down into checking the structure and performance.

In both cases, you should check each block in the floorplan individually, then check the complete chip after assembly. Each block should be extracted, then simulated and checked with a timing verifier. Checking blocks before assembling the layout can save lots of work: the size, shape, and pinout of the block may change after a bug fix, especially if the layout was created by a synthesis tool. But the fact that each block works doesn't imply that the chip will work. Besides wiring errors, the most common chip-level bugs are interface errors, such as one block emitting an active-low signal and the receiving block expecting an

active-high signal. Delay problems may also explode at the chip level, either due to unanticipated long wires or very long chains of logic that were not recognized earlier.

The amount of design-rule checking required depends on the CAD tools used to build the chip and your willingness to catch layout errors after fabrication. Layouts designed using editing systems that don't provide design-rule checking should definitely be checked by a separate system—the probability of a person designing a large layout with no errors is close to zero. Running a final design-rule check on the complete layout is still standard practice at many companies, even though correct-by-construction CAD tools are in common use. The cost of an error in both money and time is large enough that a final check is prudent.

Beyond checking for layout errors, you should check the assumptions on which your delay calculations were made. Extract parasitics, check their values for reasonableness, then rerun timing verifications and simulations to be sure the circuits are fast enough when driving the actual parasitics.

---

## 7.5 Off-Chip Connections

---

### *packaging*

A chip isn't very useful if you can't connect it to the outside world. You rarely see chips themselves because they are encased in **packages**. A complete discussion of packaging and its engineering problems fills several books [Bak90, Ser89]. The packaging problem most directly relevant to the designer is the pads that connect the chip's internals to the package and surrounding circuitry—the chip designer is responsible for designing the pad assembly. But first, we will briefly review packages and some of the system and electrical problems they introduce.

### 7.5.1 Packages



Chips are much too fragile to be given to customers in the buff. The package serves a variety of important needs: its pins provide manageable solder connections; it gives the chip mechanical support; it conducts heat away from the chip to the environment; ceramic packages in particular protect the chip from chemical damage.

### *package structure*

Figure 7-20 shows a schematic of a simple package (high-density packaging technologies often have very different designs). The chip sits

---

---

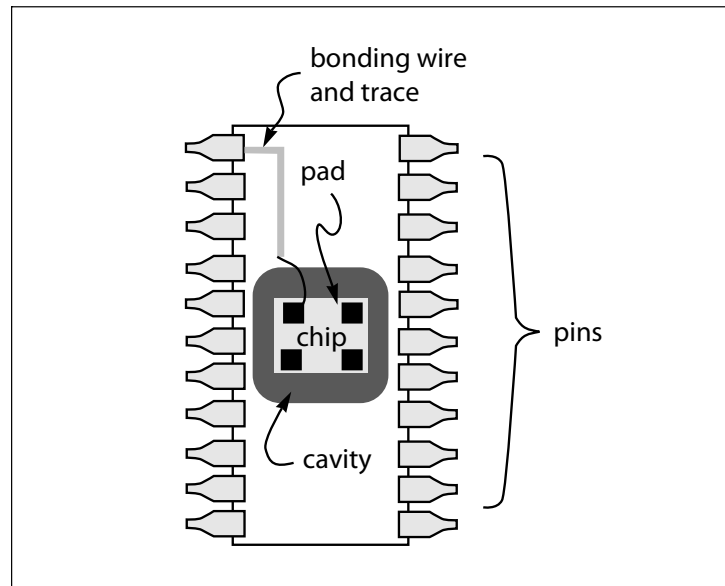 **Figure 7-20** Structure of a typical package.**Figure 7-21** An empty package showing the substrate contact and bonding areas.

in a cavity. The circuit board connects to the pins at the edge (or sometimes the bottom) of the package. Wiring built into the package (called traces) goes from the pins to the edge of the cavity; very fine **bonding wires** that connect to the package's leads are connected by robot machines to the chip's pads. The **pads** are metal rectangles large enough

to be soldered to the leads. Figure 7-21 shows a photograph of a package before a chip has been bonded to it. The cavity is gold-plated to provide a connection to the chip's substrate for application of a bias voltage. Bonding pads connected to the package's pins surround the four sides of the cavity. In a ceramic package, the cavity is sealed by a lid; to make a plastic package, the chip is soldered to a bare wiring frame, then the plastic is injection-molded around the chip-frame assembly. Ceramic packages offer better heat conductivity and environmental protection.

#### *types of packages*

Figure 7-22 shows several varieties of packages. These packages vary in cost and the number of available pins; as you would expect, packages with more pins cost more money. The **dual in-line package** (DIP) is the cheapest and has the fewest number of pads, usually no more than 40. The **plastic leadless chip carrier** (PLCC) has pins around its four edges; these leads are designed to be connected to printed circuit boards without through-board holes. PLCCs typically have in the neighborhood of 128 pins. The **pin grid array** (PGA) has pins all over its bottom. The **ball grid array** (BGA) uses solder balls to connect to the package across the entire bottom of the package. The **plastic quad flat pack** (PQFP), which is not shown, resembles the PLCC in some respects, but has a different pin geometry.

#### *pinout limitations*


Modern high-end packages may have as many as 3000 pins. Even so, off-chip bandwidth is still a major problem. When you have hundreds of millions of transistors on the chip, 3000 pins is not so many pins to use to communicate with the logic.

#### *Rent's Rule*

The best characterization of the relationship between logic and pins was provided by E. F. Rent of IBM in 1960. He gathered data from several designs and plotted the number of pins versus the number of components. He showed that the data fit a straight line on a log-log plot. This gives the relationship known as **Rent's Rule**:

$$N_p = K_p N_g^\beta, \quad (\text{EQ 7-1})$$

where  $N_p$  is the number of pins and  $N_g$  is the number of logic gates. The formula includes two constants:  $\beta$  is Rent's constant while  $K_p$  is a proportionality constant. These parameters must be determined empirically by measuring sample designs. The parameters vary somewhat depending on the type of system being designed. For example, Rent measured the parameters on early IBM mainframes as  $\beta = 0.6$  and  $K_p = 2.5$ ; others have measured the parameters for modern microprocessors as  $\beta = 0.45$  and  $K_p = 0.82$ .

 

**Figure 7-22** Common package types.


*electrical properties of packages*

Packages also introduce electrical problems, notably due to inductance of the pins. Inductive power supply noise has been a problem at the package level for much longer than it has been at the chip level.
 
### Example 7-4 Power line inductance

Inductance causes the most problems on the power line because the largest current swings occur on that pin. (Inductance can also cause problem for signals in very high-frequency parts.) Package inductance caused headaches for early VLSI designers, who didn't expect the package to introduce such serious problems. However, these problems can be easily fixed once they are identified.

The system's complete power circuit looks like this:



An off-chip power supply is connected to the chip. The inductance of the package and the printed circuit board trace is in series with the chip. (The chip also contributes capacitance to ground on the  $V_{DD}$  and  $V_{SS}$  lines which we are ignoring here.) The voltage across the inductance is


$$v_L = L \frac{di_L}{dt}.$$

In steady state there is no voltage drop across the inductance. But, if the current supplied by the power supply changes suddenly,  $v_L$  momentarily increases, and since the inductance and chip are in series, the power supply voltage seen at the chip decreases by the same amount. How much will the voltage supplied to the chip drop? Assume that the power supply current changes by 1 A in 1 ns, a large but not impossible value. A typical value for the package and printed circuit board total inductance is 0.5 nH [Ser89]. That gives a peak voltage drop of  $v_L = 0.5 \times 10^{-9} H \cdot 1 A / 1 \times 10^{-9} s = 0.5 V$ , which may easily be large enough to cause dynamic circuits to malfunction. We can avoid this problem by introducing multiple power and ground pins. Running current through several pins in parallel reduces  $di/dt$  in each pin, reducing the total voltage drop. A typical package today has half of its pins used for power distribution.

### 7.5.2 The I/O Architecture

Pads and their associated drivers are distributed around the edge of the chip. (Advanced, high-density packaging schemes devote a layer of metal to pads and distribute them across the entire chip face.) Each pad must be large enough to have a wire (or a solder bump) soldered to it; it must also include input or output circuitry, as appropriate.

**Figure 7-23** Architecture of a pad frame.

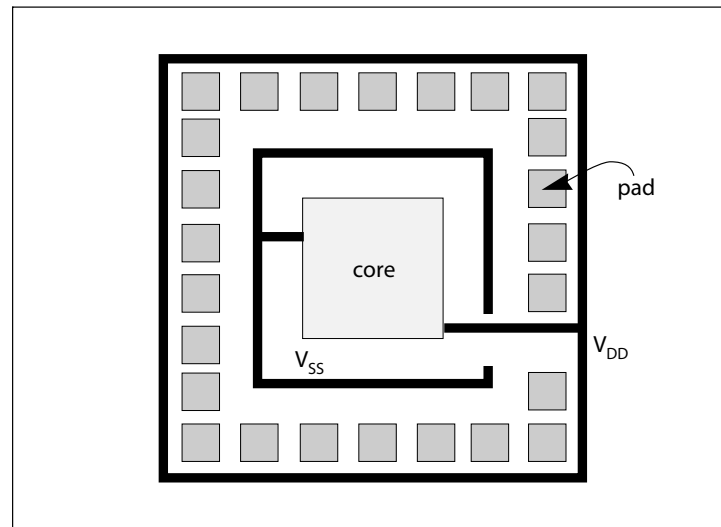

#### *pad frames*

A typical **pad frame** is shown in Figure 7-23. Each pad is built to a standard width and height, for simplicity. Each pad has large  $V_{DD}$  and  $V_{SS}$  lines running through it. A pad includes a large piece of metal to which the external wire is soldered. If the pad requires external circuitry, it is usually put on the side of the pad closest to the chip core. The **chip core** fits in the middle of the pad ring. If the pad ring is not completely filled with pads, spacers are added to keep the power lines connected. The placement of pads around the ring is usually determined by the required order of pins on the package—the wires to the package cannot be crossed without danger of shorting, so if the package pins are required in a certain order, the pads must be arranged in that order. The order of pins on the package determines routability of the board and electrical noise among other things; the order of pins on a package has been known to determine which candidate design wins a design contest.

$V_{DD}$  and  $V_{SS}$  pads are the easiest pads to design because they require no circuitry—each is a blob of metal connected to the appropriate ring.



How much current can be supplied by one of these pads? The pad is much larger than any single wire connected to it, so the current in each direction is limited by the outgoing wire. If we want to use multiple power pins to limit inductive voltage drop, we can use several  $V_{DD}$  and  $V_{SS}$  pads around the ring.

### 7.5.3 Pad Design

#### *pads and pad circuitry*

Pads used for input and output signals require different supporting circuitry. A pad used for both input and output, sometimes known by its trade name of Tri-state pin<sup>1</sup>, combines elements of both inputs and output pads.

#### *input pads*

The input pad may include circuitry to shift voltage levels or otherwise condition the signal. The main job of an input pad is to protect the chip core from static electricity. People or equipment can easily deliver a large static voltage to a pin when handling a chip. MOS circuits are particularly sensitive to static discharge because they use thin oxides—the transistor photomicrograph in Chapter 2 shows how small the gate oxide is in comparison with the submicron-length channel. The gate oxide, which may be a few hundred Angstroms thick, can be totally destroyed by a single static jolt, shorting the transistor's gate to its channel.

An input pad puts protective circuitry between the pad itself and the transistor gates in the chip core. Electrostatic discharge (ESD) can cause two types of problems: dielectric rupture and charge injection [Vin98]. When the dielectric ruptures, chip structures can short together. The charge injected by an ESD event can be sufficient to damage the small on-chip devices.


#### *ESD protection*

A commonly used ESD protection circuit [Gla85] uses a resistor that is usually made of a long diffusion run between the pad and the protection circuitry to help limit the current caused by a voltage spike. Parasitic bipolar transistors are used as diodes to draw excess current from the output node. The npn transistor limits the negative-going voltage swing to  $0.7 V$  below  $V_{SS}$ , while the pnp transistor limits the positive-going swing to  $0.7 V$  above  $V_{DD}$ . The standard masks can be used to create both the pnp and npn transistors, but the layout must be carefully designed to minimize the chance of latch-up.

---

1. Tri-state is a trademark of National Semiconductor.


**Figure 7-24** An output pad circuit.

 

*output pads*


Electrostatic discharge protection is not needed for an output pad because the pad is not connected to any transistor gate. The main job of an output pad is to drive the large capacitances seen on the output pin. Within the chip,  $\lambda$  scaling ensures that we can use smaller and smaller transistors, but the real world doesn't shrink along with our chip's channel length. The output pad's circuitry, shown in Figure 7-24, includes a chain of inverters to drive the large off-chip load. Figure 7-26 shows the layout of an SCMOS output pad from MOSIS. Because the final stages use very large transistors, creative layout techniques are used to reduce the pad's size. Transistors are often folded to reduce the pad's height; the transistors may also be wrapped around the extra space surrounding the pad.

**Figure 7-25** A three-state pad circuit.

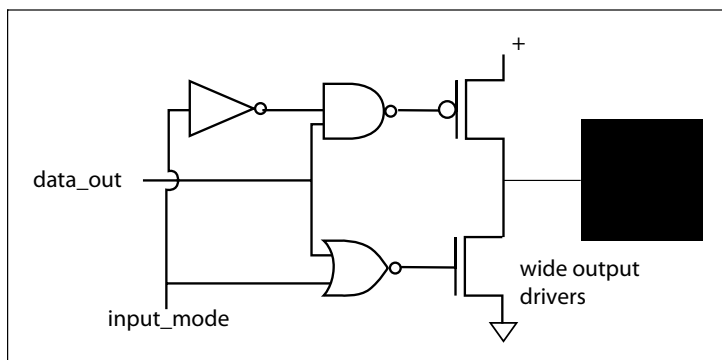

*three-state pads*

Three-state pads, used for both input and output, help solve the pin count crunch—if we don't need to use all combinations of inputs and outputs simultaneously, we can switch some pins between input and output. The pad cannot, of course, be used as an input and output simul-

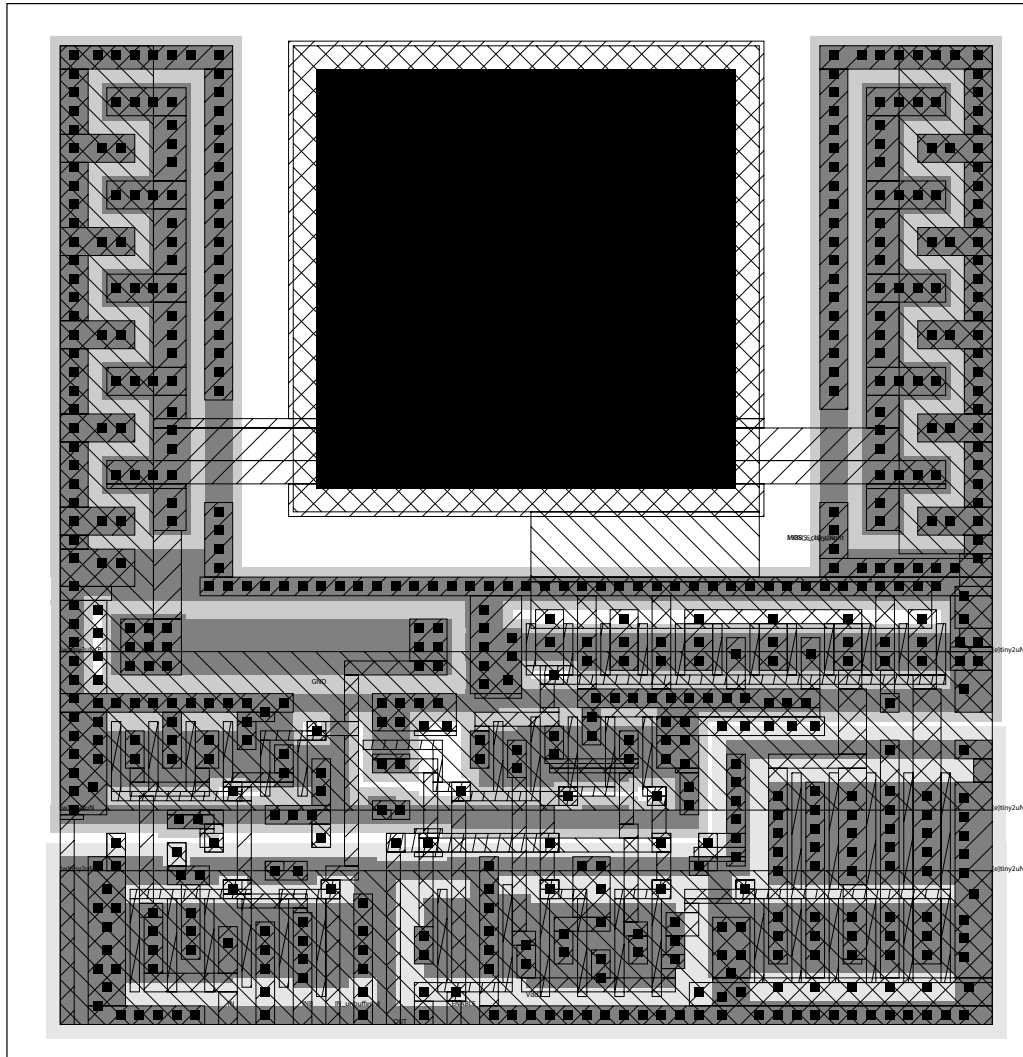

**Figure 7-26** Layout of a MOSIS-supplied SCMOS output pad.

taneously—the chip core is responsible for switching between modes. The pad requires electrostatic discharge protection for when the pad is used as an input, an output driver for when it is used as an output, plus circuitry to switch the pad between input and output modes. The circuit of Figure 7-25 can be used for mode switching. The n-type and p-type

## 7.6 References

461

transistors are used to drive the pad when it is used as an output—the logic gates are arranged so that the output signal turns on exactly one of the two transistors when `input_mode` is 0. To use the pad as an input, `input_mode` is set to 1: the NOR gate emits a 0, turning off the pull-down, and the NAND gate emits a 1, turning off the pullup. Since both driver transistors are disabled, the pad can be used as an input. (The required ESD circuitry is not shown in the schematic.)

*boundary scan for pads*

Pads may also include circuitry to support **boundary scan** [Par92], which configures the chip's pins as an LSSD chain. Chips that support boundary scan can be chained to form a single scan path for all the chips on a printed circuit board. Boundary scan makes the printed circuit board much easier to test because it makes the chips separately observable and controllable. Boundary scan support requires some circuitry on the pins corresponding to the chip's primary inputs and outputs, along with a small controller and a few pins dedicated to boundary scan configuration.

---

## 7.6 References

Sherwani's book [She98] and *Physical Design Automation of VLSI Systems* [Pre88] includes chapters on placement and routing, which cover a variety of algorithms. Glasser and Dobberpuhl [Gla85] describe pad buffer design and electrostatic discharge protection. Friedman's edited volume of collected papers on clock distribution [Fri95] provides a valuable overview of the electrical problems of clock distribution.

---


---

## 7.7 Problems


---

Q7-1. Divide the routing area of each of these floorplans into channels:

a)

 


b)

 

7.7 Problems


463

c)

 


Q7-2. Find a global route for each signal in these floorplans. Try to equalize channel utilization and minimize wire lengths.


a)

 

b)

 


c)

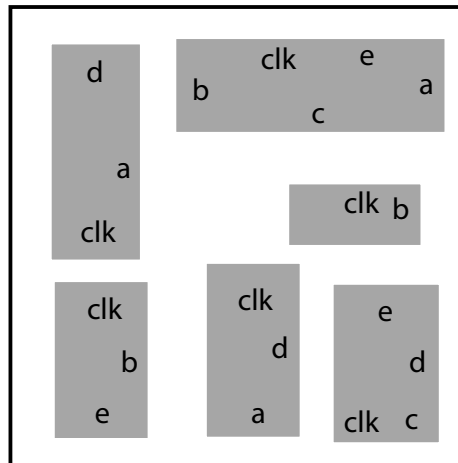


Q7-3. Which of these floorplans is a slicing structure? Explain.

a)

 

b)

 


---

---




c)

 

Q7-4. For each of these floorplans, draw a channel graph and give a feasible order for routing the channels.


a)

 


7.7 Problems

467

b)

 


c)

 


Q7-5. For each floorplan below, determine whether it can be routed with planar power and ground nets.


a)

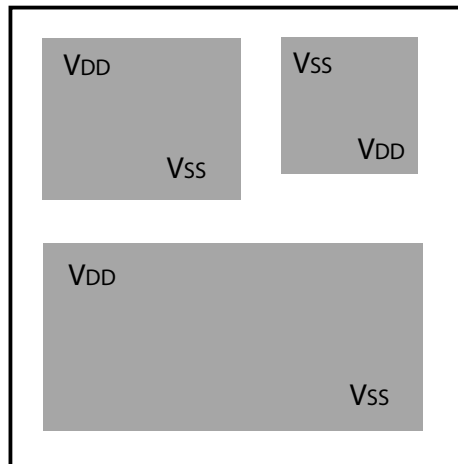

b)

 

c)

 

Q7-6. Draw a cross section of a chip with six layers of metal, with a buffer inserted along a wire on metal 4. Show generally the relationship between wires, vias, and transistors in the cross section.

Q7-7. Draw a transistor-level schematic of an inverter, power supply, and decoupling capacitor.

Q7-8. Using the Rent's Rule parameters for modern microprocessors ( $\beta = 0.45$ ,  $K_p = 0.82$ ), plot pins vs. gates for a range of 100,000 gates to 500,000,000 gates.





8

# Architecture Design

## Highlights:

Hardware description languages (HDLs).

Register-transfer design.


Pipelining.

High-level synthesis.

Low-power architectures.

Architecture testing.

Design methodologies.

 

A scheduled and bound data flow graph (Example 8-2).

---

## 8.1 Introduction

---

A good digital system design is more than a jumble of components. You must design an **architecture** that executes the desired function and that meets area, performance, and testability constraints. Simply executing the specified function is the easy part—there are many candidate architectures that will execute almost any function. What makes chip design challenging is sorting through all the possible designs to find those few that are small and fast enough.

We will start with a review of hardware description languages (HDLs). HDLs allow us to capture designs at a variety of levels of abstraction. Section 8.3 concentrates on register-transfer design, which is the foundation of architecture design. A register-transfer is a complete specification of what the chip will do on every cycle. Section 8.4 looks in detail at pipelining, a specialized but very important means of improving system performance. Section 8.5 considers high-level synthesis. By studying scheduling and binding, we can understand how to optimize a register-transfer design to improve area, speed, and testability. Section 8.6 looks at architecture design for low-power systems. Section 8.7 introduces globally asynchronous, locally synchronous (GALS) design as an architectural solution to clock distribution problems. Section 8.8 considers architecture-level testing. Section 8.9 talks about IP components in architecture design. Section 8.10 describes design methodologies for chip design. Section 8.11 wraps up with a description of multiprocessor systems-on-chips.

---

## 8.2 Hardware Description Languages

---

This section introduces some basic concepts of hardware description languages. We briefly introduce two widely used languages, Verilog and VHDL. This section is not intended as a comprehensive guide to either of these languages; that has been the sole topic of many books. However, this section touches upon some aspects of these languages that will be useful throughout the chapter.

---

---



## 8.2.1 Modeling with Hardware Description Languages

### *HDLs*

**Hardware description languages (HDLs)** are the most important modern tools used to describe hardware. HDLs become increasingly important as we move to higher levels of abstraction. While schematics can convey some information very clearly, they are generally less dense than textual descriptions of languages. Furthermore, a textual HDL description is much easier for a program to generate than is a schematic with pictorial information such as placement of components and wires.

### *Verilog and VHDL*

In this section we will introduce the use of the two most widely used hardware description languages, **Verilog** [Tho02,Smi00] and **VHDL** [IEE93,Bha95], in architectural and logical modeling. Since both these languages are built on the same basic framework of event-driven simulation, we will start with a description of the fundamental concepts underlying the two languages. We will then go on to describe the details of using VHDL and Verilog to model hardware. We don't have room to discuss all the details of Verilog and VHDL modeling, but this brief introduction should be enough to get you started with these languages. We will also briefly consider the use of C as a hardware modeling language.

### *EDIF*

Both Verilog and VHDL started out as simulation languages—they were designed originally to build efficient simulations of digital systems. Some other hardware description languages, such as **EDIF**, were designed to describe the structure of nets and components used to build a system. Simulation languages, on the other hand, are designed to be executed. Simulation languages bear some resemblance to standard programming languages. But because they are designed to describe the parallel execution of hardware components, simulation languages have some fundamental differences from sequential programming languages.

### *simulation vs. programming*

There are two important differences between simulation and sequential programming languages. First, statements are not executed in sequential order during simulation. When we read a sequential program, such as one written in C, we are used to thinking about the lines of code being executed in the order in which they were written. In contrast, a simulation may describe a series of logic gates all of which may change their outputs simultaneously. If you have experience with a parallel programming language, you may be used to this way of thinking. Second, most simulation languages must support some notion of real time in order to provide useful results. Even parallel programming languages usually do not explicitly support real time. Time may be measured in nanoseconds for more realistic simulation or in some more abstract unit such as gate delays or clock cycles in faster, more abstract simulators. One important

job of the simulator is to determine how long it takes to compute a given value. Delay information determines not only clock speed but also proper operation: glitches caused by unbalanced delays may, for example, cause a latch to be improperly clocked. Simulating functional behavior in the absence of time can be relatively easy; however, the simulator must go to a great deal of effort to compute the time at which values are computed by the simulated hardware.

*event-driven simulation*

Simulation languages serve as specialized programming languages for the **simulation engines** that execute simulations. Both VHDL and Verilog are built on top of **event-driven simulators**.

Event-driven simulation is a very efficient algorithm for hardware simulation because it takes advantage of the activity levels within the hardware simulation. In a typical hardware design, not all the nets change their values on every clock cycle: having fewer than 50% of the nets in a system keep their value on any given clock cycle is not unusual. The most naive simulation algorithm for a clocked digital system would scan through all the nets in the design for every clock cycle. Event-driven simulation, in contrast, ignores nets that it knows are not active.

*events as time/value pairs*



An **event** has two parts: a value and a time. The event records the time at which a net takes on a new value. During simulation, a net's value does not change unless an event records the change. Therefore, the simulator can keep track of all the activity in the system simply by recording the events that occur on the nets. This is a sparse representation of the system's activity that both saves memory and allows the system activity to be computed more efficiently.

Figure 8-1 illustrates the event-driven simulation of gates; the same principle can be applied to digital logic blocks at other levels of abstraction as well. The top part of the figure shows a NAND gate with two inputs: one input stays at 0 while the other changes from a 0 to a 1. In this case, the NAND gate's output does not change—it remains 1. The simulator determines that the output's value does not change. Although the gate's input had an event, the gate itself does not generate a new event on the net connected to its output. Now consider the case shown on the bottom part of the figure: the top input is 1 and the bottom input changes from 0 to 1. In this case, the NAND gate's output changes from 1 to 0. The activity at the gate's input in this case causes an event at its output.

*simulator control  
by timewheel*


The event-driven simulator uses a **timewheel** to manage the relationships between components. As shown in Figure 8-2, the timewheel is a list of all the events that have not yet been processed, sorted in time. When an event is generated, it is put in the appropriate point in the time-

**Figure 8-1** Event-driven simulation of a gate.

 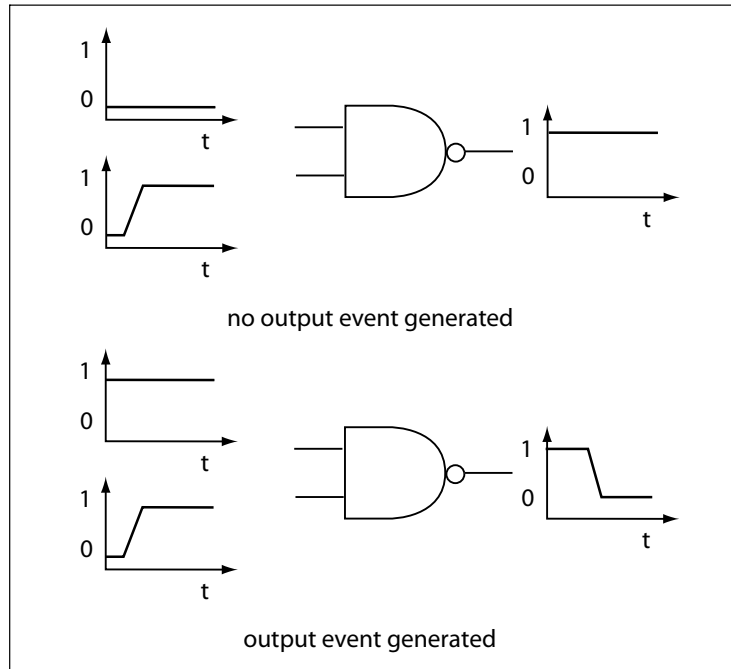

**Figure 8-2** The event-driven timewheel.

wheel's list. The simulator therefore processes events in the time order in which they occur by pulling events in order from the head of the timewheel's list. Because a component with a large internal delay can generate an event far in the future from the event that caused it, operations during simulation may occur in a very different order than is apparent from the order of statements in the HDL code.

 

**Figure 8-3** Order of evaluation in event-driven simulation.

As shown in Figure 8-3, an event caused by the output of one component causes events to appear at the inputs of the components being driven by that net. As events are put into the timewheel, they are ordered properly to ensure causality, so that the simulator events are processed in the order in which they occur in the hardware. In the figure, the event at the input causes a cascade of other events as activity flows through the system.

*structural vs. behavioral modeling*

There are two ways to describe a design for simulation: **structural** or **behavioral modeling**. A structural model for a component is built from smaller components. The structural model specifies the external connections, the internal components, and the nets that connect them. The behavior of the model is determined by the behavior of the components and their connections. A behavioral model is more like a program—it uses functions, assignments, etc. to describe how to compute the component’s outputs from its inputs. However, the behavioral model deals with events, not with variables as in a sequential programming language. Simulation languages define special constructs for recognizing events and for generating them.

Whether a component is described structurally or behaviorally, we must define it and use it. As in a programming language, a hardware description language has separate constructs for the type definition of a component and for instantiations of that component in the design of some larger system. In C, the statement `struct { int a; char b; } mydef;` defines a data structure called `mydef`. However, that definition does not allocate any instances of the data structure; memory is committed for an instance of the data structure only by declaring a variable of type

`mydef`. Similarly, in order to use a component, we must have a definition of that component available to us. The module that uses the component does not care whether the component is modeled behaviorally or structurally. In fact, we often want to simulate the system with both behavioral and structural models for key components in order to verify the correctness of the behavioral and structural models. Modern hardware description languages provide mechanisms for defining components and for choosing a particular implementation of a component model.

#### *using the simulator*

We can use the simulator to exercise a design as well as describe it. Testing a design often requires complex sequences of inputs that must be compared to expected outputs. If you were testing a physical piece of hardware, you would probably wire up a test setup that would supply the necessary input vectors and capture and compare the resulting output vectors. We can do the equivalent during simulation. We build components to generate the inputs and test the outputs; we then wire them together with the component we want to test and simulate the entire system. This sort of simulation setup is known as a **testbench**.

#### *synthesis from HDLs*

Both VHDL and Verilog were originally designed as simulation languages. However, one of their principal uses today is as a synthesis language. A VHDL or Verilog model can be used to define the functionality of a component for logic synthesis (or for higher levels of abstraction such as behavioral synthesis). The synthesis model can also be simulated to check whether it is correct before going ahead with synthesis. However, not all simulatable models can be synthesized. Synthesis tools define a **synthesis subset** of the language that defines the constructs they know how to handle. The synthesis subset defines a modeling style that can be understood by the synthesis tool and also provides reasonable results during simulation. There may in fact be several different synthesis subsets defined by different synthesis tools, so you should understand the synthesis subset of the tool you plan to use.

The most common mode of synthesis is **register-transfer synthesis**. RT synthesis uses logic synthesis on the combinational logic blocks to optimize their implementations, but the registers are placed at the locations specified by the designer. The result is a sequential machine with optimized combinational logic. The signals in the combinational section of the model may or may not appear in the synthesized implementation, but all the registers appear in the implementation. (Some register-transfer synthesis tools may use state assignment algorithms to assign encodings to symbolic-valued symbols.) Although there are several RT synthesis tools on the market, the most commonly used RT syn-

thesis subset is the one defined for the Synopsys Design Compiler™, which is accepted by that tool and several others.

One item to look out for in RT synthesis is the **inferred storage element**. A combinational logic block is defined by a set of assignments to signals. If those signals form a cycle, many synthesis tools will insert a storage element in the loop to break the cycle. While the inferred storage element can be handy if you want it to appear, it can cause confusion if the combinational cycle was caused by a bug in the synthesis model. The synthesis tool will emit a warning message when an inferred storage element is inserted into an implementation; that warning is generally used to warn of an unintended combinational cycle in the design.

## 8.2.2 VHDL

VHDL is a general-purpose programming language as well as a hardware description language, so it is possible to create VHDL simulation programs ranging in abstraction from gate-level to system. VHDL has a rich and verbose syntax that makes its models appear to be long and verbose. However, VHDL models are relatively easy to understand once you are used to the syntax. We will concentrate here on register-transfer simulation in VHDL, using the sequencer of the traffic light controller of Section 5.6.2 as an example. The details of running the simulator will vary substantially depending on which VHDL simulator you use and your local system configuration. We will concentrate here on basic techniques for coding VHDL simulation models.

**Figure 8-4** Abstract types in VHDL.

```
package lights is
  -- this package defines constants used by the
  -- traffic light controller light encoding
  subtype light is bit_vector(0 to 1);
  constant red : light := B"00";
  constant green : light := B"01";
  constant yellow : light := B"10";
end lights;
```

*types in VHDL*

VHDL provides extensive type-definition facilities: we can create an abstract data type and create signals of that data type, rather than directly write the simulation model in terms of ones and zeroes. Abstract data types and constants serve the same purposes in hardware modeling that they do in programming: they identify design decisions in the source code and make changing the design easier. Figure 8-4 shows a set of type definitions for the traffic light controller. These data types

are defined in a **package**, which is a set of definitions that can be used by other parts of the VHDL program. Since we encode traffic light values in two bits, we define a data type called **light** to hold those values. We also define the constants **red**, **green**, and **yellow** and their encoding; the syntax **B"00"** defines a constant bit vector whose value is 00. If we write our program in terms of these constants, we can change the light encoding simply by changing this package. (VHDL is case-insensitive: **yellow** and **YELLOW** describe the same element.) When we want to use this package in another section of VHDL code, the **use** statement imports the definitions in the package to that VHDL code.

**Figure 8-5** A VHDL entity declaration.

```
-- define the traffic light controller's pins
entity tlc_fsm is
  port( CLOCK: in BIT; -- the machine clock
        reset : in BIT; -- global reset
        cars : in BIT; -- signals cars at farm road
        short, long : in BIT; -- short and long timeouts
        highway_light : out light := green; -- light values
        farm_light : out light := red ;
        start_timer : out BIT -- signal to restart timer
        );
end;
```

#### *entity declaration*

VHDL requires an entity declaration for each model; Figure 8-5 shows the entity declaration for the traffic light controller. The entity declaration defines the model's primary inputs and outputs. We can define one or more bodies of code to go with the entity; that allows us to, for example, simulate once with a functional model, then swap in a gate-level model by changing only a few declarations.

**Figure 8-6** A process in a VHDL model.

```
combin : process(state, hg)
begin
  highway_light <= green;
end process combin;
```

#### *process and sensitivity list*

The basic unit of modeling in VHDL is the **process**. A process defines the actions that are taken whenever any input to the process is activated by an event. As shown in Figure 8-6, a process starts with the name of the process and a **sensitivity list**. The sensitivity list declares all the signals to which the process is sensitive: if any of these signals changes, the process should be evaluated to update its outputs. In this case, the process **proc1** is sensitive to **a**, **b**, and **c**. Assignment to a signal are

defined by the `<=` symbol. The first assignment is straightforward, assigning the output `x` to the or of inputs `a` and `b`.

**Figure 8-7** Conditional assignment in VHDL.

<pre> if (b or c) = '1' then   y &lt;= '1'; else   y &lt;= '0'; </pre> <p style="text-align: center;"><b>assignment to y</b></p>	<pre> if (b or c) = '1' then   y &lt;= '1' else   z &lt;= a or b; </pre> <p style="text-align: center;"><b>assignment to y or z</b></p>
--	---

*assigning to signals*

The second statement in the example defines a conditional assignment to the signal `y`. The value assigned to `y` depends on the value of the conditional's test. Figure 8-7 shows the combinational logic that could be used to implement this statement.

What if a signal is not assigned to in some case of a conditional? Consider, for example, the conditional of Figure 8-7. If `(b or c) = '1'` then `y` is assigned a value; if not, then `z` is assigned a value. This statement illustrates some subtle differences between the semantics of simulation and synthesis:

- During simulation, the simulator would test the condition and execute the statements in the selected branch of the conditional. The signal referred to in the branch not taken would retain its value since no event is generated for that signal. This case is somewhat similar to sequential software.
- Synthesis may interpret this statement as don't-care conditions for both `y` and `z`: `y`'s value is a don't-care if `(b or c)` is not `'1'`, while `z` is a don't care if `(b or c)` is `'1'`. However, unlike in software, both `y` and `z` are always evaluated. Although a C program with this sort of conditional would assign to either `y` or `z` but not both, the logic shown in the figure makes it clear that both `y` and `z` are combinational logic signals.

These differences are minor, but they do highlight the differences between simulation and logic synthesis. A simulation run results in a single execution of the machine; with different inputs, the simulation would have produced different outputs. Don't-care values could be used in simulation, but they can cause problems for later stages of logic that may not know what value to produce. Logic synthesis, in contrast, results in the structure of the machine that can be run to produce desired values. Don't-care values are very useful to logic synthesis during minimization.



**Table 8-1** Some elements of VHDL syntax.

a and b	<b>Boolean AND</b>
a or b	<b>Boolean OR</b>
not a	<b>Boolean NOT</b>
a <= b	<b>signal assignment, less than or equal to</b>
a = b	<b>equality</b>
a = b	<b>equality</b>
after 5 ns	<b>time</b>

*syntactic elements*

Table 8-1 shows the syntax of a few typical VHDL expressions. VHDL modelers can build complex signals with arrays of signals and bundles of different signals. Signals also need not carry binary values. By defining a series of VHDL functions, one can create a signal definition that works on a variety of logical systems: three-valued logic (0, 1, x); or symbolic logic such as the states of a state machine (s1, s2, s3). VHDL defines a basic bit type that provides two values of logic, '0' and '1'. The library IEEE.std\_logic\_1164 defines a nine-valued signal type known as std\_ulogic.

*traffic light controller in VHDL*

Here is a complete, simple VHDL model of the traffic light controller:

```

Library IEEE;
use IEEE.std_logic_1164.all;
use work.lights.all; -- use the traffic light controller data types

-- define the traffic light controller's pins
entity tlc_fsm is
  port( CLOCK: in BIT; -- the machine clock
        reset : in BIT; -- global reset
        cars : in BIT; -- signals cars at farm road
        short, long : in BIT; -- short and long timeouts
        highway_light : out light := green; -- light values
        farm_light : out light := red ;
        start_timer : out BIT -- signal to restart timer
        );
end;

-- define the traffic light controller's behavior
architecture register_transfer of tlc_fsm is

```

```

-- internal state of the machine
-- first define a type for symbolic control states,
-- then define the state signals
type ctrl_state_type is (hg,hy,fg,fy);
signal ctrl_state, ctrl_next : ctrl_state_type := hg;

begin

-- the controller for the traffic lights
ctrl_proc_combin : process(ctrl_state, short, long, cars)
begin
if reset = '1' then
-- reset the machine
ctrl_next <= hg;
else
case ctrl_state is
when hg =>
-- set lights
highway_light <= green; farm_light <= red;
-- decide what to do next
if (cars and long) = '1' then
ctrl_next <= hy; start_timer <= '1';
else -- state doesn't change
ctrl_next <= hg; start_timer <= '0';
end if;
when hy =>
-- set lights
highway_light <= yellow; farm_light <= red;
-- decide what to do next
if short = '1' then
ctrl_next <= fg; start_timer <= '1';
else
ctrl_next <= hy; start_timer <= '0';
end if;
when fg =>
-- set lights
highway_light <= red; farm_light <= green;
-- decide what to do next
if (not cars or long) = '1' then
-- sequence to yellow
ctrl_next <= fy; start_timer <= '1';
else
ctrl_next <= fg; start_timer <= '0';
end if;
when fy =>
-- set lights
highway_light <= red; farm_light <= yellow;
-- decide what to do next
if short = '1' then
ctrl_next <= hg; start_timer <= '1';
else

```

---



---

```

        ctrl_next <= fy; start_timer <= '0';
    end if;
end case; -- main state machine
end if; -- not a reset
end process ctrl_proc_combin;

-- the sync process updates the present state of the controller
sync: process(CLOCK)
begin
    wait until CLOCK'event and CLOCK = '1';
    ctrl_state <= ctrl_next;
end process sync;

end register_transfer;

```

The description has several parts. The first statements declare the libraries needed by this model. The VHDL simulator or synthesis tool gathers the declarations and other information it needs from these libraries. The next statement is the entity declaration. After the entity declaration, we can have one or more architecture statements. An architecture statement actually describes the component being modeled for simulation or synthesis. We may want to have several architecture descriptions for a component at different levels of abstraction or to have faster simulation models for some purpose. The architecture of this model is named `register_transfer`; this name has no intrinsic meaning in VHDL and is used only to identify the model. After the architecture declaration proper, we can define signals, required type definitions, etc.

This model has two processes, one for the combinational behavior and another for the sequential behavior. Each process begins with its sensitivity list—the signals that should cause this process to be reevaluated when they change. The **combinational process** first uses an if to check for reset, then uses a case statement to choose the right action based on the machine's current state. In each case, we may examine primary inputs that help determine the proper action in this state, then set outputs and the next state as appropriate. There may be several combinational processes in a register-transfer model, which would correspond to a system partitioned into several communicating machines.

The **sequential process** is written in a particular style that is recognized by synthesis and works properly during simulation. The sequential process is activated by activity on the clock or reset lines. A reset causes the machine's state to be reset. A clock edge is tested for by the condition (CLOCK'event AND CLOCK = '1'), which checks for an event on CLOCK and a '1' value for CLOCK after the event takes place. During simulation, this statement ensures that the machine's state changes only on a positive clock edge. Logic synthesis looks for this statement to

identify the sequential process, which tells the synthesis tool what signals need flip-flops to hold the machine's state.

**Figure 8-8** Several useful VHDL constructs.

```

avec : out std_logic_vector(11 downto 0);
vector
    constant zerovec:
        std_logic_vector(0 to 7) := "00000000";
constant vector
    sum <= a + b;
adder

```

#### *VHDL constructs*

Figure 8-8 shows several useful constructs in VHDL. The output `avec` is defined as a vector using the `std_logic_vector` type defined by the `std_logic` library. This definition defines the bits of the vector from 11 down to 0, rather than from 0 up to 11; this makes a difference if two 12-bit vectors with opposite endianness are connected together. The constant `zerovec` is a constant value of a vector type; constants may also be scalars. The last construct shows an adder; the `+` symbol is overloaded by the library to provide the necessary functionality.

#### *inferred latches*

Logic synthesizers will generally add **inferred latches** to break combinational cycles. Such inferred latches should be carefully inspected to be sure that they are not the result of errors in the combinational logic description.

#### *exercising the simulation model*

We need to execute this process on simulation vectors to be sure it is correct. Your simulator may have a graphical user interface which lets you enter and see waveforms on your screen. It is also possible to write a VHDL model that exercises the simulator. The virtue of this approach is that it captures your simulation vector set, allowing you to run the vectors many times on the design as it evolves and save the exerciser program as documentation of your design.

Here is a testbench for the traffic light controller:

```

Library IEEE;
use IEEE.std_logic_1164.all;
use work.lights.all;
use work.tlc_fsm;

entity tlc_fsm_exerciser is
    -- this entity declaration is purposely empty
end;

architecture stimulus of tlc_fsm_exerciser is

```

```

component tlc_fsm -- tlc_fsm is the circuit under test
-- this port declaration is a copy of the declaration
-- in the tlc_fsm register_transfer model
port( CLOCK: in BIT; -- the machine clock
      reset : in BIT; -- global reset
      cars : in BIT; -- signals cars at farm road
      short, long : in BIT; -- short and long timeouts
      highway_light : out light := green; -- light values
      farm_light : out light := red ;
      start_timer : out BIT -- signal to restart timer
    );
end component;

-- the signals which connect to the
-- circuit under test
signal clock, reset, cars, short, long, start_timer : BIT;
signal highway_light, farm_light : light;

begin

-- connect the exerciser's signals to the
-- circuit under test
    tlc_fsm_cut : tlc_fsm port
map(clock,reset,cars,short,long,
highway_light,farm_light,start_timer);

-- the tester process generates outputs and checks inputs
tester : process
begin
-- reset the circuit under test
reset <= '1';
clock <= '0'; wait for 5 ns; clock <= '1'; wait for 5 ns; -- tick
reset <= '0';
-- check that machine is in HG state
assert(highway_light = green);
assert(farm_light = red);
-- put a car at the farm road
-- should respond after long timeout
cars <= '1';
clock <= '0'; wait for 5 ns; clock <= '1'; wait for 5 ns; -- tick
assert(highway_light = green);
assert(farm_light = red);
long <= '1';
clock <= '0'; wait for 5 ns;
assert(start_timer = '1');
clock <= '1'; wait for 5 ns; -- tick
assert(highway_light = yellow);
assert(farm_light = red);
end process tester;

end stimulus;

```

---



---

```

-- tell VHDL which tlc_fsm to use
configuration stimulate of tlc_fsm_exerciser is
  for stimulus
    for all : tlc_fsm
      use entity work.tlc_fsm(register_transfer);
    end for;
  end for;
end stimulate;

```

This code isn't meant to be a thorough test of the machine, but an example of how to write such exerciser programs. We used the `assert` statement to test the values emitted by the sequencer: if the condition specified in the assertion isn't true, the simulator stops and flags the error. This testbench assumes that the traffic light controller model was separately compiled and available to the compiler. The testbench includes one architecture declaration that has no inputs or outputs. It defines an instance of the traffic light controller component to be tested, naming the component UUT. (UUT stands for **unit under test**, a testing term for the component being tested.) The port declaration in this architecture provides the local names for the signals wired to `tlc_fsm`. The testbench has two processes that apply signals to `tlc_fsm`: one applies a reset signal; the other applies a simple sequence of inputs. Simulators generally let you interactively examine signals so no explicit output is necessary. The final declaration in the testbench is the configuration statement, which binds the instantiated component UUT to a particular entity, namely `tlc_fsm`, stored in a library.

### 8.2.3 Verilog

Verilog is in many respects a very different language from VHDL. Verilog has much simpler syntax and was designed for efficient simulation (although it has a synthesis subset).

#### *simple Verilog example*

Figure 8-9 gives a simple Verilog structural model of an adder. The module statement and the succeeding input and output statement declare the adder's inputs and outputs. The following statements define the gates in the adder and the connections between them and the adder's pins. The first gate is an XOR; the `#2` modifier declares that this gate has a delay of two time units. The XOR's name is `s` and its parameters follow. In this case, all the XOR's pins are connected directly to other pins. The next statements define the AND and OR gates used to compute the carry out. Each of these gates is defined to have a delay of one time unit. The carry out requires internal wires `c1`, `c2`, and `c3` to connect the AND gates to the OR gate. These names are not declared in the module so Verilog assumes that they are wires;

**Figure 8-9** A structural Verilog model.

```

// this is a comment
module adder(a,b,cin,sum,cout);
  input a, b, cin;
  output sum, cout;

  // sum
  xor #2
    s(sum,a,b,cin);
  // carry out
  and #1
    c1(x1,a,b);
    c2(x2,a,cin);
    c3(x3,b,cin);
  or #1
    c4(cout,x1,x2,x3);
endmodule
    
```

wires may also be explicitly declared using the wire statement at the beginning of the module.

**Table 8-2** Some elements of Verilog syntax.

a & b	<b>Boolean AND</b>
a   b	<b>Boolean OR</b>
~a	<b>Boolean NOT</b>
a = b	<b>assignment</b>
a <= b	<b>concurrent assignment, less than or equal to</b>
a >= b	<b>greater than or equal to</b>
==	<b>equality</b>
2'b00	<b>two-bit binary constant with value 00</b>
#1	<b>time</b>

Table 8-2 summarizes some basic syntax for Verilog expressions. We can use the 'define compiler directive (similar to the C #define preprocessor directive) to define a constant:

```
'define aconst 2'b00
```

*four-valued logic*

Verilog uses a four-valued logic that includes the value *x* for unknown and *z* for high-impedance. Table 8-4 and Table 8-3 show the truth tables

**Figure 8-10** A Verilog testbench.

```

module testbench;
    // this testbench has no inputs or outputs
    wire awire, bwire, cinwire, sumwire, coutwire;

    // declare the adder and its tester
    adder a(awire,bwire,cinwire,sumwire,coutwire);
    adder_teser at(awire,bwire,cinwire,sumwire,coutwire);
endmodule

module adder(a,b,cin,sum,cout);
    input a, b, cin;
    output sum, cout;

    // sum
    xor #2
        s(sum,a,b,cin);
    // carry out
    and #1
        c1(x1,a,b);
        c2(x2,a,cin);
        c3(x3,b,cin);
    or #1
        c4(cout,x1,x2,x3);
endmodule

module adder_teser(a,b,cin,sum,cout);
    input sum, cout;
    output a, b, cin;
    reg a, b, cin;

    initial
        begin
            $monitor($time,,
                "a=%b, b=%b, cin=%cin, sum=%d, cout=%d",
                a,b,cin,sum,cout);
            // waveform to test the adder
            #1 a=0; b=0; cin=0;
            #1 a=1; b=0; cin=0;
            #2 a=1; b=1; cin=1;
            #2 a=1; b=0; cin=1;
        end
endmodule

```

for four-valued AND and OR functions. These additional logic values help us better simulate the analog behavior of digital circuits. The high-impedance Z captures the behavior of disabled three-valued gates. The unknown value is a conservative, pessimistic method for dealing with



**Table 8-3** Truth table for OR in four-valued logic.

	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

**Table 8-4** Truth table for AND in four-valued logic.

	0	1	x	z
0	0	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x

unknown values and is particularly helpful in simulating initial conditions. A circuit often needs a particular set of initial conditions to behave properly, but nodes may come up in unknown states without initialization. If we assumed that certain nodes were 0 or 1 during simulation, we may optimistically assume that the circuit works when, in fact, it fails to operate in some initial conditions. The unknown  $x$  is an absorbing node value, as illustrated by a comparison of the four-valued AND and OR functions. The AND function's output is unknown if either of the inputs is  $x$  (or  $z$ ). That is because the AND's value is 1 only when both inputs are 1; when we do not know one of the inputs, we cannot know whether the output is 0 or 1. The OR function, in contrast, has an  $x$  output only when one of the inputs is 0 and the other is  $x$ ; if one input is 1, the output is known to be 1 independent of the other input's value.

*Verilog testbench*

Figure 8-10 shows a testbench for the adder. The testbench includes three modules. The first is the testbench itself. The testbench wires together the adder and the adder tester; it has no external inputs or outputs since none are needed. The second module is the adder, which is unchanged from Figure 8-9. The third module is the adder's tester. `adder_test` generates a series of inputs for the adder and prints the results. In order to hold the adder's inputs for easier observation of its behavior, `adder_test`'s outputs are declared as registers with the `reg` statement. The initial statement allows us to define the initial behavior of the module, which in this case is to apply a stimulus to the adder and print the results. The `$monitor` statement is similar to a C `printf` statement. The succeeding statements define the changes to signals at different times. The first `#1` line occurs one time unit after simulation starts; the second statement occurs one time unit later; the last two each occur two time units apart. At each time point, the `$monitor` statement is used to print the desired information.

*traffic light controller in Verilog*

Here is a synthesizable register-transfer Verilog model for the sequencer of the traffic light controller of Section 5.6.2 as an example.

```

module tlc_fsm(clock,reset,cars,short,long,
              highway_light,farm_light,start_timer);
    input clock, reset, cars, short, long;
    output [1:0] highway_light, farm_light;
    output start_timer;

    reg [1:0] highway_light, farm_light;
    reg start_timer;

    reg [1:0] current_state, next_state;

    // light encoding: 11 = green, 00 = red, 10 = yellow
    'define GREEN '2b11
    'define RED '2b00
    'define YELLOW '2b10

    // state encoding: 00 = hwy-green, 01 = hwy-yellow,
    // 10 = farm-green, 11 = farm-yellow
    'define HG '2b00
    'define HY '2b01
    'define FG '2b10
    'define FY '2b11

    // combinational portion
    always @(ctrl_state or short or long or cars) begin
    case (ctrl_state)
        when HG: begin // state hwy-green
            // set lights
            highway_light = GREEN;

```

```

        farm_light = RED;
        // decide what to do next
        if (cars & long) then
            begin ctrl_next = HY; start_timer = 1; end
        else begin ctrl_next = HG; start_timer = 0; end
        end
    when HY: begin // state highway-yellow
        // set lights
        highway_light = YELLOW;
        farm_light = RED;
        // decide what to do next
        if (short) then begin ctrl_next = FG; start_timer = 1; end
        else begin ctrl_next = H $\bar{Y}$ ; start_timer = 0; end
        end
    when FG: // state farm-green
        // set lights
        highway_light = RED;
        farm_light = green;
        // decide what to do next
        if (~cars | long) then
            begin ctrl_next = FY; start_timer = 1; end
        else begin ctrl_next = FG; start_timer = 0; end
        end
    when FY: // state farm-yellow
        // set lights
        highway_light = RED;
        farm_light = YELLOW;
        // decide what to do next
        if (short) then begin ctrl_next = HG; start_timer = 1; end
        else begin ctrl_next = F $\bar{Y}$ ; start_timer = 0; end
        end
    endcase
end
// sequential portion
always @(posedge clock or negedge reset) begin
    if (~reset)
        ctrl_state <= 0;
    else
        ctrl_state <= ctrl_next;
    end
endmodule

```

The model defines internal multi-bit signals to hold the machine's current and next state; those signals are registered to maintain the machine's state. The model has two sections, one for the combinational logic and another to hold the machine's state. Each section is defined as a process using the `always` statement. The synthesis tool relies on this syntactic structure to determine the various components of the synthesizable model.

Each section is guarded by an always statement that defines when each is evaluated. The combinational portion is executed when any of the combinational logic's inputs (including the machine's current state) changes as specified by the @() expression that guards the combinational portion. All the combinational inputs need to be included in the guard statement and each output should be assigned to in every case of the combinational block. The combinational section uses a case statement to extract out the various possible states, which in this case are given a specific binary encoding.

The sequential portion is executed on either a positive clock edge or a downgoing reset signal. The reset condition should be specified first, with the clock edge behavior written in the final else clause. The sequential portion uses a new form of assignment, the <= for non-blocking assignment. This form of assignment ensures that all the bits of the FSM's state are updated concurrently. The sequential portion changes little from synthesizable model to synthesizable model, unlike the combinational section, which defines the machine's unique logic.

**Figure 8-11** A synthesizable Verilog description written with continuous assigns.

```

module adder2(a,b,cin,sum,cout);
  input a, b, cin;
  output sum, cout;

  // use continuous assign
  assign sum = a ^ b ^ cin; ^ is xor
  assign cout = (a and b) or (a and cin) or (b and cin);
endmodule;

```

#### *continuous assignment*

Figure 8-11 shows an alternative synthesizable description of the adder. This model uses the assign statement, also known as the **continuous assign**. A continuous assign always drives values onto the net, independent of whether the assign's inputs have changed. The function is not implemented with logic gate models which would generate events only when their outputs changed.

**Figure 8-12** A loop in synthesizable Verilog.

```

for (i=0; i<N; i=i+1)
  x[i] = a [i] & b[i];

```

We can use for loops in synthesizable Verilog to perform similar functions over arrays of signals. Figure 8-12 shows a for loop that is used to assign the value to each member of the array x[].

We can use the `x` value to specify don't-cares for logic synthesis. Assigning an `x` to a signal specifies a don't-care condition that can be used during logic synthesis.

#### *inferred storage elements*

Logic synthesis will create inferred storage elements when an output is not assigned to in a combinational section. Inferred storage elements should be carefully examined to ensure that they are wanted and not the result of a mistake in the combinational logic description.

### 8.2.4 C as a Hardware Description Language

Even if you can't use your program as the source for synthesis, the experience of writing and executing a register-transfer simulator is invaluable.

**Figure 8-13**  
Register-transfer  
simulators in  
VHDL and C.

<pre> sync: process begin   wait until CLOCK'event     and CLOCK='1';   state &lt;= state_next;   x &lt;= x_next; y &lt;= y_next; end process sync;  combin: process begin   case state is     when S0 =&gt;       x_next &lt;= a + b;       state_next &lt;= S1;     when S1 =&gt;       y_next &lt;= a - c;       if i1 = '1' state_next &lt;= S3;       else state_next &lt;= S2;       end if;     ...   end case; end process combin; </pre> <p style="text-align: center;"><b>VHDL</b></p>	<pre> while (TRUE) {   switch (state) {     state S0:       x = a + b;       state = S1;       break;     state S1:       if (i1)         y = a - c;       if (i1)         state = S3;       else         state = S2;       break;     ...   } } </pre> <p style="text-align: center;"><b>C</b></p>
--	---

When implementing hardware in a general-purpose programming language, you must add some simple mechanisms to keep the simulation going. The C program you write will be a special-purpose simulator designed to simulate one particular piece of hardware. In contrast, VHDL and Verilog use simulation engines that take in a separate

description of the hardware to be simulated; as a result, these simulation engines can be used to simulate any sort of hardware model.

Figure 8-13 shows register-transfer simulator fragments in VHDL and C. In both languages, the simulation mechanism is based on a global variable (named `state` here) that holds the machine's current state; the states are defined by the constants `S0`, `S1`, etc. In VHDL, the machine's state (as well as the state of each register) is held in a pair of signals: one for the present value and another for the next value. When the `CLOCK` signal is applied to the simulation, the next-state signal is copied into the state signal. The machine's next-state and output logic is contained in a separate process. A case statement tests the current state. Each when clause may set outputs either conditionally or unconditionally and sets the next state variable. C uses a similar mechanism: the switch statement acts as the next-state and output logic in the FSM—given a present state, it selects a case. However, the C program must provide its own clock by repeatedly executing the register-transfer code within a while loop: one execution of the while corresponds to one clock cycle. Registers are held in global variables in this scheme.

C is widely used in chip design for initial design capture. Some synthesis tools use a subset of C as a hardware description language. Other tools use a more general form of C for simulation. The fact that C does not capture the parallel nature of hardware description can be an advantage when creating an initial functional description of a chip. C becomes more important as levels of integration increase and chips implement more complex functions. The **SystemC** language has been created as an industry standard for system-level modeling. SystemC provides some mechanisms for the simulation of parallel processes, but it has a much simpler simulation engine than do VHDL or Verilog. The **SpecC** language is another industrial system-level modeling language. SpecC has more complex simulation semantics than does SystemC but is also aimed at the system-level design problem.

---

## 8.3 Register-Transfer Design


---

*register-transfer and  
sequential logic*

A register-transfer system is a pure sequential machine. It is specified as a set of memory elements and combinational logic functions between those elements, as shown in Figure 8-14. We don't know the structure of the logic inside the combinational functions—if we specify an adder, we don't know how the logic to compute the addition is implemented. As a


---

---

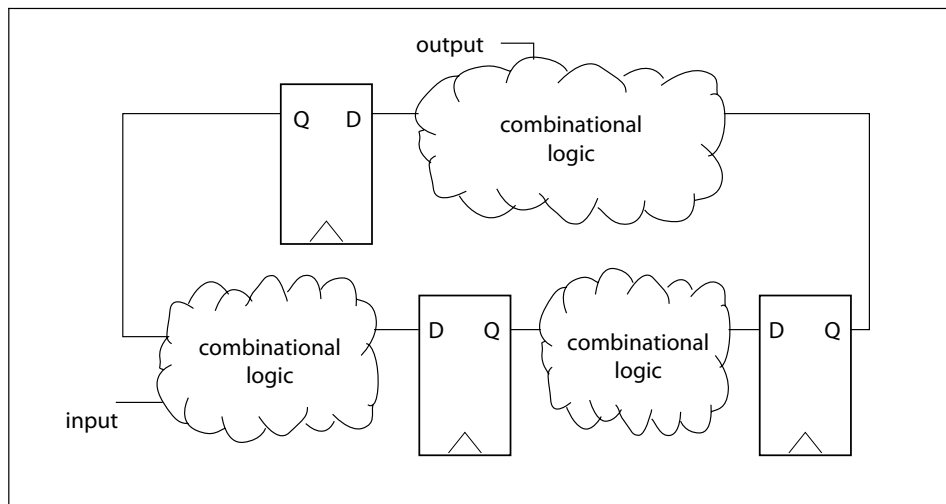

**Figure 8-14** A register-transfer system.

result, we don't know how large or how fast the system will be. To make the sequential part more abstract, we can specify the logic over symbolic, rather than binary values—for example, specifying the output of a function to range over  $\{\alpha, \beta, \gamma, \delta\}$ . The registers are generic flip-flops—we don't worry about clocking disciplines at this stage of design. Once the register-transfer has been completed, it can be mapped into a sequential system with a clocking discipline appropriate to the memory elements used.

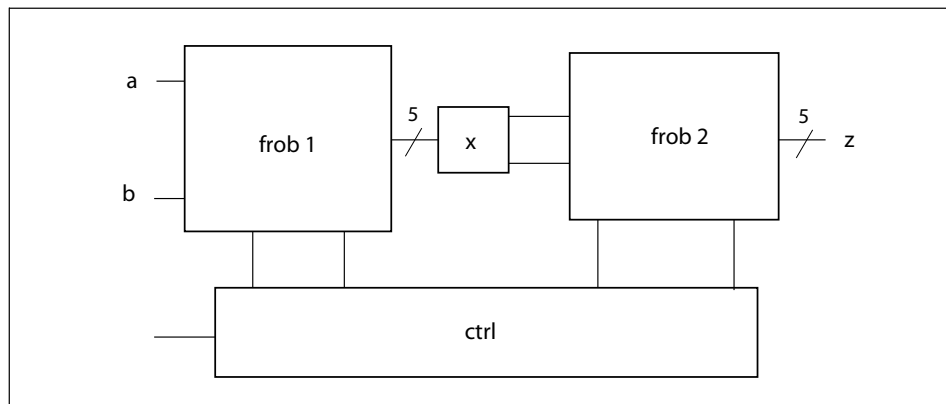

**Figure 8-15** A typical block diagram.

*block diagrams*

The most common register-transfer description is the **block diagram**. A typical block diagram is shown in Figure 8-15. A block diagram is a purely structural description—it shows the connections between boxes. (The slash and 5 identify each of those wires as a bundle of five wires, such as the five bits in a data word.) If we know the boxes' functions, we can figure out the function of the complete system. However, many designers who sketch block diagrams are cavalier about defining their primitive elements and drawing all the wires. Wires may go into boxes with unclear functions, leaving the reader (for example, the person who must implement those blocks or the person who must figure out why the system doesn't work) at a loss. The block diagram also may not show all connections or may leave out some small bits of logic. While such omissions may make the major elements of the system easier to identify in the figure, it renders the diagram problematic as a specification of the design.

Register-transfer designs are often described in terms of familiar components: multiplexers, ALUs, etc. Standard components can help you organize your specification and they also give good implementation hints. But don't spend too much time doing logic design when sketching your block diagram. The purpose of register-transfer design is to correctly specify sequential behavior.

*register-transfers*

We can also describe register transfers using a simple language. For example, the statement

$$Z = A + B;$$

means that register  $Z$  is assigned the value  $A + B$ . This happens on every clock cycle. We can also make conditional assignments:

$$\text{cond: } Z = A + B;$$

means that  $Z$  is assigned the value  $A+B$  only when the Boolean condition is true. (If we want to assign a different value to  $Z$  under different conditions, we can use a separate conditional register transfer.)


### 8.3.1 Data Path-Controller Architectures

*data paths and controllers*

One very common style of register-transfer machine is the **data path-controller** architecture. We typically break architectures into data and control sections for convenience—the data section includes loadable registers and regular arithmetic and logical functions, while the control section includes random logic and state machines. Since few machines are either all data or all control, we often find it easiest to think about the system in this style.



**Figure 8-16** Data and control are equivalent.

 



*data vs. control*

The distinction between data and control is useful—it helps organize our thinking about the machine’s execution. But that distinction is not rigid; data and control are equivalent. The two VHDL statements in Figure 8-16 correspond to the same combinational logic: the if statement in the control version corresponds to an OR in the data version that determines which value is assigned to the o1 signal. We can use Boolean data operations to compute the control flow conditions, then add those conditions to any assignments to eliminate all traces of the control statement. The process can be reversed to turn data operations into control.

Operators such as adders are easily identifiable in the architectural description. As shown in Figure 8-17, some hardware is implicit. The if statement defines conditions under which a register is loaded and the source of its new value. Those conditions imply, along with control logic to determine when the register is loaded, a multiplexer to route the desired value to the register. We generally think of such multiplexers as data path elements in block diagrams, but there is no explicit mux operator in the architectural description.

**Figure 8-17** Multiplexers are hidden in architectural models.

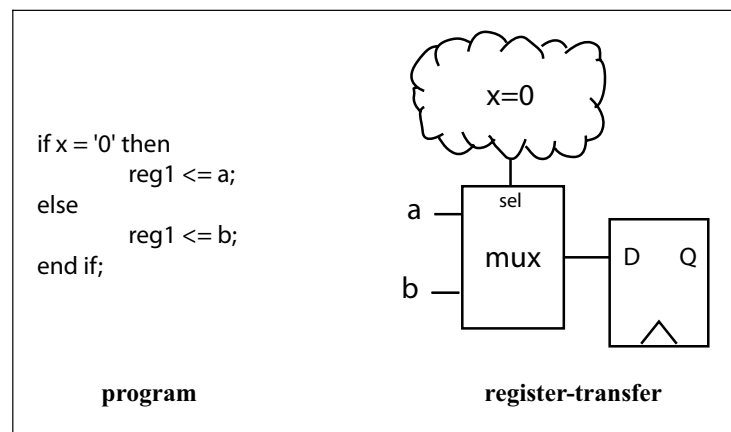

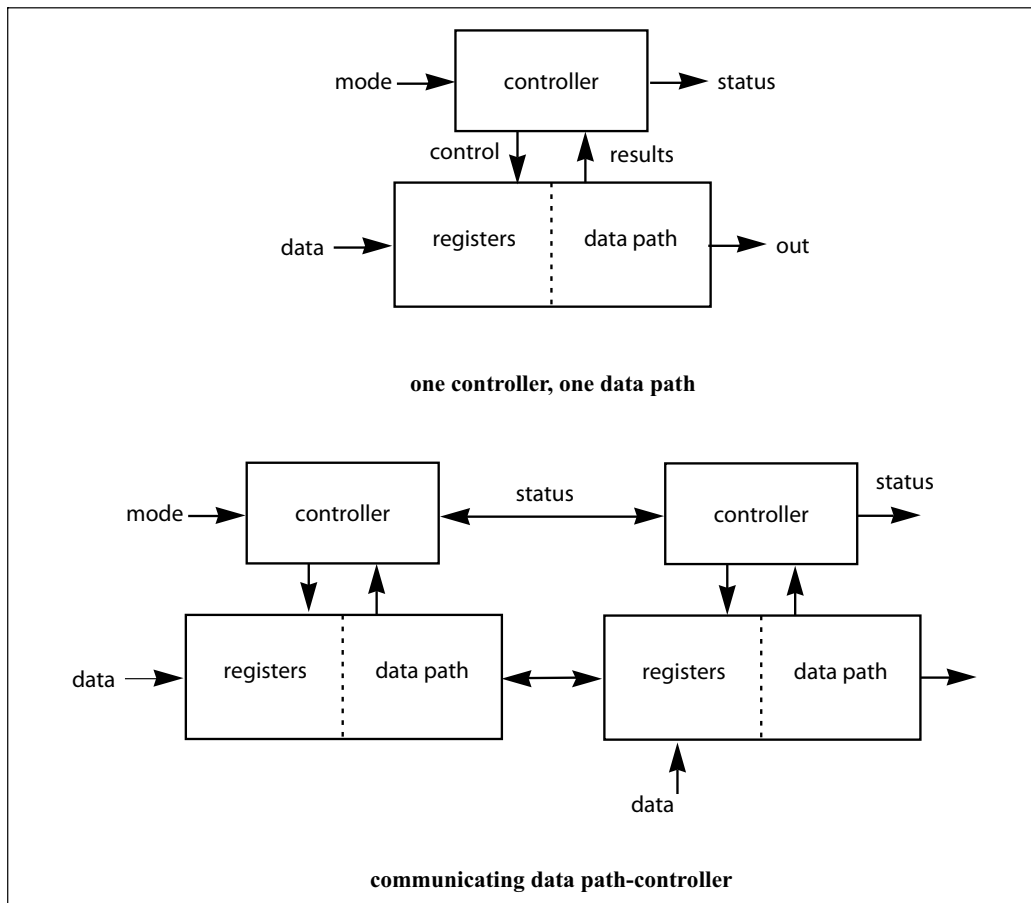

**Figure 8-18** The data path-controller architecture.

Very few architectures are either all control (simple communications protocols, for example) or all data (digital filters). Most architectures require some control and some data. Separating the design into a controller and a data path helps us think about the system's operation. Separating control and data is also important in many cases to producing a good implementation—we saw in Chapter 6 that data operators have specialized implementations and that control structures require very different optimization methods from those used for data. Figure 8-18 shows how we can build a complex system from a single controller for a


single data path, or by dividing the necessary functions between communicating data path-controller systems.

### 8.3.2 ASM Chart Design

*ASM charts combine control and data*

The **ASM chart** [Cla73] is a very useful abstraction for register-transfer design because it helps us to avoid over-specifying the partitioning of logic and to concentrate on correctness. An ASM chart, such as the one in Figure 8-19, looks like a flowchart, but unlike a flowchart, it has precisely-defined hardware semantics. An ASM chart is a specification of a register-transfer system because it defines what happens on every cycle of operation. It is more of a functional specification than a block diagram—the flow of control from state to state is clearly shown. And, unlike a block diagram, it doesn't imply any partitioning of the functions to be executed.

**Figure 8-19** An ASM chart.

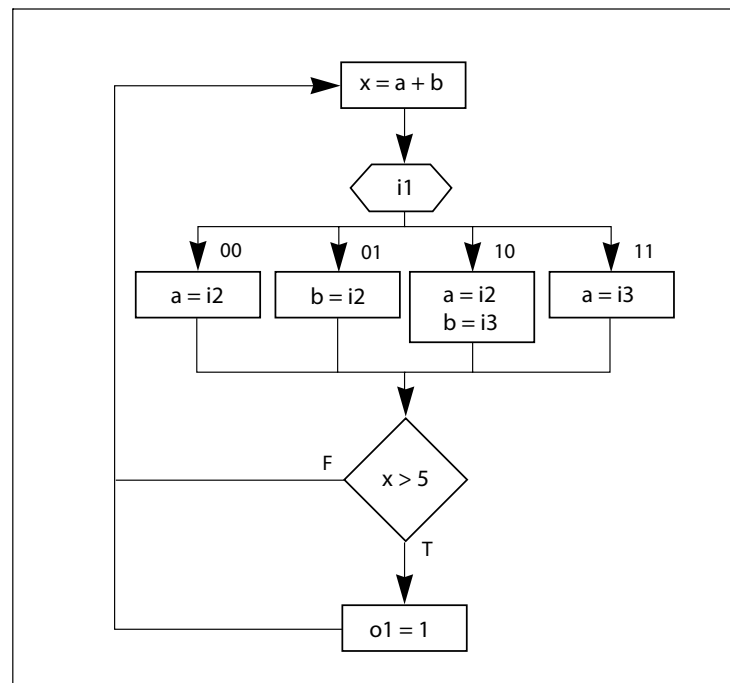


An ASM chart specification is particularly well-suited to data path-controller architectures. The operations in the boxes, which are generally

regular data operations, are executed in the data path; the ASM chart's boxes and edges give the state transition graph for the controller.

#### ASM states

The most basic element of the ASM chart is the state; an example is shown in Figure 8-20. A state is represented in the ASM as a rectangle, with an optional name for the state given in a nearby circle. The state is decorated with a number of operations shown inside the box. All the operations in a state are executed on the same cycle—a state in the ASM chart corresponds to a state in the register-transfer system. (Actually, an ASM state corresponds to a state in the system's controller and to many states in the complete system, since data operations such as  $x = a + b$  can induce many states, depending on the values of  $a$  and  $b$ . The ASM chart is a powerful notation because it simply and cleanly summarizes the system's state.)

**Figure 8-20** An ASM state.

 




You can put as many operations as you want into a state, though adding more operations will require more hardware. The only proviso is that a single variable can be the target of an assignment only once in a state—this is known as the **single assignment** requirement. Consider the two states of Figure 8-21. State **s1** specifies a single operation. A block diagram which implements this state would include the registers for the three variables and a single adder. State **s2** requires two additions. To implement this state, we must include two adders in the block diagram, since both additions must be done in the same cycle.

What effect does assigning twice to the same variable in a state have? In Figure 8-22, the variable  $x$  is assigned to twice, which requires loading the  $x$  register twice in a single clock cycle. We obviously can't load a register twice per cycle in a strict sequential system.

It is, however, perfectly acceptable to assign a value to a variable in distinct states. In Figure 8-23,  $x$  is assigned to in both states **s1** and **s2**. It is perfectly fine to load a register in two successive cycles. Presumably, some other part of the system or the outside world looks at  $x$  between the two assignments. But even if this ASM chart is a poorly thought-out specification, it is a valid register-transfer system.

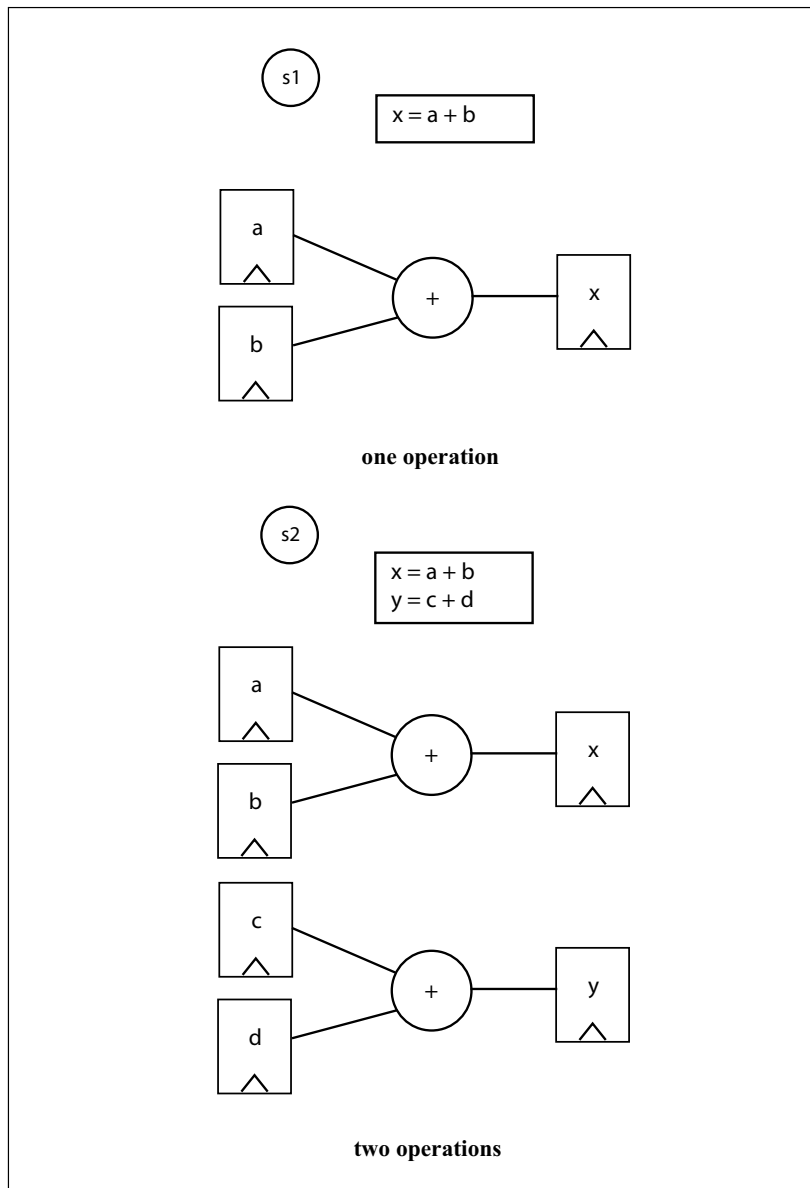  **Figure 8-21** How to implement operations in an ASM state.

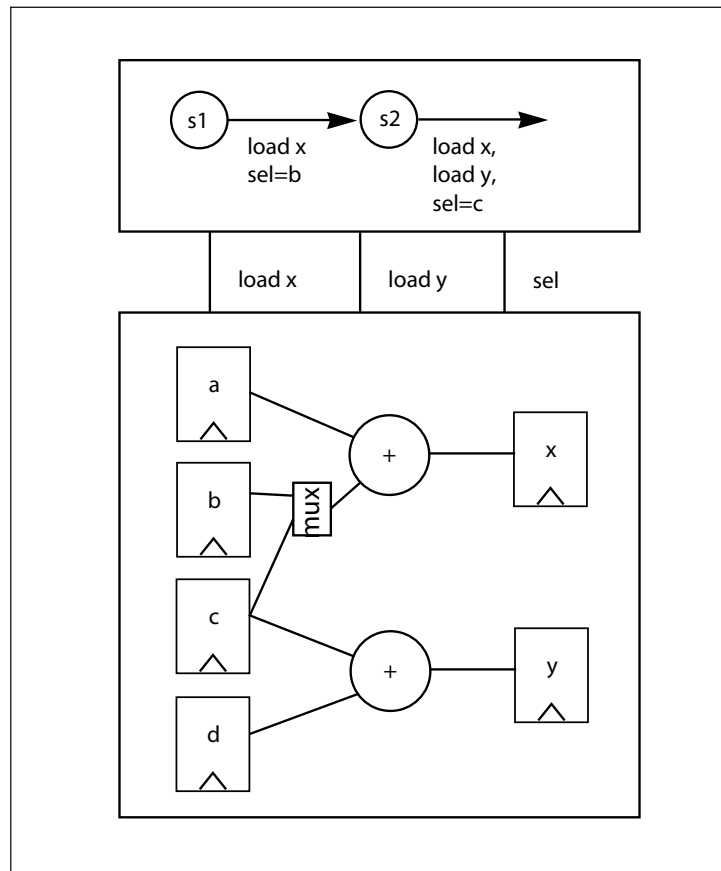


**Figure 8-22** Multiple assignment in an ASM state.**Figure 8-23** Sequential states in an ASM chart.

The presence of multiple states makes it a little harder to design an efficient block diagram. Let's assume that our registers all have load signals to allow us to set their values only when desired. All the operations within a state require distinct hardware units, called **function units**, to implement the operations such as  $+$ , since those operations must be done simultaneously. The simplest way to implement operations in sequential states is to assign a different function unit to each operation. That option is extremely wasteful—the ASM of Figure 8-23 would require three adders, even though at most two are used at one time. In practice, we will want to share function units across states, as shown in Figure 8-24. The minimum number of function units we need in the block diagram is the number required in any one state. To reuse a function unit, we put multiplexers on its inputs, as shown in the figure. The top adder can have its second input selected to be either  $b$  or  $c$ . The second adder doesn't need multiplexed inputs because it is only used once.

We can now start to understand how an ASM chart can be implemented as a data path plus controller. Figure 8-24 shows a system that implements the ASM chart fragment of Figure 8-23. The data path section includes the registers and the logic for the regular operations specified in the ASM states. The controller includes a controller that determines the sequence of actions to be performed. The states of the controller determine when we move from ASM state  $s1$  to ASM state  $s2$ . In each state, the controller sets control signals which tell the data path what to do: in the first state, it sets the load signal for  $x$  and the multiplexer select signals to send the right operands to the adder; in the second state, it sets the load signals for  $x$  and  $y$ , along with a new set of mux select signals. Strictly speaking, the data path can go into many states, depending on the values of its registers. But the structure of states and transi-

**Figure 8-24** How sequential ASM states are implemented as data path and controller.




tions in the controller component mirrors the structure of the ASM chart.

*ASM conditions*

An ASM chart with only unconditional transitions has limited charms. Branches are represented as diamonds of any shape—typically the four-sided diamond is used for two- or three-way branches, while the six-sided diamond is used for more numerous branches. The condition for the branch is given in the diamond, and each transition is labeled with the values that cause that condition to be true. The branch condition may be a direct test of a primary input, such as  $i1 = 0$ , where all the logic for the test is in the controller; it may also be computed in the controller. For example, to test  $x = y$ , we may subtract  $y$  from  $x$  in the data path, test the result to check for 0, and send a single signal from the data path to the controller giving the result of the test.

**Figure 8-25** Symbols for branches in an ASM chart.

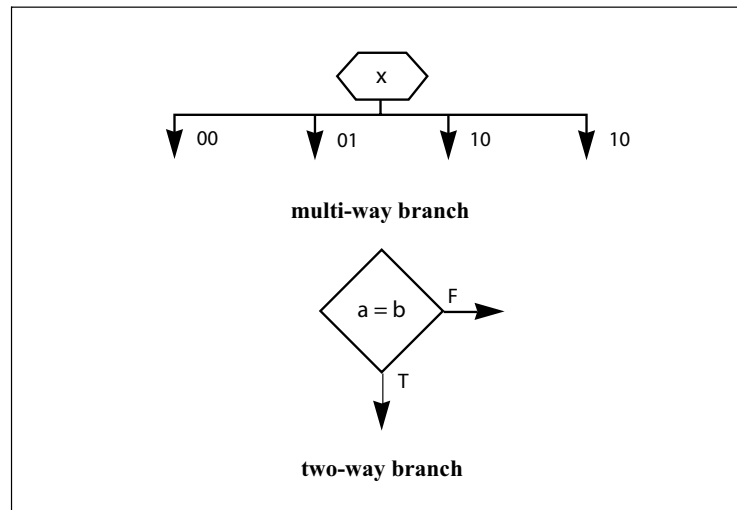


The condition is tested on the same cycle as the state preceding the branch. With this definition, the ASM chart corresponds to a traditional Moore machine. Figure 8-26 shows how the structure of a Moore machine corresponds to the structure of a state plus branch in an ASM chart. The Moore machine remembers its present state and accepts its inputs; from that information, its next-state logic computes the machine's next state. Similarly, given an ASM state, a given value at a branch selects an ASM transition that leads to the next ASM state.

#### *ASM conditional outputs*

Specifying a Mealy machine in an ASM chart requires conditional outputs. As shown in Figure 8-27, conditional outputs in an ASM chart are given in rounded boxes. A conditional output is not a state and does not consume a clock cycle. If, in the figure, the branch leading to the conditional output is taken, the  $y = c + d$  action occurs on the same cycle as the  $x = a + b$  action. This corresponds to computing the output value of the Mealy machine based on the FSM's inputs, as well as its present state. Compare the Mealy controller FSM of Figure 8-27 to the Moore controller of Figure 8-26: the Moore controller, for example, executes  $y = c + d$  in state  $s_2$ , while the Mealy controller executes that action on one transition out of state  $s_1$ . The restrictions on conditional ASM outputs are the same as those on Mealy machines—if a Mealy machine or ASM is connected to external logic which creates a combinational cycle between its conditional outputs and its inputs, the resulting logic is not a legal sequential system.




**Figure 8-26** Implementing an ASM branch in a Moore machine.

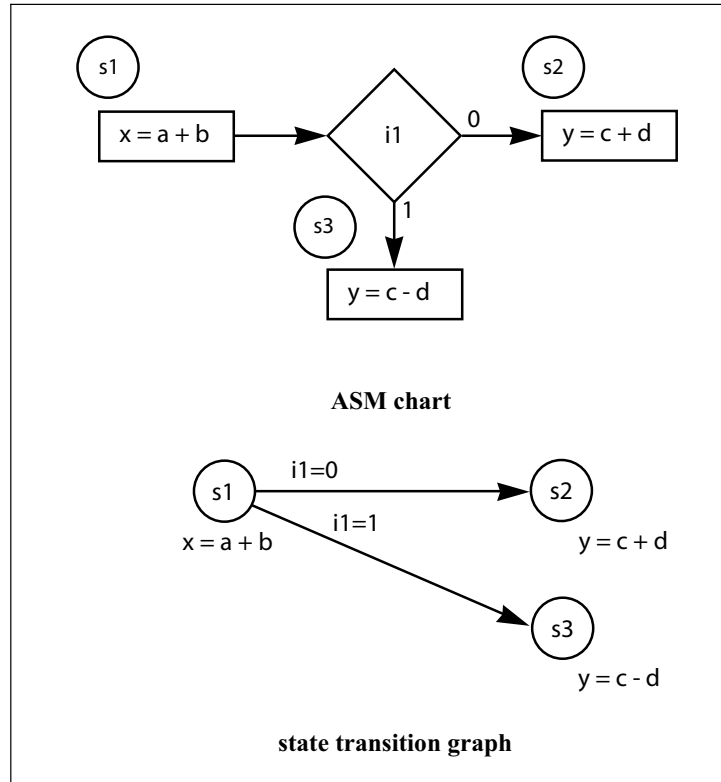

*ASMs and register-transfer*


Since a Mealy machine is a general sequential machine, ASM chart notation lets us specify arbitrary register-transfer systems. The ASM chart is particularly powerful when the system performs a mixture of control and data operations. For a system that is mostly control, like the 01-string recognizer of Example 5-4, an ASM chart is no easier to use than a state transition graph. If we specify a data-rich system, such as a CPU, with a state transition graph, we must simultaneously design the data path upon which those operations will be executed. The ASM chart lets us write down the operations without worrying about whether a particular operation goes into the data path or controller, or the exact structure of the data path. Once we have made sure the ASM chart is correct, we can refine the design to specify the data path structure and control signals. Think of pulling the operations out of the ASM states to produce the data path, as shown in Figure 8-28. The data path operations drag behind them the control signals required to select the appropriate actions at each cycle; the signals that cross the data path-controller

**Figure 8-27** A conditional output in an ASM chart.

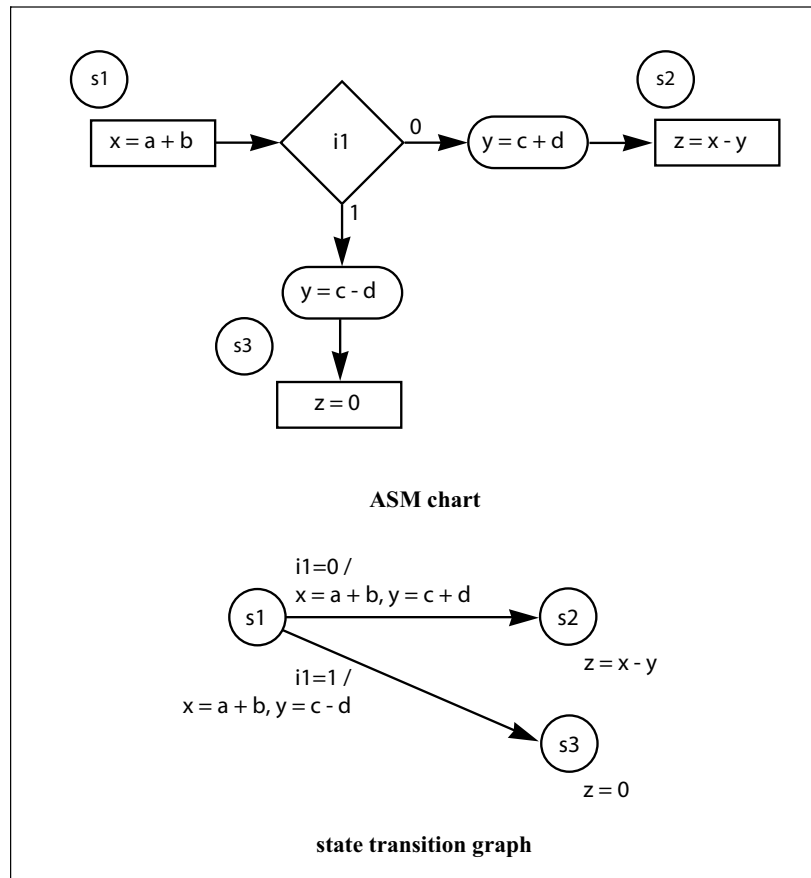


boundary, along with the system inputs and outputs, form the controller's inputs and outputs. The skeleton of the ASM chart left when the data path operations are extracted gives the structure of the controller's state transition graph.

**Figure 8-28**  
Extracting a data path and controller from an ASM chart.

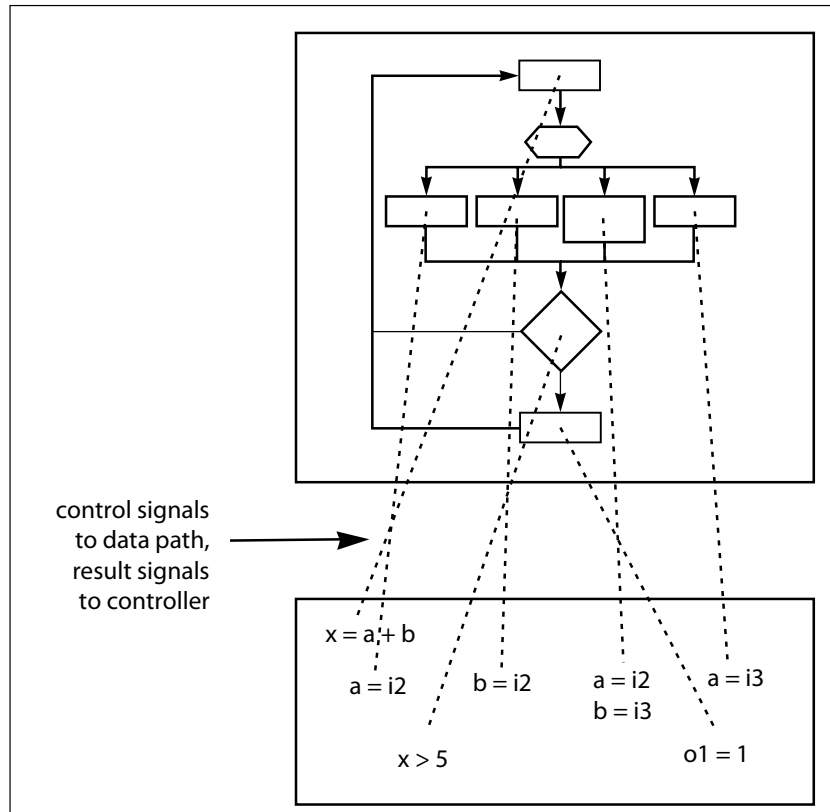

## 8.4 Pipelining

**Pipelining** is a well-known method for improving the performance of digital systems. Pipelining exploits concurrency in combinational logic in order to improve system throughput. Pipelining changes the sequential behavior of the system—it changes the number of cycles required to perform the operation. Pipelined and non-pipelined versions of a function have different ASM charts and different register-transfers. This change in sequential behavior requires us to ensure that other parts of the system look for the outputs of the pipelined unit at the right times. But pipelining can offer substantial performance advantages, given the proper definition of performance.

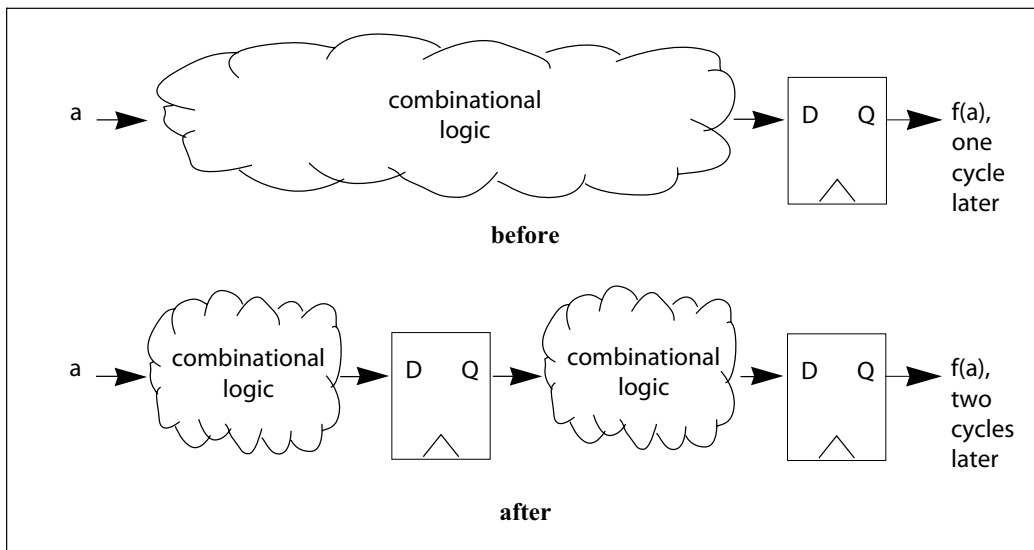

**Figure 8-29** Adding pipelining.

*adding registers to  
increase throughput*

Figure 8-29 illustrates the fundamentals of pipelining. We start with a block of combinational logic that computes some function  $f(a)$ . That logic has some intrinsic delay. If we introduce a rank of registers into the logic properly, we can split it into two separate blocks of combinational logic. (We must be sure that the registers cut all the paths between the two logic blocks.) Each resulting block has a smaller delay; if we have done a good job, each block has about half the delay of the original block. Because each block has its own registers, we can operate the two

blocks independently, working on two values at the same time. The left-hand block would start computing  $f(a)$  for a new input while the right-hand block would complete the function for the value started at the last cycle. Furthermore, we have reduced the cycle time of the machine because we have cut the maximum delay through the combinational logic.

*throughput and latency*

It is important to keep in mind that pipelining does not reduce the amount of time it takes to compute  $f(a)$ . In fact, because the register in the middle of the machine has its own setup and propagation times, the time it takes for a value to go through the system goes up slightly with pipelining. This time is known as **latency**. But we have increased the machine's **throughput**—the number of results that we can compute in a given amount of time. Assume that the delay through a single combinational logic block that computes  $f(a)$  is  $D$ . Call latency  $L$  and throughput  $T$ . If we ignore register setup and hold times for the moment, we can write these definitions for the unpipelined system:

$$L = D, \quad (\text{EQ 8-1})$$

$$T = 1/D. \quad (\text{EQ 8-2})$$

If we pipeline the logic perfectly so that it is divided into two blocks with equal delay, then  $L$  remains the same but  $T$  becomes  $2/D$ . If we perfectly pipeline the logic into  $n$  blocks, we have

$$L = D, \quad (\text{EQ 8-3})$$


$$T = n/D. \quad (\text{EQ 8-4})$$

The clock period is determined by the delay  $D$  and the number of pipeline stages:

$$P = \frac{D}{n} \quad (\text{EQ 8-5})$$

Figure 8-30 shows how clock period and throughput change with the number of pipeline stages. Throughput increases linearly with pipeline depth. Clock period decreases dramatically with the first few pipeline stages. But as we add more pipeline stages, we are subdividing a smaller and smaller clock period and we obtain smaller gains from pipelining. We could ultimately pipeline a machine so that there is a register between every pair of gates, but this would add considerable cost in registers.


**Figure 8-30** Clock period and throughput as a function of pipeline depth.

 


#### *adding pipeline registers*

If we want to pipeline a combinational system, we need to add registers at the appropriate points. The register addition process resembles the timing analysis we performed in Section 5.4. We can use a graph to represent the structure of the logic, with one node per logic element or gate and an edge that represent electrical connections. In timing optimization we must improve timing across a cutset of the timing graph. Similarly, we must add a **rank** of registers across a cutset of the logic graph. (Remember, a cutset of a graph is a set of edges that breaks all paths between two sets of nodes. In this case, we want to add registers between all possible paths from inputs to outputs.) Figure 8-31 shows the logic of Figure 4-12 and two of the many possible cutsets through the logic graph. Adding registers across any cutset is sufficient to ensure that the logic's functionality is not destroyed. However, the best cutsets divide the logic into blocks of roughly equal delay. We can use retiming, introduced in Section 5.4.4, to determine the best places to put the pipelining registers. Retiming will duplicate and merge registers as necessary to preserve functionality.

What happens if we do not add registers across an entire cutset? Consider Figure 8-32, in which a cut through the logic is made that does not

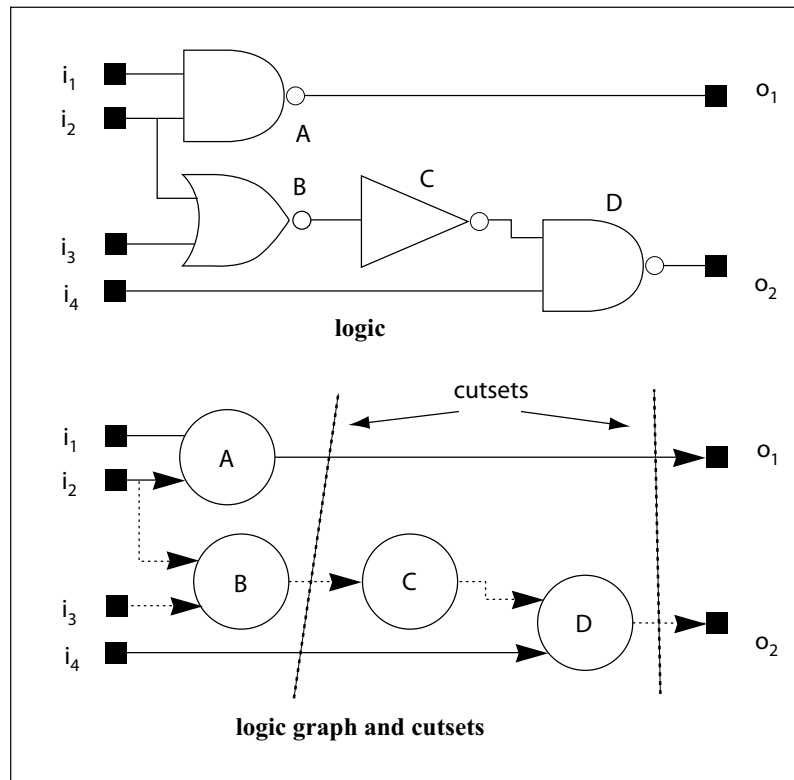

**Figure 8-31** Logic and cutsets for pipelining.

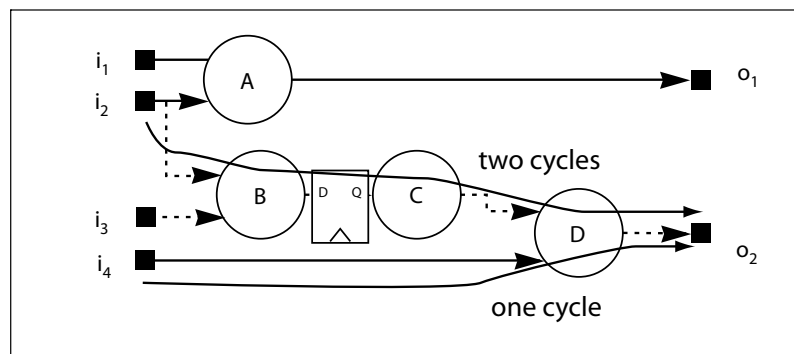

**Figure 8-32** A bad cutset for pipelining.

place registers along all the paths from inputs to outputs. There is no register along the path from  $i_4$  to  $o_2$ , but there is one register along the  $i_2$ -  $o_2$  path. As a result, when the inputs are presented to the logic, the D gate will receive its two inputs from two different clock cycles. The resulting output will be garbage.

A pipelined unit produces its outputs on a later clock cycle than does a non-pipelined unit. This is fine in some cases, while other logic designs are intolerant to the latency introduced by pipelining. We need to be careful when we are adding pipelines to a more abstract design than the logic gates since the abstraction may obscure some of the important details.

In steady state, an ideal pipeline produces an output on every cycle. However, when you start the pipe, it takes  $n$  cycles for an  $n$ -stage pipeline to produce a result. Similarly, when you stop putting data in the pipe, it takes  $n$  stages for the last value to come out of the pipe. The initialization time reduces the average pipeline utilization when we have short bursts of data. If we have  $D$  clock cycles' worth of data in an  $n$ -stage pipeline, then the utilization is


$$\frac{D}{D + n} \tag{EQ 8-6}$$

As  $D$  approaches infinity—that is, as we move toward operating the pipeline continuously—this utilization approaches 1. When  $D$  and  $n$  are near equal, then the utilization goes down.

*pipelines with control*

More complex pipelines, such as those in CPUs, have controllers that cause the pipeline to do different things on different cycles. In the case of the CPU, the pipeline must perform different operations for different instructions. When designing non-ideal pipelines with control, we must be sure that the pipeline always operates properly.

**Figure 8-33** A pipeline with a feedforward constraint.

 



Some control operations are straightforward. Figure 8-33 shows a pipeline in which one stage computes the opcode for the ALU to be used in the next stage. So long as we pipeline the opcode so that it arrives at the right time, this works fine.

**Figure 8-34** A pipeline with a backward constraint.

 


Figure 8-34 shows a more complex case. Here, the result of the ALU operation causes us to change what we do in a previous stage. A good example is a conditional jump in a CPU, where the result of one instruction causes us to change which instructions are to be executed next in time (corresponding to earlier in the pipe). Here we must make sure that the pipeline does not produce any erroneous results as a result of the change in condition.

**Figure 8-35** A pipeline with hardware shared across several stages.


 


Figure 8-35 shows a still more complicated situation. In this case, a single ALU is shared by two different stages. Small CPUs may share an ALU or other logic in order to reduce the size of the logic. Here we must be very careful that the two stages do not try to use the shared hardware at the same time. The losing stage of the pipeline would probably not be able to detect the error and would take a bad result.

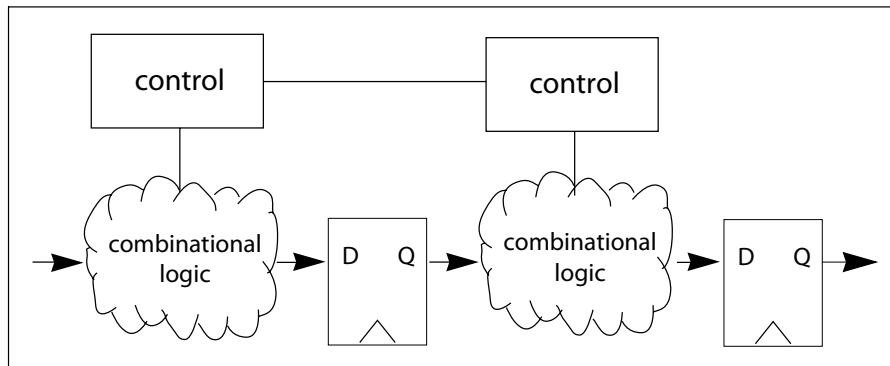

**Figure 8-36** A pipeline with distributed control.


#### *pipeline control*

How do we design controllers for pipelines? The most common form of pipeline control is **distributed control**, illustrated in Figure 8-36. Rather than design one large state machine that simultaneously controls all the stages of the pipe, we typically design one controller for each stage. As shown in the figure, the controllers communicate in order to coordinate the actions across stages. Distributed control has some advantages in both specification and implementation. It is often easier to write the description of what a stage does than it is to write the entire pipeline operation for a single cycle. But the main reason for distributed control is that distributing the logic to be near the stage it controls helps to reduce delays.

When we design a pipeline with control, we must also worry about verifying that the pipeline operates correctly. Because they have a large amount of state, pipelines can be hard to verify. Distributed control makes some aspects of design and verification easier and some other aspects harder. Distributed control is harder simply because we do not have all the control information in one place. When we distribute the control formulas, it is harder for a person to look at the control actions and see that they always do what was intended.

When we write the control for a pipeline stage, we often use **symbolic FSM** notation. The transitions in a symbolic FSM may contain not just constants but also the names of registers in the pipeline data path. If we look at the state of the entire machine, we would have to write states for every different data path register value. But because we are interested in the operations on these states, symbolic FSMs allow us to factor out the control from the data path.

**Figure 8-37** A simple symbolic FSM for pipeline control.

 

A simple case of a pipeline control machine is shown in Figure 8-37. This machine describes the control for the ALU of the pipeline in Figure 8-33. The controller makes no decisions but needs a register to hold the ALU opcode. On every clock cycle, the ALU opcode register may receive a new value from the previous pipeline stage, causing the ALU to perform a different operation, but this does not require an explicit control decision.

**Figure 8-38** A condition in pipeline control.



 


Figure 8-38 shows a symbolic FSM with a condition. Here, some operation, probably from the previous stage, may cause the state machine to issue an ALU opcode of either + or -. Because the pipeline stage is only one cycle long, the conditions all return to the initial state.

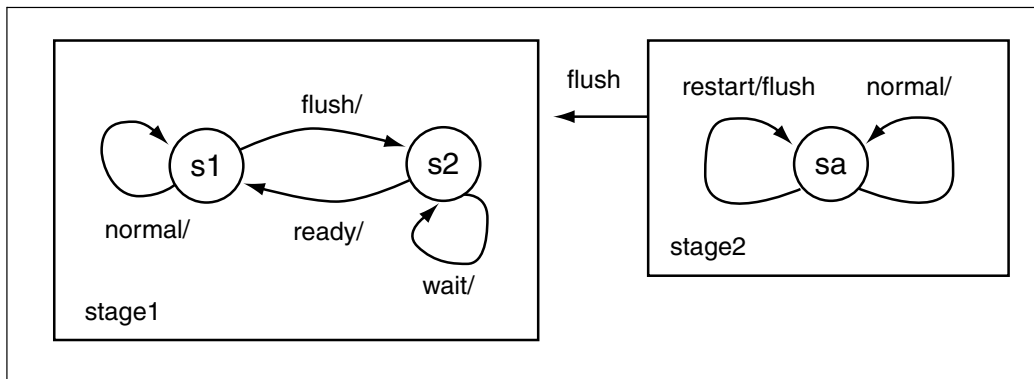

**Figure 8-39** Distributed control for a pipeline flush.

Figure 8-39 shows one possible description of distributed control for a pipeline flush like that illustrated in Figure 8-34. Stage 2 receives a restart signal from its own logic. This causes it to issue a flush command to stage 1. Stage 1 then enters a separate state in which it waits for the flush to end; this may be controlled by a timer or some other external event. The stage then returns to normal operation.

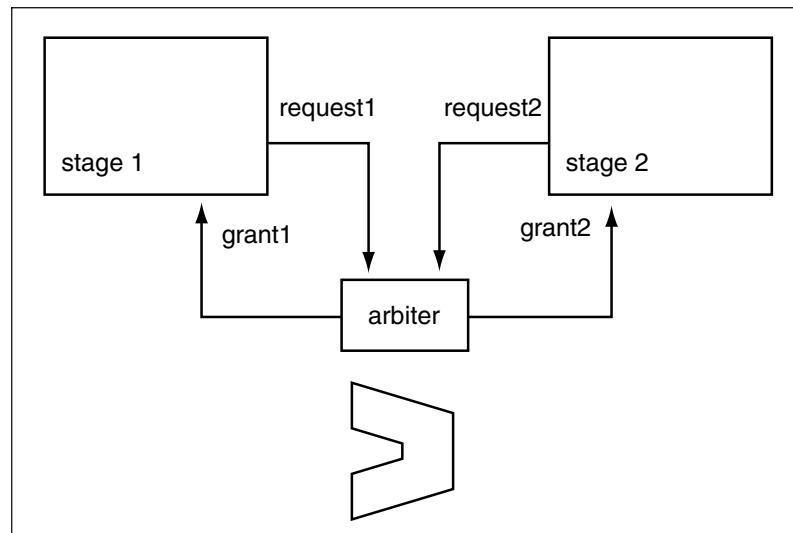


**Figure 8-40** Control for hardware sharing.

Figure 8-40 shows control logic for shared hardware like that of Figure 8-35. This scheme is similar to arbitration on a bus. Arbitration logic determines which stage gets the shared hardware (the ALU) on each cycle. Each stage uses a request line to signal the arbiter; each stage watches its own grant line to see when it has the shared logic. In this setup, if each pipe stage is only one cycle long, the arbiter would have to be combinational to ensure that the answer came within the same cycle. The stages would have to hold request for the remainder of the cycle to ensure that the arbiter output didn't change.

#### *pipeline verification*

Distributed control can be hard to verify because we do not have a single description that tells us what all of the pipeline does in every stage. However, we can form the product machine of the distributed control stages to help us see the global results of control. Figure 8-41 shows the product machine for the distributed pipeline flush of Figure 8-39. Forming the product machine of a symbolic FSM takes some more work than

**Figure 8-41** Product machine formed from distributed control.

 

forming the product of a pure FSM, but it is not difficult. The product machine makes it easier to verify that:

- the control enters all the required states and performs all the required operations in those states;
- the control does not enter any undesired states.

One technique used for pipeline verification is **symbolic simulation**. If we tried to simulate the pipeline with all known data and control register values, we would quickly find that the simulation was much too long. Pipelines have large numbers of states that blow up simulation times. However, by simulating the data register values symbolically, we can collapse many of those states. A relatively small number of simulations can then cover the various cases in the control logic.

## 8.5 High-Level Synthesis

*behavior vs.  
register-transfer*

A register-transfer isn't the most abstract, general description of your system. The register-transfer assigns each operation to a clock cycle, and those choices have a profound influence on the size, speed, and testability of your design. If you think directly in terms of register-transfers, without thinking first of a more abstract **behavior** of your system, you will miss important opportunities. Consider this simple sequence of operations:

```

x <= a + b;
y <= c + d;
if z > 0 then
  w <= e + f;
end if;
  
```

How many clock cycles must it take to execute these operations? The assignments to *x* and *y* and the test of *z* are all unrelated, so they could

be performed in the same clock cycle; though we must test *z* before we perform the conditional assignment to *w*, we could design logic to perform both the test and the assignment on the same cycle. However, performing all those operations simultaneously costs considerably more hardware than doing them in successive clock cycles.

*high-level synthesis*

**High-level synthesis** (also known as **behavioral synthesis**) constructs a register-transfer from a behavior in which the times of operations are not fully specified. The external world often imposes constraints on the times at which our chip must execute actions—the specification may, for example, require that an output be produced within two cycles of receiving a given input. But the behavior model includes only necessary constraints on the system’s temporal behavior.

*scheduling and binding*

The primary jobs in translating a behavior specification into an architecture are **scheduling** and **binding** (also called allocation). The specification program describes a number of operations that must be performed, but not the exact clock cycle on which each is to be done. Scheduling assigns operations to clock cycles. Several different schedules may be feasible, so we choose the schedule that minimizes our costs: delay and area. The more hardware we allocate to the architecture, the more operations we can do in parallel (up to the maximum parallelism in the hardware), but the more area we burn. As a result, we want to allocate our computational resources to get maximum performance at minimal hardware cost. Of course, exact costs are hard to measure because architecture is a long way from the final layout: adding more hardware may make wires between components longer, adding delay that actually slows down the chip. However, in many cases we can make reasonable cost estimates from the register-transfer design and check their validity later, when we have a more complete implementation.

### 8.5.1 Functional Modeling Programs

*functional models*

A program that models a chip’s desired function is given a variety of names: functional model, behavior model, architectural simulator, to name a few. A specification program mimics the behavior of the chip at its pins. The internals of the specification need have nothing to do with how the chip works, but the input/output behavior of the behavior model should be the same as that of the chip. For the moment, we just need to understand the relationship between program models and hardware.

Figure 8-42 shows a fragment of a simple VHDL functional model. This code describes the values to be computed and the decisions to be made based on inputs. What distinguishes it from a register-transfer

**Figure 8-42** Fragment of a VHDL functional model.

```
o1 <= i1 or i2;
if i3 = '0' then
  o1 <= '1';
  o2 <= a + b;
else
  o1 <= '0';
end if;
```

description is that the cycles on which these operations are to occur are not specified. We could, for example, execute `o1 <= '1'` and `o2 <= a + b` on the same cycle or on different cycles.

#### *data dependencies*

Reading inputs and producing outputs for a functional model requires more thought than for a register-transfer model. Since the register-transfer's operations are fully scheduled, we always know when to ask for an input. The functional model's inputs and outputs aren't assigned particular clock cycles yet. Since a general-purpose programming language is executed sequentially, we must assign the input and output statements a particular order of execution in the simulator. Matching up the results of behavioral and register-transfer simulations can be frustrating, too. The most important information given by the functional model is the constraints on the order of execution: e.g., `y = x + c` must be executed after `x = a + b`. A **data dependency** exists between the two statements because `x` is written by the first statement and used by the second; if we use `x`'s value before it is written, we get the wrong answer. Data flow constraints are critical pieces of information for scheduling and binding.


### 8.5.2 Data

#### *data flow models*


The most natural model for computation expressed entirely as data operations is the **data flow graph**. The data flow graph captures all data dependencies in a behavior that is a **basic block**: only assignments, with no control statements such as `if`. The following example introduces the data flow graph by building one from a language description.

 **Example 8-1**  
**Program code**  
**into data flow**  
**graph**

The first step in using a data flow graph to analyze our basic block is to convert it to single-assignment form:



 Now construct a graph with one node for each data operator and directed edges for the variables (each variable may have several sinks but only one source):



The data flow graph is a **directed acyclic graph** (DAG), in which all edges are directed and there is no cycle of edges that form a path from a node back to that node. A data flow graph has primary inputs and primary outputs like those in a logic network. (We may want to save the value of an intermediate variable for use outside the basic block while still using it to compute another variable in the block.) We can execute this data flow graph by placing values for the source variables on their corresponding DAG edges. A node *fires* when all its incoming edges have defined values; upon firing, a node computes the required value




and places it on its outgoing edge. Data flows from the top of the DAG to its bottom during computation.

*implementing data flow models*

How do we build hardware to execute a data flow graph? The simplest—and far from best—method is shown in Figure 8-43. Each node in the data flow graph of the example has been implemented by a separate hardware unit that performs the required function; each variable carrier has been implemented by a wire. This design works, but, as we saw in Section 8.3.2, it wastes a lot of hardware. Our execution model for data flow graphs tells us that not all of the hardware units will be working at the same time—an operator fires only when all its inputs become available, then it goes idle. This direct implementation of the data flow graph can waste a lot of area—the deeper the data flow DAG, the higher the percentage of idle hardware at any moment.

**Figure 8-43**  
An overgenerous implementation of a data flow graph.

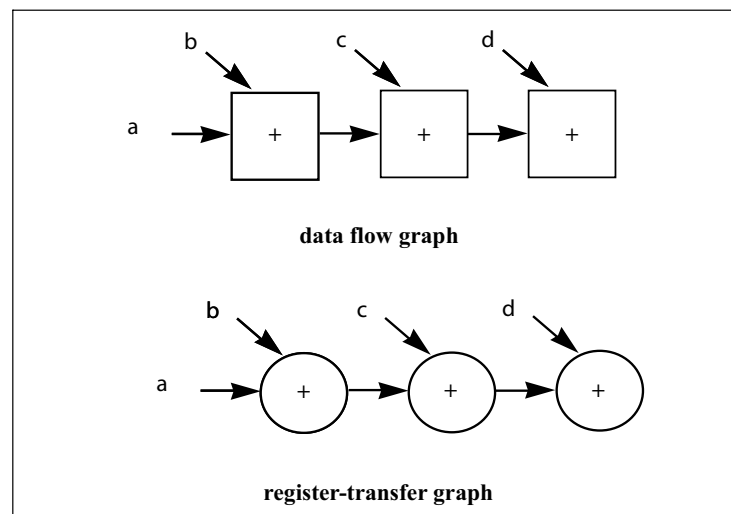

*data vs. control cost*


We can save hardware for the data operators at the cost of adding hardware for memory, sequencing, and multiplexing. The result is our canonical data path-plus-controller design. The data path includes registers, function units, and multiplexers that select the inputs for those registers and function units. The controller sends control signals to the data path on each cycle to select multiplexer inputs, set operations for multi-function units, and to tell registers when to load. We have already seen how to design the data path and controller for an ASM chart, which has fixed scheduling. The next example shows how to schedule and bind a data flow graph to construct a data path-controller machine.

**Example 8-2**  
**From data flow to**  
**data path-**  
**controller**


We will use the data flow graph of Example 8-1. Assume that we have enough chip area to put one multiplier, one adder, and one subtractor in the data path. We have been vague so far about where primary inputs come from and where primary output values go. The simplest assumption for purposes of this example is that primary inputs and outputs are on pins and that their values are present at those pins whenever necessary. In practice, we often need to temporarily store input and output values in registers, but we can decide how to add that hardware after completing the basic data path-controller design.

We can design a schedule of operations for the operations specified in the data flow graph by drawing cut lines through the data flow—each line cuts a set of edges that, when removed from the data flow graph, completely separate the primary inputs and primary outputs. For the schedule to be executable on our data path, no more than one multiplication and one addition or subtraction can be performed per clock cycle.

 Here is one schedule that satisfies those criteria:



 All the operations between two cut lines are performed on the same clock cycle. The next step is to bind variables to registers. Values must be stored in registers between clock cycles; we must add a register to store each value whose data flow edge crosses a cut. The simplest binding is one register per cut edge:




But, as with data path operators, one-to-one binding wastes area because not all values must be stored at the same time. In this graph, we can overwrite  $x_1$ 's register with  $x_2$ 's value since both are not needed at the same time. We can also share the three additions over one adder.

Now that we have scheduled operations, bound data operations to data function units, and allocated values to registers, we can deduce the multiplexers required and complete the data path design. The subtractor and multiplier each have their own unit, so their inputs won't require multiplexers. The adder requires multiplexers on each of its inputs, as does the register shared by  $x_1$  and  $x_2$ . For each input to a shared function unit or register, we enumerate all the signals that feed the corresponding

input on the operator; all of those signals go into a multiplexer for that input. For example, the left-hand inputs to the adder are  $a$  and the output of the  $x_1/x_2$  register. Imagine laying all the addition operators in the registered data flow graph on top of each other, with the input lines for the addition stretched to follow the operator. All the input lines that flow to the same point at the stacked-up additions require a multiplexer to make sure that exactly one value gets to that input at any given time.


The final data path looks like this:

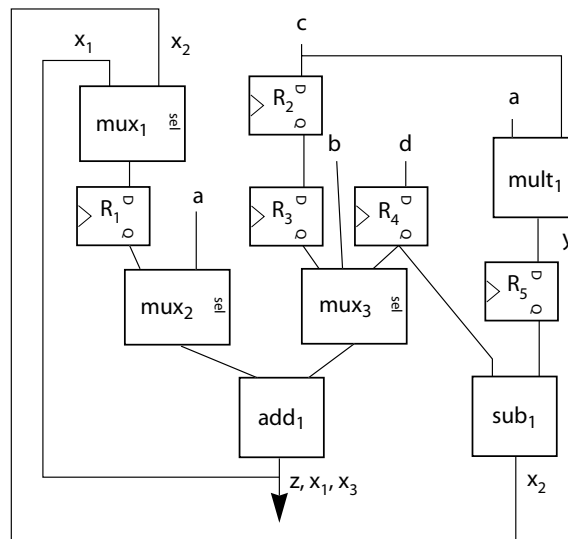

Note that when an input is used on two different cycles, we must add registers to save the value until the last cycle on which it is needed.

Now that we have the data path, we can build a controller that repeatedly executes the basic block. The state transition graph has a single cycle, with each transition executing one cycle's operation. The controller requires no inputs, since it makes no data-dependent branches. Its outputs provide the proper control values to the data path's multiplexers and function units at each step.

The controller looks like this:

 

Once we wire together the data path and controller, the implementation is complete.

#### *alternative implementations*

In the last example, we made a number of arbitrary choices about when operations would occur and how much hardware was available. The example was designed to show only how to construct a machine that implements a data flow graph, but in fact, the choices for scheduling—deciding when to execute an operation—and binding—deciding which hardware unit should store a value or execute an operation—are the critical steps in the design process. Now that we understand the relationship between a data flow graph and a data path-controller machine, we need to study what makes one data path-controller implementation better than another.

#### *scheduling and binding interact*

Obviously, scheduling and binding decisions depend on each other. The choice of a schedule limits our binding options; but we can determine which schedule requires the least hardware only after binding. We need to separate the two decisions as much as possible to make the design task manageable, but we must keep in mind that scheduling and binding depend on each other.

#### *implementation costs*

To a first approximation, scheduling determines time cost, while binding determines area cost. Of course, the picture is more complex than that: binding helps determine cycle time, while scheduling adds area for multiplexers, registers, etc. But we always evaluate the quality of a schedule by its ultimate hardware costs:

- **Area.** Area of the data path-controller machine depends on the amount of data operators saved by sharing vs. the hardware required for multiplexing, storage, and control.

- **Delay.** The time required to compute the basic block's functions depends on the cycle time and the number of cycles required. After the easy victories are won by obvious data hardware sharing, we can generally reduce area only by increasing delay—performing data operations sequentially on fewer function units.
- **Power.** The power consumption of the system can be greatly affected by scheduling and allocation, as we will see in Section 8.6.

*scheduling*


There are many possible schedules that satisfy the constraints in a data flow graph. Figure 8-44 shows how to find two simple schedules. In this example we assume that we can perform as many additions as possible in parallel but no more than one addition in series per cycle—**chained** additions stretch the clock period. The **as-soon-as-possible** (ASAP) schedule is generated by a breadth-first search from the data flow sources to the sinks: assign the source nodes time 0; follow each edge out to the next rank of nodes, assigning each node's time as one greater than the previous rank's; if there is more than one path to a node, assign its time as the latest time along any path. The simplest way to generate the **as-late-as-possible** (ALAP) schedule is to work backward from the sinks, assigning negative times (so that the nodes just before the sinks have time -1, etc.), then after all nodes have been scheduled, adjust the times of all nodes to be positive by subtracting the most negative time for any node to the value of each node. The ASAP and ALAP schedules often do not give the minimum hardware cost, but they do show the extreme behaviors of the system.

*critical paths in data flow*


The ASAP and ALAP schedules help us find the critical paths through the data flow graph. Figure 8-45 shows the critical path through our data flow graph—the long chain of additions determines the total time required for the computation, independent of the number of clock cycles used for the computation. As in logic timing, the critical path identifies the operations that determine the minimum amount of time required for the computation. In this case, time is measured in clock cycles.

*cost estimation*

Before we consider more sophisticated scheduling methods, we should reflect on what costs we will use to judge the quality of a schedule. We are fundamentally concerned with area and delay; can we estimate area and delay from the data path-controller machine implied by a schedule without fleshing out the design to layout?

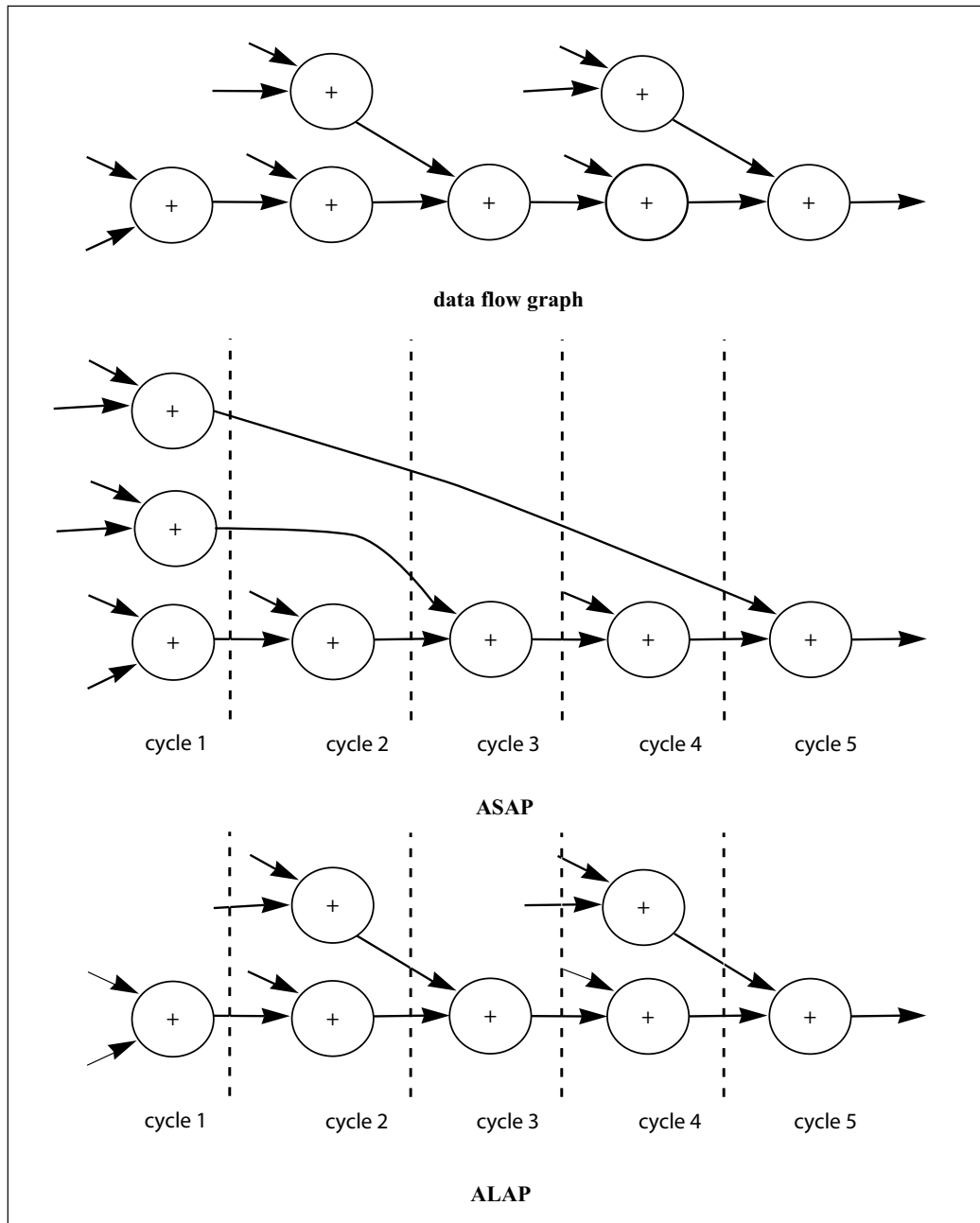

**Figure 8-44** ASAP and ALAP schedules.

 

**Figure 8-45** Critical path of a data flow graph.

Consider area costs first. A binding of data path operators to function units lets us estimate the costs of the data operations themselves. After assigning values to registers, we can also estimate the area cost of data storage. We also compute the amount of logic required for multiplexers. Estimating the controller's area cost is a little harder because area can't be accurately estimated from a state transition graph. But we can roughly estimate the controller's cost from the state transitions, and if we need a more accurate estimate, we can synthesize the controller to logic or, for a final measure, to layout.


Now consider delay costs: both the number of clock cycles required to completely evaluate the data flow graph and the maximum clock rate. We have seen how to measure the number of clock cycles directly from the data flow graph. Estimating cycle time is harder because some of the data path components are not directly represented in the data flow graph.

One subtle but important problem is illustrated by Figure 8-46: the delay through a chain of adders (or other arithmetic components) is not additive. The simplest delay estimate from the data flow graph is to assign a delay to each operator and sum all the delays along a path in each clock cycle. But, as the figure shows, the critical path through a chain of two adders does not flow through the complete carry chain of both adders—it goes through all of the first adder but only the most significant bit of the second adder. The simple additive model for delay in data flow graphs is wildly pessimistic for adders of reasonable size. For accurate estimates, we need to trace delays through the data path bit by bit.

If you are worried about delay, multiplexers added for resource sharing should concern you. The delay through a multiplexer can be significant, especially if the multiplexer has a large number of data inputs.



**Figure 8-46** Delay through chained adders is not additive.

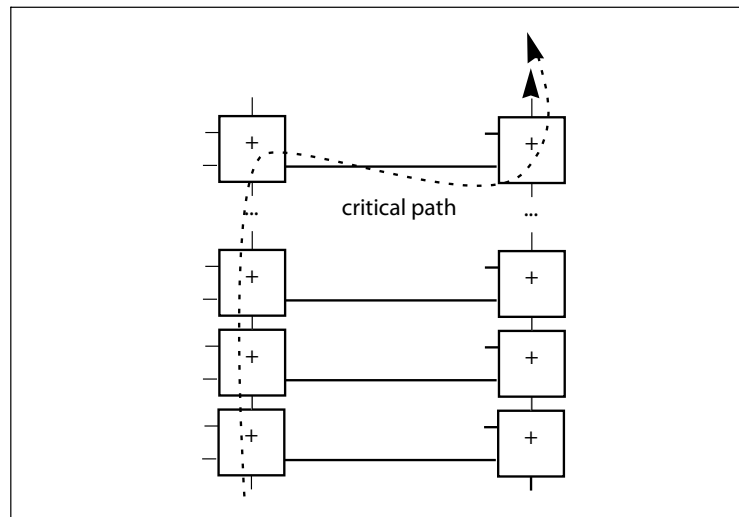

### 8.5.3 Control

#### *control optimization techniques*


One important reason to separate control from data is that arithmetic-rich and control-rich machines must be optimized using very different techniques to get good results—while optimization of arithmetic machines concentrates on the carry chain, the optimization of control requires identifying Boolean simplification opportunities within and between transitions. We typically specify the controller as a state transition graph, though we may use specialized machines, such as counters, to implement the control.

In Chapter 5 we studied how to design a logic implementation of an FSM given a state transition graph. The high-level synthesis problem for control is one step more abstract—we must design the state transition graph which executes the desired algorithm. Consider the simple example of Figure 8-47. The two controllers are clearly not equivalent in the automata-theoretic sense: we can easily find one input sequence that gives different output sequences on the two machines, since the two machines don't even use the same number of cycles to compute the two additions. But even though the two controllers are not sequentially equivalent, they both satisfy the behavior specification.

#### *evaluating controllers*

How do we judge the quality of a controller that implements the control section of a program? That, of course, depends on our requirements. As usual, we are concerned with the area and delay of the FSM. The behavior specification may give us additional constraints on the number of

**Figure 8-47** How the controller changes with the data path schedule.

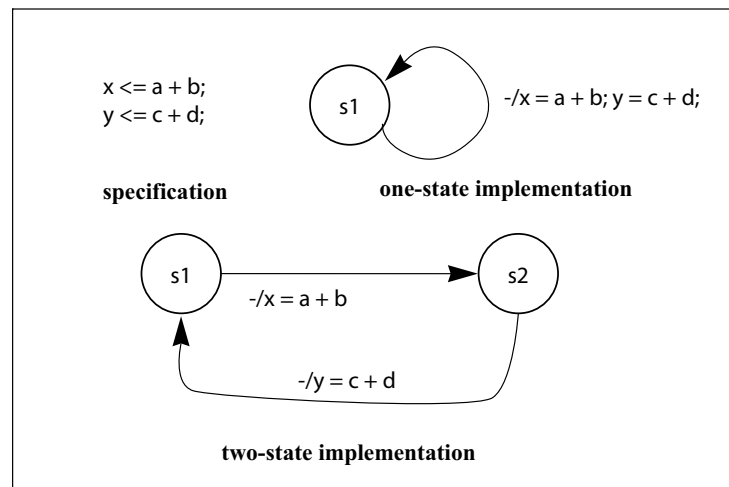

cycles between actions in the program. We may have to satisfy strict sequencing requirements—when reading a random RAM, for example, we supply the address on one clock cycle and read the data at that location exactly one clock cycle later. We often want to minimize the number of cycles required to perform a sequence of operations—the number of cycles between reading a value and writing the computed result, for instance. To compute a result in the minimum number of cycles, we must perform as many operations as possible on each clock cycle. That requires both scheduling operations to take best advantage of the data path, as we saw in the last section; it also requires finding parallelism within the control operations themselves.


#### *generating a controller*

For now we will assume that the data path is given; in the next section we will look at how to choose the best trade-off between controller and data path requirements. The construction of a controller to execute a behavior specification proceeds as follows:

- Each statement in the behavior model is annotated with data path signals: arithmetic operations may require operation codes; multiplexers require selection signals; registers require load signals.
- Data dependencies are identified within each basic block.
- In addition, **control dependencies** are identified across basic blocks—a statement that is executed in only one branch of a control statement must be executed between the first and last states of that conditionally executed basic block. If the same statement appears in every branch, it is not dependent on the control signal and can be moved outside the control statement.

- External scheduling constraints, which reflect the requirements of the other machines to which this one will be connected, are added. External scheduling constraints are those that cannot be determined by looking at the behavior specification itself but that are required when the machine is connected to its intended working environment.
- Each program statement is scheduled—assigned an execution clock cycle that satisfies all the data and control dependencies.
- The controller’s state transition graph can be constructed once the schedule is known.

**Figure 8-48** Constructing a controller from a program.

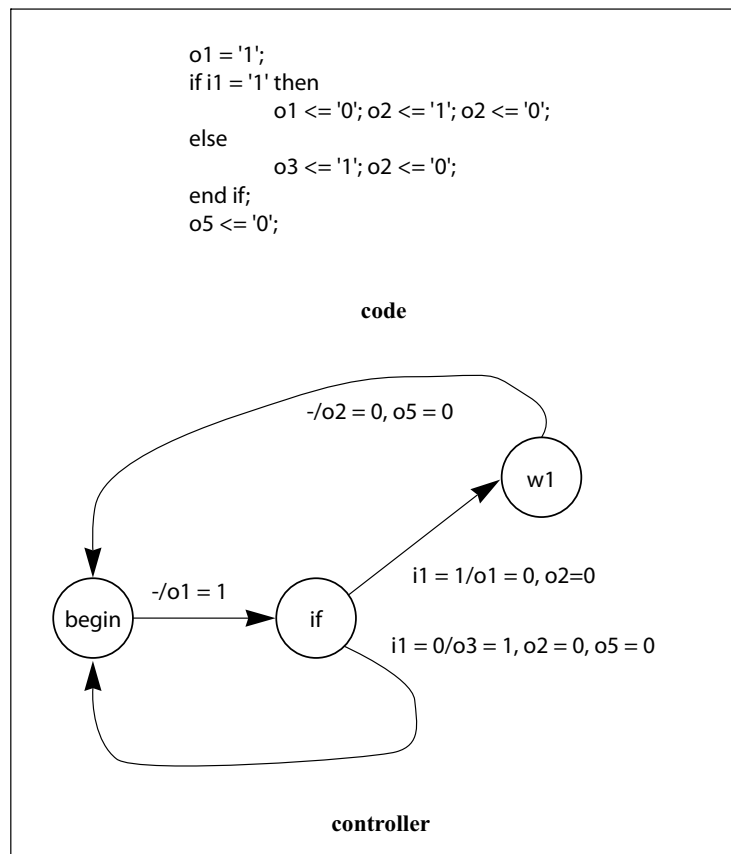


*finding parallelism*

Figure 8-48 shows how some opportunities for parallelism may be hidden by the way the program is written. The statements `o1 <= '1'` and `o5 <= '0'` are executed outside the if statement and, since they do not have any data dependencies, can be executed in any order. (If, however, one

of the if branches assigned to o5, the o5 <= '0' assignment could not be performed until after the if was completed.) The assignment o2 <= '0' occurs within *both* branches of the if statement and data dependencies do not tie it down relative to other statements in the branches. We can therefore pull out the assignment and execute a single o2 <= '0' before or after the if. If a statement must be executed within a given branch to maintain correct behavior, we say that statement is control-dependent on the branch.

**Figure 8-49**  
Rewriting a  
behavior in  
terms of  
controller  
operations.

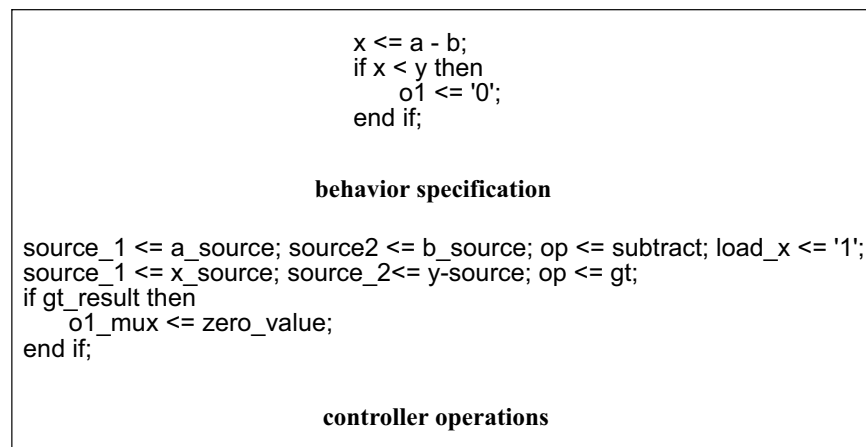


*matching controller  
to data path*

If we want to design a controller for a particular data path, two complications are introduced. First, we must massage the behavior specification to partition actions between the controller and data path. A statement in the behavior may contain both data and control operations; it can be rewritten in terms of controller inputs and outputs that imply the required operations. Figure 8-49 gives a simple example. The first assignment statement is replaced by all the signals required to perform the operation in the data path: selecting the sources for the ALU's operands, setting the operation code, and directing the result to the proper register. The condition check in the if statement is implemented by an ALU operation without a store. We must also add constraints to ensure that these sets of operations are all executed in the same cycle. (Unfortunately, such constraints are hard to write in VHDL and are usually captured outside the behavior model.) Those constraints are external because they are imposed by the data path—the data path cannot, for example, perform an ALU operation on one cycle and store the result in a temporary register for permanent storage on a later cycle. We also need constraints to ensure that the ALU operation for the assignment is

performed on the same cycle as the test of the result, or the comparison result will be lost.

The second complication is ensuring that the controller properly uses the data path's resources. If we have one ALU at our disposal, the controller can't perform two ALU operations in one cycle. The resource constraints are reflected in the controller's pins—a one-ALU data path will have only one set of ALU control signals. We may, however, have to try different sequences of data path operations to find a legal implementation with both a good controller and the desired data path.

**Figure 8-50** Breaking a pair of tests into distributed control.

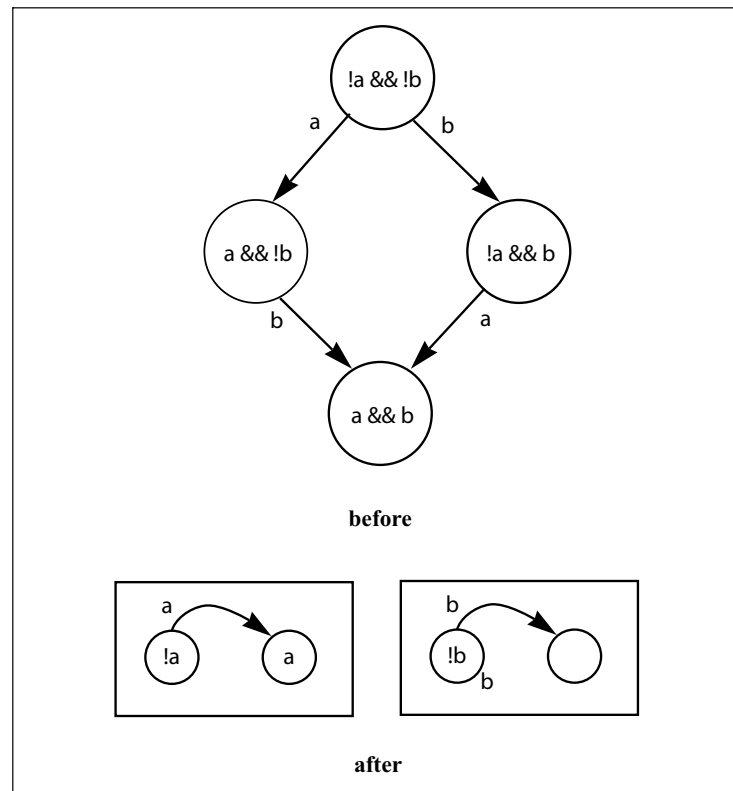


*controller implementation*

Finally, a word about controller implementation styles. You may have learned to implement a controller as either a **hardwired machine** or a **microcoded machine**. As shown in Figure 8-51, a hardwired controller is specified directly as a state transition graph, while a microcoded controller is designed as a microcode memory with a microprogram counter. (The microcoded controller also requires control logic to load the

$\mu$ PC for branches.) It is important to remember that these are implementation styles, not different schedules. The hardwired and microcoded controllers for a given design are equivalent in the automata-theoretic sense—we can't tell which is used to implement our system by watching only its I/O behavior. While one may be faster, smaller, or easier to modify than another for a given application, changing from one style to another doesn't change the scheduling of control operations in the controller. You should first use control scheduling methods to design the controller's I/O behavior, then choose an implementation style for the machine.

**Figure 8-51** Controller implementation styles.

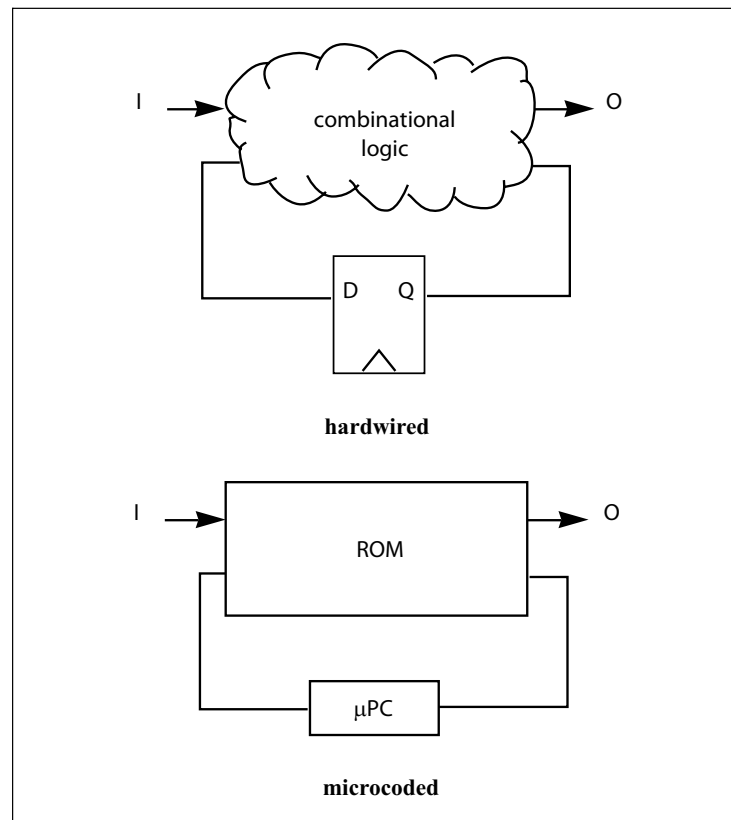


### 8.5.4 Data and Control

*data and control interactions*

So far, we have designed the data path and controller separately. Dividing architecture design into sub-problems makes some issues clearer,

but it doesn't always give the best designs. We must consider interactions between the two to catch problems that can't be seen in either alone. Once we have completed an initial design of the data path and controller individually, we need to plug them together and optimize the complete design.

**Figure 8-52** Adding hardware to reduce the number of clock cycles required for an operation.

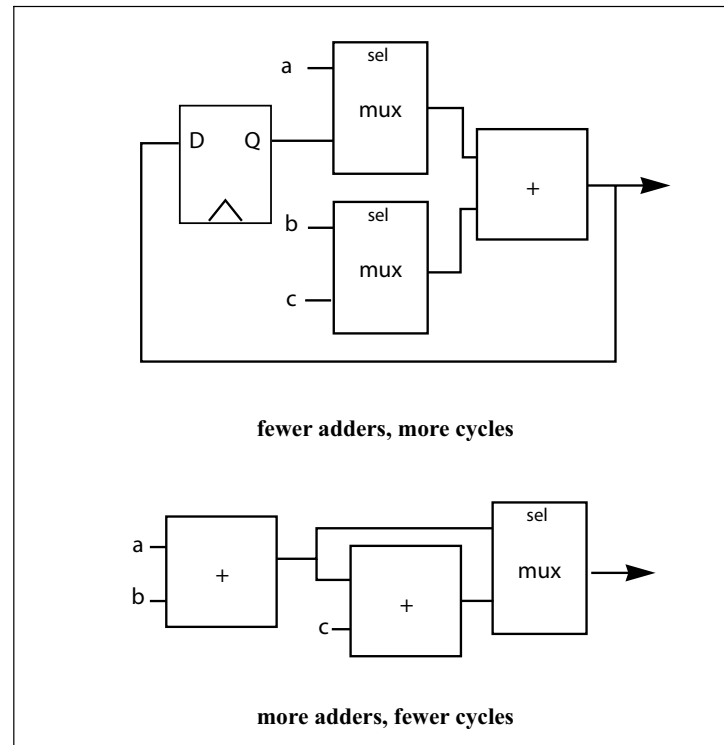


#### *cleaning up the hardware*

The first, obvious step is to eliminate superfluous hardware from the data path. A schedule may have been found for a controller that doesn't require all the hardware supplied by the data path. A more sophisticated step is to add hardware to the data path to reduce the number of cycles required by the controller. In the example of Figure 8-52, the data path has been designed with one adder. The *true* branch of the if can be executed in one cycle if another adder is put into the data path. Of course, the second adder is unused when the false branch is executed. The second adder also increases the system's clock period; that delay penalty must be paid on every cycle, even when the second adder is not used. Whether the second adder should be used depends on the relative impor-

tance of speeding up the true branch and the cost in both area and delay of the second adder.

**Figure 8-53** Delay through a data path controller system.

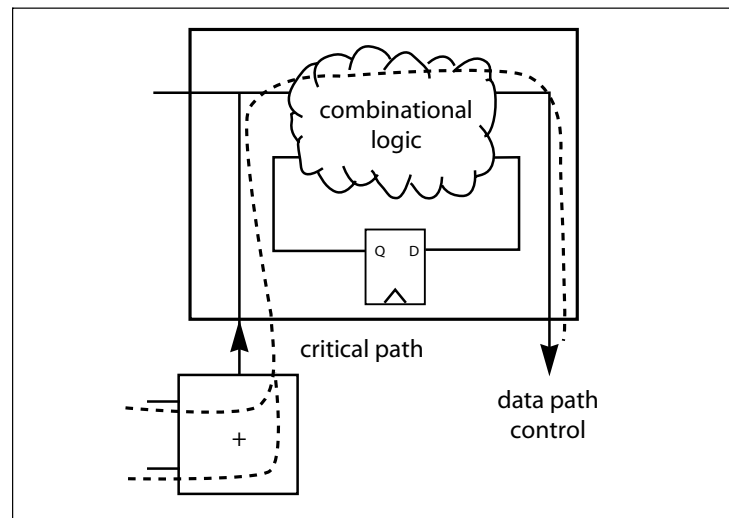

#### *cycle time optimization*

Another important optimization is adjusting the cycle time through the combined system. Even though the delay through each subsystem is acceptable, the critical path through the combination may make the cycle time too long. Overly long critical paths are usually caused by computations that use the result of a data path operation to make a control decision, or by control decisions that activate a long data path operation. In the example of Figure 8-53, the critical path goes through the carry chain of the ALU and into the next-state logic of the controller. We can speed up the clock by distributing this computation over two cycles: one cycle to compute the data path value, at which point the result is stored in a memory element; and a second cycle to make the control decision and execute it in the data path. One way to view the effect of this pipelining is that it moves the control decision ahead one cycle, increasing the number of cycles required to compute the behavior. However, it may not always be necessary to add cycles—if the adder is free, rather than move the control decision forward, we can move the addition back one cycle, so that the result is ready when required by the controller.



### 8.5.5 Design Methodology

High-level synthesis allows designers to concentrate on the architectural design, rather than spend a great deal of time mapping the architecture to logic or layout. High-level synthesis can produce useful productivity gains when used to automate the transformation of the architecture to register-transfer form, but high-level synthesis can aid productivity in other ways, as described in the next example.

---

#### **Example 8-3** **The IBM High-Level Synthesis System**

The IBM High-Level Synthesis System (HIS) [Ber95] was one of the first industrial high-level synthesis systems. It accepts design descriptions in VHDL or Verilog and produces register-transfer designs that can be input to the IBM BooleDozer logic synthesis system.

The main steps followed by HIS during synthesis include:

- **Data model generation.** Control flow and data flow graphs are generated from the input high-level description.
- **Data flow analysis.** Variable lifetimes are determined, explicit clocking constraints are analyzed, etc.
- **Scheduling and allocation.** The operations in the behavior are scheduled, registers and multiplexers are allocated, control signals are generated, etc.
- **Data path optimizations.** Data path optimizations try to efficiently share resources.
- **Control optimizations.** Behavioral don't-care conditions, state assignment, etc.

One major use of HIS is as a front-end to logic synthesis which allows designers to directly manipulate the architecture. Considerable time can be saved when changes to an architecture are made (as is common), since the designer need not translate the architectural changes to logic. However, high-level synthesis has also seen several other uses: as a fast synthesizer for designs input to logic emulation machines; as a fast synthesizer for verification systems; as a fast mapper for cycle-based simulation; and for early estimation and analysis. In all these cases, the ability to generate a design from a higher-level description saves time otherwise required by the designer to map the architecture into logic.

---

## 8.6 Architectures for Low Power

A variety of architectural techniques can be used to reduce and manage power consumption. Many of these techniques take advantage of the varying nature of the data and workload being processed by temporarily reducing clock frequency, putting gates on standby, *etc.* We can use parallelism to reduce the operating frequency and voltage of the system.

*power, thermal, and reliability*

As we saw in Section 2.6.2, Section 3.3.4, Section 3.7.1, and Section 7.3.1, high temperatures and thermal effects can cause severe reliability problems. High temperatures and temperature gradients can cause delays to change, which may cause transient failures. High temperatures can also cause chips to permanently fail. Low-power design therefore becomes a critical concern because of its dual implications: the high cost of high energy and power consumption itself, and the thermal barriers to reliability.

**Power controllers** are in charge of **dynamic power management** on a chip or a section of the chip. Power controllers are common in modern microprocessors and large ASICs. A chip may have more than one power controller, each managing a different part of the chip. These power controllers are generally controlled by software.

**Figure 8-54** A power controller and its connections to the rest of the system.

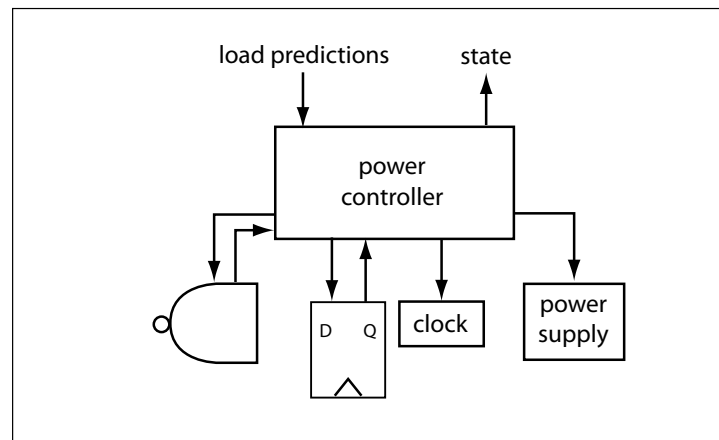


Figure 8-54 shows a generic model of a power controller. The controller itself is an FSM. The power controller's interface to the rest of the chip accepts inputs, which may tell the power controller when it may power down and for how long. It also includes outputs that tell the rest of the system when the logic is useful. On the other side of the unit, the power

controller sends commands to a variety of units: the clock generator, registers, power modes in combinational logic, or to the power supply. It may also take inputs, either from the power-managed logic itself or from units such as the power supply.

*power minimization  
through control*

Implementing a power-down mode requires implementing three major changes to the system architecture:

- conditioning the clock in the powered-down section by a power-down control signal;
- adding a state to the affected section's control that corresponds to the power-down mode;
- further modifying the control logic to ensure that the power-down and power-up operations do not corrupt the state of the powered-down section or the state of any other section of the machine.

*initialization*

The logic being powered down may need to be reinitialized before it can be used again. Powered-down logic may lose state because it contains dynamic latches; the logic's state may become desynchronized with that of the surrounding logic; or for many other reasons, the existing state of the powered-down logic may not be immediately useful. In such cases, the power controller must manage the initialization process. A handshake protocol can be used to tell the rest of the system when the unit is available. In complex machines, initialization may take several cycles.

In the rest of this section, we will look at several different power reduction techniques that can be controlled by a power controller: gate-level methods, data latching, clock gating, and architecture-driven voltage scaling.

### 8.6.1 Gate Power Control

*gate and power supply*

Depending on the type of gate used, its power consumption may be controlled in several ways, as we saw in Section 3.6. The gate's power supply voltage may be controlled directly, in which case the power controller would talk to the power supply module. (The design of multiple-voltage power supplies is a subject beyond the scope of this book.) A related technique is changing the substrate voltage in a region, as is done for VTCMOS gates; this requires fabrication support, such as triple wells. Some gates, such as MTCMOS, are controlled by a direct input.

### 8.6.2 Data Latching

We saw in Section 4.5 and Section 5.7 that glitch reduction reduces power consumption by eliminating unnecessary circuit activity. If we will not use the output of a unit, then we should not allow its inputs to change, which would cause unnecessary transitions to flow through the unit.

*new and existing latches*

We can use conditional clocks on existing latches to hold data values that are not used. We can also add latches to units with combinational inputs; of course, that requires adjusting the overall clocking to ensure that values arrive at the proper times.

### 8.6.3 Clock Gating

*conditional clocks*

The conditional clock for the power-down mode must be designed with all the caveats applied to any conditional clock—the conditioning must meet skew and edge slope requirements for the clocking system. Static or quasi-static memory elements must be used in the powered-down section for any state that must be preserved during power-down (it may be possible to regenerate some state after power-up in some situations).

*mode changes*

The power-down and power-up control operations must be devised with particular care. Not only must they put the powered-down section in the proper state, they must not generate any signals that cause the improper operation of other sections of the chip, for example by erroneously sending a *clear* signal to another unit. Power-down and power-up sequences must also be designed to keep transient current requirements to acceptable levels—in many cases, the system state must be modified over several cycles to avoid generating a large current spike.

### 8.6.4 Architecture-Driven Voltage Scaling


*power and supply voltage*

As was noted in Section 3.3.5, the power consumption of static CMOS gates varies with the square of the power supply voltage. The delay of a gate does not decrease as quickly as power consumption. **Architecture-driven voltage scaling** [Cha92] takes advantage of this fact by adding parallelism to the architecture to make up for the slower gates produced by voltage scaling. Even though the parallel logic adds power, the transformation still results in net power savings.

*trading parallelism  
for clock rate*

This effect can be understood using the generic register-transfer design of Figure 8-55. A basic architecture would evaluate its inputs (clocked into registers in this case) every clock cycle using its function unit. If we

**Figure 8-55** Increasing parallelism to counteract scaled power supply voltage.

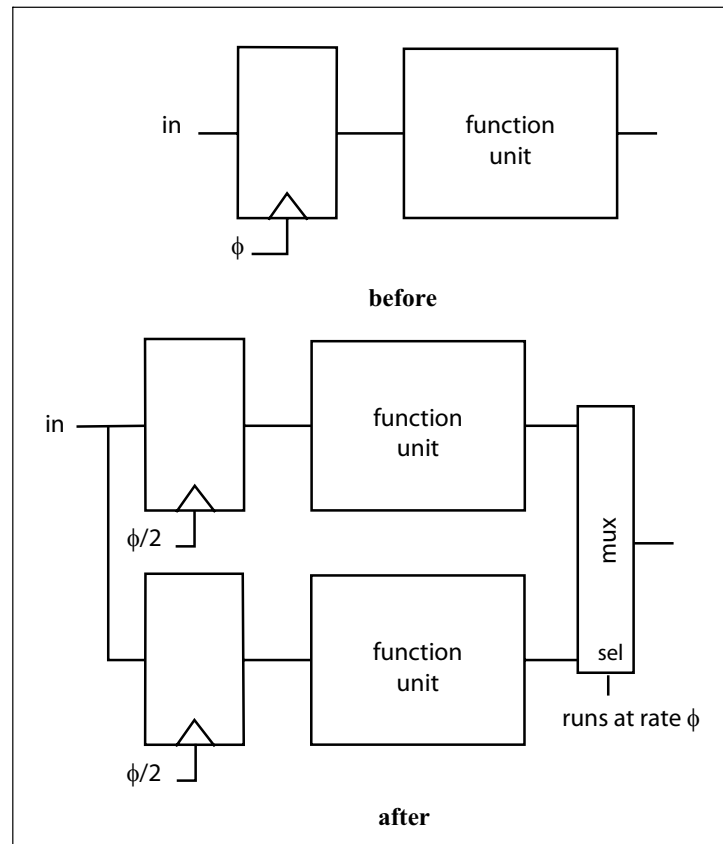

slow down the operating frequency of the function unit by half, we can still generate outputs at the same rate by introducing a second function unit in parallel. Each unit gets alternate inputs and is responsible for generating alternate outputs. Note that the effective operation rate of the system is different in different components: the outputs are still generated at the original clock rate while the individual function units running at half that rate. Parallelism does incur overhead, namely the extra capacitance caused by the routing to/from the function units and the multiplexer. This overhead is, however, usually small compared to the savings accrued by voltage scaling.

Parallelism can also be introduced by pipelining. If the logic has relatively little feedback and so is amenable to pipelining, this technique

will generally result in less overhead capacitance than parallel-multiplexed function units.

*power improvement*

The power improvement over a reference power supply voltage  $V_{ref}$  can be written as [Cha92]:

$$P_n(n) = \left[ 1 + \frac{C_i(n)}{nC_{ref}} + \frac{C_x(n)}{C_{ref}} \right] \left( \frac{V}{V_{ref}} \right), \quad (\text{EQ 8-7})$$

where  $n$  is the number of parallel function units,  $V$  is the new power supply voltage,  $C_{ref}$  is the reference capacitance of the original function unit,  $C_i$  is the capacitance due to interprocessor communication logic, and  $C_x$  is the capacitance due to the input/output multiplexing system. Both  $C_i$  and  $C_x$  are functions of the number of parallel function units.

### 8.6.5 Dynamic Voltage and Frequency Scaling

**Dynamic voltage and frequency scaling (DVFS)** [Wei94] was developed to control the power consumption of microprocessors. Like architecture-driven voltage scaling, DVFS relies on the fact that performance varies as  $V$  while power consumption varies as  $V^2$ . However, unlike architecture-driven voltage scaling, DVFS is a dynamic technique—both the clock frequency and power consumption vary during operation.

*dynamic workloads*

DVFS relies on the fact that microprocessors do not always have to run at full speed in order to finish all their tasks. If the microprocessor's workload does not require all available CPU performance, then we can slow down the microprocessor to the lowest available performance level that meets the current demand.


*DVFS controller*

The power controller for DVFS controls the microprocessor power consumption through a combination of clock frequency and power supply changes. The power controller needs a simple algorithm to determine the proper clock frequency and power supply settings from a load estimate. A software interface allows the operating system or other programs to tell the power controller the required performance. This software interface updates a register that is visible to the power controller; that register is the interface between the system-level load estimate and the commands to the clock generator and power supply.

## 8.7 GALS Systems

As chips grow larger, it becomes harder to distribute the clock reliably to all parts of the chip. One architectural solution to this problem is **globally asynchronous, locally synchronous (GALS)** design, which relaxes the strict synchronous assumptions at several boundaries within the chip.

**Figure 8-56** Clock domains and interfaces in a GALS system.

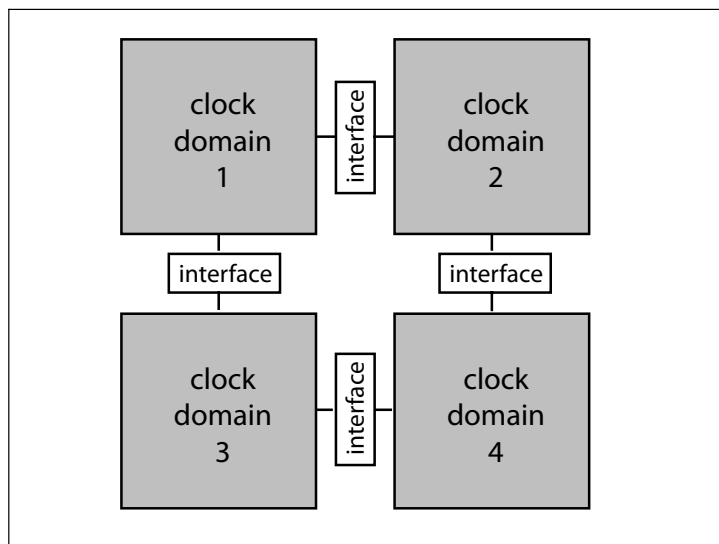

*clock domains*

As illustrated in Figure 8-56, a GALS system is divided into several different **clock domains**. Each clock domain operates synchronously. However, the different clock domains are not synchronized relative to each other. As a result, communication between domains must be mediated by an interface that adjusts for the differences in timing.

*GALS styles*

There are several different ways to organize the timing in a GALS system, each with its own interface. Teehan *et al.* [Tee07] identified three major styles of GALS systems:

- **Pausable clocks** use special clock generators in each domain that can be paused. When one module wants to communicate with another, the receiver pauses its clock until after the data arrives. Because the data has settled by the time the clock is restarted, the transfer has been synchronized.

- **Asynchronous interfaces** assume no relationship between the clocks and the clocks do not stop. Specially-designed synchronizer circuits capture the data at the transmitter/receiver interface. These asynchronous circuits are very tricky to design; Teehan *et al.* caution that Spice simulations may not be accurate enough to verify the proper operation of a synchronizer; they suggest that these circuits are best acquired as verified IP blocks.
- **Loosely synchronous interfaces** couple blocks with some bounds on their relative frequencies. These loose timing relationships keep us from needing to design fully asynchronous interfaces. Messerschmitt [Mes90] defined three types of loosely synchronous systems: **mesochronous** blocks operate at exactly the same frequency with an unknown but stable phase difference; **pleisochronous** senders and receivers operate at the same average frequencies but with some small allowable drift; **heterochronous** blocks operate at different average frequencies.

GALS systems have two advantages as means of avoiding global clock distribution problems. First, they allow us to use standard synchronous IP in each clock domain. Second, they reduce the interface problem to relatively small blocks that can usually be treated as IP. In contrast, clock distribution networks must be designed for each chip, though tools can help with this task.

---

## 8.8 Architecture Testing

---

Making sure an architecture is testable is a balancing act, just as is making sure that it runs fast enough. The simplest way to make a system run fast usually requires too much hardware, so we look for judicious ways to reuse hardware without compromising performance. Similarly, brute force application of extra testing hardware usually makes the system both too big and too slow. Luckily, we can usually make the system more easily testable with relatively simple fixes.


*partial scan*

We studied LSSD design in Section 5.9. Scan latches add both area and delay. We can reduce the cost of scan design by using **partial scan**—making only some of the memory elements in the system scannable. Figure 8-57 shows why scan latches are more useful in some locations than others. The value of a latch that is in the middle of the pipeline is guaranteed to be available at the primary outputs after  $n$  clock cycles. The value at the pins will be determined by the combina-

---

---



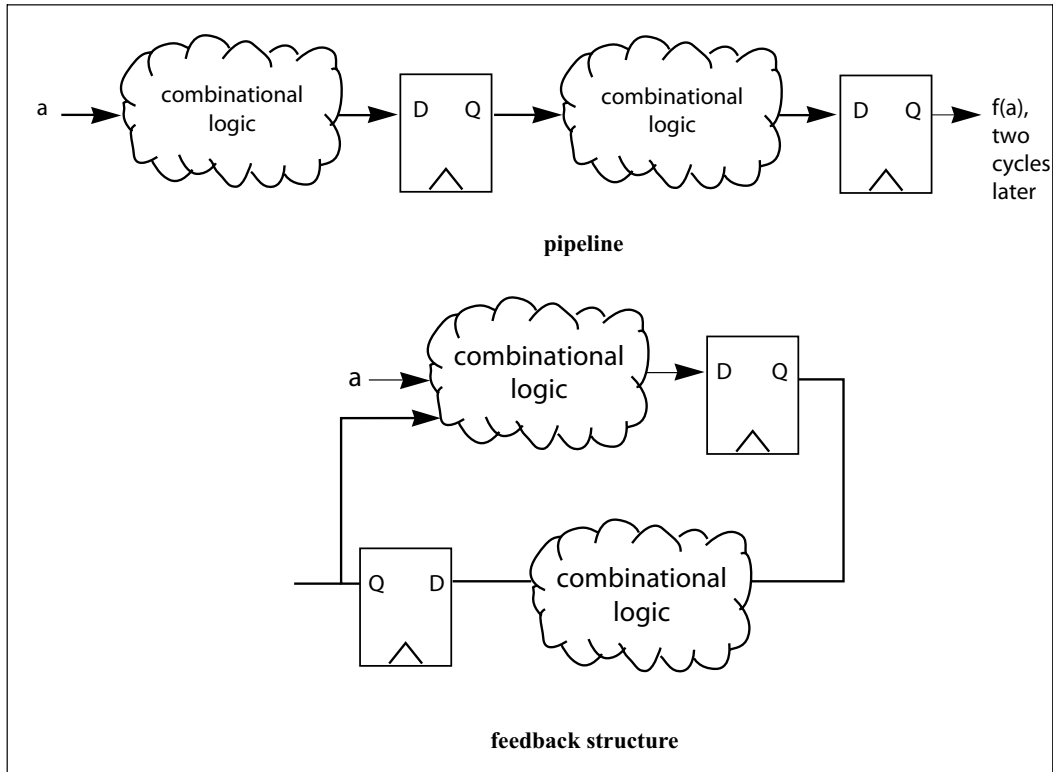


**Figure 8-57** Some scan latches are more useful than others.

tional logic between the latch and the pin, but we can reverse-engineer the latch’s value (perhaps with some ambiguity caused by the combinational functions performed). The situation in a general sequential machine, like the FSM shown, is more complex. Some latch values may be immediately accessible, while others may not show their effects at the pins for many cycles. A scan latch for a value that can be directly viewed is much less useful than a scan latch for the value that recirculates before becoming visible.

*sequential depth and testability*

Registers become harder to test as their distance from primary inputs or outputs increases [Fri76]. We can identify high-payoff locations for scan latches by building a **register graph** [Che89], as shown in Figure 8-58. Nodes in the graph represent memory elements; an edge is drawn between two nodes if there is any combinational path between the two

**Figure 8-58** The register graph.

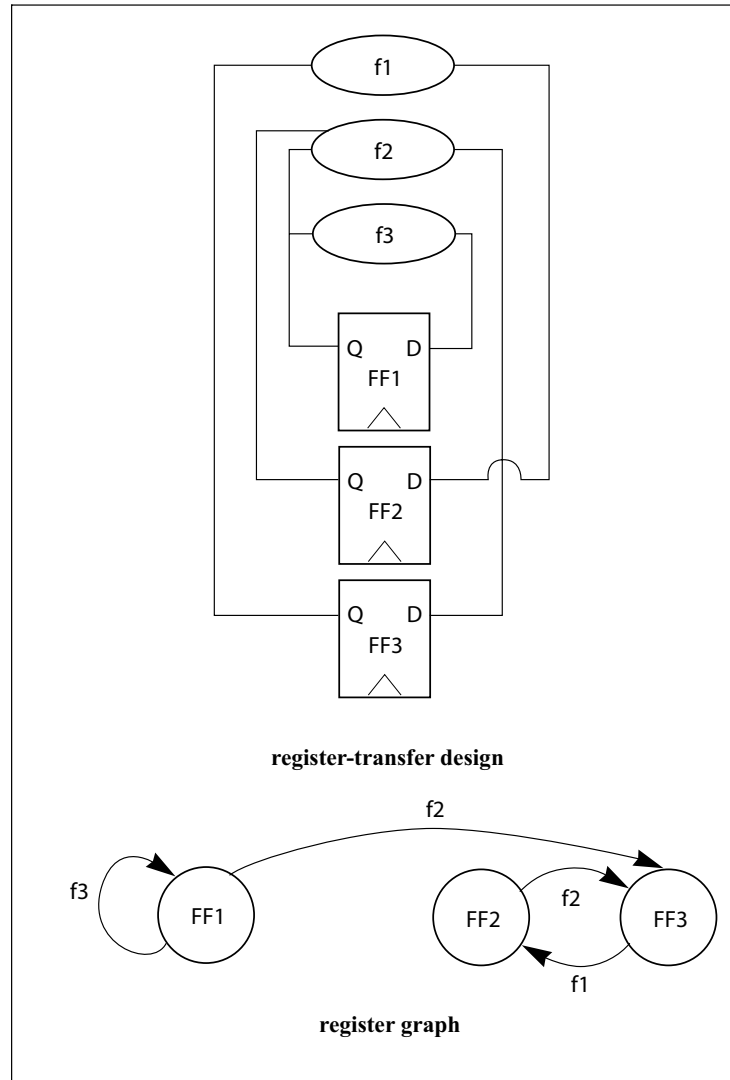


memory elements. The shortest distance to a given node from any node that is a primary input is called the **sequential depth** of that node; the graph's sequential depth is the largest sequential depth of any of its nodes. Cycles in the graph show feedback paths for state—memory elements in a cycle compute their value at least partially from other internal information, rather than from the primary inputs. Self-loops—edges that



A **linear feedback shift register** (LFSR) can be used to generate a pseudo-random sequence. One possible structure of an LFSR is shown in Figure 8-59. The memory elements hold the current pseudo-random value; XORs between stages compute the next value. Not all of the dotted connections are actually made—by making different feedback connections, we can generate different pseudo-random sequences. (If a feedback connection is not made, the corresponding XOR is not necessary.) An LFSR can also be used to store and compress a sequence of binary words, a technique commonly known as **signature analysis**. (Signature analysis was originally developed by Hewlett-Packard for printed circuit board testing.) If we want to record a sequence of values, we can add those values as additional inputs to the XORs, causing them to be added into the pseudo-random sequence. This scheme loses information—there may be several sequences of inputs that produce the same value in the LFSR. However, a relatively small LFSR can give a very low probability of aliasing, making the LFSR a very good compression scheme.

**Figure 8-60** A logic block configured for built-in self-test.

 

The testing configuration of a built-in self-test system is shown in Figure 8-60. One LFSR is used to generate inputs for the logic to be tested while another LFSR is used as a signature register. A multiplexer is used to switch between normal and test modes by switching the circuit under test's inputs between the primary inputs and the LFSR. A fault simulator is used to simulate the circuit under test's response to the sequence generated by the input LFSR. The signature register's value can either be compared against a single signature that indicates correct operation or the register can be made available at the chip's pins.

---

## 8.9 IP Components

---

### *sources of IP*

A wide range of IP components are useful when designing an SoC architecture. These components may be come from within your company, from the foundry, or from outside sources. How you acquire the IP will depend on where it comes from.

One useful source of IP is [opencores.org](http://www.opencores.org) (<http://www.opencores.org>). This site is a forum that allows developers of IP modules to post and share their designs. Components range from debug interfaces up through CPUs. The licensing agreement required to use a module is up to the contributor of the module, but most contributors use an open source agreement such as GNU or BSD.

### *selecting IP*

With luck, you will be able to choose between several different IP modules that meet your basic requirements. The final selection of an IP module can be made on some combination of several grounds:

- **Area or performance.** These characteristics must be determined through synthesis; the module's documentation may give sample values.
- **Testability and debugging.** Scan registers or other features may make it easier to test and debug the cell; if your chip uses a particular methodology for testability, you should prefer an IP module whose own testability features are compatible with yours.
- **Cost.** If the module must be paid for, at least different licensing models are used by IP vendors. Fixed-price licenses require an up-front fee that allows you to use the module in a chip design with no further fees. Royalty-based licenses require payments for each chip sold.
- **Software support.** In the case of complex modules, software support, either on the debugging host or on one of the on-chip cores, may make the difference between a usable and an unusable cell.

### *integrating IP into designs*

The IP module has been verified by its designers, but you must verify that it is used properly in your chip. The test vectors for the module may help you generate a set of tests for the module *in situ*. However, your tests should concentrate on debugging the interactions between the module and your logic that connects to the module. These tests will include two types of sequences: values generated by your logic that cause the IP module to generate some output; and values generated by the IP module that cause a reaction in your logic.


---

---

## 8.10 Design Methodologies

The exact sequence of steps you follow to design a chip will vary with your circumstances: what type of chip you are designing; size and performance constraints; the design time allowed; the CAD tools available to you; and many other factors.

**Figure 8-61** A generic integrated circuit design flow.

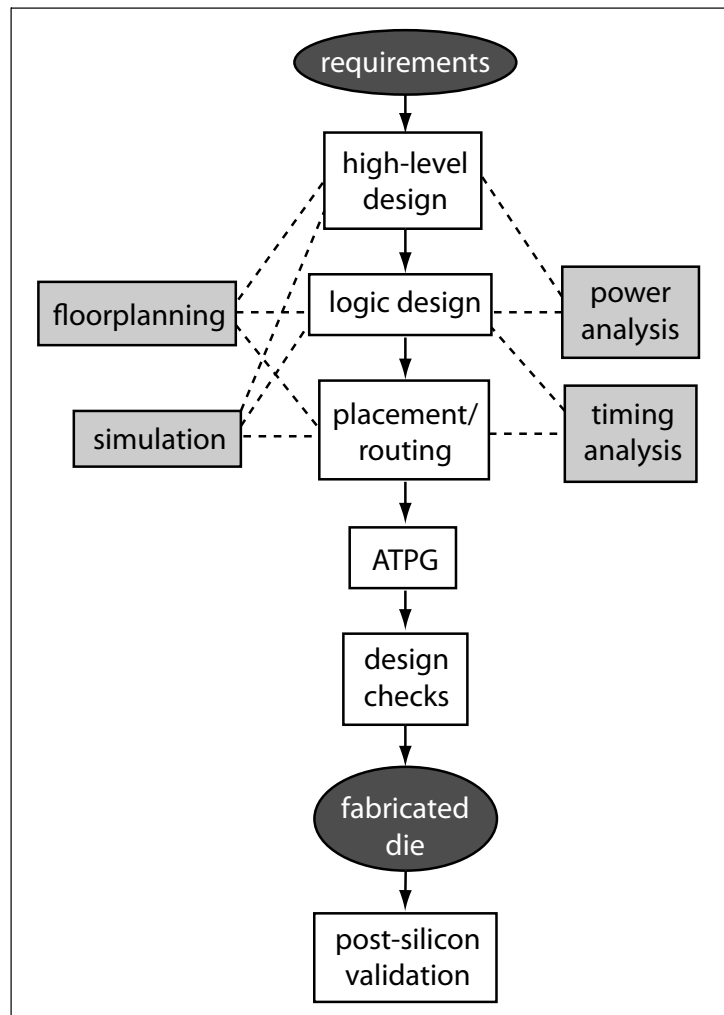

*methodologies and flows*

A **design methodology** is frequently called a **design flow** since the flow of data through the steps in the methodology may be represented in a block diagram. Figure 8-61 shows a generic design flow for VLSI systems. While all design methodologies will vary from this in practice, this flow shows some basic steps that must be considered in almost any design.

*requirements*

The initial **requirements** for a system are often specified in English and may be vague; while many designs are follow-ons to previous designs, any new features must be described in some way that may lead to misunderstandings. Problems in translating the requirements into architectures can and should be caught early to avoid the embarrassment of implementing the wrong chip.

*high-level, logical, physical design*

High-level design may be performed manually or using high-level synthesis tools, but somehow an initial set of functions must be translated into a register-transfer design. Similarly, logic and physical design may be performed by CAD tools, manually, or in some combination.

*testing and verification*

Automatic test pattern generation (ATPG) generates test vectors for manufacturing test. ATPG is, of course, no substitute for the creation of functional test vectors that will be used by simulators to validate the design at all levels of abstraction. Several sorts of design checks, including design-rule checking, electrical checking, and timing analysis are all important at the end of the design process to be sure that no fundamental errors have been inadvertently introduced. Once die are returned from manufacturing, they must be evaluated to be sure that the design not only runs at the proper speed, but runs at a range of power supply voltages and other checks that ensure adequate yields. The importance of post-silicon electrical testing will be discussed in Example 8-5.

Figure 8-61 shows several analysis steps connected to synthesis-oriented design steps by dotted lines. Simulation, floorplanning, timing analysis, and power analysis (among other analysis steps) are all important and must be performed at several different levels of abstraction. Early design stages rely on estimates that may be supplied by tools; those estimates must be verified as the design is refined and, if necessary, used to drive the redesign to meet requirements that have been missed.

*the design process*

Let's consider this process in more detail:

- **Architecture.** If a chip is a rework of an existing design—a design shrink, a few added features, etc.—then the architectural design is simple. But when designing something new, a great deal of work is required to transform the requirements into a detailed microarchitec-

ture ready for logic design. Architectural design requires construction of a microarchitectural simulator that is sufficiently detailed to describe the number of clock cycles required for various operations yet fast enough to run a large number of test vectors. A test suite must also be constructed that adequately covers the design space; if the design is a rework of a previous architecture, then the vectors for that system are a starting point that can be augmented with new tests. Architectural design requires extensive debugging for both functionality and performance; errors that are allowed to slip through this phase are much more expensive to fix later in the design process.

- **Logic design and verification.** Logic design may be performed manually or using logic synthesis tools. In either case, the design will probably go through several refinement steps before completion. Initial design verification steps will concentrate on logical correctness and basic timing properties. Once the basic structure of the logic has taken shape, scan registers can be inserted and power consumption can be analyzed. A more detailed set of timing checks can also be performed, including delay, clock skew, and setup/hold times. In extreme cases, perhaps because of a limited number of choices in the gate and register libraries, it may be necessary to make more drastic changes to the logic to correct problems found late in the logic design process.
- **Physical design.** Physical design starts with floorplanning to determine the overall structure of the layout. If the logic was designed in large blocks, it may be necessary to partition those large blocks into smaller pieces at this point. Placement and routing will generate layouts of blocks, or layouts can be designed by hand. Once the layout is complete, the wiring parasitics must be extracted and back-annotated to the logic design. The back-annotated design can then be simulated to verify that layout did not violate any timing constraints. Hopefully, problems can be fixed with minor modifications to the layout but changes to the logic design may be required.
- **Back-end checks.** ATPG must be performed late to ensure that minor design changes did not inadvertently cause testability problems. Similarly, design-rule and electrical checks of the complete layout are an important sanity check to ensure that shorts or opens were not introduced late in design.

*using hard IP*

Making use of hard IP blocks for modules requires some adjustment of the design process. A hard IP block will generally be represented as a blank space by tools during the early physical design stages. The tools have a description of the pins on the IP block so they can route to the



module. The boundary between the hard IP block and the rest of the layout will have to be carefully checked for design rule violations.

*debugging*

Integrated circuits are notoriously hard to debug after fabrication. The few hundred pins on a large chip cover only a tiny fraction of the state contained in the multiple millions of electrical nodes in a large VLSI IC. While it may be possible to deduce the internal behavior of the chip, some errors may be difficult to detect and may also mask other flaws. **Voltage contrast** [Ben95] is a technique for observing the chip's internal behavior using a scanning electron microscope (SEM). The electron beam of the SEM is reflected differently off electrical nodes at high and low voltages; a raster scan of the chip by the SEM results in a picture of the voltages across the chip. Voltage contrast also requires expensive equipment but practitioners have found it very valuable in tracking down certain types of bugs.

*documentation*

One constant through all circumstances is the importance of good design documentation. You should write down your intent, your process, and the result of that process at each step. Documentation is important for both you and the others with whom you work:

- Written descriptions and pictures help you remember what you have done and understand complex relationships in the design. A paper trail also makes the design understandable by others. If you leave the organization while designing a complex chip, leaving only a few scribbled notes on the backs of envelopes and napkins, your colleagues may not be able to reconstruct your work.
- **Design reviews** are very valuable tools for finding bugs early. A design review is a meeting in which the designer presents the design to another group of designers who comment on it. In preparation for review, the designer prepares documentation that describes the component or system being designed: purpose of the unit, high-level design descriptions, detailed designs, procedures used to test the design, etc. During the design review, the audience, led by a review leader, listens to the designer describe this information and comment on it (politely, of course). Many bugs will simply be found by the designer during the course of preparing for the meeting; many others will be identified by the audience. Design reviews also help the various members of a team synchronize—at more than one design review, two members of the same design team have realized that they had very different understandings of the interface between their components.

Even after the chip is done, documentation helps fix problems, answer questions about its behavior, and serves as a starting point for the next-

---

---

*minimize design errors*

generation design. You will find that a little time spent on documentation as you go more than pays for itself in the long run.

One thing to keep in mind is that methodology helps ensure that things aren't overlooked. A large chip is complex with many opportunities for error. Unfortunately, even some small errors can completely disable a chip, causing expensive and frustrating delays. Methodologies are put in place to minimize the chance of error. Each company generally develops its own design methodology based on its experience, including its earlier mistakes. Different methodologies can work equally well so long as they are followed carefully and with an understanding of their intent.

The next three examples give much more specific examples of design flows for three different categories of chip design: ASICs, CPUs, and SoCs.

---

**Example 8-4**  
**Design**  
**methodology**  
**for IBM ASICs**

ASICs are in general designed in a partnership of the ASIC's customer and its manufacturer—the manufacturer handles most design tasks closely tied to manufacturing, while the customer takes care of elements of the design unique to the customer's needs.

The first steps in the IBM ASIC design flow [Eng96] require cooperation between the customer and the manufacturer's design house:

- **Design entry.** Designs are entered in a hardware description language such as VHDL or Verilog. Schematic entry is also supported.
  - **Logic synthesis.** IBM logic synthesis tools are used to map the design into a gate-level design in the IBM cell library. Logic synthesis also ensures that the design is appropriate for LSSD.
  - **Simulation.** The design can be supported either at the functional or gate level. Gate-level netlists can be back-annotated with timing information for delay simulation.
  - **Floorplanning.** Floorplanning can be used to estimate wiring capacitance, area, and wiring congestion. Floorplanning also allows the user to create bit-slice designs.
  - **Test structure verification.** This step ensures that the design satisfies a set of IBM-defined rules that ensure the design—including RAM, etc.—is in compliance with the requirements for LSSD.
  - **Static timing analysis.** This step analyzes the worst-case clock speed for the implementation.
  - **Formal verification.** The design is checked for equivalence with a Boolean specification using efficient algorithms for solving the Boolean equivalence problem.
- 
-

- **CMOS checks.** This step checks fan-out, I/O, boundary scan, and other low-level circuit checks.
- **Design hand-off.** When the design is ready for physical design, a netlist, timing assertion data, pad placement, and floorplanning information are given to the IBM design center.

At this point, physical design is handled by the manufacturing center:

- **Front-end processing.** Clock trees and test logic are generated at this step and static timing analysis is used to check performance.
- **Pre-layout sign-off.** This step allows the customer to ensure that no errors have been introduced by front-end processing.
- **Layout.** Detailed layout is performed by automatic tools guided by professional designers. Layout can be performed either on a flat or hierarchical design.
- **Post-layout sign-off.** Verifying the logic and timing at this step ensures that no errors were introduced during layout.
- **Tape-out to manufacturing.** Automatic test pattern generation is used to generate test vectors and the mask data is generated and sent to the manufacturing line.

Die are delivered to the customer after fabrication and manufacturing testing.

---

The next example illustrates the design of a CPU. CPU design projects take advantage of previous CPU designs, but also break new ground to meet more aggressive requirements.

---

### **Example 8-5** **Design** **methodology for** **the HP 7100LC**

The HP 7100LC CPU contains approximately 905,000 transistors. The design methodology for the 7100LC [Bas95] was designed to support the design decisions on the microprocessor.

The control logic for the 7100LC was designed using commercial tools for logic synthesis (from Synopsys) and for placement-and-routing (from Cadence). The previous-generation CPU, the 7100, had used a PLA-based methodology. The control logic equations from the PLA-based design could be reused, but timing budgets had to be more carefully allocated and enforced in the synthesis-based methodology. While PLAs have easy-to-estimate delays that are roughly equal for all outputs, synthesized logic can show widely varying changes both from output to output and design iteration to design iteration. The designers judged the overall results of this technique to be good. The 7100LC

---

---

added integer superscalar execution and memory and I/O control, yet it occupies about half the area of the 7100 PLA-based control.

The CPU went through several levels of verification before fabrication of the first samples. Behavioral modeling was used extensively to verify the design. The behavioral models were created in Verilog. The Verilog model was no faster than one created in a proprietary HP simulation environment, but allowed the design team to use industry-standard tools for timing verification, synthesis, etc. The CPU, memory controller, and I/O controller were verified separately for reasons of efficiency. Functional models were created in C or other high-level languages to stimulate these blocks during stimulation. Watchdog code was also inserted to flag errors during simulation. In addition to behavioral simulation, switch-level models of the implementation were also created to verify the transistor-level circuit extracted from the implementation.

Considerable effort goes into the post-silicon validation of any part as complex as a CPU. The 7100LC design team found electrical verification—including timing, shorts, etc.—to be very important. Only the most obvious electrical problems cause total system failure. Many electrical problems are reflected in lowered yields—chips do not run at certain frequencies, supply voltages, etc. The design team also put a great deal of effort into making sure that the chips could be quickly tested with high coverage during manufacture to ensure that systems could be reliably constructed from the chip.

---

The next example describes the design methodology for a system-on-chip.

---

### **Example 8-6 Design of the Viper digital video chip**

The Viper [Dut01] is a system-on-chip designed by Philips for digital television and set-top boxes. This system-on-chip includes 35 million transistors and was fabricated in a 0.18  $\mu\text{m}$  process. The Viper includes two CPUs: a TriMedia VLIW processor and a MIPS CPU. The chip also contains a number of I/O devices and a synchronous DRAM memory controller.

The Viper was designed to meet the Philips DVP standard. This standard defines architectures and interfaces that make it easier to design scalable digital video systems-on-chips. Early in the design, a number of standardized blocks such as interrupts and debug interfaces were designed so that they could be used at several places in the chip.

---

---

A number of register-transfer design rules were followed during RT design:

- All high-bandwidth peripherals used the Philips DVP standard for DMA.
- All low-bandwidth peripherals and MMIO used the Philips PI-bus standard specified by DVP.
- Miscellaneous interface signals (reset, interrupts, etc.) were implemented according to the DVP standard.
- Signals such as resets and interrupts were implemented using standard modules.

The design was verified at both the register-transfer and gate levels. A regression set of tests was executed every week. This test took about 72 hours to execute using 60 CPUs. Emulators were also used to verify the design.

The chip was designed to be fully scan testable. Both structural stuck-at tests and functional tests were used. Some large memories and caches were created with built-in self-test logic. The tests were developed module by module, with each designer responsible for achieving 99% or better fault coverage on his or her component. Buses and interconnect were tested with interconnect tests.

The entire Viper could be synthesized with logic synthesis in about eight hours running on multiple CPUs. After logic synthesis, the scan chains were inserted. The netlist was then partitioned and laid out. The physical hierarchy used for layout was not the same as the logical hierarchy used for register-transfer design. The design was partitioned into chiplets of 200K cells or fewer, with a total of nine chiplets in Viper. Three hard IP blocks were used: the TriMedia CPU, the MIPS CPU, and a custom analog block. Signals between chiplets were connected via abutment.

Timing closure was achieved in two stages. First, each chiplet was analyzed for timing and budgets for input and output timing were set up. Next, the entire chip was analyzed and optimized. Clock connections between chiplets were carefully designed and verified to be sure that the clocks were phase-aligned and met their required timing. A great deal of work went into design-for-manufacturability, including design rule checking, removing antennas, and doubling vias where possible.

---

---

## 8.11 Multiprocessor System-on-Chip Design

---

A **multiprocessor system-on-chip (MPSoC)** [Wol06,Wol07] is a system-on-chip with multiple processing elements. These processing elements may be general-purpose CPUs or DSPs that are referred to as embedded CPUs or embedded DSPs; they may also be specialized units. An MPSoC, because it is programmable, provides flexibility to add features and create several different systems out of the same chip. And because the architecture of the MPSoC is designed for a family of applications, it is more efficient than a general-purpose architecture.

### *MPSoC architectures*

While some MPSoCs have regular architectures, many MPSoCs are heterogeneous. Heterogeneity comes in several different forms:

- Several different types of processing elements, either different instruction sets or specialized accelerators.
- A non-uniform memory system in which not all processing elements have access to all of memory.
- An irregular interconnect system in which not all paths between processing elements and memory have the same bandwidth, etc.

### *why MPSoCs?*

An irregular architecture is hard to program but it provides substantial benefits in real-time responsiveness and power consumption. Matching the processing element to the task can lead to lower power per operation on the types of algorithms for which the processing element is designed. Non-uniform memory systems can guard against irrelevant memory accesses from one processor delaying the time-critical accesses of another. Specialized interconnect can give lower power per bit transmitted, much as specialized processing elements provide better computational efficiency.

### *MPSoCs and IP*

MPSoCs contain large amounts of IP components. A large multiprocessor is much too complex to be designed entirely by hand. Even if all of the components of the MPSoC are IP components that were acquired from other sources, the configuration of the multiprocessor and the programs that run on the multiprocessor make for a unique system.

The next example describes a system-on-chip for multimedia applications that makes use of a sophisticated embedded CPU.

---

---

---

**Example 8-7**  
**The TriMedia**  
**TM-1300**  
**Programmable**  
**Media Processor**


The TriMedia TM-1300 is a system-on-chip for multimedia applications built around a **VLIW** embedded processor. A VLIW (very-long instruction word) processor allows multiple functions to be specified in each instruction. VLIW processors are widely used in multimedia systems because they allow compilers and programmers to take advantage of the data parallelism built into many multimedia algorithms. The TM-1300's VLIW CPU has a 128-bit register file that holds 32-bit operands. It has 27 functional units, with room in each instruction to schedule operations on five of those function units per instruction. The VLIW processor can be programmed in C or C++ using a programming environment hosted on a PC.

The chip has 5.6 million transistors in a six-metal layer 0.25  $\mu\text{m}$  process. It operates at 2.5 V at the core and 3.3V at the pins. It runs at 143, 166, 180, and 200 MHz at minimum voltage. The chip is 58  $\text{mm}^2$  and its package is a 292-pin ball grid array.

---


---

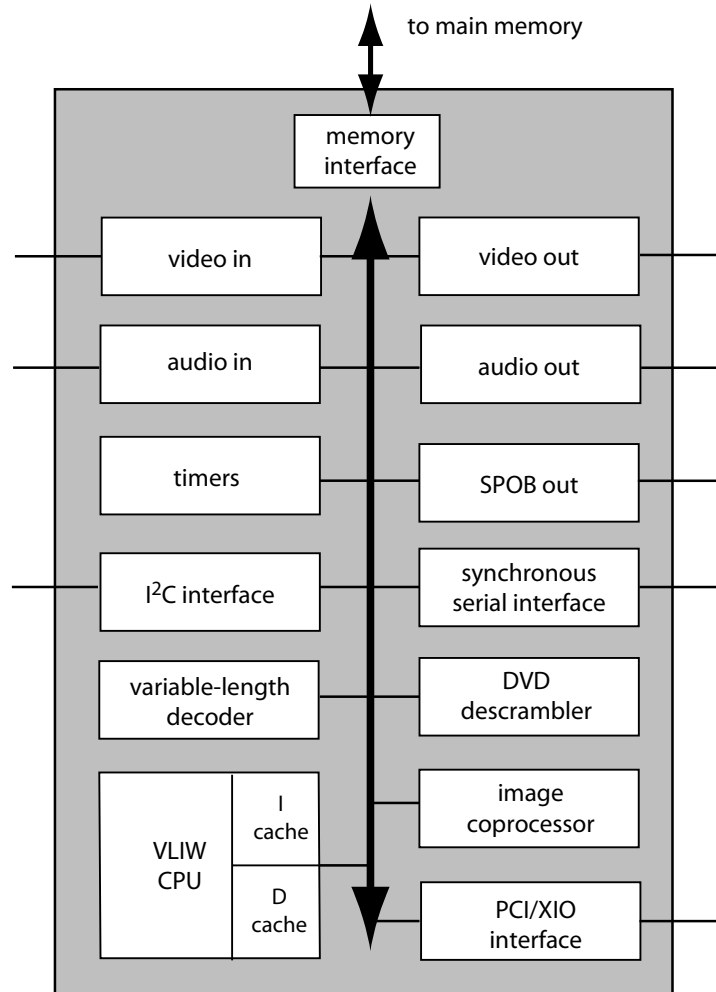Here is the TM-1300 system block diagram:





 And here is a photomicrograph of the chip:



courtesy Philips

The system-on-chip includes a variety of I/O devices and accelerators as well as the VLIW CPU. The I/O devices are chosen to satisfy a variety of needs for multimedia systems. Audio and video input and output are clearly important; the I<sup>2</sup>C interface talks to an industry standard bus that is often used for chip-to-chip communication of low-rate control information. Accelerators are chosen to augment the VLIW CPU's capabilities and speed up critical operations, such as variable-length (Huffman) coding and descrambling of encrypted DVD bit streams.

---

The next example describes another MPSoC for digital media.

---

### **Example 8-8** **The DaVinci** **media processor**


DaVinci [Tal07] is a family of digital media processors designed to provide core functions for portable (i.e., battery-operated) and non-portable media systems.

The Texas Instruments DaVinci uses two programmable cores. One is an ARM processor, designed to run scalar code, the host operating system, *etc.* The other is a VLIW processor that runs most of the signal and image processing code. DaVinci also includes a number of I/O interfaces (USB, I<sup>2</sup>C, *etc.*) and bulk memory interfaces.

---

---

Here is a die photo of the chip:

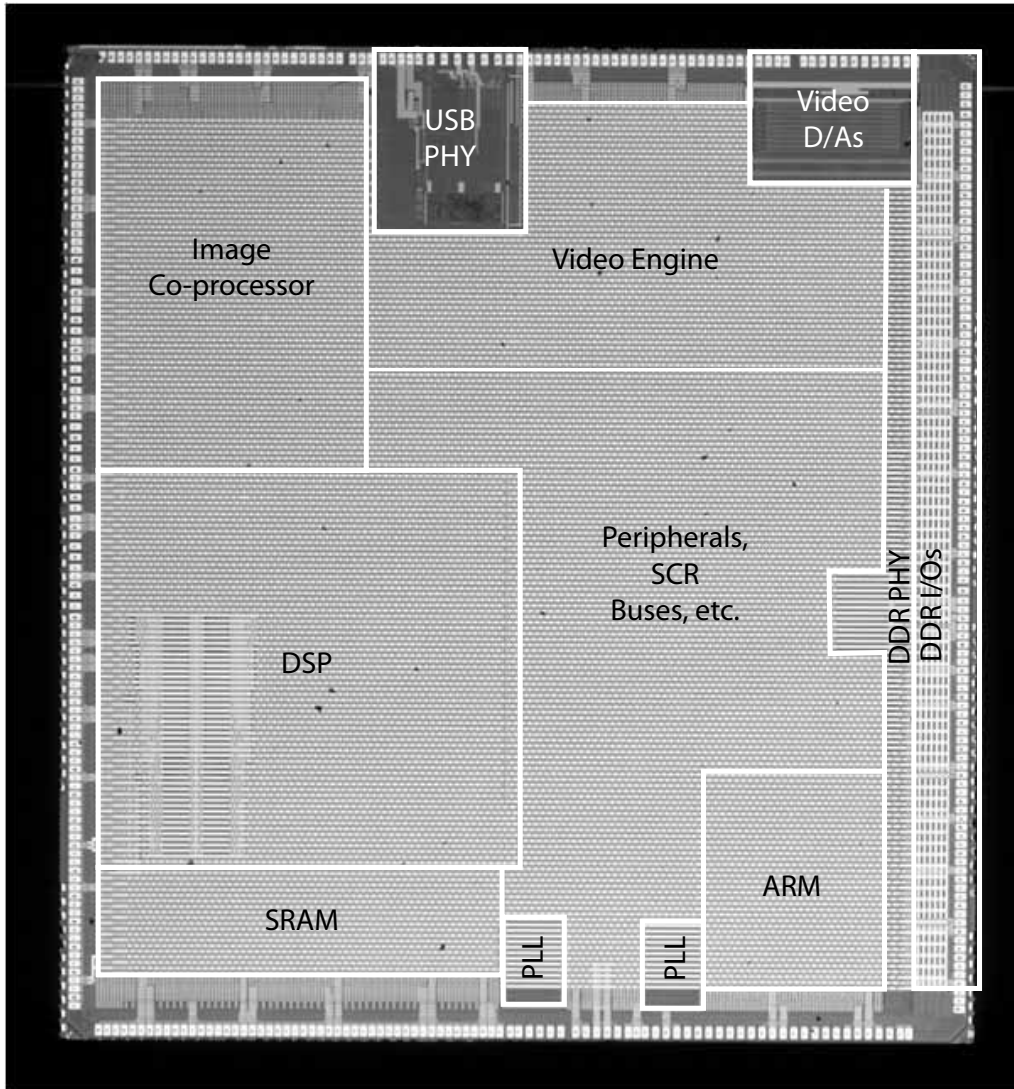

Courtesy Texas Instruments

This photo shows the main components: the ARM and DSP are the main programmable processors; the video engine and image co-processor perform specialized operations; some SRAM is provided; SCR stands for switched central resource, an  $n \times m$  interconnection network; a number of I/O devices are provided, including USB (PHY stands for physical, meaning the physical layer of the USB system); phase-locked loops generate clocks; the pins on the right-hand side support double-data rate (DDR) RAM.

---

## 8.12 References

---

Landman et al. [Lan96] describe a CAD system for architectural power optimization. Lee *et al.* [Lee92] discuss how to automatically allocate registers to improve system testability; Papachristou and Chiu [Pap90] discuss related techniques for built-in self-test. The built-in self-test techniques used in the Intel 80386 have been described by Gelsing [Gel86, Gel87]. General principles of built-in self-test are described by McCluskey [McC86] and Abramovici *et al.* [Abr90]. Lyon *et al.* describe design-for-testability of the Motorola 68HC16Z1 embedded controller [Lyo91]; Bishop *et al.* describe testability considerations in the design of the Motorola MC68340 peripheral [Bis90].

## 8.13 Problems

---

Q8-1. Describe each of these functions in functional VHDL:

- a) a NAND b NAND c.
- b) a + b.
- c)  $y = \text{MUX}(a,b,c,d,\text{ctrl})$ .

Q8-2. Describe each of these functions in functional Verilog:

- a) a NAND b NAND c.
  - b) a + b.
  - c)  $y = \text{MUX}(a,b,c,d,\text{ctrl})$ .
- 
-

Q8-3. Describe these operations in register-transfer form:

- a)  $z = a + b$ .
- b) if (c) then  $z = a + b$  else  $z = c + d$ .
- c)  $z = a + b$ ,  $y = a - c$ .

Q8-4. Design an ASM chart for a machine that recognizes the sequence 11010 from a serial input and asserts the FOUND output when the sequence has been found.

Q8-5. Draw a gate-level block diagram for a four-bit adder that has been pipelined to operate over two clock cycles. Design the adder using XOR, AND, OR, NAND, NOR, and inverters.

Q8-6. Add registers to the multiplier block diagram of Figure 6-12 to pipeline the multiplier over two clock cycles. Show the critical delay path through each stage of the pipeline.

Q8-7. Draw a data flow graph for each of these program fragments:

- a)  $w = a + b$ ;  $y = a - c + d$ .
- b)  $w = a - b + c$ ;  $x = d + e$ ;  $y = w + x$ .
- c)  $w = a - b$ ;  $x = w + c$ ;  $y = x + d$ ;  $z = y - e$ .

Q8-8. Put each of these program fragments into single assignment form:

- a)  $w = a + b$ ;  $y = a - c + d$ ;  $w = y + e$ .
- b)  $w = a - b + c$ ;  $w = d + e$ ;  $w = w + x$ .
- c)  $w = a - b$ ;  $x = w + c$ ;  $w = x + d$ ;  $x = y - e$ .

Q8-9. You are given this code fragment:

```
x <= a + b;  
y <= c + d;
```

Design a data path and controller for this code fragment that executes in:

- a) 1 clock cycle.
  - b) 2 clock cycles.
- 
-

Q8-10. You are given this code fragment:

```
if (c) then
    x <= a + b;
else
    y <= c + d;
```

Design a data path and controller for this code fragment that executes in:

- 1 clock cycle.
- 2 clock cycles.

Q8-11. For each of these program fragments, show the ASAP and ALAP schedules and identify which operations are on the critical path.

- $w = a + b$ ;  $y = a - c + d$ ;  $z = w + y$ .
- $w = a - b + c$ ;  $x = d + e$ ;  $y = w + x$ ;  $z = a - b$ .
- $w = a - b$ ;  $x = w + c$ ;  $y = x + d$ ;  $z = y - e$ .

Q8-12. You are designing a system with a  $C_{ref}$  of 100 minimum-size inverters. assume that  $C_i$  is  $1.5^n$  and  $C_x$  is  $1.1^n$  relative to  $C_{ref}$ . Plot power improvement as given by (EQ 8-7) for a  $V_{ref}$  of 1.2 V,  $V$  ranging from 0.8 to 1.2 V, and with  $n$  ranging from 1 to 4.

Q8-13. Assuming that each of the left-hand side variables in this code is a register, draw the register graph for each code fragment.

- $w = a + b$ ;  $y = a - c + d$ ;  $z = w + y$ .
  - $w = a + x$ ;  $x = d + w$ ;  $y = w + x$ ;  $z = a - b$ .
  - $w = a - z$ ;  $x = w + y$ ;  $y = x + w$ ;  $z = y - e$ .
- 
-



# Appendices

---







A

# A Chip Designer's Lexicon

Thanks to John Redford and Derek Beatty for many colorful terms.

- 3-D integration** Any of several methods for building VLSI systems with transistors and interconnections spread over three dimensions. (See Chapter 2.)
- ALU** Arithmetic logic unit, which can perform several different arithmetic and logic operations as determined by control signals. (See Chapter 6.)
- AOI** An and-or-invert gate. (See Chapter 3.)
- ALAP** As-late-as-possible, a schedule that performs operations at the last possible time. (See Chapter 8.)
- ASAP** As-soon-as-possible, a schedule that performs operations at the earliest possible time. (See Chapter 8.)
- ASIC** Application-specific integrated circuit. (See Chapter 1.)
- ASM chart** A technique for register-transfer design. Elements of the chart correspond to states and transitions in the register-transfer machine. Data path operations can be specified as annotations to those states and transitions. (See Chapter 8.)
- ATPG** See *automatic test pattern generation*.
- 
-

<b>abutment</b>	A connection between two layout blocks formed without additional wiring. (See Chapter 7.)
<b>allocation</b>	The assignment of operations to function units. (See Chapter 8.)
<b>aggressor net</b>	In crosstalk, the net that generates the noise. (See Chapter 4.)
<b>AND plane</b>	The block of logic in a PLA that computes the AND part of the required sum-of-products. (See Chapter 6.)
<b>area router</b>	A router that can operate in non-rectangular, arbitrary-shaped regions. (See Chapter 7.)
<b>architecture-driven voltage scaling</b>	A technique for reducing power consumption in which the power supply voltage is reduced and logic operating in parallel is increased to make up for the performance deficiency. (See Chapter 8.)
<b>array multiplier</b>	A multiplier built from a two-dimensional array of adders and additional logic. (See Chapter 6.)
<b>arrival time</b>	The time at which a signal transition arrives at a given point in a logic network. (See Chapter 5.)
<b>aspect ratio</b>	The width/height ratio of a layout block. (See Chapter 7.)
<b>automatic test pattern generation</b>	Use of a program to generate a set of manufacturing tests. (See Chapter 5.)
<b>balanced tree</b>	In clock distribution, a wiring tree synthesized with RC loads that are balanced across each set of branches of the tree. (See Chapter 7.)
<b>Baugh-Wooley multiplier</b>	A multiplication algorithm for two's-complement signed numbers. (See Chapter 6.)
<b>bed of nails</b>	A set of probes used to test a printed circuit board.
<b>behavioral synthesis</b>	See <i>high-level synthesis</i> .
<b>belt buckle</b>	An extremely large chip. See <i>lots per die</i> .
<b>BGA</b>	Ball-grid array, a type of package. (See Chapter 7.)
<b>binding</b>	In high-level synthesis, synonym for <i>allocation</i> .

---

---

<b>BIST</b>	See built-in self-test.
<b>bit-slice</b>	One bit of a regular, n-bit design. Refers to design styles in both logic and layout. (See Chapter 4.)
<b>body effect</b>	Variation of threshold voltage with source/drain voltage. (See Chapter 2 for the definition of body effect and Chapter 3 for its effect on logic gate design.)
<b>Booth encoding</b>	A technique for reducing the number of stages in array multipliers. (See Chapter 6.)
<b>bottle</b>	CRT in a terminal or workstation (West Coast USA).
<b>bottomwall capacitance</b>	Junction capacitance from the bottom of a diffusion region to the substrate. (See Chapter 2.)
<b>buffer</b>	An amplifier inserted in a wiring network to improve performance. (See Chapter 3.)
<b>built-in self-test</b>	A testing scheme that uses logic built into the chip to test the remainder of the chip. (See Chapter 8.)
<b>burn-in</b>	The initial operation of a part before it leaves the factory. See <i>infant mortality</i> .
<b>bus</b>	A common connection.
<b>CPU</b>	Central processing unit.
<b>carry-lookahead adder</b>	An adder that evaluates propagate and generate signals in a carry-lookahead network that directly computes the carry out of a group of bits. (See Chapter 6.)
<b>carry-select adder</b>	An adder that first generates alternate results for different possible carry-ins, then selects the proper result based on the actual carry-in. (See Chapter 6.)
<b>carry-skip adder</b>	An adder that recognizes certain conditions for which the carry into a group of bits may be propagated directly to the next group of bits. (See Chapter 6.)

---

---

<b>ceramic package</b>	A package for an integrated circuit made from ceramics, which offers better thermal conductivity and isolation from the elements than a plastic package. (See Chapter 7.)
<b>chaining</b>	Performing two data operations, such as two additions, in the same clock cycle. (See Chapter 8.)
<b>channel</b>	A rectangular routing region. (See Chapter 4.)
<b>channel graph</b>	A graph that describes the connections between channels in a floorplan. (See Chapter 7.)
<b>channel router</b>	A routing program designed to route within a rectangular routing region. (See Chapter 4.)
<b>channel utilization</b>	The number of wires that flow through a channel. (See Chapter 7.)
<b>charge sharing</b>	Storing charge in parasitic capacitances such that the circuit produces erroneous results. (See Chapter 4.)
<b>circuit under test, CUT</b>	Testing terminology for the logic undergoing testing.
<b>clock</b>	A signal used to load data into a memory element.
<b>clocked inverter</b>	An inverter with additional transistors that cause its output to be in a high-impedance state when the clock is not active. (See Chapter 4.)
<b>color plan</b>	A sketch of wiring over a chip or a large section of the chip that has been drawn in color to emphasize relationships between the layers and that emphasizes the decisions on how layers are to be used in the layout design. (See Chapter 7.)
<b>control dependency</b>	An operation that depends on a control decision. (See Chapter 8.)
<b>controllability</b>	The ability to set (directly or indirectly) the value of a node on chip. See also <i>observability</i> . (See Chapter 4.)
<b>controller</b>	A state machine designed primarily to generate control signals. (See Chapter 8.)
<b>core-limited</b>	A chip whose size is determined by its core logic, not its pad frame.

---

---

<b>clock distribution</b>	The problem of distributing a clock signal to all points within a chip with acceptable delay, skew, and signal integrity. (See Chapter 7.)
<b>clocked inverter</b>	An inverter with extra transistors that cause the inverter's output to be an open circuit when the clock input is disabled. (See Chapter 5.)
<b>clocking discipline</b>	A set of rules that, when followed, ensure that a sequential system will operate correctly across a broad range of clock frequencies. (See Chapter 5.)
<b>crosstalk</b>	Noise generated by one line interfering with another. (See Chapter 4.)
<b>DCSL</b>	A low-power variant of DCVSL. (See Chapter 3.)
<b>DCVSL</b>	A logic family that uses a latched pullup stage. (See Chapter 3.)
<b>DIP</b>	Dual in-line package, a type of package. (See Chapter 7.)
<b>DRAM</b>	Dynamic random-access memory. A three-transistor cell was an early form; the one-transistor cell is universal in commodity DRAM and increasingly used in logic chips. See also <i>embedded RAM</i> . (See Chapter 6.)
<b>data dependency</b>	A relationship between two data computations in which the result of one is needed to compute the other. (See Chapter 8.)
<b>data path</b>	A unit designed primarily for data-oriented operations. Often designed in <i>bit-slice</i> style. (See Chapter 6.)
<b>data path-controller architecture</b>	A sequential machine built from a data path plus a controller that responds to the data path's outputs and provides the data path's control inputs. (See Chapter 8.)
<b>database</b>	A program that provides access to and maintains the consistency of data.
<b>decoupling capacitors</b>	Capacitors added either on-chip or off-chip to reduce power/ground noise. (See Chapter 7.)
<b>delay</b>	In logic gate design, input/output timing, particularly measured between 50% points in the waveform. (See Chapter 3.)

---

---

<b>departure time</b>	The time at which a signal transition leaves a given point in a logic network. (See Chapter 5.)
<b>design flow</b>	A series of steps used to design a chip. (See Chapter 8.)
<b>design-for-manufacturing</b>	A methodology that improves manufacturing yield. (See Chapter 1.)
<b>design-for-yield</b>	A methodology that improves chip yield for an advanced process. (See Chapter 2.)
<b>design methodology</b>	Generally similar to a design flow, though this is perhaps a more general term. (See Chapter 8.)
<b>design rule</b>	In general, a rule that governs design procedures. Most frequently applied to layout rules. (See Chapter 2.)
<b>detailed routing</b>	The determination of the exact layout of a set of wires; compare to <i>global routing</i> . (See Chapter 7.)
<b>dice</b>	1. ( <i>verb</i> ) To cut a wafer into die. 2. ( <i>noun</i> ) Singular form of <i>die</i> .
<b>diffusion</b>	Generic term for any n-type or p-type region that is used to form transistors or wires. (See Chapter 2.)
<b>die</b>	Chips after slicing from the wafer but before packaging.
<b>direct write</b>	Exposing photoresist by writing directly on the wafer without masks using an electron beam or x-ray lithography system.
<b>distributed control</b>	A controller built from several communicating machines. (See Chapter 8.)
<b>dog and pony show</b>	A presentation to management.
<b>dogleg</b>	A style of channel routing that allows multiple horizontal segments. (See Chapter 4.)
<b>domino</b>	A common form of dynamic logic gate. (See Chapter 3.)
<b>dot-com</b>	An extinct form of company to which many CAD engineers went to seek their fortunes, only to return empty-handed.

---

---

<b>drain</b>	One of the transistor terminals connected to the channel. (See Chapter 2.)
<b>drawn length</b>	The length of the transistor channel as drawn in the layout sent to manufacturing. The masks are often post-processed after tapeout and before manufacturing, making the fabricated and drawn lengths of the gate different. (See Chapter 2.)
<b>drop-in</b>	See <i>test structure</i> .
<b>dynamic latch</b>	A latch that uses gate capacitance as a storage element and is volatile. (See Chapter 5.)
<b>dynamic logic</b>	Logic that relies on charge stored on a transistor's gate capacitance. (See Chapter 4.)
<b>e-beam</b>	An electron beam lithography machine. See also <i>direct write</i> .
<b>effective capacitance</b>	A capacitance value chosen to estimate the gate delay induced by a wiring load. (See Chapter 4.)
<b>Elmore delay</b>	A wiring delay model for RC transmission lines. (See Chapter 3.)
<b>embedded CPU</b>	A CPU used in a larger system design. (See Chapter 8.)
<b>embedded RAM</b>	Memory fabricated on the same die as logic components. (See Chapter 6.)
<b>emulator</b>	An FPGA-based machine into which a logic design can be compiled to be executed at relatively high speeds for prototyping and debugging.
<b>FPGA</b>	Field-programmable gate array. (See Chapter 6.)
<b>fanin</b>	All the gates that drive a given input of a logic gate.
<b>fanout</b>	All the gates driven by a given gate.
<b>flash memory</b>	An EEPROM memory that can be erased and reprogrammed using typical digital voltages and whose erasure circuitry works in large blocks. (See Chapter 6.)
<b>flip-flop</b>	A type of memory element not normally transparent during clocking. (See Chapter 4.)

---

---



<b>floorplan</b>	A sketch used to plan a layout design. (See Chapter 7.)
<b>framework</b>	A style of CAD database that provides utilities used by a variety of CAD tools.
<b>functional testing</b>	Testing of a component at low speed.
<b>fringe capacitance</b>	Capacitance around the edges of a pair of parallel plates. (See Chapter 2.)
<b>full adder</b>	An adder that generates both a sum and a carry. (See Chapter 6.)
<b>GDS2</b>	A common data format used to deliver mask information.
<b>gate</b>	1. The transistor terminal that controls the source-drain current. (See Chapter 2.) 2. Short for <i>logic gate</i> . (See Chapter 3.)
<b>global routing</b>	Determining the paths of wires through channels or other routing areas without determining the exact layout of those wires; compare to <i>detailed routing</i> . (See Chapter 7.)
<b>ground bounce, ground noise</b>	Variations in ground voltage due to impedance on the ground wires. (See Chapter 7.)
<b>ground plane</b>	A large section of metallization used to provide coupling to ground and reduce the effect of other signal coupling. (See Chapter 7.)
<b>hard failure</b>	A failure from which the system cannot recover. (See Chapter 2.)
<b>H tree</b>	A style of clock distribution network in which wires are organized as a hierarchy of Hs. (See Chapter 7.)
<b>half adder</b>	An adder that puts out only a sum. (See Chapter 6.)
<b>hard IP</b>	Intellectual property that is delivered as a layout. (See Chapter 1.)
<b>hardware/software co-design</b>	The simultaneous design of an embedded CPU system and the software that will execute on it.
<b>hardwired controller</b>	A controller that is designed using random logic; compare to <i>micro-coded controller</i> . (See Chapter 8.)

---

---

<b>high-level synthesis</b>	CAD techniques for allocation, scheduling, and related tasks. (See Chapter 8.)
<b>Hightower routing</b>	A common algorithm for area routing.
<b>hit by a truck</b>	The canonical means of losing a key technical person at a critical point in a project.
<b>hold time</b>	The interval for which a memory element data input must remain stable after the clock transition. (See Chapter 5.)
<b>ITRS</b>	See <i>International Technology Roadmap for Semiconductors</i> .
<b>infant mortality</b>	The failure of chips during their first few hours of operation. See <i>burn-in</i> .
<b>intellectual property</b>	Generally, any intangible good that is a product of the mind. Specifically, design elements that are acquired and integrated into a system. (See Chapter 1.)
<b>International Technology Roadmap for Semiconductors</b>	A document produced by the semiconductor industry that maps out goals for future generations of semiconductor manufacturing. (See Chapter 2.)
<b>LFSR</b>	Linear feedback shift register, a sequential machine used to generate pseudo-random sequences. (See Chapter 8.)
<b>LSSD</b>	Level-sensitive scan design, a method by which registers are operated in a shift mode during testing to observe and set state internal to the chip. (See Chapter 5.)
<b>latch</b>	A type of memory element that is transparent when the clock is active. (See Chapter 5.)
<b>linear region</b>	The region of transistor operation in which the drain current is a strong function of the source/drain voltage. (See Chapter 2.)
<b>logic synthesis</b>	The automatic design of a logic network implementation.
<b>lot</b>	A set of wafers run through fabrication simultaneously; the basic unit of production.
<b>lots per die</b>	A yield measure for extremely large chips. See <i>belt buckle</i> .

---

---

<b>MTCMOS</b>	Multiple threshold CMOS, a low-power logic family. (See Chapter 3.)
<b>MTTF</b>	See <i>mean-time-to-failure</i> .
<b>Manchester carry chain</b>	A form of precharged carry chain that uses pass transistors. (See Chapter 6.)
<b>Manhattan geometry</b>	Masks that use only 90-degree angles.
<b>mean-time-to-failure</b>	The mean time between successive system failures. (See Chapter 2.)
<b>memory element</b>	A generic term for any storage element: flip-flop, latch, RAM, etc. (See Chapter 5.)
<b>metal migration</b>	A failure mode of metal wires caused by excessive current relative to the size of the wire. (See Chapter 2.)
<b>microcoded controller</b>	A controller that is designed using a microsequencer; compare to <i>hard-wired controller</i> . (See Chapter 8.)
<b>MPSoC</b>	See <i>multiprocessor system-on-chip</i> .
<b>multiplexer</b>	A combinational logic unit that selects one out of $n$ inputs based on a control signal.
<b>multiprocessor system-on-chip</b>	A system-on-chip that contains more than one CPU, DSP, and/or specialized processor. (See Chapter 8.)
<b>NORA</b>	A style of precharged logic.
<b>nanometer technology</b>	Generally speaking, a technology with feature sizes less than 100 nm. (See Chapter 2.)
<b>n-type diffusion</b>	An n-doped region. (See Chapter 2.)
<b>no-op</b>	1. A CPU instruction that performs no operation. 2. A useless person.
<b>OAI</b>	An or-and-invert gate. (See Chapter 3.)
<b>observability</b>	The ability to determine (directly or indirectly) the value of a node on a chip. See also <i>controllability</i> .

---

---

<b>one-hot code</b>	A unary code used for state assignment or other codes in which each symbol is represented by a single true bit. (See Chapter 5.)
<b>one-transistor DRAM</b>	A dynamic RAM circuit that uses one capacitor to store the value and one transistor to access the value. Also called <i>one-T DRAM</i> . (See Chapter 6.)
<b>OR plane</b>	The block of logic in a PLA that computes the OR part of the required sum-of-products. (See Chapter 6.)
<b>overdamped</b>	An RLC circuit that does not oscillate.
<b><math>\pi</math> model</b>	A model for the load on a gate that uses two capacitors bridged by a resistor. (See Chapter 4.)
<b>p-type diffusion</b>	A p-doped region. (See Chapter 2.)
<b>PCB</b>	Printed circuit board.
<b>PGA</b>	Pin grid array, a type of package. (See Chapter 7.)
<b>PLA</b>	Programmable logic array. (See Chapter 6.)
<b>PLCC</b>	Plastic leadless chip carrier, a type of package. (See Chapter 7.)
<b>PLL</b>	See <i>phase-locked loop</i> .
<b>PODEM</b>	A test generation algorithm.
<b>PG</b>	See <i>pattern generator</i> .
<b>PVT</b>	Acronym for <i>process, supply voltage, and temperature</i> , three critical sources of variations. (See Chapter 2.)
<b>package</b>	Any carrier for an integrated circuit. (See Chapter 7.)
<b>pad</b>	A large metal region used to make off-chip connections. (See Chapter 7.)
<b>pad frame</b>	A set of pads and associated circuitry arranged around the edges of a rectangle, with room for logic in the middle. (See Chapter 7.)
<b>pad-limited</b>	A chip whose size is limited by its pad frame, not its core logic.

---

---

<b>parametric testing</b>	Testing for process-determined parameters: $k'$ , $V_{T0}$ , etc.
<b>pass transistor</b>	A single transistor (usually n-type) used for switch logic. (See Chapter 4.)
<b>pattern generator</b>	A machine that makes masks for fabrication. Pattern generator machines are replaced by electron beam machines for fine-line masks—see <i>e-beam</i> .
<b>performance testing</b>	Testing the speed at which a component runs.
<b>phase</b>	A clock signal that has a specified relationship to other clock phases. (See Chapter 5.)
<b>phase-locked loop</b>	A circuit that is often used to generate an internal clock from a slower external clock source. (See Chapter 7.)
<b>pin</b>	The connection between a package and a board. (See Chapter 7.)
<b>pipelining</b>	A logic design technique that adds ranks of memory elements to reduce clock cycle time at the cost of added latency. (See Chapter 8.)
<b>placement</b>	The physical arrangement of elements. (See Chapter 4 for gate placement and Chapter 7 for more global placement considerations.)
<b>plastic package</b>	A package made from plastic with metal leads for electrical connections. Is cheaper than a ceramic package but provides lower thermal conductivity. (See Chapter 7.)
<b>plate capacitance</b>	A capacitance between two parallel plates. The capacitance mechanism for transistor gates and metal capacitance. (See Chapter 2.)
<b>polysilicon</b>	Material used for transistor gates and wires. (See Chapter 2.)
<b>power-down mode</b>	An operating mode of a digital system in which large sections are turned off.
<b>precharging</b>	Charging a storage node for possible later discharge. (See Chapter 3.)
<b>primary input</b>	An input to the complete system, as opposed to an input to a logic gate in the system.

---

---

<b>primary output</b>	An output of the complete system, as opposed to an output of a logic gate in the system.
<b>probe card</b>	Used to connect a tester to an unpackaged integrated circuit.
<b>propagation time</b>	The time required for a signal to travel through combinational logic. (See Chapter 5.)
<b>pseudo-nMOS</b>	A circuit family that uses a p-type resistive load. (See Chapter 3.)
<b>pulldown</b>	Any transistor used to pull a gate output toward $V_{SS}$ . (See Chapter 3.)
<b>pulldown network</b>	The network of transistors in a logic gate responsible for pulling the gate output toward $V_{SS}$ . (See Chapter 3.)
<b>pullup</b>	Any transistor used to pull a gate output toward $V_{DD}$ . (See Chapter 3.)
<b>pullup network</b>	The network of transistors in a logic gate responsible for pulling the gate output toward $V_{DD}$ . (See Chapter 3.)
<b>QIP metric</b>	A metric used to improve the quality of IP modules (See Chapter 6.)
<b>RAM</b>	Random-access memory. May be dynamic or static. (See Chapter 6.)
<b>ROM</b>	Read-only memory. (See Chapter 6.)
<b>real estate</b>	Chip area.
<b>recirculating latch</b>	A latch with cross-coupled inverters to provide non-volatile storage. (See Chapter 5.)
<b>redundant</b>	Incombinational logic, an expression that is not minimal. (See Chapter 3.)
<b>refresh</b>	Restoring the dynamically-stored value in a memory. (See Chapter 6.)
<b>register</b>	Generally used as synonymous with memory element. (See Chapter 5.)
<b>register graph</b>	A graph used in test generation that describes the connections between registers. (See Chapter 8.)
<b>reliability</b>	The rate of failures of a system, as measured by metrics such as mean-time-to-failure. (See Chapter 2.)

---

---

<b>reticle</b>	An alternate form of mask that covers only a small part of the wafer and is repeated across the wafer surface.
<b>retiming</b>	Moving memory elements through combinational logic to change the clock period. (See Chapter 5.)
<b>river routing</b>	Routing in which wires form meandering paths but do not cross one another.
<b>routing</b>	The physical design of wiring. (See Chapters 4 and 7.)
<b>rubylith</b>	Early material for generating masks—a red sheet of plastic over a clear plastic base sheet that could be cut and peeled away to produce artwork for photographic reduction.
<b>SCR</b>	See <i>silicon-controlled rectifier</i> .
<b>SRAM</b>	Static read-only memory. (See Chapter 6.)
<b>saturation region</b>	The region of transistor operation that is roughly independent of the source/drain voltage. (See Chapter 2.)
<b>scan chain, scan path</b>	A set of registers that can be operated as a shift register for reading and writing during testing. See also <i>LSSD</i> . (See Chapter 5.)
<b>scheduling</b>	The assignment of operations to clock cycles. (See Chapter 8.)
<b>sense amplifier</b>	A differential amplifier used to sense the state of bit lines in memories. (See Chapter 6.)
<b>sequential depth</b>	The number of intervening registers between a selected register and a primary input. (See Chapter 8.)
<b>setup time</b>	The time by which a memory element's data input must arrive for it to be properly stored by the memory element. (See Chapter 5.)
<b>shifter</b>	A logic unit designed for shift operations. (See Chapter 6.)
<b>short circuit power</b>	The power consumed by a logic gate or network when both pullup and pulldown transistors are on. (See Chapter 3.)
<b>sidewall capacitance</b>	Junction capacitance from the side of a diffusion region to the substrate. (See Chapter 2.)

---

---

<b>signal probability</b>	The probability that a signal will switch, used in power analysis. (See Chapter 5.)
<b>silicide</b>	An improved gate material.
<b>silicon-controlled rectifier</b>	In digital VLSI circuits, a parasitic device that can cause the chip to latch up. (See Chapter 2.)
<b>sign-off</b>	The approval of a design for manufacturing (or possibly some intermediate point in the design).
<b>signature analysis</b>	A built-in self-test technique. (See Chapter 8.)
<b>skin effect</b>	The result of electromagnetic fields in low-resistance conductors that causes current to be carried primarily along the conductor's skin. (see Chapter 2.)
<b>slicing structure</b>	A floorplan that can be sliced into two sections without cutting any block, making it easier to route. (See Chapter 7.)
<b>soft IP</b>	Intellectual property that is not delivered as a layout, rather as gates, HDL, <i>etc.</i> (See Chapter 1.)
<b>solder bump</b>	A technique for making connections to a chip across its entire surface, not just at the periphery.
<b>source</b>	One of the transistor terminals connected to the gate. (See Chapter 2.)
<b>spin</b>	A workaholic's term for a <i>turn</i> .
<b>state</b>	The current values of the memory elements. (See Chapter 5.)
<b>state assignment</b>	The selection of binary codes for symbolic states. (See Chapter 5.)
<b>state transition graph</b>	A specification of a sequential machine, equivalent to a <i>state transition table</i> . (See Chapter 5.)
<b>state transition table</b>	A specification of a sequential machine, equivalent to a <i>state transition graph</i> . (See Chapter 5.)
<b>static logic</b>	Logic that does not rely on dynamically-stored charge.
<b>step-and-repeat</b>	The process of patterning a wafer with a reticle.

---

---



<b>stuck-at-0/1</b>	A fault model that assumes that a faulty gate's output is always either 0 or 1. (See Chapter 4.)
<b>stuck-at-open</b>	A fault model that assumes that a faulty gate's output is always either electrically open or electrically closed. (See Chapter 4.)
<b>subthreshold current</b>	A current through a transistor that flows when the gate voltage is below the device's threshold voltage. (See Chapter 2.)
<b>suit</b>	A manager. See <i>no-op</i> .
<b>switchbox</b>	A rectangular routing region with pins on all four sides. (See Chapter 7.)
<b>synthesis subset</b>	A subset of a hardware description language that can be synthesized into hardware. (See Chapter 8.)
<b>tape out</b>	Generate a tape for pattern generation. When working for a munificent employer, the precondition for a major party.
<b>tapered wire</b>	A wire whose width varies along its width, usually to reduce the wire delay. (See Chapter 3.)
<b>test structure</b>	Features added to the wafer for measuring processing parameters.
<b>test synthesis</b>	The creation of test vectors from a state transition diagram or other non-gate description of the logic.
<b>testbench</b>	An HDL module (particularly in VHDL) that is used to execute a test of another HDL module. (See Chapter 8.)
<b>tester</b>	A machine that applies test vectors to chips on the manufacturing line.
<b>threshold voltage</b>	The gate voltage at which a transistor's drain current is deemed to be significant. (See Chapter 2.)
<b>toaster</b>	1) An extremely cost-sensitive application. 2) A chip that greatly exceeds its power budget.
<b>transistor sizing</b>	The determination of the appropriate W/Ls for transistors for performance or other design goals. (See Chapter 3.)
<b>transmission gate</b>	A pair of n-type and p-type transistors connected in parallel and used to build switch logic. (See Chapter 3.)

---

---

<b>transient failure</b>	A failure from which the system can recover. (See Chapter 2.)
<b>transition time</b>	The time it takes a gate to rise or fall, often measured from 10% to 90% for rise time and <i>visè versa</i> for fall time. (See Chapter 3.)
<b>tube</b>	CRT in a terminal or workstation (East Coast USA).
<b>turn</b>	One iteration of the complete design cycle.
<b>underdamped</b>	An RLC circuit that oscillates.
<b>unknown voltage</b>	A voltage that represents neither logic 0 nor logic 1. (See Chapter 3.)
<b>VHDL</b>	Acronym for <i>VHSIC Hardware Description Language</i> . (See Chapter 8 and Appendix B.)
<b>VTCMOS</b>	Variable threshold CMOS, a low-power logic family. (See Chapter 3.)
<b>vector</b>	Inputs applied to a chip.
<b>Verilog</b>	A hardware description language. (See Chapter 8 and Appendix B.)
<b>via</b>	A hole in the chip's insulating layer that allows connections between different layers of interconnect. (See Chapter 2.)
<b>victim net</b>	In crosstalk, the net that receives the noise. (See Chapter 3.)
<b>voltage contrast</b>	A technique for reading voltages on an operating chip by scanning the chip with an electron beam and measuring the deflected current. (See Chapter 8.)
<b>voltage scaling</b>	Any one of several techniques for reducing the power supply voltage of a chip to lower its power consumption. (See Chapter 8.)
<b>wafer start</b>	A unit of production—the start of one wafer through the fabrication line. Both fab line capacity and chip production are measured in units of wafer starts.
<b>Wallace tree</b>	A design for high-speed multiplication. (See Chapter 6.)
<b>wave pipelining</b>	An advanced logic design methodology in which more than one signal is traveling through the logic between successive ranks of memory elements.

---

---

<b>win the lottery</b>	To get a much higher salary from a competitor.
<b>windmill</b>	A configuration of routing channels for which there is no unique routing order of the channels. (See Chapter 7.)
<b>xter, xstr</b>	Synonyms for transistor.
<b>zipper</b>	A logic design family similar to domino logic but without the output-stage inverter.

---

---

**B**

# Hardware Description Languages

## B.1 Introduction

---

This section briefly reviews the Verilog and VHDL hardware description languages. These are both complex languages and this section is not intended to be a complete guide by any means. Hopefully, these sections can help remind you of some basic syntactic elements of the languages.

## B.2 Verilog

---

The IEEE standard defines Verilog. Books by Thomas and Moorby [Tho98], Smith and Franzon [Smi00], and Ciletti [Cil03] are useful guides to the language.

### B.2.1 Syntactic Elements

Verilog has two forms of comments:

```
/* this is a  
   multiline comment */  
// this is a comment
```

Verilog defines the value set [ 0 1 x z ] of signal values. The value x is the unknown value, while z is a high impedance.

---

---

## B.2.2 Data Types and Declarations

The type `wire` is used to carry signal values. If the wire is not driven, it is assigned the default value `z`.

A hardware register is of type `reg`. A register is assigned the default value `x`.

An integer can be written in a variety of bases; the general form for an integer is

```
size'base number
```

The `timescale` statement can be used to specify the units of time in printouts, etc:

```
'timescale 10 ns / 1 ns
```

The first number is the units used and the second number is the least-significant digit.

A `wire` or `reg` may be declared as an array:

```
wire [ expr1 : expr2 ] wire_name ;  
reg [ expr1 : expr2 ] reg_name ;
```

A `parameter` declaration defines a constant in a module:

```
parameter param_name = value ;
```

A preprocessor directive can be used to define constants that can be used in a variety of ways:

```
'define const_name value
```

## B.2.3 Operators

Boolean logical operators include:

```
&& (and) || (or) ~ (not)
```

Verilog provides bitwise Boolean operators that can be applied to wire arrays:

```
& (and) ~& (nand) ^ (xor) ~^ (xnor) | (or) ~| (nor)
```

If these operators are used as binary operators, then they perform bitwise operations. If they are used as unary operators, then they combine the bits in the wire array using the operator, such as ANDing together all the bits in a wire array.

Shift operators include

<< (left shift) >> (right shift)

Relational operators include

< (less than) <= (less than or equal to) >= (greater than or equal to) > (greater than) == (equal) != (not equal)

Arithmetic operators include

+ - \* (multiply) / (divide) % (modulus)

Synthesis of multiply, divide, and modulus require access to hardware modules for these operators. They are, of course, large blocks of logic.

Curly braces can be used to concatenate signals:

{a,b}

forms a vector from *a* and *b*.

## B.2.4 Statements

An assignment statement has the form

```
assign net_name = expression ;
```

The concatenation operator can be used to put together signals into a bundle, for example

```
assign {asig, bsig} = w1 & w2;
```

Blocking assignments are performed in order:

```
v1 = val1;  
v2 = val2;
```

Non-blocking assignments are performed concurrently:

```
sig1 <= a;  
sig2 <= b;
```

A statement block is a set of statements in between **begin** and **end**.

The **always** block repeats a block of code until the simulation terminates:

```
always @(event_expression)  
    statement_block ;
```

The event controlling the **always** may be one of several types: a level type triggers the block whenever a named set of signals changes; an

---

---

edge type, such as `posedge sig` or `negedge sig` looks for an edge in a particular direction.

The if statement has the form

```
if (expression) block
{ elsif (expression) block }
[ else block ] ;
```

The case statement has the form

```
case (expression)
  { value : block; }
  [ default: block;]
endcase
```

The case statement has two important variants: `casez` treats `z` or `?` values as don't-cares; `casex` treats `z`, `x`, or `?` values as don't-cares.

The for loop has the form

```
for (initial_index; terminal_index; step) block;
```

The for statement can be synthesized if it is used to iterate in space over an array of signals, using an integer for the index.

## B.2.5 Modules and Program Units

A module is the basic unit of hardware specification. A module description has the form

```
module module_name( port_list );
  parameter_list
  port_declarations
  wire wire_declarations
  reg reg_declarations
  submodule_instantiations
  body
endmodule
```

A port may be declared to be in, out, or inout:

```
module foo(a, b, c, d)
input a;
output b, c;
inout d;
endmodule;
```

---

---

Submodule instantiations include functions and tasks. A function is a single-output, executes in zero time, and cannot contain timing control statements. A function has the form

```
function [range] function_name;  
    parameters  
    input input_declarations  
    reg reg_declarations  
    body  
endfunction
```

A task is more general, though its outputs must be registered:

```
task task_name;  
    parameters  
    input input_declarations  
    output output_declarations  
    reg reg_declarations  
    body  
endtask
```

### B.2.6 Simulation Control

The `$monitor` statement prints a formatted string every time one of the signals in its list changes. The `$monitor` statement is similar to the C `printf` statement.:

```
$monitor(format_string,signal,...);
```

The formatting string is enclosed by quotes (“ and ”). Formatting directives in the monitor statement include `%d` (decimal), `%b` (binary), `%x` (hex), and `%o` (octal). A newline is denoted by `\n` and a tab by `\t`.

The pound sign can be used to advance the simulation clock:

```
#10
```

This statement advances the simulation clock by 10 time units.

The `initial` block defines a set of code that is executed once at the start of simulation:

```
initial begin  
end
```

The `$stop` command suspends simulation. The `$finish` command terminates the simulation run. Both are terminated by a semicolon.

---

---



---

## B.3 VHDL

---

The IEEE standard defines VHDL [IEE93]. Bhasker's book [Bha95] is a useful introduction to the language.

### B.3.1 Syntactic Elements

A comment in VHDL looks like this:

```
-- This is a comment until the end of the line.
```

VHDL is case-insensitive and generally provides free-form syntax.

A library is used in a module with this declaration:

```
library library_name [, library_name_list];
```

### B.3.2 Data Types and Declarations

VHDL allows the declaration of enumeration types, for example:

```
type enum_1 is (a, w, xxx);
```

The language defines several enumeration types: `character`, `bit` (with values '0' and '1'), `boolean` (with values `true` and `false`), `severity_level`, `file_open_kind`, and `file_open_status`.

VHDL also allows the declaration of integer subranges:

```
type subrange1 is range 1 to 32;
```

An array declaration may make use of any base type:

```
type array1 is array (0 to 15) of bit;
```

A record in VHDL is similar to the structures or records of other modern programming languages:

```
type rec1 is
  field1 : integer;
  field2 : bit;
  field3 : array (0 to 31) of bit;
```

A constant declaration looks like this:

```
constant const_name := value ;
```

A variable declaration has the form:

---

---

variable *variable\_name* : *type\_name* ;

A signal declaration has a similar form:

signal *signal\_name* : *type\_name* ;

### B.3.3 Operators

Logical operators include:

and or nand nor xor xnor not

Relational operators include:

= /= <= < > >=

The /= operator is the not equals operator.

Shift operators include:

sll srl sla sra rol ror

Addition operators include:

+ - &

The & operator is the concatenation operator.

Multiplication operators include:

\* / mod rem

Other operators include:

abs \*\*

The \*\* operator is the exponentiation operator.

### B.3.4 Sequential Statements

A signal assignment looks like this:

*signal* <= *expression* [after *delay\_value*];

The wait statement has several forms:

wait on *sensitivity\_list*;  
wait until *boolean\_expression*;  
wait for *time\_expression*;

The wait on statement waits for an event on one of the signals on the sensitivity list. The wait until statement waits until the expression

---

---

becomes true. The `wait for` statement waits for the specified amount of time.

The `if` statement has the form

```
if boolean_expression then
    sequential_statements
{elsif boolean_expression then
    sequential_statements}
[else
    sequential_statements]
end if;
```

The `case` statement has the form

```
case expression is
    when choices => sequential_statements
    [ when others => sequential_statements ]
end case;
```

The `for` statement has the form

```
for identifier in range loop
    sequential_statements
end loop;
```

The `while` statement has the form

```
while boolean_expression loop
    sequential_statements
end loop;
```

The general loop statement has the form

```
label: loop
    sequential_statements
    exit when boolean_expression;
end loop label;
```

The `assertion` statement has the form

```
assert boolean_expression
    [ report string_expression ]
    [ severity expression ];
```

If the assertion's condition fails, the run time system puts out a warning message.

---

---

### B.3.5 Structural Statements

A declaration of a component instance looks like this:

```
instance_name: type_name port map (pin1, pin2);
```

The *instance\_name* is the name of this instantiation of the component while *type\_name* is the name of the type of component to be instantiated. The list of pins shows how signals are to be connected to the instance's pins.

### B.3.6 Design Units

VHDL defines five types of design units:

- Entity declaration.
- Architecture body.
- Configuration declaration.
- Package declaration.
- Package body.

An entity declaration is a form of type declaration for a hardware unit. It defines the name of the entity and its ports. An entity declaration looks like this:

```
entity entity_name is
  port (a, b : in bit; c : inout bit; d, e : out bit);
end entity_name;
```

The port list following the `port` keyword gives all the ports for the entity. `in`, `out`, and `inout` are directions for the ports. The name `bit` is a type of a signal; other types of signals are also possible.

An architecture body describes the internal organization of an entity and looks like this:

```
architecture arch_name of entity_name is
  { component_list }
begin
  { structural_statements | sequential_statements }
end arch_name;
```

The *arch\_name* parameter is the name of this architecture; an entity may have several different architectures defined for it. If the architecture uses structural statements to connect components, the components needed are declared like this:

---

---

```
component component_name
  port ( port_list );
end component;
```

A configuration declaration declares which architecture to use for an entity and to bind components:

```
configuration config_name of entity_name is
  for arch_name
    for comp1:type1
      use entity lib1.entity1(arch);
    end for;
  end for;
```

A variety of statements can be used in the configuration declaration to determine the binding of components.

A package is a language unit that facilitates code reuse. A package declaration looks like this:

```
package package_name is
  type_declaration;
  component_declaration;
  constant_declaration;
  function_declaration;
end package_name;
```

A package body fills in the information behind the package declarations:

```
package_body package_name is
  package_contents;
end package_name;
```

### B.3.7 Processes

Processes are used to model behavior. A typical process looks like this:

```
process (a, b) is
  begin
    x <= a or b;
    wait for 2 ns;
    y <= not b;
  end process;
```

The signal list following the `process` keyword is the sensitivity list of signals to be observed by the process. The process is activated when any signal on the sensitivity list changes. The process body may include any sequential statement.

---

---

# References

- [Abr90] Miron Abramovici, Melvin A. Breuer, and Arthur D. Friedman, *Digital System Testing and Testable Design*, Computer Science Press, Rockville, MD, 1990.
- [Aga07] Kanak Agarwal and Sani Nassif, "Characterizing process variation in nanometer CMOS," in *Proceedings, DAC 2007*, ACM Press, 2007, pp. 396-399.
- [Ake67] S. B. Akers, "A modification of Lee's path connection algorithm," *IEEE Transactions on Electronic Computers*, February, 1967, pp. 97-98.
- [ARM08] ARM, "Standard cell libraries overview," <http://www.arm.com/products/physicalip/standardcell.html>, accessed May 26, 2008.
- [Alt06] Josep Altet, Wilfrid Clayes, Stefan Dilhaire, and Antonio Rubio, "Dynamic surface temperature measurements in ICs," *Proceedings of the IEEE*, 94(8), August 2006, pp. 1519-1533.
- [Bak90] H. B. Bakoglu, *Circuits, Interconnections, and Packaging for VLSI*, Addison-Wesley, 1990.
- [Bak05] R. Jacob Baker, *CMOS: Circuit Design, Layout, and Simulation*, second edition, IEEE Press, 2005.
- [Bas95] Mick Bass, Terry W. Blanchard, D. Douglas Josephson, Duncan Weir, and Daniel L. Halperin, "Design methodologies for the PA 7100LC microprocessor," *Hewlett-Packard Journal*, 46(2), April, 1995, pp. 23-35.
- [Bau73] Charles R. Baugh and Bruce A. Wooley, "A two's complement parallel array multiplication algorithm," *IEEE Transactions on Computers*, C-22(12), December, 1973, pp. 1045-1047.
- [Ben95] Jack D. Benzel, "Bugs in black and white: imaging IC logic levels with voltage contrast," *Hewlett-Packard Journal*, 46(2), April, 1995, pp. 102-106.
- [Ber95] R. A. Bergamaschi, R. A. O'Connor, L. Stok, M. Z. Moricz, S. Prakash, A. Kuehlmann, and D. S. Rao, "High-level synthesis in an industrial environment," *IBM Journal of Research and Development*, 39(1/2), January/March, 1995, pp. 131-148.
- [Bha95] J. Bhasker, *A VHDL Primer*, revised edition, Englewood Cliffs NJ: Prentice Hall, 1995.
- 
-

- [Bis90] Philip E. Bishop, Grady L. Giles, Sudarshan N. Iyengar, C. Thomas Glover, and Wai-on Law, "Testability considerations in the design of the MC68340 integrated processor unit," *Proceedings, 1990 International Test Conference*, IEEE Computer Society Press, 1990, pp. 337-346.
- [Boe93] K. D. Boese, A. B. Kahng, B. A. McCoy, and G. Robins, "Fidelity and near-optimality of Elmore-based routing constructions," in *Proceedings, ICCD '93*, IEEE Computer Society Press, 1993, pp. 81-84.
- [Boo51] Andrew D. Booth, "A signed binary multiplication technique," *Quart. Journal of Mech. and Appl. Math.*, Vol. IV, Pt. 2, 1951, pp. 236-240.
- [Bor03] Shekhar Borkar, Tanay Karnik, Siva Narendra, Jim Tschanz, Ali Keshavarzi, and Vivik De, "Parameter variations and impact on circuits and microarchitecture," in *Proceedings, 2003 Design Automation Conference*, ACM, 2003, pp. 338-342.
- [Bow95] William J. Bowhill, Shane L. Bell, Bradley J. Benschneider, Andrew J. Black, Sharon M. Britton, Ruben W. Castelino, Dale R. Donchin, John H. Edmondson, Harry R. Fair III, Paul E. Gronowski, Anil K. Jain, Patricia L. Kroesen, Marc E. Lamere, Bruce J. Loughlin, Shekhar Mehta, Robert O. Mueller, Robert P. Preston, Sribalan Santhanam, Timothy A. Shedd, Michael J. Smith, and Stephen C. Thierauf, "Circuit implementation of a 300-MHz 64-bit second-generation CMOS Alpha CPU," *Digital Technical Journal*, 7(1), 1995, pp. 100-118.
- [Boy70] W. S. Boyle and G. E. Smith, "Charge coupled semiconductor devices," *Bell System Technical Journal*, 49, 1970, p. 587.
- [Bre77] Melvin A. Breuer, "A class of min-cut placement algorithms," *Proceedings, 14<sup>th</sup> Design Automation Conference*, ACM/IEEE, 1977, pp. 284-290.
- [Bro93] T. Brodnax, M. Schiffl, and F. Watson, "The PowerPC 601 design methodology," in *Proceedings, ICCD '93*, IEEE Computer Society Press, 1993, pp. 248-252.
- [Bry87B] Randal E. Bryant, "Algorithmic aspects of symbolic switch network analysis," *IEEE Transactions on CAD/ICAS*, CAD-6(4), July, 1987, pp. 618-633.
- [Cal90] Richard E. Calcagni and Will Sherwood, "VAX 6000 Model 400 CPU chip set functional design verification," *Digital Technical Journal*, 2(2), Spring 1990, pp. 64-72.
- [Cal96] Thomas K. Callaway and Earl E. Schwartzlander, Jr., "Arithmetic Components," Chapter 7 in Jan M. Rabaey and Massoud Pedram, eds., *Design Methodologies*, Norwell MA: Kluwer Academic Publishers, 1996.
- [Cha72] T. J. Chaney and C. E. Molnar, "Anomalous behavior of synchronizer and arbiter circuits," *IEEE Transactions on Computers*, C-22(4), April 1973, pp. 421-422.
- [Cha92] Anantha P. Chandrakasan, Samuel Sheng, and Robert W. Brodersen, "Low-power CMOS digital design," *IEEE Journal of Solid-State Circuits*, 27(4), April, 1992, pp. 473-484.
- [Cha01] Anantha Chandrakasan, William J. Bowhill, and Frank Fox, eds., *Design of High-Performance Microprocessor Circuits*, New York: IEEE Press, 2001.
- 
-

## References

601

- [Cha93] K. Chaudhary, A. Onozawa, and E. S. Kuh, "A spacing algorithm for performance enhancement and cross-talk reduction," in *ICCAD-93 Digest of Technical Papers*, IEEE Computer Society Press, 1993, pp. 697-702.
- [Che84] C. F. Chen and P. Subramaniam, "The Second Generation MOTIS Timing Simulator—An Efficient and Accurate Approach for General MOS Circuits," *Proceedings of the IEEE International Symposium on Circuits and Systems*, 1984, pp. 538-542.
- [Che89] K.-T. Cheng and V. D. Agrawal, "An economical scan design for sequential logic test generation,," *Digest of Papers, 19th International Symposium on Fault-Tolerant Computing*, IEEE Computer Society Press, Los Alamitos, CA, 1989, pp. 28-35.
- [Che00] Chung-Kuan Cheng, John Lillis, Shen Lin, and Norman Chang, *Interconnect Analysis and Synthesis*, New York: Wiley Interscience, 2000.
- [Cho89] Paul Chow, ed., *The MIPS-X Microprocessor*, Norwell MA: Kluwer Academic Publishers, 1989.
- [Cho92] K. Choi and W. S. Adams, "VLSI implementation of a 256 x 256 crossbar interconnection network," in *Proceedings, International Parallel Processing Symposium*, IEEE, March 1992, pp. 289-293.
- [Cil03] Michael D. Siletti, *Advanced Digital Design with the Verilog HDL*, Prentice Hall, 2003.
- [Cla73] Christopher R. Clare, *Designing Logic Using State Machines*, McGraw-Hill, 1973.
- [Con93] Jason Cong and Kwok-Shing Leung, "Optimal wiresizing under the distributed Elmore delay model," in *Proceedings, ICCAD-93*, IEEE Computer Society Press, 1993, pp. 634-939.
- [Cor90] Thomas H. Cormen, Charles E. Leiserson, and Ronald L. Rivest, *Introduction to Algorithms*, McGraw-Hill/MIT Press, 1990.
- [Dav05] W. Rhett Davis, John Wilson, Stephen Mick, Jian Xu, Hao Hua, Christopher Mineo, Ambarish M. Sule, Michael Steer, and Paul D. Franzon, "Demystifying 3D ICs: the pros and cons of going vertical," *IEEE Design & Test of Computers*, 22(6), November-December 2005, pp. 498-510.
- [De01] Vivek De, Yibin Ye, Ali Keshavarzi, Siva Narendra, James Kao, Dinesh Somasekhar, Raj Nair, Shekhar Borkar, "Techniques for leakage power reduction," Chapter 3 in Anantha Chandrakasan, William J. Bowhill, and Frank Fox, eds., *Design of High-Performance Microprocessor Circuits*, New York: IEEE Press, 2000.
- [DeM94] Giovanni De Micheli, *Synthesis of Digital Circuits*, McGraw-Hill, 1994.
- [DeM96] G. De Micheli and M. Sami, eds., *Hardware/Software Co-Design*, Norwell MA: Kluwer Academic Publishers, NATO ASI Series, 1996.
- [DeM01] Giovanni De Micheli, Rolf Ernst, and Wayne Wolf, *Readings in Hardware/Software Co-Design*, San Francisco: Morgan Kaufman, 2001.
- [DeM06] Giovanni De Micheli and Luca Benini, *Networks on Chips*, San Francisco: Morgan Kaufman, 2006.
- 
-



- [Den74] Robert H. Dennard, Fritz H. Gaensslen, Hwa-Nien Yu, V. Leo Rideout, Ernest Bassous, and Andre R. LeBlanc, "Design of ion-implanted MOSFETs with very small physical dimensions," *IEEE Journal of Solid-State Circuits*, SC-9(5), October, 1974, pp. 256-268.
- [Den85] Peter Denyer and David Renshaw, *VLSI Signal Processing: A Bit-Serial Approach*, Addison-Wesley, 1985.
- [Deu76] David N. Deutsch, "A 'dogleg' channel router," *Proceedings, 13<sup>th</sup> Design Automation Conference*, ACM/IEEE, 1976, pp. 425-433.
- [Die78] Donald L. Dietmeyer, *Logic Design of Digital Systems*, second edition, Allyn and Bacon, 1978.
- [Dob92] D. W. Dobberpuhl, R. T. Witek, R. Allmon, R. Anglin, D. Bertucci, S. Brittoni, L. Chao, R. A. Conrad, D. E. Dever, B. Gieseke, S. M. N. Hassoun, G. W. Hoepfner, K. Kuchler, M. Ladd, B. M. Leary, L. Madden, E. J. McLellan, D. R. Meyer, J. Montanaro, D. A. Priore, V. Rajagopalan, S. Samudral, and S. Santhanam, "A 200-MHz 64-b Dual-Issue CMOS Microprocessor," *IEEE Transactions on Solid-State Circuits*, 27(11), November, 1992, pp. 1555-1568.
- [Dua02] Jose Duato, Sudkahar Yalamanchili, and Lionel Ni, *Interconnection Networks*, Morgan Kaufman, 2002.
- [Dun85] Alfred E. Dunlop and Brian W. Kernighan, "A procedure for placement of standard-cell VLSI circuits," *IEEE Transactions on CAD/ICAS*, CAD-4(1), January, 1985, pp. 92-98.
- [Dut98] Santanu Dutta, Kevin J. O'Connor, Wayne Wolf, and Andrew Wolfe, "A design study of a 0.25  $\mu\text{m}$  video signal processor," *IEEE Transactions on Circuits and Systems for Video Technology*, 8(4), August, 1998, pp. 501-519.
- [Dut01] Santanu Dutta, Rune Jensen, and Alf Rieckmann, "Architecture and implementation of VIPER: a multiprocessor SOC for ASTB and DTV systems," *IEEE Design & Test of Computers*, July-August 2001.
- [Elm48] W. C. Elmore, "The transient response of damped linear networks with particular regard to wideband amplifiers," *Journal of Applied Physics*, 19, January, 1948, pp. 55-63.
- [Eng96] J. J. Engel, T. S. Guzowski, A. Hunt, D. E. Lackey, L. D. Pickup, R. A. Proctor, K. Reynolds, A. M. Rincon, and D. R. Stauffer, "Design methodology for IBM ASIC products," *IBM Journal of Research and Development*, 40(4), July, 1996, pp. 387-406.
- [Ern03] Dan Ernst, Nam Sung Kim, Shidhartha Das, Sanjay Pant, Rajeev Rao, Toan Pham, Conrad Ziesler, David Blaauw, Todd Austin, Krisztian Flautner, and Trevor Mudge, "Razor: a low-power pipeline based on circuit-level timing speculation," in *Proceedings of the 36<sup>th</sup> Annual Symposium on Microarchitecture, MICRO-36*, IEEE Computer Society Press, 2003.
- [Fil08] Jonathan Fildes, "Chips pass two billion transistor milestone," BBC News, February 4 2008, <http://news.bbc.co.uk/1/hi/technology/7223145.stm>, read May 25, 2008.
- 
-

## References

603

- [Fis95] J. P. Fishburn and C. A. Schevon, "Shaping a distributed-RC line to minimize Elmore delay," *IEEE Transactions on CAS-I*, 42, December, 1995, pp. 1020-1022.
- [Fos95] Eric R. Fossum, "CMOS image sensors: electronic camera on a chip," in *International Electron Devices Meeting, 1995*, IEEE, 1995, pp. 17-25.
- [Fri75] A. D. Friedman and P. R. Menon, *Theory and Design of Switching Circuits*, Rockville, MD: Computer Science Press, 1975.
- [Fri86] Eby G. Friedman and Scott Powell, "Design and analysis of a hierarchical clock distribution system for synchronous standard cell/macrocell VLSI," *IEEE Journal of Solid-State Circuits*, SC-21(2), April, 1986, pp. 240-246.
- [Fri95] Eby G. Friedman, ed., *Clock Distribution Networks in VLSI Circuits and Systems*, IEEE Press, 1995.
- [For87] Mark Forsyth, William S. Jaffe, Darius Tanksalvala, John Wheeler, and Jeff Yetter, "A 32-bit VLSI CPU with 15-MIPS peak performance," *IEEE Journal of Solid-State Circuits*, SC-22(5), October, 1987, pp. 768-775.
- [Gal80] J. Gality, Y. Crouze, and M. Verginault, "Physical vs. logical fault models for MOS LSI circuits: impact on their testability," *IEEE Transactions on Computers*, C-29(6), June, 1980, pp. 527-531.
- [Gaj92] Daniel Gajski, Nikil Dutt, Allen Wu, and Steve Lin, *High-Level Synthesis: Introduction to Chip and System Design*, Kluwer Academic Publishers, 1992.
- [Gao94] T. Gao and C. L. Liu, "Minimum crosstalk switchbox routing," in *ICCAD-94 Digest of Technical Papers*, IEEE Computer Society Press, 1994, pp. 610-615.
- [Gar79] Michael R. Garey and David S. Johnson, *Computers and Intractability: A Guide to the Theory of NP-Completeness*, W. H. Freeman and Company, 1979.
- [Gei90] Randall L. Geiger, Phillip E. Allen, and Noel R. Strader, *VLSI: Design Techniques for Analog and Digital Circuits*, McGraw-Hill, 1990.
- [Gel86] Patrick P. Gelsinger, "Built in self test of the 80386," *Proceedings, ICCD-86*, IEEE Computer Society, 1986, pp. 169-173.
- [Gel87] Patrick P. Gelsinger, "Design and test of the 80386," *IEEE Design & Test of Computers*, June, 1987, pp. 42-50.
- [Gha94] Sorab K. Ghandhi, *VLSI Fabrication Principles: Silicon and Gallium Arsenide*, second edition, John Wiley and Sons, 1994.
- [Gie97] Bruce A. Gieseke, Randy L. Allmon, Daniel W. Bailey, Bradley J. Benschneider, Sharon M. Birtton, John D. Clouser, Harry R. Fair III, James A. Farrell, Michael K. Gowan, Christopher L. Houghton, James B. Keller, Thomas H. Lee, Daniel L. Liebholz, Susan C. Lowell, Mark D. Matson, Richard J. Matthew, Victor Peng, Michael D. Quinn, Donald A. Priore, Michael J. Smith, and Kathryn E. Wilcox, "A 600 MHz superscalar RISC microprocessor with out-of-order execution," in *Digest of Technical Papers, 1997 IEEE International Solid-State Circuits Conference*, Castine ME: John H. Wuorinen, 1997, pp. 176-177.
- 
-

- [Gla85] Lancer A. Glasser and Daniel W. Dobberpuhl, *The Design and Analysis of VLSI Circuits*, Addison-Wesley, 1985.
- [Has71] Akihiro Hashimoto and James Stevens, "Wire routing by optimizing channel assignment within large apertures," *Proceedings, 8th Design Automation Workshop*, SHARE Committee, 1971, pp. 155-169.
- [Hat87] M. Hatamian and G. Cash, "Parallel bit-level pipelined VLSI designs for high-speed signal processing," *Proceedings of the IEEE*, 75(9), September, 1987, pp. 1192-1202.
- [Hig69] D. W. Hightower, "A solution to line-routing problems on the continuous plane," *Proceedings, 6th Design Automation Workshop*, SHARE Committee, 1969, pp. 1-24.
- [Hod83] David A. Hodges and Horace G. Jackson, *Analysis and Design of Digital Integrated Circuits*, McGraw-Hill, 1983.
- [Hoo90] Donald F. Hooper and John C. Eck, "Synthesis in the CAD system used to design the VAX 9000 system," *Digital Technical Journal*, 2(4), Fall, 1989, pp. 118-129.
- [Hor83A] Mark Horowitz, *Timing Models for MOS Circuits*, Ph.D. Thesis, Stanford University, December, 1983.
- [Hor83B] M. Horowitz and R. W. Dutton, "Resistance Extraction from Mask Layout Data," *IEEE Transactions on CAD/ICAS*, CAD-2(3), 1983, pp. 145-150.
- [Hwa91] C.-T. Hwang, J.-H. Lee, and Y.-C. Hsu, "A formal approach to the scheduling problem in high-level synthesis," *IEEE Transactions on CAD/ICAS*, 10(4), April, 1991, pp. 464-475.
- [IEE93] IEEE, *IEEE Standard VHDL Language Reference Manual*, Std 1076-1993, New York: IEEE, 1993.
- [Ism00] Yehea I. Ismail and Eby G. Friedman, "Effects of inductance on the propagation delay and repeater insertion in VLSI circuits," *IEEE Transactions on VLSI Systems*, 8(2), April 2000, pp. 195-206.
- [Jae75] Richard C. Jaeger, "Comments on 'An optimized output stage for MOS integrated circuit'," *IEEE Journal of Solid-State Circuits*, SC10(3), June, 1975, pp. 185-186.
- [Jai83] S. K. Jain and V. D. Agrawal, "Test generation for MOS circuits using the D algorithm," *Proceedings, 20th Design Automation Conference*, IEEE Computer Society, 1983, pp. 64-70.
- [Jan03] Axel Jantsch and Hannu Tenhunen, eds., *Networks on Chip*, Boston MA: Kluwer Academic Publishers, 2003.
- [Jha90] Niraj K. Jha and Sandip Kundu, *Testing and Reliable Design of CMOS Circuits*, Kluwer Academic Publishers, 1990.
- [Jou84] Norman P. Jouppi, *Timing Verification and Performance Improvement of MOS VLSI Designs*, Ph.D. Thesis, Stanford University, October, 1984.
- 
-

## References

605

- [Kah97] Andrew B. Kahng and Sudhakar Muddu, "An analytical delay model for RLC interconnects," *IEEE Transactions on VLSI Systems*, 16(12), December 1997, pp. 1507-1514.
- [Kei01] Doris Keitel-Schulz and Norbert Wehn, "Embedded DRAM development: technology, physical design, and application issues," *IEEE Design & Test of Computers*, May-June 2001, pp. 7-15.
- [Ker78] Brian W. Kernighan and Dennis M. Ritchie, *The C Programming Language*, Prentice-Hall, 1978.
- [Keu91] Kurt Keutzer, Sharad Malik, and Alexander Saldanha, "Is redundancy necessary to reduce delay?," *IEEE Transactions on CAD/ICAS*, 10(4), April, 1991, pp. 427-435.
- [Kir94] D. Kirkpatrick and A. Sangiovanni-Vincentelli, "Techniques for crosstalk avoidance in the physical design of high-performance digital systems," in *ICCAD-94 Digest of Technical Papers*, IEEE Computer Society Press, 1994, pp. 616-619.
- [Kog95] Peter M. Kogge, Toshio Sunaga, Hisatada Miyataka, Koji Kitamura, and Eric Retter, "Combined DRAM and logic chip for massively parallel systems," in W. J. Dally, J. W. Poulton, and A. T. Ishii, eds., *16<sup>th</sup> Conference on Advanced Research in VLSI*, IEEE Computer Society Press, 1995, pp. 4-16.
- [Kor93] Israel Koren, *Computer Arithmetic Algorithms*, Prentice Hall, 1993.
- [Kra82] R. H. Krambeck, C. M. Lee, H. F. S. Law, "High-Speed Compact Circuits with CMOS," *IEEE Journal of Solid-State Circuits*, SC-17(3), June, 1982, pp. 614-619.
- [Kur96] T. Kuroda, T. Fujita, S. Mita, T. Nagamatsu, S. Yoshioka, K. Suzuki, F. Sano, M. Norishima, M. Murota, M. Kato, M. Kinugawa, M. Kakumu, and T. Sakurai, "A 0.9V, 150 MHz, 10-mW, 4mm<sup>2</sup>, 2-D discrete cosine transform core processor with variable threshold-voltage (VT) scheme," *IEEE Journal of Solid-State Circuits*, 31(11), November 1996, pp. 1770-1779.
- [Kur06] Volkan Sursun and Eby G. Friedman, *Multi-Voltage CMOS Circuit Design*, New York: John Wiley and Sons, 2006.
- [Lan96] Paul Landman, Renu Mehra, and Jan M. Rabaey, "An integrated CAD environment for low-power design," *IEEE Design & Test of Computers*, Summer, 1996, pp. 72-82.
- [Lan91] Dirk Lanneer, Stefaan Note, Francis Depuydt, Marc Pauwels, Francky Catthoor, Gert Goossens, and Hugo De Man, "Architectural synthesis for medium and high throughput signal processing with the new CATHEDRAL environment," in Raul Camposano and Wayne Wolf, eds., *High-Level VLSI Synthesis*, Norwell MA: Kluwer Academic Publishers, 1991.
- [Lee92] Tien-Chien Lee, Wayne H. Wolf, Niraj K. Jha, and John M. Acken, "Behavioral synthesis for easy testability in data path allocation," *Proceedings, ICCD-92*, IEEE Computer Society Press, 1992, pp. 29-32.
- [Leh61] M. Lehman and N. Burla, "Skip techniques for high-speed carry-propagation in binary arithmetic units," *IRE Transactions on Electronic Computers*, December, 1961, pp. 691-698.
- 
-

- [Lei83] Charles E. Leiserson, Flavio M. Rose, and James B. Saxe, "Optimizing synchronous circuitry by retiming," *Proceedings, Third Caltech Conference on VLSI*, Randal Bryant, ed., Rockville, MD: Computer Science Press, 1983, pp. 87-116.
- [Lig88] Michael Lightner and Wayne Wolf, "Experiments in logic optimization," *Proceedings, ICCAD-88*, ACM/IEEE, 1988, pp. 286-289.
- [Lin87] Chin Jen Lin and Sudhakar M. Reddy, "On delay fault testing in logic circuits," *IEEE Transactions on CAD/ICAS*, CAD-6(5), September, 1987, pp. 694-703.
- [Lip90A] R. J. Lipton, D. N. Serpanos, and W. H. Wolf, "PDL++: an optimizing generator language for register-transfer design," *Proceedings, ISCAS-90*, IEEE Circuits and Systems Society, May, 1990, pp. 1135-1138.
- [Lip90B] Roger Lipsett, Carl Schaefer, and Cary Ussery, *VHDL: Hardware Description and Design*, Kluwer Academic Publishers, Norwell, MA, 1990.
- [Liu93] Dake Liu and Christer Svensson, "Trading speed for by choice of supply and threshold voltages," *IEEE Journal of Solid-State Circuits*, January 1993, pp. 10-17.
- [Loh07] Gabriel H. Loh, Yuan Xie, and Bryan Black, "Processor design in 3D die-stacking technologies," *IEEE Design & Test of Computers*, 27(3), May-June 2007, pp. 31-48.
- [Lyo91] Jose A. Lyon, Mike Gladden, Eytan Hartung, Eric Hoang, and K. Raghunathan, "Testability features of the 68HC16Z1," *Proceedings, 1991 International Test Conference*, IEEE Computer Society Press, 1991, pp. 122-130.
- [Mai91] Frederic Mailhot and Giovanni De Micheli, "Algorithms for technology mapping based on binary decision diagrams and on Boolean operations," Stanford University Computer Systems Laboratory Technical Report No. CSL-TR-91-486, August, 1991.
- [Mal87] W. Maly, *Atlas of IC Technologies: An Introduction to VLSI Processes*, Benjamin-Cummings, 1987.
- [Mal90] Sharad Malik, *Combinational Logic Optimization Techniques in Sequential Logic Synthesis*, Ph.D. Thesis, University of California, Berkeley, November, 1990.
- [Man96] John G. Maneatis, "Low-jitter and process-independent DLL and PLL based on self-biased techniques," in *Digest of Technical Papers, 1996 IEEE International Solid-State Circuits Conference*, Castine ME: John Wuorinen, 1996.
- [Mar92] John Markoff, "Rethinking the national chip policy," *New York Times*, July 14, 1992.
- [Mau88] Peter M. Maurer, "Design verification of the WE 32106 math accelerator unit," *IEEE Design & Test of Computers*, June, 1988, pp. 11-21.
- [Maz92] Stanley Mazor and Patricia Langstraat, *A Guide to VHDL*, Kluwer Academic Publishers, 1992.
- [Mes90] D. G. Messerschmitt, "cSynchronization in digital system design," *IEEE Journal on Selected Areas in Communications*, 8(8), October 1990, pp. 1404-1419.
- 
-

## References

607

- [Mic92] Petra Michel, Ulrich Lauther, and Peter Duzy, eds., *The Synthesis Approach to Digital System Design*, Kluwer Academic Publishers, 1992.
- [Min95] Mindshare, Inc., *PCI System Architecture*, third edition, Addison-Wesley, Inc., 1995.
- [McC86] Edward J. McCluskey, *Logic Design Principles with Emphasis on Testable Semicustom Circuits*, Prentice-Hall, 1986.
- [McW80] T. M. McWilliams, *Verification of Timing Constraints on Large Digital Systems*, Ph.D. Thesis, Stanford University, May, 1980.
- [Mea80] Carver Mead and Lynn Conway, *Introduction to VLSI Systems*, Addison-Wesley, 1980.
- [Mik68] K. Mikami and K. Tabuchi, "A computer program for optimal routing of printed circuit connectors," *IFIPS Proceedings*, H47, 1968, pp. 1745-1478.
- [MSU89] Center for Integrated Systems, Mississippi State University, *SCMOS Standard Cell Library*, 1989.
- [Mon93] José Montiero, Srinivas Devadas, and Abhijit Ghosh, "Retiming sequential circuits for low power," in *Proceedings, ICCAD-93*, IEEE Computer Society Press, 1993, pp. 398-402.
- [Mul77] Richard S. Muller and Theodore I. Kamins, *Device Electronics for Integrated Circuits*, New York: John Wiley and Sons, 1977.
- [Mur93] Shyam P. Murarka, *Metallization: Theory and Practice for VLSI and ULSI*, Butterworth-Heinemann, 1993.
- [Mut95] S. Mutoh, T. Douseki, Y. Matsuya, T. Aoki, S. Shigematsu, and J. Yamada, "1-V power supply high-speed digital circuitry with multithreshold CMOS," *IEEE Journal of Solid-State Circuits*, 30(8), August 1995, pp. 147-854.
- [Nag75] L. W. Nagel, "SPICE 2: A Computer Program to Simulate Semiconductor Circuits," UCB/ERL M520, University of California, Berkeley, May 1975.
- [Nak06] Junichi Nakamura, ed., *Image Sensors and Signal Processing for Digital Still Cameras*, Boca Raton, FL: CRC Press, 2006.
- [Nie91] Thomas Niermann and Janak H. Patel, "HITEC: a test generation package for sequential circuits," *Proceedings of the European Conference on Design Automation*, 1991, IEEE Computer Society Press, Los Alamitos, CA, pp. 214-218.
- [Noi82] David Noice, Rob Mathews, and John Newkirk, "A Clocking Discipline for Two-Phase Digital Systems," *Proceedings, International Conference on Circuits and Computers*, IEEE Computer Society, 1982, pp. 108-111.
- [Ope02] Opencores Organization, *Specification for the WISHBONE System-on-Chip (SoC) Interconnection Architecture for Portable IP Cores*, Revision: B.3, September 7, 2002.
- 
-

- [Ost83] John K. Osterhout, "Crystal: A Timing Analyzer for nMOS VLSI Circuits," *Proceedings, Third Caltech Conference on VLSI*, Randal Bryant, ed., Rockville, MD: Computer Science Press, 1983, pp. 57-69.
- [Ost84] John K. Osterhout, Gorton T. Hamachi, Robert N. Mayo, Walter S. Scott, and George S. Taylor, "Magic: A VLSI Layout System," in *Proceedings, 21st Design Automation Conference*, ACM/IEEE, 1984, pp. 152-159.
- [Ott80] R. H. J. M. Otten, "Complexity and diversity in IC layout design," *Proceedings of the International Conference on Circuits and Computers*, IEEE Computer Society, 1980, pp. 464-467.
- [Pap90] Chris Papachristou and Scott Chiu, "High level synthesis with self testability," *Proceedings, Techcon '90*, Semiconductor Research Corporation, October, 1990, pp. 407-410.
- [Par92] Kenneth P. Parker, *The Boundary-Scan Handbook*, Kluwer Academic Publishers, 1992.
- [Ped06] Massoud Pedram and Shahin Nazarian, "Thermal modeling, analysis, and management in VLSI circuits: principles and methods," *Proceedings of the IEEE*, 94(8), August 2006, pp. 1487-1501.
- [Pet67] Richard L. Petritz, "Current status of large scale integration technology," *IEEE Journal of Solid-State Circuits*, SC-2(4), December, 1967, pp. 130-147.
- [Pet04] Laura Peters, "Demystifying design-for-yield," *Semiconductor International*, July 1, 2004, <http://www.semiconductor.net/article/CA430963.html>, read May 26, 2008.
- [Pil90] Lawrence T. Pillage and Ronald A. Rohrer, "Asymptotic waveform evaluation for timing analysis," *IEEE Transactions on CAD/ICAS*, 9(4), April 1990, pp. 352-366.
- [Pop06] Mikhail Popovich, Eby G. Friedman, Michael Sotman, Avinoam Kolodny, and Radu M. Secareanu, "Maximum effective distance of on-chip decoupling capacitors in power distribution grids," in *Great Lakes Symposium on VLSI '06*, IEEE, 2006, pp. 173-179.
- [Pre79] Bryan T. Preas, *Placement and Routing Algorithms for Hierarchical Integrated Circuit Layout*, Ph.D. Thesis, Stanford University, August, 1979.
- [Pre88] Bryan T. Preas and Michael J. Lorenzetti, eds. *Physical Design Automation of VLSI Systems*, Benjamin-Cummings, 1988.
- [Qia94] Jessica Qian, Satyamurthy Pallela, and Lawrence Pillage, "Modeling the 'effective capacitance' for the RC interconnect of CMOS gates," *IEEE Transactions on CAD/ICAS*, 13(12), December 1994, pp. 1526-1535.
- [Rab75] Lawrence R. Rabiner and Bernard Gold, *Theory and Application of Digital Signal Processing*, Prentice Hall, 1975.
- [Rab03] Jan M. Rabaey, Anantha Chandrakasan, and Borivoje Nikolic, *Digital Integrated Circuits: A Design Perspective*, second edition, Prentice Hall, 2003.
- [Ram65] Simon Ramo, John R. Whinnery, and Theodore van Duzer, *Fields and Waves in Communication Electronics*, New York: John Wiley and Sons, 1965.
- 
-



## References

609

- [Raz98] Behzad Razavi, *RF Microelectronics*, Upper Saddle River NJ: Prentice Hall PTR, 1998.
- [Reg70] William M. Regitz and Joel A. Karp, "Three-transistor-cell 1024-bit 500-ns MOS RAM," *IEEE Journal of Solid-State Circuits*, SC-5(5), October, 1970, pp. 181-186.
- [Ren06] Renesas Technology, *Semiconductor Reliability Handbook*, REJ27L0001-0100, Rev. 1.00, August 31, 2006.
- [Roy93] Kaushik Roy and Sharat C. Prasad, "Circuit activity based logic synthesis for reliable operations," *IEEE Transactions on VLSI Systems*, 1(4), December, 1993, pp. 503-513.
- [Roy00] Kaushik Roy and Sharat C. Prasad, *Low-Power CMOS VLSI Circuit Design*, New York: Wiley Interscience, 2000.
- [Rub83] J. Rubinstein, P. Penfield, Jr., and M. A. Horowitz, "Signal Delay in RC Tree Networks," *IEEE Transactions on CAD/ICAS*, CAD-2(3), July, 1983, pp. 202-211.
- [Sai93] A. Saini, "Design of the Intel Pentium™ Processor," in *Proceedings, ICCD '93*, IEEE Computer Society Press, 1993, pp. 248-252.
- [Sak92] K. A. Sakallah, T. N. Mudge, and O. A. Olukotun, "Analysis and design of latch-controlled synchronous digital circuits," *IEEE Transactions on CAD/ICAS*, 11(3), March, 1992, pp. 322-333.
- [Sak93] Takayasu Sakurai, "Closed-form expressions for interconnect delay, coupling, and crosstalk in VLSI's," *IEEE Transactions on Electron Devices*, 40(1), January 1993, pp. 118-124.
- [Sal89] Alexander Saldanha, Albert R. Wang, Robert K. Brayton, and Alberto L. Sangiovanni-Vincentelli, "Multi-level logic simplification using don't-cares and filters," *Proceedings, 26th Design Automation Conference*, IEEE Computer Society Press, 1989, pp. 277-282.
- [Sap00] Sachin S. Sapatnekar, "A timing model incorporating the effects of crosstalk on delay and its application to optimal channel routing," *IEEE Transactions on CAD/ICAS*, 19(3), May 2000, pp. 550-559.
- [Sat05] Takashi Sato, Junji Ichimiya, Nobuto Ono, Koutaro Hachiya, and Masanori Hashimoto, "On-Chip Thermal Gradient Analysis and Temperature Flattening for SoC Design," *IEICE Transactions on Fundamentals of Electronics, Communications and Computer Sciences*, E88-A(12), December 2005, pp. 3382-3389.
- [Sec85] Carl Sechen and Alberto Sangiovanni-Vincentelli, "The TimberWolf placement and routing package," *IEEE Journal of Solid-State Circuits*, SC-20(2), April, 1985, pp. 510-522.
- [Ser89] Donald P. Seraphim, Ronald Lasky, and Che-Yu Li, *Principles of Electronic Packaging*, McGraw-Hill, 1989.
- [Ser07] Dimitrios Serpanos and Wayne Wolf, "VLSI models of network-on-chip interconnect," in *Proceedings, 15<sup>th</sup> Annual IFIP International Conference on Very Large Scale Integration*, IFIP, 2007.
- [Sha38] Claude E. Shannon, "A symbolic analysis of relay and switching circuits," *Transactions of the AIEE*, 57, 1938, pp. 713-723.
- 
-




- [She98] Naveed A. Sherwani, *Algorithms for Physical VLSI Design Automation*, third edition, Springer Verlag, 1998.
- [Shi93] Katsuhiko Shimonhigashi and Koichi Seki, "Low-voltage ULSI design," *IEEE Journal of Solid-State Circuits*, 28(4), April, 1993, pp. 408-413.
- [Sho81] M. Shoji, "Electrical design of the BELLMAC-32A microprocessor," in *Proceedings, IEEE International Conference on Circuits and Computers*, IEEE Computer Society Press, 1982, pp. 1132-115.
- [Sho88] Masakazu Shoji, *CMOS Digital Circuit Technology*, Prentice Hall, 1988.
- [Shu91] C. B. Shung, R. Jain, K. Rimey, E. Wang, M. B. Srinistava, B. C. Richards, E. Lettang, S. K. Azim, L. Thon, P. N. Hilfinger, J. M. Rabaey, and R. W. Brodersen, "An integrated CAD system for algorithm-specific IC design," *IEEE Transactions on CAD/ICAS*, 10(4), April, 1991, pp. 447-463.
- [Sie98] Daniel P. Siewiorek and Robert S. Swarz, *Reliable Computer Systems: Design and Evaluation*, A K Peters, 1998.
- [Sin88] Kanwar Jit Singh, Albert R. Wang, Robert K. Brayton, and Alberto Sangiovanni-Vincentelli, "Timing optimization of combinational logic," *Proceedings, ICCAD-88*, IEEE Computer Society Press, 1988, pp. 282-285.
- [Smi00] David R. Smith and Paul D. Franzon, *Verilog Styles for Synthesis of Digital Systems*, Prentice Hall, 2000.
- [Sno78] Edward A. Snow, *Automation of Module Set Independent Register-Transfer Level Design*, Ph.D. Thesis, Carnegie-Mellon University, April, 1978.
- [Sta98] J. Staunstrup and W. Wolf, eds., *Hardware/Software Co-Design: Principles and Practice*, Norwell MA: Kluwer Academic Publishers, 1998.
- [Sun84] Hideo Sunami, Tokuo Kure, Norikazu Hashimoto, Kiyoo Itoh, Toru Toyabe, and Shojiro Asai, "A corrugated capacitor cell (CCC)," *IEEE Transactions on Electron Devices*, ED-31(6), June, 1984, pp. 746-753.
- [Sut99] Ivan Sutherland, Bob Sproull, and David Harris, *Logical Effort: Designing Fast CMOS Circuits*, San Francisco: Morgan Kaufman, 1999.
- [Sye82] Zahir A. Syed and Abbas El Gamal, "Single layer routing of power and ground networks in integrated circuits," *Journal of Digital Systems*, 6(1), 1982, pp. 53-63.
- [Syl01] Dennis Sylvester and Chenming Hu, "Analytical modeling and characterization of deep-sub-micrometer interconnect," *Proceedings of the IEEE*, 89(5), May 2001, pp. 634-664.
- [Sze81] S. M. Sze, *Physics of Semiconductor Devices*, second edition, New York: John Wiley and Sons, 1981.
- [Sze85] S. M. Sze, *Semiconductor Devices: Physics and Technology*, New York: John Wiley and Sons, 1985.
- 
-

## References

611

- [Szy85] T. G. Szymanski, "Dogleg channel routing is NP-complete," *IEEE Transactions on CAD/ICAS*, CAD-4(1), January, 1985, pp. 31-41.
- [Tak85] Yoshihiro Takemae, Taiji Ema, Masao Nakano, Fumio Baba, Takashi Yabu, Kiyoshi Miyakasa, and Kazunari Shirai, "A 1 Mb DRAM with 3-dimensional stacked capacitor cells," in *Digest of Technical Papers, 1985 IEEE International Solid-State Circuits Conference*, IEEE, 1985, pp. 250-251.
- [Tal07] Deepu Talla and Jeremiah Golston, "Using DaVinci technology for digital video devices," *IEEE Computer*, 40(10), October 2007, pp. 53-61.
- [Tee07] P. Teehan, M. Greenstreet, and G. Lemieux, "A survey and taxonomy of GALS design styles," *IEEE Design & Test of Computers*, 24(5), September-October 2007, pp. 418-428.
- [Tho91] Donald E. Thomas and Philip Moorby, *The Verilog Hardware Description Language*, Kluwer Academic Publishers, 1991.
- [Tho02] Donald E. Thomas and Philip R. Moorby, *The Verilog Hardware Description Language*, Fifth Edition, Norwell MA: Kluwer Academic Publishers, 2002.
- [Tri94] Stephen M. Trimberger, ed., *Field-Programmable Gate Array Technology*, Kluwer Academic Publishers, 1994.
- [Ung69] Stephen H. Unger, *Asynchronous Sequential Switching Circuits*, Wiley-Interscience, 1969.
- [Uye92] John P. Uyemura, *Circuit Design for CMOS VLSI*, Kluwer Academic Publishers, 1992.
- [VHD88] VHDL Standards Committee, *IEEE Standard VHDL Language Reference Manual*, IEEE Std 1076-1977, 1988.
- [van90] Lukas P. P. van Ginneken, "Buffer placement in distributed RC-tree networks for minimal Elmore delay," in *Proceedings, ISCAS*, IEEE, 1990, pp. 865-868.
- [Vin98] James E. Vinson and Juin J. Liou, "Electrostatic discharge in semiconductor devices: an overview," *Proceedings of the IEEE*, 86(2), February 1998, pp. 399-418.
- [Wal64] C. S. Wallace, "A suggestion for a fast multiplier," *IEEE Transactions on Electronic Computers*, EC-13(1), February, 1964, pp. 14-17.
- [Was78] R. L. Wasdak, "Fault modeling and logic simulation of CMOS and MOS integrated circuits," *Bell System Technical Journal*, 57, May-June, 1978, pp. 1474-1499.
- [Wei94] M. Weiser, B. Welch, A. Demers, and S. Shenker, "Scheduling for reduced CPU energy," in *Proceedings, First USENIX Symposium on Operating Systems Design and Implementation (OSDI '94)*, 1994, pp. 13-23.
- [Wil81] T. W. Williams and N. C. Brown, "Defect level as a function of fault coverage," *IEEE Transactions on Computers*, C-30(12), December, 1981, pp. 987-988.
- 
-

- [Wil83] Thomas W. Williams and Kenneth P. Parker, "Design for testability—a survey," *Proceedings of the IEEE*, 71(1), January, 1983, pp. 98-112. Reprinted in Vishwani D. Agrawal and Sharad C. Seth, *Test Generation for VLSI Chips*, IEEE Computer Society Press, 1988.
- [Wol00] Wayne Wolf, *Computers as Components: Principles of Embedded Computing System Design*, Morgan Kaufman, 2000.
- [Wol06] Wayne Wolf, *High Performance Embedded Computing*, Morgan Kaufman, 2006.
- [Wol07] Wayne Wolf, Ahmed Jerraya, and Grant Martin, "Multiprocessor Systems-on-Chips," *IEEE Transactions on CAD/ICAS*, 27(10), October 2008, pp. 1701-1713.
- [Xue96] T. Xue, E. S. Kuh, and D. Wang, "Post global routing crosstalk risk estimation and reduction," in *ICCAD-96 Digest of Technical Papers*, IEEE Computer Society Press, 1996, pp. 302-309.
- [Yan78] Edward S. Yang, *Fundamentals of Semiconductor Devices*, McGraw-Hill, 1978.
- [You92] Ian A. Young, Jeffrey K. Greason, and Keng L. Wong, "A PLL clock generator with 5 to 110 MHz of lock range for microprocessors," *IEEE Journal of Solid-State Circuits*, 27(11), November, 1992, pp. 1599-1607.
- 
-




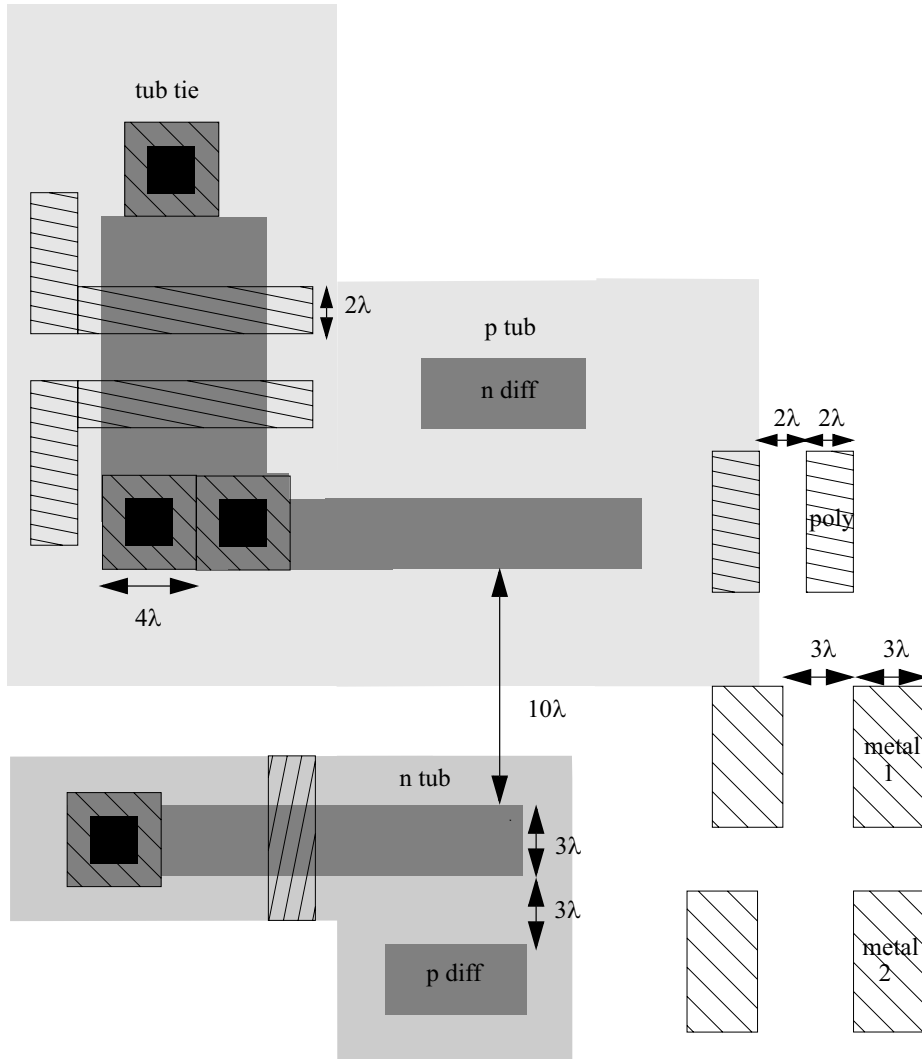



**SCMOS Design Rules**



n-type transconductance	$k'_n$	$170\mu\text{A}/\text{V}^2$
p-type transconductance	$k'_p$	$-30\mu\text{A}/\text{V}^2$
n-type threshold voltage	$V_{tn}$	0.5V
p-type threshold voltage	$V_{tp}$	-0.5V
n-diffusion bottomwall capacitance	$C_{ndiff,bot}$	$940\text{aF}/\mu\text{m}^2$
n-diffusion sidewall capacitance	$C_{ndiff,side}$	$200\text{aF}/\mu\text{m}$
p-diffusion bottomwall capacitance	$C_{pdiff,bot}$	$1000\text{aF}/\mu\text{m}^2$
p-diffusion sidewall capacitance	$C_{pdiff,side}$	$200\text{aF}/\mu\text{m}$
n-type source/drain resistivity	$R_{ndiff}$	$7\Omega/\square$
p-type source/drain resistivity	$R_{pdiff}$	$7\Omega/\square$
poly-substrate plate capacitance	$C_{poly,plate}$	$63\text{aF}/\mu\text{m}^2$
poly-substrate fringe capacitance	$C_{poly,fringe}$	$63\text{aF}/\mu\text{m}$
poly resistivity	$R_{poly}$	$8\Omega/\square$
metal 1-substrate plate capacitance	$C_{metal1,plate}$	$36\text{aF}/\mu\text{m}^2$
metal 1-substrate fringe capacitance	$C_{metal1,fringe}$	$54\text{aF}/\mu\text{m}$
metal 2-substrate capacitance	$C_{metal2,plate}$	$36\text{aF}/\mu\text{m}^2$
metal 2-substrate fringe capacitance	$C_{metal2,fringe}$	$51\text{aF}/\mu\text{m}$
metal 3-substrate capacitance	$C_{metal3,plate}$	$37\text{aF}/\mu\text{m}^2$
metal 3-substrate fringe capacitance	$C_{metal3,fringe}$	$54\text{aF}/\mu\text{m}$
metal 1 resistivity	$R_{metal1}$	$0.08\Omega/\square$
metal 2 resistivity	$R_{metal2}$	$0.08\Omega/\square$
metal 3 resistivity	$R_{metal3}$	$0.03\Omega/\square$
metal current limit	$I_{m,max}$	$1\text{mA}/\mu\text{m}$


### Typical 180 nm process parameters

  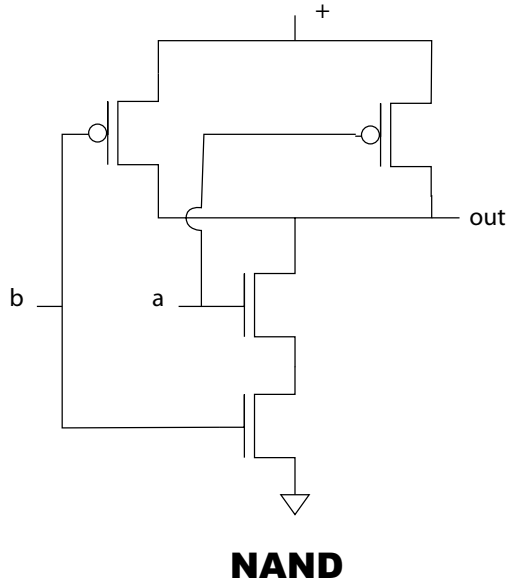 

 

 
**dynamic latch**

$R_n$  6.47 k $\Omega$   
 $R_p$  29.6 k $\Omega$   
 $C_l$  0.89 fF



**timing diagram**

**transistor parameters**

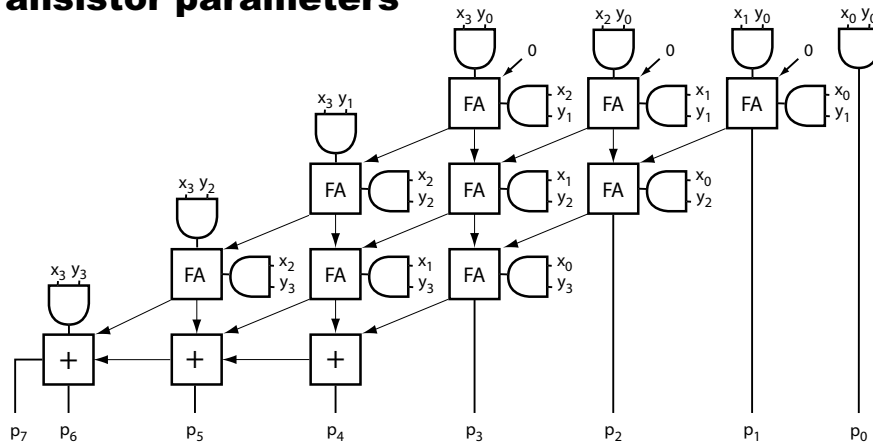

**array multiplier**